

Switching-supply stars blaze to new performance highs

THE ELECTRONIC BREADBOARD ...or a fresh look at using resistors.

Lots of people can sell you resistors. We'd rather sell you costeffective resistance. For starters, we'd like to help you be more selective. Our Resistor Selection Guide puts a choice of nearly 200 standard resistors at your fingertips. Wirewound, metal film, carbon film...commercial, industrial, precision, E-Rel.

But that's only the beginning. Our Resistor Network brochure gives you broad capability in DIPs, SIPs and flat-packs, including MIL-R-83401. And when standard won't do, we're ready with the industry's largest selection of pre-tested special discrete resistor designs.

Write or call today. We can help you take a fresh look at saving time, space and money.



Dale makes your basics better:

• GET THESE TOOLS FOR RESISTOR SELECTION

For Resistor Network Brochure circle **79**



For Resistor Selection Guide circle 80

DALE ELECTRONICS, INC. 2064 12th Ave., Columbus, NE 68601 Tel.402-564-3131 A subsidiary of The Lionel Corporation In Europe: Dale Electronics GmbH, 8039 Puchheim, W. Ger.



Now Available...

0.05-1200 MHz from \$199


- Broadband ... each model multi-octave (see table)
- High linear output ... up to 30 dBm (1 W)
- Gain ... available from 16 dB to 27 dB
- Very flat gain response ... ±1 dB
- · Connectors ... BNC Std; SMA, TNC, N available
- Compact ... 3.75" × 2.60" × 1.92" (ZHL-A Models) 4.75" × 2.60" × 2.22" (ZHL Models)
- Self-contained heat sink
- One-week delivery

If your application requires up to 1 watt for intermodulation testing of components ... broadband isolation ... flat gain over a wide bandwidth ... or much higher output from your frequency synthesizer or signal/sweep generator ... MiniCircuits' ZHL power amplifiers will meet your needs, at surprisingly low prices. Five models are available, offering a selection of bandwidth and gain.

Using an ultra-linear Class A design, the ZHL is unconditionally stable and can be connected to any load impedance without amplifier damage or oscillation. The ZHL is housed in a rugged 1/8 inch thick aluminum case, with a self-contained hefty heat sink. BNC connectors are supplied; however, SMA, TNC and Type N connectors are also available. Of course, our one-year guarantee applies to each amplifier.

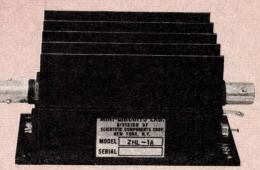So from the table below, select the ZHL model for your particular application now ... we'll ship within one week!





ZHL-1A

MODEL	FREQ.	GAIN	GAIN FLATNESS	MAX. POWER OUTPUT dBm	NOISE FIGURE	INTERCEPT POINT	DC P	OWER	PRI	CE
NO.	MHz	dB	dB	1-dB COMPRESSION	dB	3rd ORDER dBm	VOLTAGE	CURRENT	\$ EA.	QTY.
ZHL-32A	0.05-130	25 Min.	±1.0 Max.	+29 Min.	10 Typ.	+38 Typ.	+24V	0.6A	199.00	(1-9)
ZHL-3A	0.4-150	24 Min.	±1.0 Max.	+29.5 Min.	11 Typ.	+38 Typ.	+24V	0.6A	199.00	(1-9)
ZHL-1A	2-500	16 Min.	±1.0 Max.	+28 Min.	11 Typ.	+38 Typ.	+24V	0.6A	199.00	(1-9)
ZHL-2	10-1000	15 Min.	± 1.0Max.	+29 Min.	18 Typ.	+38 Typ.	+24V	0.6A	349.00	(1-9)
ZHL-2-8	10-1000	27 Min.	±1.0 Max.	+29 Min.	10 Typ.	+38 Typ.	+24V	0.65A	449.00	(1-9)
ZHL-2-12	10-1200	24 Min.	±1.0 Max.	+29 Min.*	10 Typ.	+38 Typ.	+24V	0.75A	524.00	(1-9)

Total safe input power +20 dBm, operating temperature 0° C to +60° C, storage temperature -55° C to +100° C, 50 ohm impedance, input and output VSWR 2.1 max. *+28.5 dBm from 1000-1200 MHz

For detailed specs and curves, refer to 1980/81 MicroWaves Product Data Directory, Gold Book, or EEM

2625 East 14th Street Brooklyn, New York 11235 (212) 769-0200 **Domestic and International Telex 125460** International Telex 620156



INTRODUCING THE SMALLEST FLATPACK MIXERS

Mini-Circuits ultra-compact ASK series measures only 0.3 by 0.27 inches or .081 square inches and more than doubles packaging density on a PC board layout. Mini-Circuits can offer the ASK-1 for the unbelievably low price of only \$5.95 in quantities of 10 because of its high production techniques. Production quantities are ready NOW for immediate delivery. Each unit is manufactured under the high quality standards of Mini-Circuits, the world's largest manufacturer of double-balanced mixers, and comes with a one-year guarantee.

FEATURES:

Wide Frequency	and the second
Range:	1-600 MHz
Smallest Size Mixer	
available:	.3 x .27"
Low Conversion Loss:	6 dB
Plastic Case	
Cost:	\$5.95 (10-49)

DESCRIPTION:

Approximately one-half the size of competitive flatpack mixers, the tiny units of the new ASK series provide high isolation and low conversion loss at about one-fifth the cost. Because of Mini-Circuits high volume production technology and superior quality control techniques, the new ASK series is a breakthrough in today's technology. With lead spacing of .3" between rows, the ASK mixers can be used with standard IC sockets. Although specified to 600 MHz these little units operate up to 1 GHz. Internal construction and bonding techniques enable these units to be used in rugged environments.

SPECIFICATIONS:

Frequency Range:	RF, LO	1-600 MHz DC-600 MHz
Conversion Loss: One Octave from Band Edge Mid-Range		8.5 dB Max. 7.0 dB Max.
Isolation:	L-R L-I	45 dB Typ. 30-dB Typ.
Absolute Maximum Ratings:		oo ab typ.
Total Input Power		50 mW
Total Input Current,	peak	20 mA
Operating Temperature		-55°C to + 100°C
Storage Temperature		-55°C to + 100°C
Pin Temperature	(10 sec.)	+260°C
WEIGHT:	.35 grams	.01 ounces

World's largest manufacturer of Double Balanced Mixers



A Division of Scientific Components Corporation

2625 East 14th Street, Brooklyn, New York 11235 (212) 769-0200 Domestic Telex 125460 International Telex 620156

For more information, Circle No 2

(10-49) quantities MODEL: ASK-1


B51 Rev. Orig.



FEBRUARY 4, 1981 • VOLUME 26, NUMBER 3 • EXCLUSIVELY FOR DESIGNERS AND DESIGN MANAGERS IN ELECTRONICS



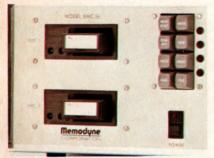Advances in small disk drives pose tough decisions for system designers (pg 45).



Bubbles sub for tape in 128k-bit data logger (pg 81).



On the cover: Switching power supplies are rocketing into new applications, thanks to several technical advances. Turn to pg 94 for the details. (Photo courtesy Power/Mate Corp)



DESIGN FEATURES

Guidelines for gatherings help you meet with success113 As group leader or participant, you can minimize time spent with colleagues and transform dull meetings into effective forums.

Extend your design options with a new comparator IC117 More than an over/undervoltage protector, a new multicomparator IC combines programmable hysteresis with dual high-current outputs.

Network-analysis program runs on small computer system 126 A program for a desktop computer lets you take advantage of circuitanalysis techniques without the problems of time-shared computers.

Analyze size, maintenance to ensure memory reliability 155 By analyzing the effects of RAM size and error-maintenance techniques, you can determine how to design-in memory-system reliability.

TECHNOLOGY NEWS

Small-disk-drive advances promise tough design choices 45 Practical and blue-sky technology to share spotlight at ISSCC 81 (pg 55) . . . Wavelength multiplex, demultiplex devices emerge from fiber-optic research (pg 73).

NEW PRODUCTS

Instrumentation & Power Sources . . 171 ICs & Semiconductors . . 182 Components & Packaging . . 175 Computer-System Subassemblies . 183 Computers & Peripherals . . 186

DEPARTMENTS

Books ... 8 News Breaks ... 15 Signals and Noise ... 20 The Editor's Column ... 33 Editorial Staff ... 34 Leadtime Index . . . 40 µC Design Techniques . . . 87 Literature . . . 189 Career Opportunities . . . 196 Advertisers Index . . . 201 202

Looking Ahead . . . 202

EDN (ISSN 0012-7515) is published biweekly (except monthly in July and December) by Cahners Publishing Company, Division of Reed Holdings, Inc, 221 Columbus Avenue, Boston, MA 02116. Norman L Cahners, Chairman; Saul Goldweitz, President; William M Platt, President, Boston Division. Controlled Circulation paid at Pontiac, IL 61764 and Oakland, CA 94623. Postmaster: Send Form 3579 to EDN, 270 St Paul St, Denver, CO 80206. Advertising and editorial offices: 221 Columbus Ave, Boston, MA 02116. Phone (617) 536-7780. \$2/copy (special issues may vary), \$30/year; international subscriptions: \$5/copy (\$3/copy in Canada) (special issues may vary), \$70/year (\$40/year in Canada), with air mail delivery available for \$150. Send requests for qualification forms and/or change of address to subscription office. © 1981 by Cahners Publishing Company, Division of Reed Holdings, Inc. All rights reserved.

EDN FEBRUARY 4, 1981

Powerful HP Series 9800 desktog acquisition and control: the tim

Imagine a computer with the interfacing power to automate your test and measurement system in days, instead of weeks or months. A computer that puts the entire system under your personal control—even if you're not a programmer.

Imagine how much more productive you could be with an HP Series 9800 computer.

A balance of power.

If you've been thinking that a desktop computer just isn't powerful enough for data acquisition and instrument control, think about this:

Today's Series 9800 desktop systems let you send completely formatted data at rates up to 16K bytes per second and handle up to fourteen channels of vectored interrupt (with high and low priorities). Direct Memory Access (DMA) permits capture of real-time data from high-speed devices at up to 800K bytes per second. And, with user-addressable memories ranging from 62K to 449K bytes, built-in magnetic tape drives, optional I/O ROMs and a wide variety of peripherals to choose from, the Series 9800 delivers big system power you'd never have thought possible in such compact and conveniently integrated packages.

Pick a card. Any card.


Interfacing to your instruments and any combination of HP printers, plotters, and storage devices has never been so easy. Just choose the plug-in interface card that's right for your needs: HP-IB, Bit-Parallel, BCD or RS-232-C. The I/O drivers are already built-in, so you can concentrate on your applications, and not on system configurations. The result? Less development time (which means a lower total cost), and a more productive system all around.

Plenty of room for growth.

The Series 9800 represents a wide range of desktop computers, so you can start building the system that makes sense for your jobs.

Our high-speed HP 9825, for example, is ideal for interactive device control. The System 35 gives you the option of an alphanumeric CRT and Assembly-language programming. The System 45 offers advanced graphics. And our new HP 85 personal computer provides an excellent balance between power and price for lowcost automation.

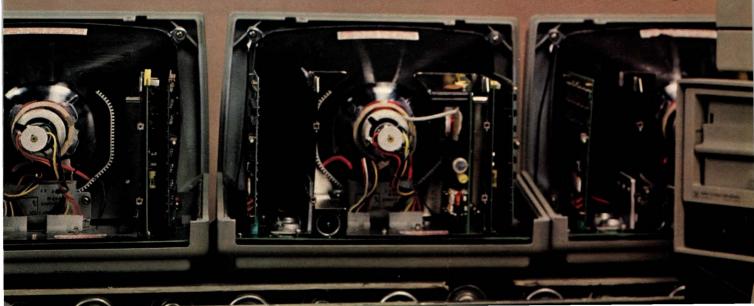What's more, if your applications warrant it, you can get an added dimension of versatility by linking your desktop computer to our powerful HP 1000 minicomputer system. Communication is easily managed, and by combining the



omputers for data hey save is your own.

relative strengths of desktops and minis, you'll get a remarkable degree of flexibility and efficiency for test, measurement, and control jobs.

If you'd like to find out more about how HP Series 9800 desktop computer systems can help you improve your engineering productivity, just contact your local HP sales office listed in the White Pages. Or write for more information to Hewlett-Packard, Attn: Fred Bode, Dept. 2082, 3404 East Harmony Road, Fort Collins CO 80525.

000

HEWLETT

812822



Circle No 3

Now RCA CMOS bursts into color.

New video interface Microboard has all you need to design a custom terminal.

For the first time; a CMOS Microboard with:

- up to 128 user-programmable characters
- 8 programmable colors, or
- black and white display
- audio output for tones or white noise
- parallel input port for keyboard
- graphics and motion
- NTSC and PAL versions. So you can:
- program graphs, charts, messages
- get any combination of sounds
- add a keyboard for human interaction

- use it with any RCA Microboard computer
- use our optional programming design aid, the VIS interpreter (CDP 18S835).

Plus, you get all the advantages of CMOS, making it ideal for industrial controls.

For more information on the CDP18S661, contact any RCA Solid State sales office or appointed distributor. Or contact RCA Solid State headquarters in Somerville, N.J. Brussels, Belgium. Hong Kong. Sao Paulo, Brazil.

Or call Microsystems Marketing toll-free (800) 526-3862.



Books

Advice on protecting your innovations

Patent It Yourself! by David Pressman. 210 pgs; \$15.95; McGraw-Hill Inc, New York, 1979.

A detailed guide for the inventor, this book offers advice on developing, protecting, patenting and marketing ideas. The author draws on his experience as an electrical engineer and patent attorney in reviewing the legal and commercial pitfalls that the do-ityourselfer must avoid.

For example, he emphasizes the importance of keeping accurate records that confirm the identity of an innovation's inventor. And he shows how to maintain and witness lab notes. A collection of sample forms at the end of the book—including those used for filing disclosures, applying for a patent, providing a statement of prior art and requesting a certificate of correction—could facilitate correspondence with the Patent and Trademark Office.

This manual overflows with detailed specificationsguidance on treatment of large or formal sketches, photos and graphs; making an effective sales presentation; determining an invention's market value; and publicizing a new product. Limiting his use of legalese, Pressman suggests where to look for professional help, recognizing that not all inventors can or want to represent themselves, but that most do want to understand the legal process.

A bibliography and checklist of important steps for the inventor conclude this thorough lesson in patent protection.

- Ann Rogers

A new idea in low-cost instrument automation. Simplicity.



It's the HP 9915 Modular Computer—the first in a new generation of easy-to-use, low-cost computers for measurement automation.

The HP 9915 is priced like a board computer, but the comparison ends there. It's a powerful desktop computer, the HP-85, in a modular, rack-mountable package. We left off the keyboard and CRT to give *you* the flexibility to design just the operator interface you need.

The 9915 has the same operating system, I/O drivers, language support and ease of programming as the 85, so building your systems will be a lot simpler, and take only a fraction of the time. You'll save a bundle on development costs.

Designed for designers.

With the HP-85 as a 9915 emulator, program development couldn't be easier. Simply write and debug your application programs in BASIC, then transfer your software to the 9915 via EPROM or tape cartridge. Connect the 9915


to your system and you're ready to go. In many measurement applications, all the operator needs to know about running the system is right there on the 9915's simplified front panel. But if the job calls for a custom keyboard, or remote display, it's simple for you to connect them. No matter what the application, you pay only for the capabilities you need.

Plug-in power.

With the same flexible I/O features as the 85 (including interrupt, high-speed transfer and easy data formatting), the 9915 gets you halfway to your solution before you even start. The I/O drivers are built-in, and because the 9915 uses the same plug-in cards as the HP-85-HP-IB, RS-232-C, Bit-Parallel and BCD-interfacing to your instruments is a snap.

The 9915's 16K byte user-addressable RAM can be expanded to 32K with an optional plug-in memory module. And in addition to the available user memory, the powerful operating system (contained in 48K bytes ROM) can be expanded by adding optional ROMs for matrix math, plotter/ printer control and mass storage control.

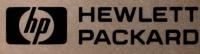For more on the HP 9915, including OEM discounts, call your HP sales office. Or write for our new OEM catalog on computer solutions to Hewlett-Packard, Attn: Jim Geer, Dept. 2090, 3404 E. Harmony Rd., Ft. Collins, CO 80525.



Technological leadership.

Lowest-power 16K to 64K from Motorola.

I TI III

5 V EPROMs Immediately available.

You'll find the ultra low-power 5 V EPROMs you're looking for in Motorola's comprehensive, quality-built 16K to 64K EPROM family.

That includes the MCM68764 and MCM68L764, far and away the lowestpower 5 V 64Ks available. The family also includes our MCM68766 and MCM68766-35 for those who need a 5V 64K with an extra-fast outputenable access time.

They're all available in volume from Motorola now.

These Motorola 5 V EPROMs are pin-compatible with the 8K through 64K industry-standard maskprogrammable ROMs, right down to using the same 24-pin packaging. Even the 64Ks are "plug-in" replacements for the 24-pin industry-standard ROMs, as well as for smaller 5 V EPROMs. The 16K, 32K, and 64K EPROMs from Motorola all have JEDEC-approved standard pinouts.

Added attractions such as on-chip overvoltage protection circuitry help put these 5 V EPROMs in a class by themselves. The higher-performance versions are all $\pm 10\%$ supply devices.

Data retention in these EPROMs is superior, consistent with the high quality of product Motorola has been noted for since the 1950s. By superior data retention, we're talking about a failure rate of only 0.001% per 1000 hours.

The MCM68766 EPROM offers all the features and performance of Motorola's original ultra low-power 64Ks except power down. It has the same access time from address and an even faster 150 ns maximum output enable access time. Order Motorola 5 V EPROMs now from your local Motorola sales office or authorized distributor. For additional information, use the coupon or write to Motorola Semiconductor Products Inc., Technical Information Center, P.O. Box 20912, Phoenix, AZ 85036.

Motorola's Comprehensive 5 V EPROM Family

Motorola Part Number	Access Time – ns	Max Active Current - mA	Max Standby Current – mA	5 V Supply Tolerance – %				
16K EPROMs								
MCM2716	450	100	25	± 5				
MCM27L16*	450	50	10	± 5				
MCM2716-35	350	100	25	±10				
MCM27L16-35*	350	50	10	±10				
MCM2532 MCM25L32*	32K E 450 450	PROMs 100 50	25 10	± 5 ± 5				
MCM2532-35*	350	100	25	±10				
MCM25L32-35*	350	50	10	±10				
64K EPROMs								
MCM68764*	450	120	25	± 5				
MCM68L764*	450	60	15	± 5				
MCM68766	450(1501)			± 5				
MCM68766-35	350(1501)	160		±10				

*Lowest power in the industry Access time from output enable

Industry-standard ROMs, 64K dynamic RAMs, fast static RAMs, and these leading 5 V EPROMs all point to one thing. Motorola has the MOS memories you need for

Innovative systems through silicon.



Please send me information	Tel. ()
Company	
Address	
City	1
State	ZIP

There's no better way

Select the right logic analyzer.

Paratronics offers you the largest selection of advanced logic analysis instruments in the industry. And each instrument can be tailored to your application through an extensive line of plug-in accessories.

Choose the features you need.

Our standard models include demultiplexing, sequential triggering and automatic comparison testing—all pioneered by Paratronics in 1977.

And many of our plug-in accessories represent industry firsts as well. Serial data analysis was offered in 1978; stimulus capability in 1979; analog waveform recording in 1980; and, most recently, we've introduced a plug-in containing counter, timer and single-node signature analysis functions.

Simplify your measurements.

But most importantly, simple keyboard commands let you combine these features to suit your application. For example, when using the PI-540 to trace events that cross between the digital and analog elements of your system, use the keyboard to link the state, timing, and waveform sections. Or, combine the front-end of a PI-600-series analyzer with its internal timer accessory to measure software execution times. Capabilities like these mean you'll need less equipment and set-up time.

Get technical support and prompt delivery.

Need help? Our applications engineers specialize exclusively in logic analysis. Whether you call them on our toll-free technical hotline or simply write in, you'll get the best applications support in the industry.

Then, when you order, you'll get the best delivery as well. During the past five years, our average delivery time has consistently been under four weeks.

Find out why Paratronics is leading the way in logic analysis. For an evaluation unit, applications assistance, or the name of your nearest sales or rental office, contact us at:

800-538-9713 (toll-free, outside California) 408-263-2252 (California) TWX: 910-338-0201



48 Channels for Advanced Software Analysis Model PI-648 Logic State Analyzer \$7,400.



o analyze your system.



32 Channels on a Budget Model PI-532 Logic State Analyzer \$3,150.



100 MHz for Hardware/Software Analysis Model PI-616 Timing/State Analyzer \$8,000.

4 Channels: The Most Powerful ogic Analysis System Available lodels PI-616 and PI-648 \$15,400. 40 Channels for Hardware/Software/ Analog Waveform Analysis Model PI-540 Logic Analysis System \$9,950.



2140 Bering Drive, San Jose, California 95131 U.S.A.

Leading the Way in Analysis Technology Circle no. 78 for additional information Circle no. 91 for a demonstration

The Remarkable Intelligent Display

It's the ideal readout for interactive systems



Want a sure way to label your "smart" system as a product of the 80's?

Give it the ability to communicate, not in lights, but in operator language.

You don't need an expensive CRT. For short alphanumeric messages, an Intelligent Display from Litronix will do the job with a minimum of circuit design.

The Intelligent Display is a 4-character, 17-segment alphanumeric module that interfaces just like a RAM and can be stacked to any length. It has a CMOS chip that includes an ASCII decoder, multiplexer, memory and LED driver. Litronix also offers a pre-engineered Intelligent Display Assembly™ with either 16 or 32 characters.

A new generation of systems that communicate interactively

Intelligent Displays are now being designed into a broad range of "smart" industrial and consumer products. They include portable data entry equipment. Point of

litronix A Siemens Company

sale systems. Business phones. Banking terminals. Security systems. And automatic test instruments.

A parking lot system in Europe actually tells drivers which number stall to take and whether the lot is full.

And don't forget personal computers.

If you are designing or updating products to take advantage of today's microprocessor technology, doesn't it make sense to take it one step further...and give your products the ability to communicate?

With a Litronix Intelligent Display it couldn't be easier. For information contact Litronix, 19000 Homestead Road, Cupertino, CA 95014. (408) 257-7910.

	Part Number	Character Height	Horizontal Row Spacing	Vertical Row Spacing	Viewing Angle	Character Positions	Character Segments		
	DL-1414	.112"	.175"	.800″	±40°	4	17		
[DL-1416	.160″	.250"	1.200"	±25°	4	16		
	DL-2416	.160″	.250"	.800"	±50°	4	17		
	IDA-2416-16. Intelligent Display Assembly, 16 characters								

IDA-2416-16, Intelligent Display Assembly, 16 characters IDA-2416-32, Intelligent Display Assembly, 32 characters

U.S. Distributors: Advent, Almac-Stroum, Arrow, Component Specialties, Gerber, Hamilton Avnet, Harvey, Kirkman, Lionex, Marshall, Moltronics, Pioneer-Standard, Summit and Zeus. Canadian Distributors: C.M. Peterson, Electro Sonic, Future, Hamilton Avnet and L.A. Varah.

News Breaks

16-BIT-µ**P FAMILY SEES FIRST SILICON, GETS SECOND SOURCE**

First wafers of the NS16032 16-bit μ P came off the line at National Semiconductor's Salt Lake City plant in mid-December and are now undergoing evaluation and debugging. The complex 84,000-mil^{*} die is the first of the NS16000 family of CPU and peripherals, which will stretch from a minimal low-cost system to a 16M-byte powerhouse that features mainframecomputer processing power.

At the same time, National announced an agreement with Fairchild Semiconductor (Mt View, CA) to second source the NS16000 family. The nonexclusive agreement covers only masks and design rules, with each company using its own proprietary, but compatible, HMOS process: XMOS for National and probably Isoplanar-H for Fairchild. National's part of the exchange involves the NS16032 CPU and systems-oriented devices; Fairchild will cover the dedicated-peripheral circuits. Both firms will develop a joint program to design future 16000 products.

A source at National says Fairchild was chosen for its strong manufacturing capability and parent company Schlumberger's known commitment to R&D. The agreement, however, does not preclude National's picking up another US source. The company is also planning on another European source in addition to Eurotechnique and several in Japan.

National expects that samples of the 16032 might be ready in May or June.--WT

1-PPM/°C VOLTAGE REFERENCES NEED NO STABILIZING OVEN

Guaranteed to spec ± 1 -mV initial accuracy and ± 1 -ppm/°C drift over 0 to 70°C, two hybrid voltage references from Analog Devices Inc (Norwood, MA) offer the best performance available without oven-temperature regulation, according to the firm.

Model 2710LD outputs + 10.000V, while the dual-output 2712LD delivers \pm 10.000V. Both devices come in 14-pin DIPs, supply 10 mA min and feature long-term stability of 25 ppm/month. In 100s, the 2710 and 2712 cost less than \$43 and \$52, respectively. The firm also offers lower cost, \pm 2-ppm/°C J versions.—WP

TEST SYSTEM HANDLES IN-CIRCUIT AND FUNCTIONAL TESTING

The latest extension to Fairchild Test Systems' Series 70 board testers accommodates both in-circuit and functional pc-board testing. With the Billerica, MA-based Technical Center's \$141,000 Model 60, you can use one bed-of-nails fixture to perform in-circuit tests or to access a card edge for functional checks. The Thinline fixtures used in this system are also employed on in-circuit testers from Fairchild's Subassembly Test Systems Div (Latham, NY). Model 60 can handle 512 test points and is expandable to 1920. Functional testing can run at clock rates to 5 MHz.—AS

PRINTER COMES IN EIGHT USER-SELECTABLE CHARACTER SETS

A low-cost addition to the Omni 800 Series telecommunications printers, the dot-matrix Model 840 from Texas Instruments (Houston) is available in eight user-selectable character sets. These sets include alphabets for the US (ASCII), France, the United Kingdom, Germany, Sweden, Denmark/Norway, Spain and Finland. The printer comes in either a KSR or RO configuration and prints 75 cps; TI plans to introduce it next month. Expect basic-unit prices of \$1300 or less.—CW

SPEAKING OF VOICE I/O ...

At the Consumer Electronics Show in Las Vegas last month, Interstate Electronics Corp (Anaheim, CA) introduced three voice-technology chip sets, marking the firm's first venture in the consumer market. Model 2A chip set provides 95% recognition accuracy for 24 phrases.

News Breaks

Model 2B is a custom version of the 2A. Model 3 furnishes speaker-independent recognition of four to eight words (85% accuracy) plus voice response. All sets are available only in minimum orders of 100,000 units.

... A package of software and two pc cards converts an Intellec development system into a workstation for designing voice-response and isolated-word- and phrase-recognition systems. The Voice Experimenter's Workstation from Technology Service Corp (TSC) (Santa Monica, CA) incorporates Interstate Electronics' Voice Recognition Module and TSC's Voice Control Unit, providing low-cost speaker-independent recognition. The Workstation without the Intellec system costs \$7500.— $\mathbb{E}T$

LEARN HOW TO MANAGE ENGINEERING PROFESSIONALS

Two seminars will examine how technical/personnel managers can develop the skills needed to deal effectively with subordinates.

One seminar, sponsored by the Boston College School of Management, will be held February 19 to 20 at BC's Putnam Center in Newton, MA. The course fee is \$395. Call (617) 969-4217 for further information.

The other forum, scheduled for February 25 to 26, will be sponsored by the California Institute of Technology and held at the Newport Beach, CA Marriott Hotel. Fee for sponsors is \$445; \$495 for others. Phone (213) 795-6811 or (714) 750-7084 (ext 1041) for details.—AR

HARDWARE / SOFTWARE PACKAGE EXPANDS UNIBUS MEMORY ADDRESSING

If you use a DEC PDP-11 computer and want to address more than 248k bytes of main memory, you need not upgrade your CPU to a Series 44 or 70. As an alternative, Periphonics Corp (Bohemia, NY) offers its \$15,000 Peripacs system, which maintains the standard Unibus structure while permitting an essentially unlimited address space. It uses an active backplane to produce a multivalued map of Unibus addesses to memory.

The software supporting Peripacs, developed by Programming Concepts Inc (Coram, NY), replaces the RSX LOADR program on the DEC-supplied RSM-11M operating systems.—WP

200W SWITCHER PASSES VDE TESTS

Model XL200-3501 from Boschert Inc (Sunnyvale, CA) is the only open-frame 200W switcher with VDE 0730 safety-spec approval, according the firm's product-development manager, Jack Tuite. He adds that this approval virtually assures compliance with VDE's planned 0806 spec, expected to replace both 0730 (now aimed at office equipment) and the less stringent 0804 (now covering computer-room equipment accessible primarily to technically skilled personnel). The switcher is also designed to meet VDE 0871 (N-12) and proposed FCC EMI regulations.

The \$385 supply furnishes 5V at 5 to 25A (with $\pm 1\%$ combined source and load regulation) and -5, -12 and +12V at 0.5 to 4A (with $\pm 9\%$ combined regulation). Noise and ripple spec at $\pm 2\%$ on all outputs. The supply operates on jumper-selectable 95 to 130V or 190 to 265V (47 to 440 Hz) inputs.

For more information on the latest switchers, turn to pg 94.-RN

VERSATILE PRINTER REPORTS MEASUREMENT RESULTS

Model 820 thermal printer from Newport Electronics (Santa Ana, CA) employs a Texas Instruments ceramic-substrate thermal head that creates 5×7 matrix characters in 20 columns. The \$543 (1000) printer accepts parallel or serial inputs and sports a time-of-day clock and a print-interval timer that allows you to select one of 16 intervals. The 820 uses a Rockwell $6500/1 \mu$ P and includes 45 special measurement-related characters. Set for introduction next month, it suits panel mounting.—CW

Now designers can eliminate snubbers from switching power supplies


(with new 60V, 175 °C, high-energy TRW Schottkys)

Test TRW's new Schottky superstars in your design — they deliver a 33% higher margin of protection against overvoltage. High reverse energy tolerance makes them damage-proof and means greater reliability. And eliminating the snubbers simplifies your design and cuts manufacturing costs. Check it out—our 60V, 175 °C Schottkys are a state-of-the-art design that can help *your* design, cut costs and improve performance. What's more, our new expanded

capability means that you can continue to rely on TRW for consistent quality, dependable delivery and advanced performance —with plenty of design leeway. Mail the coupon for a free sample, make your test and see for yourself.

Reader service inquiries will receive data information only.

TRW Power Semiconductors • 14520 Aviation Blvd., Lawndale, CA 90260									
Check the free te you'd like to recei					NAME				
	IF	VR	тј	Package	POSITION				
	75A	60V	175 °C	DO-5	COMPANY NAME				
SD-31*	30A	60V	175 °C	DO-4	MAILING STATION	PHONE			
D-231* (Dual)	30A	60V	175 °C	TO-3	ADDRESS				
*SD-31, SD-71 and SD-231 in are Trade Marks of TRW Inc		TR	RW		CITY/STATE/ZIP ER SEMICONDUCTORS aponents Division of TRW Inc.	EDN1 2/81			

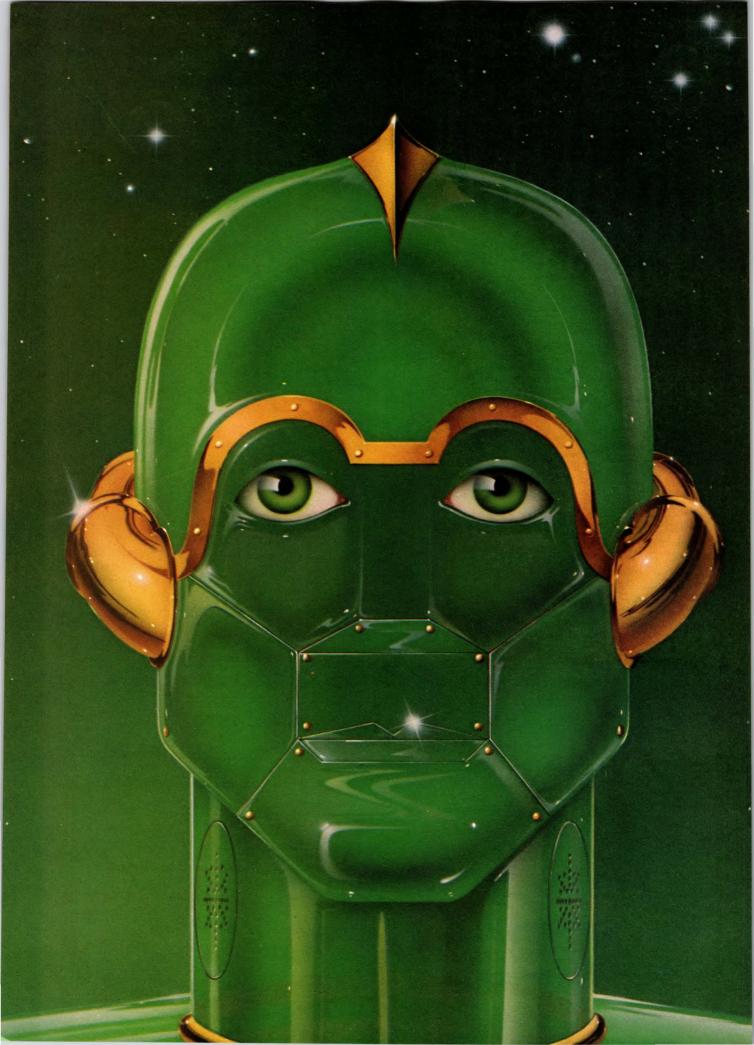

Our new Multibus memory boards are unforgettable. If the power fails, they won't.

If you've got Multibus applications that demand retaining critical data, then NEC has two solutions to your problem. Because we've just introduced two Multibus compatible boards that won't lose their memory when you lose your power.


The BP-0220 and the BP-0200 are nonvolatile 16K CMOS/RAM boards designed, developed and manufactured in the U.S. by NEC Microcomputers. Both boards come complete with an on-board self-charging battery pack, so if the power goes off, your data will be protected for a full 7 days.

The BP-0220 supports 16- and 20-bit addressing and delivers a maximum access time of 450ns. It also has sockets that allow you to add either 8-2716 or 8-2732 industry standard EPROMs, (user supplied).

The BP-0200 has all the features of the BP-0220 except EPROM sockets. Both boards give you the kind of reliability you've come to expect from NEC.

If you need to retain critical data, remember the two new boards from NEC. They're unforgettable.

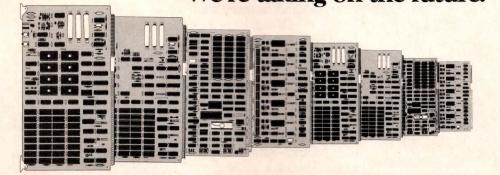For more information about our growing family of Multibus boards, call or write our Product Manager, SBC Systems, NEC Microcomputers, Inc., 173 Worcester Street, Wellesley, MA **NEC** 02180. Tel: (617) 237-1910. IM Multibus is a trademark of Intel Corporation. We're taking on the future.TM



Lugs vs. Leads? CSA, VDE or UL? Fusing?... Confusing?



The simple solution to transformer specification is Grand Transformers Incorporated.

At Grand, we're in business to do more than just manufacture top quality transformers. We're in business to serve our customers by recommending — or custom designing — the right transformer for the application.

We like to get involved from the very beginning. That way, we learn all the unique aspects of your needs and can recommend, or design, the transformer to fit them precisely. Our staff of design engineers can ensure that you get the best product possible.

At Grand, no job is too small or too large. Our multi-factory operation enables us to service every size order. Every job is important.

Of course, Grand has the experience you'd expect. We've been in business for more than 30 years, can conform to VDE, UL and CSA standards, and consider special applications like the medical and dental fields a regular part of our business.

The next time you have to spec a transformer, let Grand provide the solution. Write: Grand Transformers, Inc., 800 Beechtree, Grand Haven, Michigan, 49417. Or call 616-842-5430.



For more information, Circle No 9

Signals & Noise

Other ways available to upgrade 8-bit systems

The article "An innovative TTL chip gives 8-bit μ Ps new life" (EDN, November 5, 1980, pg 269) effectively discusses address expansion—a needed first step in upgrading an 8-bit system.

Unfortunately, the article implies that increased processing power must come from a 16-bit CPU, which is not necessarily so. You can increase the throughput of an 8-bit system many times by using multiprocessor techniques, employing more than one 8-bit CPU and distributing the computing load among them.

However, you must design systems carefully to obtain the advantages of multiprocessing. An example of a good approach to multiprocessing is master/ slave operation on the Multibus using our IM-1680 intelligent RAM, a 16k static-RAM board with an on-board Z80 that acts as a bus slave.


This arrangement results in a low-cost upgrade because the incremental cost of adding a CPU to a memory board is very small now that the price for a Z80 is less than \$10. And because every system must have memory, all you have to do to configure a multiprocessor is to use the IM-1680 intead of standard RAM boards.

By using a memory mapper like the one described in the article and memory made up of several IM-1680s, you can build a system more powerful than one based on a 16-bit CPU. And a complete rewrite of the software isn't required to accommodate a new CPU. In addition, master/slave operation simplifies coordination of system software. Alternative configurations such as multimaster operation are much more difficult to program and offer no real advantage.

A multiprocessor's effectiveness depends on the amount of parallelism inherent in the software. Our experience has been that most programs can be easily partitioned to parallelrunning subroutines, a practice that results in a modular and easy-to-maintain program. You can accomplish parallelism detection by hand or automatically using a preprocessor.

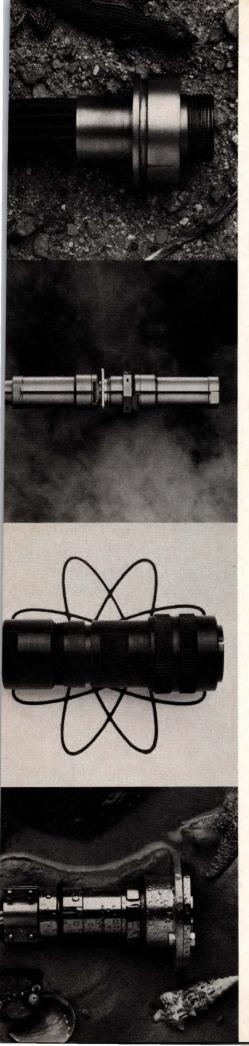Although an upgrade of an 8-bit system might not be the correct solution in every situation, you should at least consider it before jumping to a 16-bit microprocessor. Sincerely, Vassilios J Georgiou President Microsignal Santa Barbara, CA





SURVIVAL TACTICS FOR HOSTILE ENVIRONMENTS.


The tougher your requirements, the more you need connectors from ITT Cannon Electric Canada. We specialize in connectors that withstand the harshest, most severe environments found in industries such as aerospace, geophysical, nuclear, downhole mining, and marine.

Our firewall connectors are a prime example. Designed to penetrate the engine firewall of military and commercial aircraft with electrical circuits, our FRF/FVF series still maintain the integrity of the flame barrier requirements of the aircraft firewall.

These connectors protect against high temperatures, emergency fireretardant conditions, moisture and atmospheric changes, plus resist fuels, cleaning agents, coolants and hydraulic fluids. They meet MIL-C-5015 Class K specifications.

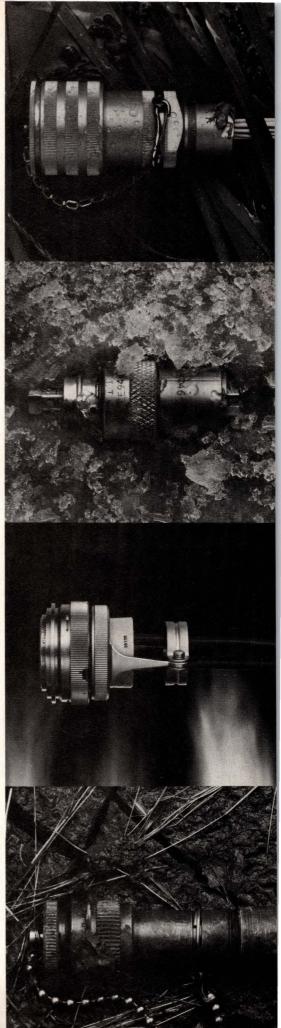So when your connectors must survive a hostile firewall environment, look to ITT Cannon Electric Canada for the right tactics. For technical information, contact ITT Cannon Electric Canada, a division of ITT Canada Limited, Four Cannon Court, Whitby, Ontario, Canada LIN 5V8. (416) 668-8881. Telex: 06-981357.





CMOS IS THE WAY HARRI

HE WORLD IS GOING. S ALREADY THERE.

Harris recognized the enormous potential of CMOS in 1971, and has pioneered this low power technology with an impressive list of Harris CMOS "firsts":

- First 4K CMOS RAM
 - First 4-inch CMOS wafers in production
 - First CMOS PROM
 - First 64K CMOS RAM module Choose from these proven Harris performers today:
 - CMOS RAMS 64K Module — $8K \times 8$ $4K - 1K \times 4$ $16K \times 4$


 - CMOS Microprocessors $4K \times 1$ $1K - 1K \times 1$ 6100 Family 256×4
 - **Peripheral Circuits**

Look for these exciting Harris developments tomorro

- 16K CMOS RAM HM 6516
- 8K CMOS EPROM HM 6758
- 4K CMOS PROM HM 6641
- 16K CMOS EPROM HM 6716

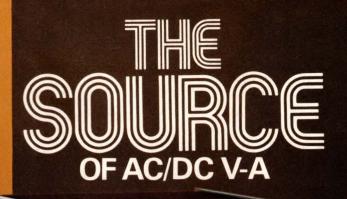A decade of technological innovation and proven performance make Harris today's recognized leader in CMOS technology — delivering years-ahead products at down-to-earth prices. Call the Harris Hotline: 1-800-528-6050, Ext. 455, for Authorized Distributor or Expedited Literature Service. Or, write: Harris Semiconductor, Dept. 53-035A, P.O. Box 883, Melbourne, FL 32901.







For high accuracy supply of AC/DC Voltage and Current

RFL's <u>new Model 828 is a</u> source of AC and DC Voltage and Current, it accurately and efficiently calibrates analog and digital meters, and is suitable for production line or field use.

FEATURES

Digital Thumbwheel Switches quickly set up output current and voltage.

Percent Error Control provides for rapid determination of error of meter under test.

Run-Up Control varies output from 0-100% to check for sticky meter movements.

Automatic protection against output short circuits and overloads.

High output stability over all ranges.

SPECIFICATIONS

Outputs: 1 Millivolt to 1100 Volts 1 Microampere to 5 Amperes Accuracy: DC Voltage ±0.05% of setting ±0.05% of range AC Voltage ±0.05% of setting±0.10% of range AC/DC Current ±0.10% of setting ±0.10% of range

Voltage Burden: 5 VA on 1 Volt Range; 10 VA all other Ranges. Current Compliance: 5 Volts up to 1 AMP 1 Volt on 5 AMP Range Percent Error Control: $\pm 2\%$ of setting Output Frequencies: 50, 60 and 400Hz Power Requirements: 100-230 Volts 50/60Hz

RFL Industries, Inc. INSTRUMENTATION DIVISION Boonton, N.J. 07005 • Tel: (201)334-3100

TWX: 710-987-8352 • Cable: RADAIRCO, N.J. For more information, Circle No 11

Signals & Noise

The real breadwinner in the power-FET market Dear Editor:

Congratulations to Bill Twaddell for his well-researched and -documented survey on power FETs (EDN, December 15, 1980, pg 116).

However, Bill's survey (like others on this subject) overlooked the real "jellybean" market for power FETs. Even though high-voltage, highcurrent and high-power devices provide the glamour and excitement, the dramatic growth in bookings, billings and profits currently lies with the industry's replacement of the ubiquitous 2N2222—a lowvoltage, 500-mA, TO-92-style, n-channel enhancement-mode MOSFET.

Given the numerous benefits expounded by Bill's article for using power FETs, we at Siliconix were both surprised and pleased that with all the competitors entering the field, Siliconix alone offers the designer a viable option to the 2N2222—the VN10KM.

Even with this oversight, Bill's article is excellent. Sincerely, Ed Oxner Staff Engineer Siliconix Inc Santa Clara, CA

Firms can cheaply upgrade CRT terminals

Dear Editor:

EDN's November 20, 1980 editorial, "Only the strong will survive," gave designers bad advice when it suggested that new CRT terminals should "incorporate only those features that customers really want and need." If manufacturers built only "plain-Jane" terminals, *Continued on pg 28*

IT'S A BETTER 6-BIT ADC FROM START TO FINISH.

If you're looking for a 6-bit A/D converter with super speed and super specs, check the ''performance chart'' on our new AD6020. At 50 MHz, it's twice as fast as the competition's fastest, and at \$84 (in 100's) it's also less expensive.

if you need even greater speed, try our AD5010. At 100 MHz, it's ultra-fast! Both ADC's are ideal for applications that require digitizing of high

fre-

quency

PERFORMANCE CHART

	Analog Devices' Winner	TRW's Entry
Word rate	50 MHz	25 MHz
Power dissipation	450 mW max	750 mW max
Size	16 pin DIP	24 pin DDIP
Conversion time	20 ns	70 ns
Aperture jitter	25 ps	30 ps
Overflow	Yes	No 🤺 🥳
100's price	\$84	\$93
100 MHz available	Yes	No

signals, such as in radar and X-ray equipment, medical systems such as ultrasound, and measurement instruments such as digital storage oscilloscopes and transient recorders. Both ADC's also include our unique overflow output feature, which allows you to place two units in cascade for 7-bit resolution, or four units in cascade for 8-bit resolution. And each is available with its own evaluation board, which includes oncard registers, regulators, clock, and DAC for easy and complete analysis.

For more information on any of our high-speed ADC's, or if you have a special highspeed ADC requirement, call Arnold Williams at (919) 292-6427.



WAYOUT IN FRONT.

Analog Devices, Inc., Box 280, Norwood, MA 02062; East Coast: (617) 329-4700; Midwest: (312) 894-3300; West Coast: (714) 842-1717; Texas: (214) 231-5094.

Burndy's new GTH[™] based IDC II Ribbon Cable Connector System:

Good as gold...



at a fraction of the cost.

Our new GTH-based IDC II connectors deliver everything you've ever wanted in a ribbon cable interconnect system: convenience features. Ease of installation. Lowest installed cost. And most important – the reliability of gold without the high cost of gold.

That's because our GTH-based IDC II system completely eliminates the need for gold – in both the connector and the circuit board – without sacrificing reliability! That can mean a 33% cut in connector costs alone. Add to that the savings you enjoy by eliminating gold on the circuit board and you're talking about savings of 60% and more. And you get all this in addition to all the convenience features you've always wanted in an IDC connector.

So why settle for less in an IDC ribbon-cable connector system when you can have it all – and save money, too! Check our performance data. Then check our prices Call me for quick action Or write: Jack

prices. Call me for quick action. Or write: Jack Miller, VP Marketing, Components Group, Burndy Corporation, Norwalk, CT 06856.



Proof of Performance* (Contact Resistance based on #28 AWG Str.)

		Milliohms				Milliohms	
Conditioning	Min.	Max.	Avg.	Conditioning	Min.	Max.	Avg.
Test Group 1			and the second	Test Group 3			and the
Initial C.R.	5.37	6.25	5.54	Initial C.R.	4.83	5.62	5.07
After Durability (25 Cycles)	5.73	7.28	6.32	After Thermal Shock	5.08	6.61	5.55
After Durability (50 Cycles)	6.39	12.43	7.84	Test Group 4			
Test Group 2				Insulation Resistance (1.000 VAC for 1 Minute)	>7x104	>8x104	>7.5x10
Initial C.R.	4.74	6.42	5.23	Dielectric withstanding Voltage	AND IN THE		
After Vibration & Shock	5.06	7.69	5.55	(No Breakdown @ 500 VAC)	1 1 10.5	PASSED	
After Humidity	5.18	14.50	6.46	*Write for complete test data			

IDC II connectors available through your local Burndy Distributor.

POWER SQUEEZE?

ARNOLD POWER SUPPLIES GIVE YOU BIG PERFORMANCE FOR SMALL SPACES!

If you're caught in a power squeeze, put the problem in our hands. Our high reliability switchers pack up to 400 watts of power into a miniaturized encapsulated package (up to 4 watts per cubic inch). You can choose from hundreds of single or multiple output versions right out of our catalog...without engineering charges or lost design time. And they're built tough enough to pass MIL-STD environmental tests per MIL-STD-810 and MIL-E-16400.

Standard unit highlights:

- Inputs—Single or dual—
- AC: 47 to 500 Hz DC: 12, 28, 48, 115 VDC
- Outputs—1 to 10 isolated— 3 to 300 VDC (400 watts total) Up to 35 amps
- Efficiencies to 80%
- Conduction cooled—no air flow required!
- 100% Burn-In Tested

28

If you need a powerful, reliable power supply,

and space is tight, come to Arnold Magnetics! Call or write for more information today.



Signals & Noise

competition would exist only at the cheapest, me-too level.

If you design a CRT terminal wisely, you can add a dozen or so features for very little extra cost—just pack the power of software into the inexpensive RAM and ROM. Then, when you put the product on the market, one or more of those bells and whistles might just give your unit the selling edge over your competitors.

Of course, this strategy backfires if the extra features cost too much and/or if they stretch out the unit's engineering design cycle to the point that the competition beats you to the market. Still, these design challenges offer sales rewards that justify the extra effort it takes to succeed.

Sincerely yours, R C Nocella Natick, MA

(Ed Note: Mr Nocella's points are well taken. However, adding extra features at minimum cost is indeed a tough design task. Moreover, large competitors, if they capture a significant market share, will enjoy significant economies of scale. This imbalance will force smaller companies to seek narrow market niches, servicing specific customer groups that will pay only for specific combinations of product features and capabilities.)

ls it an analog or digital world?

Dear Editor:

Jim Williams's article, "A few proven techniques ease sinewave-generator design," (EDN, November 20, 1980, pg 143) was very informative but a little disappointing—it made no mention of the digital generation of sine waves.

Because we live in a digital world, this important technique for generating high-quality, low-frequency sine waves (*IEEE Transactions on Instrumentation and Measurement*, Vol IM-18, June 1969) should not be sacrificed to appease the analog gods.

Very truly yours, William D Kraengel Jr Valley Stream, NY

Author's reply

Mr Kraengel is obviously misinformed—the *real* world is analog. Besides, one good op amp is worth a thousand microprocessors. Jim Williams

Editor's addendum

Add another operating system to EDN's µC Operating Systems Directory (November 5, 1980, pg 301). SDS/DOS from Scientific Data Systems Inc meets development- and general-purpose OS requirements. The software aims at 6502 8-bit CPUs using a 6502 macro assembler, extended BASIC and a data-management system. Available since June 1977 at a cost that depends on configuration, it resides in 32k bytes of RAM and on a 1.25M-byte diskette. Network support includes file transfers via RS-232C and a proprietary SDLC setup of as many as 255 nodes over a 1-km coaxial cable. For a listing of the OS's peripheral-, memory- and filemanagement capabilities, as well as other key characteristics, Circle No 370 or contact the firm directly at 344 Main St. Venice, CA 90291; phone (213) 390-8673.




Make your system safe from faults with our four-way monitor

Our new SG1547 provides all the functions necessary for monitoring multiple power supplies. This compact IC can monitor three DC supply voltages for over- and under-voltage faults and simultaneously monitor an AC line for brownout conditions. Programming total power supply fault tolerance from 0% to 25% is easy, requiring just one external fixed resistor. Externally-programmable filter and delay circuits eliminate false fault reports. Built-in hysteresis on all comparators assures clean transitions without oscillation.

The SG1547 lowers design and manufacturing costs and improves reliability by eliminating many of the components associated with power monitoring. An internal reference, trimmed to 1% tolerance, eliminates many adjustments as well. The separate under-voltage, over-voltage and line fault outputs all feature high sink current and can be pulled up to 40V or be used directly to drive 5 TTL loads . . . with no external resistors.

TYPICAL MONITORING CONFIGURATION

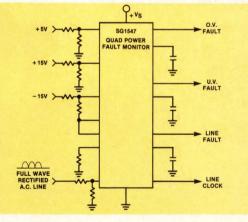

SEND FOR PROTECTION NOW

I WANT PROTECTION Send SG1547 applicat and technical specificat	
Send FREE evaluation Send FREE Silicon Ge	
Name Company	Title
	Mail Sta
	State Zip
Telephone ()	

Available in 16-pin Cerdip.

- SG1547 (-55°C to +125°C)
- SG2547 (-25°C to +85°C)
- SG3547 (0°C to +70°C)

Silicon General

Silicon General, Inc., 11651 Monarch St. Garden Grove, CA 92641, (714) 892-5531 TWX: 910-596-1804, Telex: 69-2411

the power in power control IC's

EDN FEBRUARY 4, 1981

The Minifloppy tradition. The standard is set for highperformance 96 TPI Minifloppys. And it's by Shugart. Double track and double density, the single and double-sided SA410 and SA460 Minifloppys deliver .5 or 1 MBytes of unformatted capacity on a 5¼-inch diskette. Small wonder. Designed by the company that invented the Minifloppy, the SA410 and SA460 represent the culmination of all previous 5¼inch disk drive technologies. What you get today is the most thoroughly engineered, most manufacturable, and most reliable Minifloppy drive available. The SA410/460 are the new standard in the eighties for price, performance, and capacity.

Shugart introduces of Minifloppys.

TPI

shugart

Step into the future. Innovation, experience, and proven performance have always been the hallmark of the Minifloppy tradition. And the SA410/460 are the first of the next generation in that tradition. Utilizing technology proven in our 8-inch disk drive products, the SA410 and SA460 use a multi-step positioning technique, thus eliminating pole asymmetry, an inherent source of positioning errors and degraded performance. The simplicity of this multi-step positioning motor and the HeliCam lead screw follower insure its manufacturability, consistent high performance, reliability, and low cost.

Trademark of Shugart Associates

Positioned for success. Shugart's new HeliCam[™] positioner delivers far greater accuracy than that of competitive actuators. The result is super precise positioning tolerances that virtually eliminate the problems of media interchange previously associated with 96 TPI 5¼-inch technology. The HeliCam solution means that you can reduce, by a significant margin, data handling errors—especially between systems in less than ideal environments.



¹⁰⁰⁰K6ytes

500 KBYIes

500 KBITes

the next generation SA410/460.

A new era starts today. Our commitment to the 5¼-inch disk drive market is driven by your requirements for low cost, highly reliable disk drive solutions. With unmatched commitments in manufacturing and R & D resources, we're dedicated to delivering innovative, standard-setting products that meet your needs — both today and tomorrow. And we back all our products with superior technical support, design assistance, and in-depth documentation. Call today. We'll be delivering in production volumes by early 1981. □ Shugart Associates: 475 Oakmead Parkway, Sunnyvale, CA (408) 733-0100. Sales & Service: Sunnyvale, CA; Costa Mesa, CA; Minneapolis, MN; Richardson, TX; Framingham, MA; Mt. Freedom, NJ; Atlanta, GA; Toronto, Ontario; Paris, France; Munich, Germany. □



The next generation is here.

EDN FEBRUARY 4, 1981

Free software (\$50-\$120 worth). Plus a cash rebate when you buy the programmable.



Free software plus cash rebates. A \$10 rebate on a TI-58C--\$25 rebate on a TI-59.

The TI-58C. An exceptional value. Up to 480 program steps or 60 memories. Plus Constant Memory[™] that retains data when turned off. \$130.

The TI-59. Top-of-the-Line.

Up to 960 program steps or 100 memories. Magnetic card read/ write capability. \$300.

Modules turn a programmable into a dedicated calculator. Pakettes have selected programs you key in. ALTERNATE ______ ALTERNATE _____ Send to: Texas Instruments Free Software Offer P.O. Box 725, Dept. M, Lubbock, Texas 79491 EDN Name Address City State Zip

Calculator Serial Number (from back of unit)

Return this coupon with (1) Customer Information Card (packed with calculator), (2) Dated copy of proof of purchase between January 1, 1981 — March 31, 1981. Items must be postmarked by April 14, 1981. Please allow 30 days for delivery. Offer void where prohibited. Offer good in U.S.A. TI reserves the right to substitute items. See your TI Dealer for complete details.

U.S. suggested retail prices. * For use with TI-59 only.

TEXAS INSTRUMENTS

© 1981 Texas Instruments Incorporated

45746A





Robots—Promise and peril

The headline of a recent short Associated Press news report was certain to capture any EE's attention: "Test robot attacks itself, suffers dislocated shoulder."

The story explained how a \$50,000 aluminum robotic arm went out of control and slammed itself into its supporting stand before the man controlling it could hit the Kill switch. "Luckily, nobody was in its reach or grasp," said the controller, a graduate student in the

University of Florida's Mechanical Engineering Dept. Indeed, luck was the student's ally, because the arm, measuring 5 ft long and weighing 70 lbs, could have inflicted serious injury if a person had been in the wrong place at the critical moment.

The incident, attributed to a hardware failure, "pointed out the dramatic need to us for robotic safety devices. As of now, there's really no way to prevent injury if a failure occurs," claimed the student.

What a chilling thought! Robots are widely touted as a promising solution to the US's productivity crisis, and research and development of industrial robots is accelerating rapidly. Indeed, many engineers will find challenge and opportunity in designing robots of all types.

Perhaps, then, the timing of the University of Florida accident was fortuitous, because it can serve to reawaken engineers to the fact that their creations can malfunction, creating problems ranging from mere inconvenience to life-threatening disasters.

Devotees of science fiction have undoubtedly read many novels describing the awesome consequences of robots running amok. Well, robots are no longer a dream of the future. And their arrival gives new meaning—and urgency—to fail-safe engineering.

Net let

Walt Patstone Editor

An Award*. Winning Magazine 1978 Staff-Written Series — System Design Project 1978 Contributed Series — Designer's Guide to Fiber Optics 1977 Contributed Series — Software Design Course 1976 Special Issue — Microprocessor Reference Issue 1975 Staff-Written Series — Microprocessor Design Series

*Jesse H Neal Editorial Achievement Awards are the business-press Pulitzer Prize equivalent.

Are you still design nin g with needie meters

Why short change yourself on product appearance? Or panel-meter reliability? Bowmar Solid-State Analog Panel Meters are light-years ahead of needle-type meters. Trim, compact, up-to-the-minute in styling, Bowmar meters with bright LED bargraph and setpoint displays provide accurate information at a glance. 2.5 millisecond response time, one percent



accuracy. They're immune to vibration and impact shock. They



Staff

Executive VP/Publisher

H Victor Drumm **Editorial Director** Roy Forsberg Editor Walt Patstone Managing Editor

Jordan Backler

Assistant Managing Editor **Bob Peterson**

Special Features Editors Bob Cushman, Jim McDermott **Editorial Staff**

George Kotelly, Senior Editor Tom Ormond, Senior Editor George Huffman, Associate Editor Rick Nelson, Associate Editor Edward Teja, Associate Editor Jesse Victor.

Assistant/New Products Editor Joan Morrow, Assistant Editor Ann Rogers, Assistant Editor Dale Zeskind, Contributing Editor

Editorial Field Offices Andy Santoni, Western Editor John Tsantes, Eastern Editor William Twaddell, Western Editor Carl Warren, Western Editor

Consulting Editors Jack Hemenway, Carol A Ogdin, **Robert Pease**

Editorial Services Carol Murray, Susan Rabinovitz, Carole Smith (Text processing) Art Staff

Daniel S Kicilinski, Director Vicki Blake, Assistant Wasyl Bidalack, Illustrator Joan Joos, Illustrator Susan Barrow-Williams, Illustrator

Production/Manufacturing Staff William Tomaselli, Production Supervisor

Evelyn Erwin, Production Assistant Diane Malone, Composition

Graphics Director Lee Addington **Production Director** Wayne Hulitzky

Marketing Communications Manager Alan Bergstein

Promotion Manager Ann Nickolds Senior Circulation Manager Earl Moslev

Research Director Ira Siegel **Editorial Consultant** John Peter

Editorial Office Addresses Boston (617) 536-7780, 221 Columbus Ave, Boston, MA 02116. Washington, DC Area (703) 379-1415, Box 11141, Alexandria, VA 22312. San Francisco (408) 296-0868, Sherman Bldg, 3031 Tisch Way, Suite 1000, San Jose, CA 95128. Los Angeles (714) 851-9422, 2021 Business Center Dr, Suite 208, Irvine, CA 92715.

Reprints of EDN articles are available on a custom printing basis at reasonable prices in quantities of 500 or more. For an exact quote, contact Art Lehmann, Cahners Reprint Service, 5 S Wabash, Chicago, IL 60603. Phone (312) 372-6880.

SIEMENS

Maxi-Mini[™]5¼" floppies score with immediate delivery.

Sports or business—winning demands quick reaction. That's what you get when you turn to Siemens for 51/4" Maxi-Mini drives, available for immediate delivery. You can count on Siemens drives for long-term reliability—and on the Siemens team for prompt service and total technical support.

Siemens 5¼" floppies feature anti-crunch diskette protection, precision metal lead screw for track-to-track head positioning, plus 20 ms step time. 125k byte capacity with 40 tracks; 500k byte capacity with 80 tracks. And industry compatibility.

When you turn to Siemens, you turn to the world's 5th largest electronic/electrical engineering company—which backs our team with more than \$6 million in R&D each working day. In the U.S. alone, Siemens employs more than 12,000 people in 15 manufacturing plants, two R&D facilities, and sales/service offices covering all 50 states.

Siemens—high technology with highly competitive pricing. Just ask for a quote and see for yourself. Find out how Siemens responds to your floppy disk needs. Call Barrie Clark at (714) 991-9700.

For more information, Circle No 18


Siemens Corporation

OEM Data Products Division 240 East Palais Road, Anaheim, CA. 92805 Telephone (714) 991-9700

District Offices:

Atlanta, GA	(404) 451-8157
Boston, MA	(617) 444-6580
Columbus, OH	(614) 888-3372
Dallas, TX	(817) 461-1673
Iselin, N.J.	(201) 494-5311
Sunnyvale, CA	(408) 735-7770

Siemens: Engineering Winning Drives.

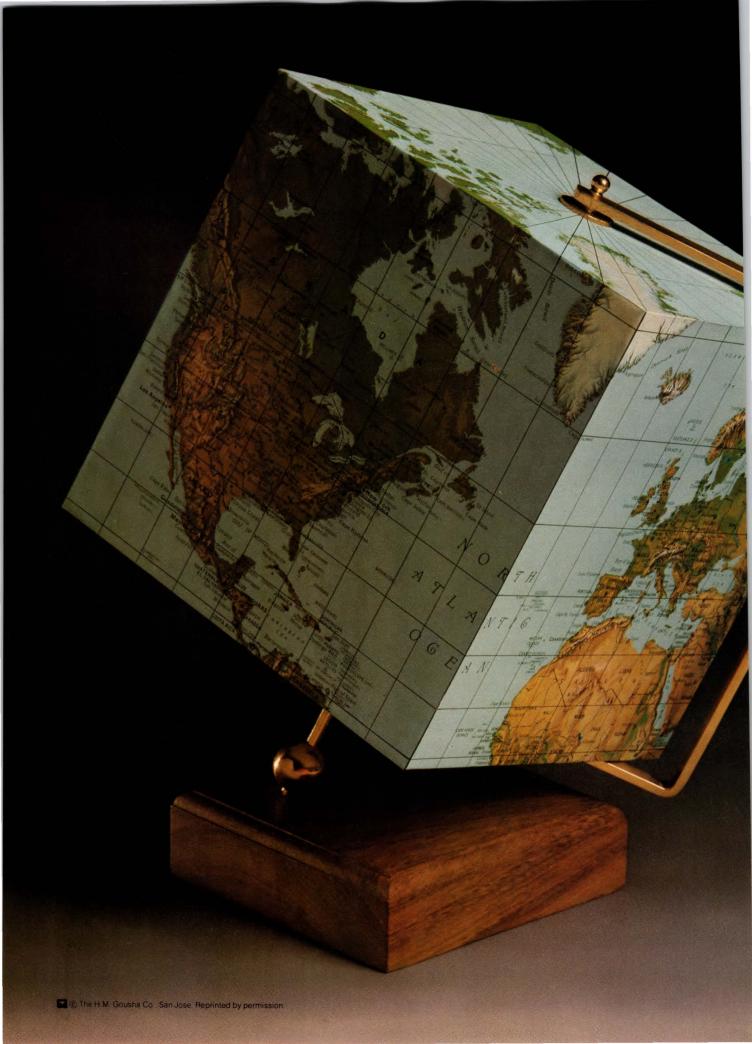

When C. Columbus challenged the status quo, a surprising thing happened to our world.

Surprising things do happen when people challenge the status quo. And often, good things happen as a result.

HP would like to ask you to challenge the status quo . . . in oscilloscopes. You may discover some pleasant surprises, and displace some earlier disappointments too. Because, like the shape of the 15th century world, HP Oscilloscopes have changed . . . dramatically. Here's how:

Triggering. Today, HP Oscilloscopes offer excellent triggering on difficult signals because of HP advances in microcircuit design. That also means triggering that's essentially unaffected by changes in trace position or temperature variation. Third channel trigger view, on many HP scopes, lets you see the fidelity of the triggering waveform, and also make timing measurements from it.

Reliability. You've told us you wanted improved reliability. We listened. The result is improved MTBF. Today, thousands of quality 1700 Series Oscilloscopes are delivering the reliable, dayto-day performance you expect from HP. Signal fidelity. With most scopes,

matching input impedances requires an external 50 Ω termination. On the HP 1700 Series, and our new fully programmable 1980 Oscilloscope Measurement System, switchable 50 Ω input terminations are built in to insure faithful reproduction of input signals

Value, Put a 1700 Series Oscilloscope next to any comparable general-purpose scope of your choice

> N C

and compare the price/performance ratio for yourself. Because HP designs and builds the critical components, you get quality performance. Many HP scopes have Delta Time capability that provides fast time interval measurements while minimizing errors. The 1743A incorporates HP counter technology for precision and semi-automatic timing measurements. For viewing low-rep-rate signals and singleshot events, HP's 1741A, 1744A, and 1727A Storage Oscilloscopes, with fast writing, integrating, variable persistence operation, provide well-defined, easily viewed traces in applications which may otherwise result in annoving flicker, or require a viewing hood or camera. What's more, with HP's storage technology there is no transfer time or reduction of variable persistence writing speed, so you won't miss the signals vou're after.

See for yourself. HP scopes have changed. And you owe it to yourself to challenge the status quo before you buy another general-purpose oscilloscope. But don't take our word for it. Call an HP Field Engineer for a hands-on demonstration of a new 1700 Series Oscilloscope. Then judge for yourself. Ask about the

1980 Oscilloscope Measure-



ment System, too. Find out how its fully programmable operation can help you deal with some of today's productivity problems. 081/1

Challenge the status quo and get a square-world mug. Free.

If you're considering the purchase of an oscilloscope, call an HP Field Engineer or use our coupon for a no-obligation demonstration. In return, we'll give you a distinctive square-world coffee mug.



For more information, Circle No 19

I would like to challenge the status quo. Contact me for a no-obligation demo of an HP EDN 2/4 Oscilloscope. And yes, I want a square-world mug.

NAME	TITLE
COMPANY	
PHONE	
ADDRESS	
CITY/STATE	

□ Yes □ No I initiate and/or approve oscilloscope purchases

Mail coupon to: Hewlett-Packard, P.O. Box 2197, Colorado Springs, CO 80901, Attn: Oscilloscope Marketing Manager. Offer expires April 30, 1981. Valid in U.S.A. and Canada only.



Every day, we produce over 5,000,000 KEMET Capacitors. So you can have the exact one you need when you need it.

The KEMET[®] Capacitor worldwide manufacturing network assures you of getting the right capacitor you need for every system design — from electronic toys to space shuttles.

And, since we produce over 5,000,000 pieces per you can always depend on the right quantity day, of KEMET Capacitors to meet your own

production schedules.

Union Carbide makes more tantalum capacitors

Union Carbide is the world's largest producer of solid tantalum capacitors. But volume is not our main


concern — high quality and performance are. When you specify KEMET tantalums, you get top-quality products for coupling or decoupling, blocking, bypassing, filtering and timing circuits.

KEMET tantalum capacitors are produced with your designs in mind. In standard and microminiature sizes — molded, dipped or hermetically sealed, with axial or radial leads. Or in space-saving chips. With a capacitance range from .001 to 1200 μ F, in voltages from 2 to 125 VDC, and operating temperatures from -65°C to +175°C

And now KEMET dipped and molded tantalum capacitors are available to meet the full requirements of MIL-C-49137!

Union Carbide makes high quality ceramic capacitors

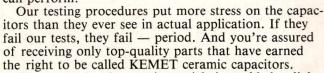We've learned a lot about monolithic ceramic capacitors since we entered the industry in 1968, especially how great they can perform.



You can order the genuine article in molded radial and axial leaded forms, "Blue Max" dipped and molded "Mighty Max" two-pin dual-in-line packages, and space-saving "Solder Guard" chips. Choose from ultrastable NPO and COG; stable BX, BR and X7R; and general-purpose Z5U dielectrics.

They are available in capacitance ranges from 1 pF to 6.8 µF in 50, 100 and 200 volt ratings, and operating temperatures from - 55°C to +125°C.

Union Carbide makes high-21/01performance thin-film capacitors

KEMET precision thinfilm capacitors offer outstanding volumetric efficiency and high performance.

KEMET thin-film capacitors give you a choice of metallized polycarbonate or parylene film dielectrics - in capacitance ranges from .001 to $47.0 \,\mu\text{F}$, in voltages from 30 to 400 VDC, and operating temperatures from -55°C to +125°C And they're available to meet MIL-C-55514,

-83421 and -39022 specifications.

Union Carbide is committed to the industry



Our five plants in the Greenville, South Carolina, area provide you with 450,000 square feet of the most modern, automated production and office facilities in the nation. We also have plants in Columbus, Georgia; Greenwood, South Carolina; Matamoros, Mexico: and Darlington, England. But they are not enough.

As the industry grows, so must we. New plants are now on the drawing boards, to permit us to meet your ever-increasing demands for high-quality KEMET capacitors. That's our commitment to you.

For prompt delivery of solid tantalum, monolithic ceramic and precision thin-film capacitors...KEMET offers you more!

For more data, write to the Electronics Division, Union Carbide Corporation, Box 5928, Greenville, SC 29606. Phone: (803) 963-6300; TWX: 810-287-2536; Telex: 57-0496. Or see your local KEMET representative.

See EEM for KEMET Capacitors General Catalog.

ELECTRONICS DIVISION UNION CARBIDE COMPONENTS DEPARTMENT

KEMET is a registered trademark of Union Carbide Corporation. In Europe: Union Carbide Europe, S.A., 5, Rue Pedro-Meylan, Geneva 17, Switzerland, Phone: 022/47 4411. Telex: 845-22253. Union Carbide U.K. Limited, Phone: 0325-315181.



For more information, Circle No 20

Leadtime Index

PASSIVE COMPONENTS

PRODUCT	LEAD Min.	Max.	WEEKS Trend	PRODUCT	LEAD Min.	DTIME IN Max.	WEEKS Tren
CAPACITORS				PRINTED CIRCUITS			an.
Ceramic, disc	7	15		Single-sided	5	10	-
Ceramic, monolithic	8	21	=	RELAYS AND TIMERS			
Electrolytic, aluminum	5	14	=	Crystal can	6	20	
Electrolytic, tantalum	7	16	-	General purpose	5	17	_
Film	7	16	-	Miniature (TO-5, square)	8	15	_
Mica	8	22	=	Reed, dry	6	11	=
Paper	4	16	=	Reed, mercury-wetted	5	9	-
Trimming	9	15	4	Solid state	5	14	_
CRYSTALS, FILTERS AND N				Telephone	8	13	_
Filter, active	13	17	=	Time delay and timer	6	13	_
Filter, EMI	8	16	_	RESISTORS, FIXED	U	15	
Filter, lumped-constant	6	14	_	Carbon film	2	15	
Filter, quartz (monolithic)	13	21	=		3	15	=
Freq. determining crystal	7	14		Composition Motel film	6 6	18	=
ENCLOSURES		14		Metal film		16	=
Custom	0	•		Network	8	14	=
	6	9	=	Wirewound	6	16	=
Modified standard	7	10	=	RESISTORS, VARIABLE			
Standard	6	9	-	Pot, nonprecision WW	4	14	=
FANS AND BLOWERS	16	26	=	Pot, precision WW	6	10	=
FRACTIONAL HP MOTORS	17	20	=	Pot, nonprecision comp.	7	15	=
INDUCTIVE COMPONENTS		-		Pot, precision comp.	6	10	=
Coil	11	15	=	Trimmer, WW	6	11	, =
Solenoid	7	12	=	Trimmer, comp.	9	11	=
Transformer, power	9	12	-	SWITCHES AND KEYBO	ARD	S	
Transformer, other	9	12	+	Circuit breaker	8	14	up
INTERCONNECTION COMPC	NEN	TS		Dual in-iine	6	10	=
Back panel	8	16	=	Keyboard and keyswitch	7	11	=
Flat cable	20	29	=	Lighted pushbutton	6	18	-
Multipin circular high-density	25	37	=	Pushbutton	5	16	=
Multipin circular standard	18	37	=	Rotary	4	12	
Packaging panel	8	13	=	Snap action	5	9	=
PC, one-piece	5	15	=	Thumbwheel	3	10	=
PC, two-piece	5	15	=	Toggle	6	14	=
Rack and panel	11	34	=	TRANSDUCERS			
RF coaxial	15	32	-	Pressure	6	15	=
Socket	3	14	=	Temperature	6	12	=
PRINTED CIRCUITS				WIRE AND CABLE			
Double-sided	6	10	=	Coaxial cable	8	12	-
Flexible	6	14	=	Flat and ribbon cable	5	10	up
Laminates	5	10	-	Hookup wire	6	10	=
Multilayer	8	11		Multiconductor cable	10	13	-

Leadtimes are based on recent figures supplied to Electronic Business magazine by a composite group of major manufacturers and OEMs. They represent the typical times necessary to allocate manufacturing capacity to build and ship a medium-sized order for a moderately popular item. Trends represent changes expected for next month.

Mepco/Electra Low Cost Metal Film Resistors add dollars to your bottom line!

SFR 1% Metal Film Resistor

> SFR 2% Metal Film Resistor

Mepco/Electra's new SFR Resistors are designed to put maximum performance into your circuits while saving you as much as 50% on resistor costs!

That's the Mepco/Electra commitment to our customers. Through the most up-to-date technology Mepco/Electra keeps the cost down and passes the savings along to you. Our SFR Series is available off-the-shelf in $\pm 1\%$, $\pm 2\%$ and $\pm 5\%$ tolerances at ¹/₄ watt (70°C) power rating.

Designed for high volume manufacturing and ease of automatic insertion, the SFR 5043E provides an economic way to upgrade your circuitry. The SFR offers the superior stability, temperature coefficient, low noise and low reactance inherent in well designed metal film resistors.

The 1% tolerance SFR has a temperature coefficient of ± 100 PPM/°C and is designed for high volume ¹/₄ watt resistor applications

requiring RN 55 performance. The 2% and 5% tolerance SFR's have a temperature coefficient of ± 200 PPM/°C and are designed for replacement of carbon composition (RC07), and older design metal film resistors such as RL07.

SFR Series! Better than Military Performance (MIL-R-10509 RN 55). Compact construction for down to .400 centers (.260 inches maximum clean lead to clean lead). Color band marking for ease of identification after mounting. And tape and reel packaging for automatic insertion.

Add dollars to your bottom line ... For the lowest price and immediate delivery on your SFR Resistors rely on Mepco/Electra, your resistor/capacitor company.

For all your SFR Resistor needs call Don Freeman now at (817) 325-7871 or your local Mepco/Electra distributor.

MEPCO/ELECTRA, INC.

Your resistor/capacitor company with the technology of the 80's edge.

P.O. Box 760, Mineral Wells, TX 76067 (817) 325-7871 TWX 910/890/5855

© 1980 Mepco/Electra, Inc.

SFR 5% Metal Film Resistor

For more information, Circle No 21

Connector shopping for the very busy.

One-stop shopping to save your valuable time. One source to solve your design problems. One name to remember: Amphenol[®] Connectors.

Amphenol 48 Series Miniature Circular Connectors. Qualified to MIL-C-26500. Lightweight

Qualified to MIL-C-26500. Lightweight. Easy-assembly crimp-removable contacts. Front release. Bayonet or threaded couplings. Circle Reader Service Number 81

Amphenol 285 Series Modular Telephone Jacks. Mount on PC boards without adapters. 8position keyed or nonkeyed, or 6-position (4 or 6 contacts). Ring or spade lugs. PC tails or stripped ends. Circle Reader Service Number 82

Amphenol FCP-type BNC Plugs and Jacks.

Assemble faster, easier than standard BNC's. Only three parts (not six) to assemble. No special tools. Trim coax, solder center contacts, and slide parts together. For RG-58/59U and 62U cable. Circle Reader Service Number 83

Amphenol 223 Series Tiny Tim[®] Connectors.

For potted-in or surface-mounted circuits, or for microminiature rackand-panel, cable-to-cable, or cable-to-panel. Five to 33 contacts, polycarbonate or nylon bodies. Circle Reader Service Number 84 Amphenol 57 Series Micro Ribbon® Connectors. Fortelephony and EDP. Highcontact density (14 to 64). Protective polarized shell. Circle Reader Service Number 85

> Amphenol 157 Series Micro-Pierce®

Connectors. Fast, solderless termination in factory or field. Portable, easy-to-use termination tools. Intermateable with currently used connectors in telephony or EDP. Circle Reader Service Number 86

Amphenol 97 Series Standard Circular Connectors.

Time-tested, highly reliable. Non-rotating, pre-aligned contacts. Rugged, with diallyl phthalate inserts and molded barriers between each contact. **Circle Reader Service** Number 89

Amphenol 801 Series Fiber Optic Connectors.

Up to 8 individual channels. Low insertion loss Environmentally sealed. Speedy rear insertion/rear removal. Adaptable to multi-fiber bundles. Optional strain-relief mechanism. Circle **Reader Service Number 87**

agaggggg **Amphenol 225 Series** Printed Circuit Connectors. Low contact resistance. Slotted bellows or folded-ribbon soldertype contacts. Low-friction mating for repeated insertion and withdrawals. Rugged, one-piece bodies. Wide range of contact positions and terminations. Circle Reader Service Number 88

Amphenol 221 Series Strip Connectors. Low-cost miniatures. High contact density. And you can cut and/or stack them to almost any shape. Circle Reader Service Number 90

For more information, technical data, dimensions and prices, contact your nearest Amphenol North America sales office or distributor.

BUNKER RAMO

AMPHENOL NORTH AMERICA

See us at **NEPCON WEST** Booth 516 Anaheim Feb. 24-26

A Division of Bunker Ramo Corporation

Amphenol North America Division Headquarters: Oak Brook, Illinois 60521

 Sales Offices: Atlanta (404) 394-6298 + Boston (617) 475-7055 + Chicago (312) 986-2330 + Dallas (214) 343-8420 + Dayton (513) 294-0461

 Denver (303) 934-2355 + Greensboro (919) 292-9273 + Houston (713) 444-4096 + Indianapolis (317) 842-3245 + Kansas City (816) 737-3937

 Knoxville (615) 690-6765 + Los Angeles (213) 649-5015 + Minneapolis (612) 835-4595 + New York (516) 364-2270 + Orlando (305) 647-5504

 Philadelphia (215) 732-1427 + Phoenix (602) 265-3227 + St. Louis (314) 569-2277 + San Diego (714) 272-5451 + San Francisco (408) 732-8990

 Seattle (206) 455-2525 + Syracuse (315) 455-5786 + Washington, DC (703) 524-8700

 Canada: Montreal (514) 482-5520 + Toronto (416) 291-4401 + Vancouver (604) 278-7636 + International: Oak Brook, Illinois TELEX 206-054

Distributors:

ALABAMA Hall-Mark Electronics Corp. Huntsville (205) 837-8700

ARIZONA Cetec Moltronics (602) 272-7951 Wyle Distribution Group (602) 249-2232

CALIFORNIA Cetec Moltronic South Gate 213) 773-6521 Kierulff Electronics Wyle Distribution Group (213) 322-8100 Cetec Moltronics (714) 278-5020 Kierulff Electronics (714) 278-2112 Wyle Distribution Group **Cetec Moltronics** (408) 263-7373 Bell Industries (408) 734-8570

Western Electromotive (408) 727-7411 Wyle Distribution Group Schweber Electronics

(714) 556-3880 COLORADO Newark Electronics Denver (303) 757-3351 Wyle Distribution Group Thornton (303) 457-9953

CONNECTICUT Connector Company New Haven (203) 624-0127 Wilshire Electronics Wallingford (203) 265-3822

FLORIDA Arrow Electronics Palm Bay (305) 725-1480 Kierulff Electronics Schweber Electronics

Hollywood (305) 921-0301 GEORGIA Arrow Electronics Norcross (404) 449-8252

MASSACHUSETTS Kierulff Electronics ILLINOIS Bell Industries v) 935-5134 weber Electronics (312) 982-9210 Newark Electronics Onicago 312) 638-4411 Ohm/Electronics, Inc

KANSAS Wichita Aircraft

Wichita (316) 838-1421

MARYLAND Arrow Electronics

301) 247-5200 Hall-Mark Electronics

301) 796-9300 Pioneer Electronics

(301) 948-0710

617) 275-5100 Wilshire Electronics 617) 272-8200 ndustrial Components Corp 312) 359-5500 Schweber Electronics Gerber Electronics Klaus Radio, Inc. (617) 769-6000 309 691-4840

MICHIGAN RS Electronics Livonia (313) 525-1155 Wedemeyer Electronic

INDIANA Graham Electronic Supply Indianapolis (317) 634-8202 Genesis Electronics South Bend (219) 287-2911 Supply Ann Arbor (313) 665-8611 MINNESOTA

Edina (612) 830-1800 Newark Electronics (612) 331-6350

MISSOURI Valters Radio Supply, Inc. (ansas City 816) 531-7015 Dlive Industrial Electronics, Inc (314) 426-4500

NEW JERSEY Schweber Electronics Wilshire Electronics (201) 340-1900 Radio Electric Service Co.

(215) 925-6900

NEW YORK Harvey Electronics, Inc. Binghamton (607) 748-8211 Genesee Radio Parts Co., Inc. 3-9661

Summit Distributors (716) 884-3450 Arrow Electronics Progress Electronics Co (516) 433-1700 Schweber Electronics (516) 334-7474 Simcona Electronics Corp 716) 328-3230

NORTH CAROLINA Arrow Electronic Winston-Salem (919) 725-8711

OHIO Schuster Electric Co. 489-1400 er Electronics 216) 587-3600 chweber Electronics Beachwood (216) 464-2970 Pioneer Electronics Dayton (513) 236-9900

OKLAHOMA Electro Enterprises Oklahoma City (405) 478-1752

OREGON Bell Industries Lake Oswego (503) 241-4115

PENNSYLVANIA Almo Electronics Corp. Philadelphia (215) 698-4000 Pyttronic Industrial, Inc. Montonmersylle CAM/RPC Industries

Pittsburgh (412) 782-3770 TENNESSEE Electra Distribution Co. Nashville (615) 329-3971

TEXAS Hamilton/Avnet Electronics (214) 659-4111


Sterling Electronics 214) 243-1600 Texas Instrument Supply Co 214) 238-6821 Allied Electronics 817) 336-5401 Sterling Electronics 713) 627-9800 Hall-Mark Electronics (214) 234-7300

UTAH UTAH Diplomat Salt Lake City (801) 486-4134 Standard Supply Co. Salt Lake City (801) 486-3371

WASHINGTON Bell Industries Bellevue (206) 747-1515 Wyle Distribution Group (206) 453-8300

WISCONSIN Electronic Expeditors, Inc. Milwaukee (414) 228-8100

CANADA: Distributors in major cities

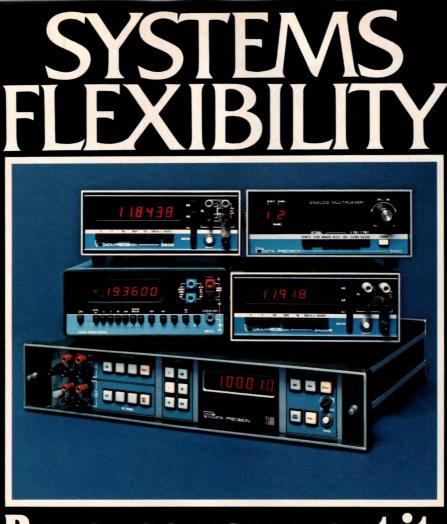

Because you want it.

Measurement, Source and Multiplexing Solutions for Your Systems Requirements

Not all systems requirements are the same. That's why Data Precision offers you a choice of instruments encompassing a wide selection of features, options and specifications. All accomplished without those burdensome customizing costs you're so familiar with.

For additional information or a demonstration contact Data Precision: (800) 343-8150, (800) 892-0528 in Massachusetts Measurement requirements can be met with a choice of $4\frac{1}{2}$ and $5\frac{1}{2}$ digit multimeters with basic accuracies of .007% and conversion speeds from 21/2 measurements/sec. up to 1000/sec. with full 51/2 digit resolution. You can choose a dedicated DVM or full function instruments with multiple ratio measurement. Programming can be accomplished through BCD, IEEE-488 or RS232 and resistance measured with either 2 or 4 wire. You can purchase only what you need now and extend your instrument's capability with field installable options later.

Source requirements, both voltage and current, can be met with our programmable calibrator which will generate a different voltage or current level every millisecond (including settling time). Accuracy is 10ppm for voltage and 100ppm for current with outputs of ± 100 nV to ± 100 V and $\pm 1\mu$ A to ± 100 mA. Capability can be extended with optional GPIB and ± 1000 V amplifier.

Multiplexing requirements can be addressed with our 8/16 channel analog multiplexer with automatic, remote, manual and slave scanning modes at rates up to 10 channels/ sec. Range is 1μ V to 250V.



Data Precision Division of Analogic Corporation, Electronics Avenue, Danvers, MA 01923, (617) 246-1600, TELEX (0650) 921819. For more information. Circle No 22

Small-disk-drive product advances promise tough design decisions

Carl Warren, Western Editor

If you're expecting halcyon days ahead for small disk storage systems, both good news and bad await you. A host of new products—some already introduced, others planned—could widen your design options and indeed signal the start of a Golden Age of disk-storage-system design. But incompatibilities among those products and a general lack of standards could also herald stormy design seas.

Since EDN's last update on this product area (May 20, 1980, pg 59), several innovative products have made their debuts, including Seagate (formerly Shugart) Technology's ST-506 Microwinchester 5.25-in. rigid-disk drive. This unit has sparked introduction of a host of similar ones, all designed to suit designers' supposed requirements.


As consultant Ray Freeman, president of Freeman Associates (Santa Barbara, CA), points out, the new small rigid-disk drives represent more of an advance in packaging than in technology. Consequently, approximately 17 companies are in the process of announcing or planning such products. Noteworthy among the first announcements are units from Seagate, Shugart Associates, Tandon, New World Computer, Irwin International and International Memories (**Table 1**).

OEMs' considerations

Choosing among the offerings from these firms (and others) will be no easy task. Jim Porter, author of *Disk Trend Report* (Mt View, CA), observes that large OEMs will require drives from sources that can produce at least 1000 units/month. But other factors, some more important, will also influence OEMs' choices:

- Pricing. This negotiable quantity will probably carry the most weight as an OEM narrows the choices (see **box**, "Pricing 5.25-in. rigid-disk drives").
- Capacity. The requirements for this parameter are heavily application dependent. It ranges from 1.8M to 11.5M bytes in currently available units.
- Second sourcing. This factor calls for compatibility, especially in interfacing.
- Access time. Like those for capacity, the requirements for

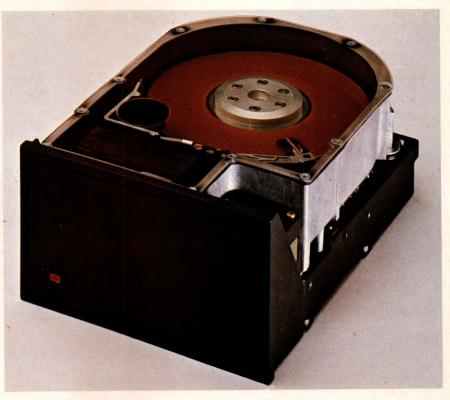Employing a plated medium, dual impellers and temperature-compensation circuitry, the International Memories 5000 Series 5.25-in. Winchesters will initially be offered with 7M-byte unformatted capacity.




Available in six versions, Tandon's TM 600 Series 5.25-in. Winchesters offer capacities ranging from 3.19M to 11.5M bytes. The units employ a rotary positioner.

TABLE 1-TYPICAL 5.25-IN. RIGID-DISK DRIVES


MANUFACTURER	MODEL	UNFORMATTED CAPACITY (MBYTES)	INTERFACE	PRICE AND AVAILABILITY	
IRWIN INTERNATIONAL 200 GREEN RD ANN ARBOR, MI 48105 (313) 663-3600	510	10 (FORMATTED)*	N/A	\$1500 (500) N/A	363
INTERNATIONAL MEMORIES 10381 BANDLEY DR CUPERTINO, CA 95014 (408) 446-9779	SERIES 5000	7 OR 14	SA1000 AND STD IMI UNIT	\$800 TO \$900 (1000) NOW	364
NEW WORLD COMPUTER CO 3176 PULLMAN ST SUITE 119 COSTA MESA, CA 92626 (714) 556-9320	MIKRO DISC V-1TF	1.8	UNDEFINED	\$900 (100) NOW	365
OLIVETTI PERIPHERAL EQUIPMENT 525 EXECUTIVE BLVD ELMSFORD, NY 10523	HD-561	6.38	MINIFLOPPY	\$720 (1000) MARCH (EVAL) AUGUST (PROD)	366
(914) 592-2864	HD-562	6.38'	MINIFLOPPY	APPROX \$850 (1000) MAX (EVAL) OCT (PROD)	
	HD-1512	11.72	BIDIRECTIONAL BUS	\$1230 (1000) JUNE (EVAL) MARCH '82 (PROD)	
SEAGATE TECHNOLOGY 360 EL PUEBLO RD SCOTTS VALLEY, CA 95066 (408) 438-6550	ST-506	6.38	SA1000	\$925 (1000) NOW	367
SHUGART ASSOCIATES 435 OAKMEAD PARKWAY SUNNYVALE, CA 94086 (409) 020 7547	SA602	3.33	SA1000 AND MINIFLOPPY	\$760 (500) APRIL (EVAL) JUNE (PROD)	368
(408) 939-7547	SA604	6.66	SA1000 AND MINIFLOPPY	\$980 (500) APRIL (EVAL) JUNE (PROD)	
	SA606	9.99	SA1000 AND MINIFLOPPY	\$1190 (500) APRIL (EVAL) JUNE (PROD)	
TANDON 9333 OSO AVE CHATSWORTH, CA 91311 (213) 933-6644	TM 601 TM 602 TM 603 TM 601E TM 602E TM 603E	3.19 6.38 9.57 3.83 7.66 11.5	SA1000 AND TM 100	LESS THAN \$1000 (1000) NOW	369

NOTES

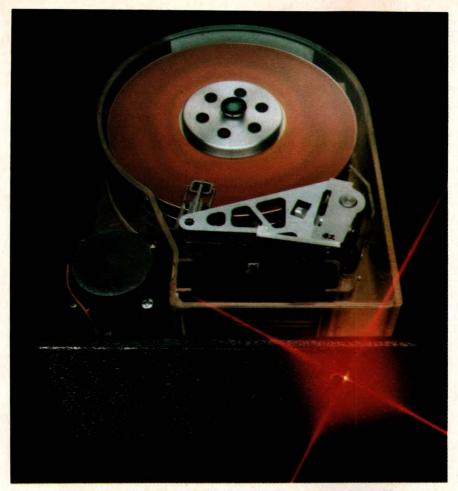1HAS FASTER STEPPING MOTOR THAN HD-561 AND ACHIEVES 35-mSEC AVERAGE ACCESS TIME 221-mSEC AVERAGE ACCESS TIME 1NCORPROATES 3M-TYPE MINI CARTRIDGE DRIVE FOR BACKUP



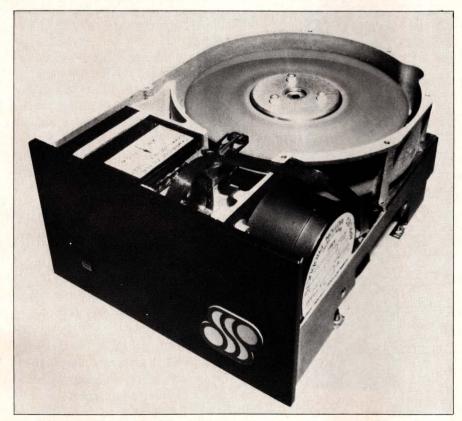With two interfaces (SA1000 and Minifloppy), Shugart Associates' Migid 5.25-in. Winchester drives incorporate electronic head-actuator damping to reduce head-mount flutter and thereby decrease head-settling time.



With an unformatted capacity of 6.38M bytes organized in 153 cylinders, Seagate Technology's ST-506 was the first 5.25-in. rigid-disk drive.

this quantity are application dependent.

• Vendor reliability.

Design differences

Although the 5.25-in. Winchesters from various manufacturers basically represent innovative packaging techniques, they exhibit some not-so-subtle technical differences as well. For example, Tandon's Models 601E, 602E and 603E (the E denotes "extended") are designed to use the entire disk surface, increasing the number of disk cylinders from 153 to 230 and providing a 20% jump in unformatted capacity compared with the firm's standard drives. The company achieves this advance by using a rotary actuator rather than a band device.


International Memories (IMI), on the other hand, employs a band actuator and a plated medium in its 7M-byte 5000 Series drive, slated for introduction this month. The drive, which will be expandable to 14M bytes, will be compatible with IMI's 8-in. units and will use dual impellers to cool the recording medium and electronics. It will also incorporate a temperaturecompensation circuit for the band actuator as part of the basic design; marketing VP Frank Iazzetta points out that temperature control can be one of the more troublesome areas in a Winchester design.

Illustrating other technical differences are devices from Shugart Associates. In its Mini Rigid Drive (Migid) 5.25-in. units, the firm employs dynamic braking and an electronic damper to improve head-settling time. The damper keeps the head mount (flexure) from fluttering while the head is accessing a track.

Possibly the most unusual design, though, comes from New World Computer Co. The \$900 (100) Mikro-Disc Model V-1TF is a modified version of standard Winchester designs, employing eight heads per data surface. These eight heads have simultaneous access to a portion of total storage equivalent to a Minifloppy 5.25-in. floppy-disk drive's capacity, permit-

TABLE	2 - SA1000-COMPATIBL	EINTERFACE	
HOST SYSTEM	FLAT RIBBON OR TWISTED PAIR, MAX 20 FT	ST-500	
A CONSIGNA	- REDUCED WRITE CURRENT	2	
	RESERVED (+5V)	4 3	
	– WRITE GATE	6	
	- SEEK COMPLETE	8 7-4	
	- TRACK 000	9-10	
	- WRITE FAULT	12 12	
E SAME	- HEAD SELECT 20	14 15	
	RESERVED (TO J ₂ PIN 7)		
	- HEAD SELECT 21		J ₁ /P ₁
	- INDEX	20	
	- READY	22 23	
	- STEP	24 25	
	- DRIVE SELECT 1	26 27	
	- DRIVE SELECT 2	28 29	
	- DRIVE SELECT 3	30 31	
and the second	- DRIVE SELECT 4	32 33	
	- DIRECTION IN	34 <u>I</u>	
	+ 5V DC		
	+5V RETURN	4	
A Constant	Q + 12V DC		J ₃ /P ₃
1 +	+ 12V RETURN	2	
DC			
GND FRAMEGND	OR LARGER)	GROUND	J ₄ /P ₄

TABLE 2 — SA1000-COMPATIBLE INTERFACE

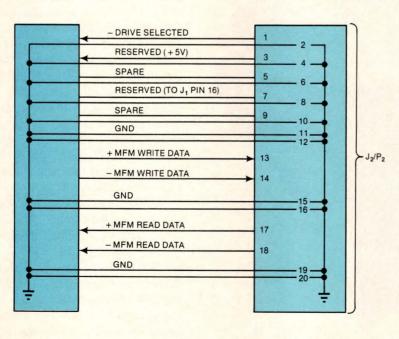

SOURCE: SEAGATE TECHNOLOGY

ting track switching within this logical space at electronic rather than mechanical speeds. The heads also move together mechanically to gain access to other Minifloppysized areas.

Although the drive's capacity is limited (1.8M bytes unformatted), the simultaneous access to a Minifloppy-sized storage space is a plus. However, the unit is a sole-source design—a potential drawback.

De-facto standard?

Because Seagate Technology was the first to announce a 5.25-in. rigid-disk drive, many observers believe the company has established a de-facto standard for the small-Winchester interface in its SA1000-compatible configuration (**Table 2**). Indeed, because of the firm's market lead, consultants like Freeman and Porter are advising their clients to opt for designs employing Seagate-lookalike interfaces. But that doesn't mean this interface is the only option.

Shugart Associates, for example, offers two interface choices in the Migid. One is an SA1000-type design similar to Seagate's but with pin 4 redefined for head select; the other supports the firm's Minifloppy and a Migid on the same daisy-chained line. Taking a similar approach with its TM 600 Series, Tandon offers SA1000an compatible interface in a pin-to-pin duplication of Seagate's and a Minifloppy interface as well.

With a horde of other 5.25-in. rigid-disk drives due to appear, other interface approaches are likely. Still, the Seagate/Shugart/Tandon approach will probably be the "standard" one, so you'd probably do well to follow Freeman and Porter's advice. Note, for example, that IMI's forthcoming drive will incorporate an SA1000compatible interface along with the firm's standard configuration.


Controllers are the key

Related to the problem of

the switch I pacitor filte (30-80% higher SPS efficiency.)

High-current limitar application For switching power supplies the evidence is conclusive. Where a filter capacitance of 50 mfd or less will do, metallized polypropylene (film) capacitors far surpass electrolytics in impedance characteristics.

EMI low-frequency Filter application

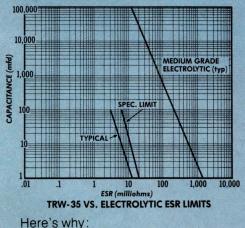

At resonance, ESR for a film capacitor is less than one-tenth that of an electrolytic. The film's

capacitance won't dwindle at higher switching rate frequencies, so you can design with a lower value cap.

With a constant 2 amp ripple current, a film cap will cut I2R losses - by orders of magnitude. Its current-carrying capacity is greater, so paralleling is usually not required. And ripple voltages are significantly less.

Film caps can be round or flatyou gain design versatility. And weight reduction: 16 grams/cu. in. vs. 26 for electrolytics. The bottom line: maximum current, minimum size and minimum loss.

At TRW, we're past pioneering a superior concept. We're delivering a buttoned-down product: the TRW-35 film capacitor is available now for input/output filtering in your state-of-the-art SPS design.

And, in addition, we offer a complete custom film package for your specific needs in the 40KHz and above SPS range.

ent DC blocking

Get the evidence in hand-send for the TRW-35 data sheet. And we'll provide you a reprint of the technical article that triggered the switch to a new SPS technology.

Send in coupon or call us at (308) 284-3611.

EDN-2 **TRW Capacitors** An Electronic Components Division of TRW Inc. 301 W."O" Street, Ogallala, Nebraska 69153 Please send data on your SPS Capacitors. Name Company Div/Dept Mail Code Address City State



interfacing the 5.25-in. drives is the design of their controllers. For although building a small rigid-disk drive apparently requires no technological breakthroughs, getting it to work *economically* in a variety of systems can present problems. Consequently, some observers believe that *cost-effective* controller design could be the one limiting factor on the growth of 5.25-in.-Winchester usage.


All of the drive manufacturers have been working closely with controller houses to develop adequate controller designs (**Table 3**). And two of these designs are especially interesting.

Xcomp's controller supports a variety of rigid-disk drives. In this 2-board design, the data-control board employs specialized TTL processor circuitry that supports an instruction set geared specifically to controlling disk drives. In it, a writeable control store permits downloadable fault-tolerance testing from the host. The second (drive-specific) board provides the actual interconnection to a drive; depending on model number, this board supports units ranging from 5.25-in. Winchesters to 14-in. cartridge drives.

Xcomp's Models ST/S and ST/R controllers serve the Seagate Technology ST-506 drive. The ST/S interfaces with the S-100 bus and is IEEE-696 compatible, while the ST/R isn't oriented to a specific bus and requires only line drivers and receivers for matching to one. Each unit costs \$980.

Another noteworthy controller is Alpha Systems' code-named "transformer," which is designed to plug directly into your current floppydisk-drive controller anywhere on the daisy chain in multidrive systems. It tricks a μ C system into viewing a 5.25-in. rigid-disk drive as the logical equivalent of approximately nine 40-track floppies.

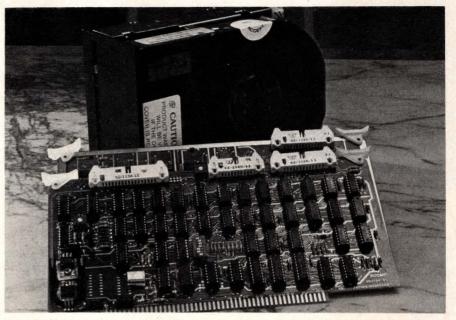Based on a Z80, the 50-in.² board fits in a standard Minifloppy enclosure, requires 5 and 12V (obtained from the primary control-



Incorporating a writeable control store for fault-tolerance testing, the Xcomp 2-board controller easily handles the requirements of the Seagate Technology ST-506 Microwinchester 5.25-in. rigid-disk drive.

MANUFACTURER	USE	CIRCLE NO
ALPHA SYSTEMS CORP 711 CHATSWORTH PL SAN JOSE, CA 95128 (408) 297-5583	GENERAL PURPOSE	347
AMERICAN COMPUTER & TELECOMMUNICATIONS 11301 SUNSET HILLS RD RESTON, VA 22090 (703) 471-6288	HEATH S-100 TRS-80	348
ANDICOMM TECHNICAL PRODUCTS 2603 COLLEGE ST TORONTO. ONTARIO, CANADA M5T 1P9 (416) 979-3328	S-100 APPLE	349
ANOVA CORP 760 LONGRIDGE RD OAKLAND, CA 94610 (415) 836-0800	MULTIBUS	350
CODATA SYSTEMS 285 N WOLFE RD SUNNYVALE, CA 94086 (408) 735-0800	MULTIBUS	351
CONTROL SYSTEMS 1317 CENTRAL KANSAS CITY, KS 66102 (913) 371-6136	GENERAL PURPOSE	352
DATA MANAGEMENT LABS 2148 BERING DR SAN JOSE, CA 95131 (408) 946-9424	S-100 MULTIBUS	353
DATA TECHNOLOGY CORP 2344A WALSH AVE SANTA CLARA, CA 95051 (408) 496-0434	GENERAL PURPOSE S-100 Z80 LSI-11 6800 SBC 80	354

EDN FEBRUARY 4, 1981

Pricing 5.25-in. rigid-disk drives

A price war among manufacturers of 5.25-in. rigid-disk drives appears to be shaping up. And in the front lines is Olivetti Peripheral Equipment, which will offer its Seagate Technology-compatible HD-561 for \$720 (1000) in August.

Other manufacturers view this pricing with mixed feelings. Some, such as Tandon VP Dan Taylor, observe that pricing is usually negotiable, depending on such factors as customers' ability to pay quickly (for which discounts are available). For this reason, some firms, such as Tandon, only quote ballpark pricing; Tandon's drives sell for "less than \$1000 (1000)," and IMI's forthcoming Series 5000 will cost \$800 to \$900 (1000).

But other firms are adamant about the firm nature of their prices: Seagate Technology executive VP Finis Connor, for example, says the Seagate ST-506's \$925 (1000) price tag is a legitimate benchmark. Similarly, Shugart Associates product manager John Sass says his firm's Seagate-lookalike Model SA604 is also competitively priced at \$980 (500).

And what of Olivetti? Director of sales and marketing Gianni Subrizi claims the firm's currently quoted prices are well within established guidelines and will probably remain firm.

MANUFACTURER	USE	CIRCLE NO
DISTRIBUTED LOGIC CORP 12800 GARDEN GROVE BLVD SUITE G GARDEN GROVE, CA 92643 (714) 534-8950	LSI-11 PDP-11	355
KONAN CORP 1448 N 27TH AVE PHOENIX, AZ 85009 (602) 269-2649	S-100	356
LOBO DRIVES 935 CAMINO DEL SUR GOLETA, CA 93017 (805) 685-4546	S-100	357
MICROCOMPUTER SYSTEMS CORP 432 LAKESIDE DR SUNNYVALE, CA 94086 (408) 733-4200	IEEE-488 MULTIBUS	358
MORROW DESIGNS 5221 CENTRAL #2 RICHMOND, CA 94804 (415) 524-2101	S-100	359
PIICEON 2350 BERING DR SAN JOSE, CA 95131 (408) 946-8030	S-100	360
WESTERN DIGITAL CORP 3125 RED HILL AVE NEWPORT BEACH, CA 92663 (714) 557-3550	GENERAL-PURPOSE	361
XCOMP 7566 TRADE ST SAN DIEGO, CA 92121 (714) 271-8730	S-100 GENERAL·PURPOSE	362
		A CONTRACTOR OF

ler connection) and incorporates a 1-track buffer. Priced at \$425 (100), it's planned for full production this month and will work with Apple DOS, TRSDOS, and CP/M operating systems, for which the manufacturer will supply the necessary patches.

Be aware, though, that the "transformer" works at floppy-drive speeds, not Winchester ones. Thus, don't consider it for use in disk-intensive systems; confine it to single-user, single-station systems where speed isn't a major consideration.


Floppy surprises coming

All of the innovations in disk-system products aren't in rigid-disk units; forthcoming floppies will pack a few surprises, too. For example, expect IOmega Corp (Ogden, UT) to introduce a very-high-density floppy by midyear; this as-yet undesignated unit will use an 8-in. floppy medium enclosed in a plastic cartridge.

The medium will have rough (Bernoulli) surfaces that will permit it to essentially "float" in its environment, increasing reliability at the medium/head contact point. However, the drive won't employ contact recording at all; instead, it will use a flying head, as do the rigid-disk drives, and will store 8M to 14M bytes. It will operate at approximately 1500 rpm and use a closed-loop-servo head-positioning system.

Company president David Bailey says the drive won't employ a separate servo track but rather will write servo information on each track. Price will run about \$1100 for the drive, and floppy cartridges will cost \$30 each.

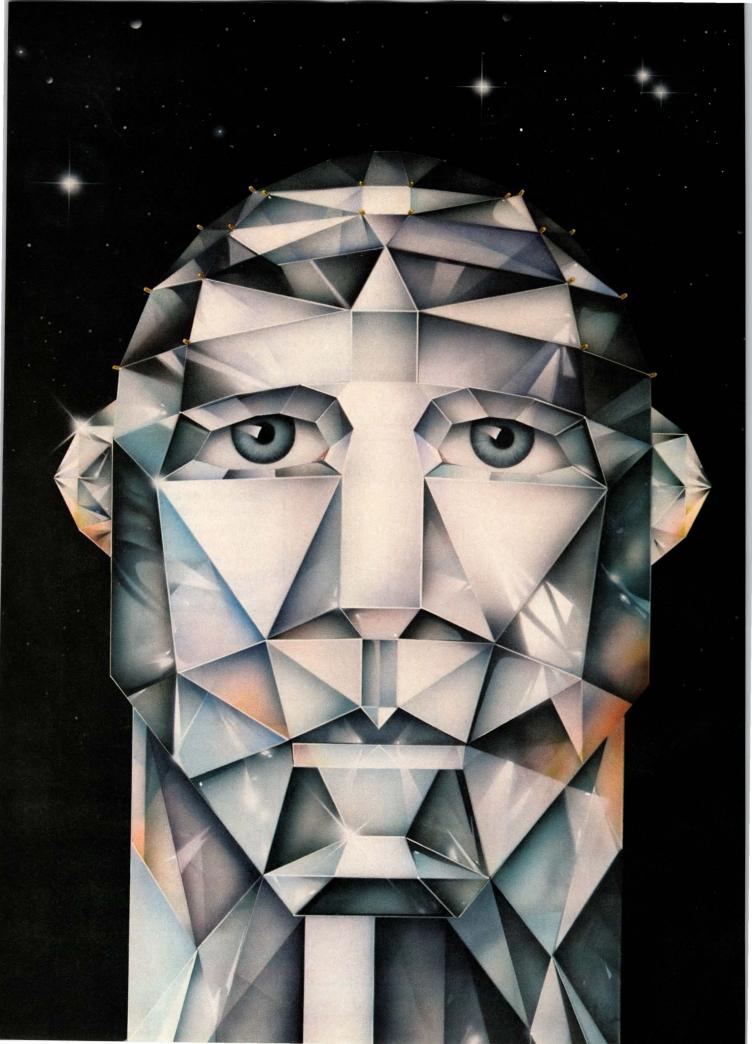Also look for the introduction of removable cartridges for 5.25-in. rigid-disk drives by the third or fourth quarter, although availability might be sparse. But the real excitement will come not in obtaining these new disk-drive products, but in incorporating them into products that end users really need. **EDN**





Buy none, get one free.

There's a new source for the 8748: NEC Microcomputers, Inc. And to prove how good our product is, we're willing to send you a μ PD8748 programmed with your code, absolutely free.

We're making this special offer for one reason: because we intend to become your major source for the 8748, and all 8048 products. And we're sure that once you try our μ PD8748, you'll come back to us for more.

If you want to make a quantity purchase, our μ PD8748 is available right now, off-the-shelf from your local distributor. But if you want to test one in your application first, here's how:


Simply send us one of your coded 8748 or 8048 chips. We'll program our chip with your code and send both chips back to you. Within three days. But hurry, this offer ends on March 31, 1981.

The μ PD8748 is just the latest addition to NEC's 8048 family – now the biggest in the world. We offer 12 different chips, including the μ PD80C48, an exclusive CMOS version available only from us.

Send for your free μ PD8748 today. We're fighting for your business. And we're starting with a free-for-all.

To get your free sample (limit one), send your coded chip along with your company letterhead to Dwain Aidala, c/o NEC Microcomputers, Inc., 173 Worcester Street, Wellesley, MA 02181, (617) 237-1910.

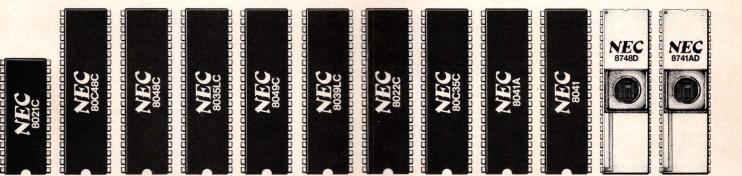NEC Microcomputers, Inc. We're taking on the future."



DC-DC converters from KEPCO/TDK

convert 12V, 24V, 48V, 130V or 260V input to 5V-28Vd-c outputs, 30-100 watts



so small and light they'll fit your product

KEPCC

- High frequency conversion for high efficiency
- Fully isolated
- Current limited
- Adjustable output
- Built-in overvoltage protection

® For complete specifications write Dept. BUF -12.

KEPCO, INC. • 131-38 SANFORD AVENUE • FLUSHING, N.Y. 11352 • (212) 461-7000 • TWX #710-582-2631 • Cable: KEPCOPOWER NEWYORK

For more information, Circle No 25

Practical and blue-sky technology to share spotlight at ISSCC 81

John Tsantes, Eastern Editor

This year's annual International Solid-State Circuits Conference, traditionally a forum for semiconductor manufacturers to air their new developments and advances, will take on a new emphasis. No longer solely a conference reporting primarily on highly theoretical and experimental devices, the gathering will also focus on actual circuits that engineers could soon be designing with.

A review of the conference's more than 80 technical papers, coauthored by more than 300 experts from around the world, leaves no doubt regarding ISSCC 81's emphases: total system integration and unprecedented device performance. Both themes will be evident throughout the 3-day gathering's 17 daytime technical sessions and 10 evening panel discussions.

Of the various topics the conference will cover in New York City this month, semiconductor memories get extensive treatment. But conspicuous by their absence will be papers on ROMs, PROMs and EPROMs: Of the 16 papers to be presented during the three memory sessions—session I ("Static RAMs"), session VIII ("Memories and Redundancy Techniques") and session XII ("Memory Techniques")—only one, in the lastnamed session, deals with a ROM.

That paper, coauthored by Synertek's M Ebel, J Wong and P Sin, describes a 45-nsec fully static 16k MOS ROM that makes extensive use of small-signal amplification and 0V-threshold devices to reduce active power dissipation to 350 mW and standby power level to 75 mW. According to the authors, the device is contactmask programmable and has a die area of 20,300 mil².

RAMs steal the show

The remaining memory-session

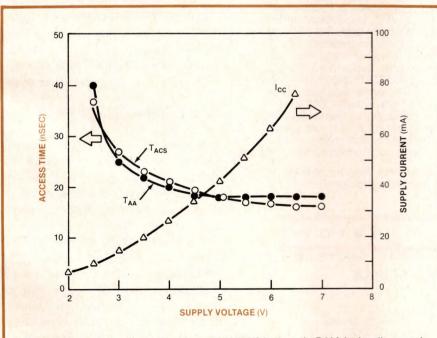


Fig 1—The performance of Toshiba's CMOS/SOS 4k static RAM (to be discussed in ISSCC session I) varies with supply voltage.

papers will emphasize RAMs. And speed is definitely the name of the game here.

Leading session I will be a paper from Toshiba typifying the type of devices covered throughout the session. It will discuss an 18-nsec CMOS/SOS 4k static RAM.

According to Toshiba designers, although scaling techniques have permitted development of several NMOS 4k static RAMs with typical access times of less than 25 nsec. most of them exhibit high operating and standby power consumption. Additionally, even with low-power CMOS RAMs, access times much shorter than 40 nsec haven't been achievable. But by employing MoSi₂-gate CMOS/SOS technology with 2-µm gate lengths and 500Å gate-oxide thickness. Toshiba has developed a fully static 18-nsec 4k×1 RAM with 200-mW active power consumption and 50-µW standby power.

The Toshiba authors explain that the CMOS/SOS structure's low parasitic capacitance has improved minimum gate delay to 250 psec in a ring-oscillator circuit with single fanout. They also note that the sheet resistivity of $MoSi_2$ -gate lines, typically as low as 3.5 Ω /square, drastically reduces the wiring RC delay along the word-select lines to one-tenth that of a conventional polysilicon gate line.

The RAM, which uses the standard 6-transistor CMOS-flipflop memory cell, features a 36×36 -µm cell size. The entire chip measures 3.11×4.07 mm and is housed in a low-cost 18-pin plastic DIP. Address access time (T_{AA}), chip-select access time (T_{ACS}) and operating current (I_{CC}) are all functions of supply voltage (V_{CC}) (**Fig 1**). The authors point out that in this memory, address access time nearly equals chip-select access

NEED TO FIT A LARGER POWER SUPPLY INTO A SMALL SPACE?

Our new switcher delivers 120 watts from 54 cubic inches, and its low component count, quality design gives 65,000 hours MTBF.

The new model Z DC switching power supply is available in ten versions. All feature a 38 KHz switching frequency, which is well above the audio range. Up to 2 watts per cubic inch power density. And nominal efficiency of 75%.

The Z's price is only \$215 for quantity orders.

OUTI	PUT VERSIO	NS	
MODEL NUMBER	*VOLTAGE	WATTS	
Z5A20	5	100	
Z6A18	6	108	
Z10A12	10	120	
Z12A10	12	120	
Z15A8	15	120	
Z18A7	18	120	
Z20A6	20	120	
Z22A6	22	120	
Z24A5	24	120	
Z28A4	28	120	

*Adjustable ±5%

The new Z measures 6x4x2¼ inches and weighs 2 lbs. Three plane mounting provides unique installation flexibility. Full 120 watt output at 75°C provides an additional thermal margin for compact high performance electronics.

Good design with less than 90 components results in a Mil 217C calculated MTBF of 65,104 hours at 50°C. Such protective features as soft start, non crowbar OVP and short circuit protection enable the Z to deliver reliable power to electronic systems that must provide long-term trouble-free performance.

Please call or send for detail specifications and additional product features.



WESTERN OFFICE 639 S. Glenwood Place Burbank, CA 91506 (213) 841-2510 EASTERN OFFICE 1224 Anderson Avenue Fort Lee, NJ 07024 (201) 224-6900

For more information, Circle No 26

News

time, and read-cycle time equals access time.

Fast 16k static RAM

Texas Instruments has developed a $16k \times 1$ fully static RAM exhibiting only slightly slower speed than the Toshiba device. Another **session I** paper will report on this 30-nsec part.

Coauthor Dan Kang, TI manager of static-RAM design, explains that the device utilizes a double-levelpoly scaled-NMOS technology to achieve both this speed and a 600-mW power dissipation. The RAM is completely asynchronous and uses no bootstrapping techniques or clocking circuitry. Although Kang won't offer many details before the ISSCC, he does say that the device embodies a new architecture and many novel circuit-design techniques.


The design employs two 128×64 memory-array blocks and uses no redundant columns to compensate for bit faults. Its 158×256 -mil memory chip will be housed in a 20-pin, 300-mil package.

Other new RAMs

Not to be outdone by TI and Toshiba, Hitachi will also report on a 4k static device in **session I**. Like the Toshiba part, this RAM specs an 18-nsec access time, but it uses a double-poly HI-CMOS II technology with 2- μ m gate lengths rather than SOS to achieve its speed. At 150-mW power dissipation, it also runs a bit cooler.

Nippon Electric (NEC) will present two papers in session I. Countering TI's part, it will reveal its own 16k static RAM, spec'ing a 25-nsec access time. The device uses a double-polysilicon/molybdenum process technology to reduce RC delays to less than 1 nsec; it's designed with 1.5-µm rules.

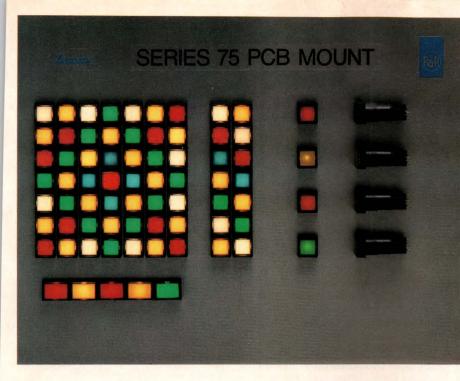A step above this 16k device is NEC's 64k static RAM, on which little detail is currently available. It, too, uses $1.5-\mu m$ design rules, and multiplexed addressing permits its assembly in a standard 300-mil,



It's what's up front (and in back) that counts

Rafi Series 75-PC switches from Ledex mount from the panel front.

Because, in the back of the panel is a socket that can be flow soldered to a PC board before assembly. This feature eliminates wicking onto the contacts and increases PC board production rates, which lowers cost.

It has standard options such as momentary and push-push action, front replaceable lamps or LED's, choice of 3 cap shapes, a key switch, and environmental sealing for rectangular bezel switches.

Other Series 75-SL switches


The SL (solder lug) Key switches have capacity to provide 12 different options for "security" switching.


The 75-SL switches are standard mounted and can be hard wired without damaging the switch body.

All Series 75 switches can be spaced as close as 19,05 mm (.75").


Proven quality

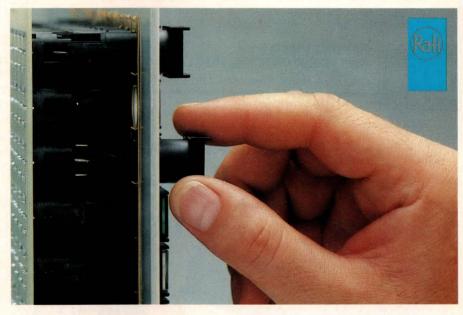Feel it, test it, price it. All Series 75 pushbutton and key switches have proven superior audible, visual, and tactile feedback. You get the "feel" and long life of a quality switch at a competitive price.



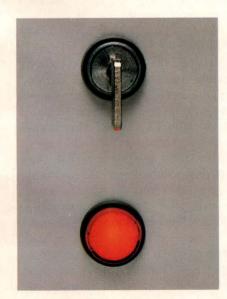

EDN FEBRUARY 4, 1981

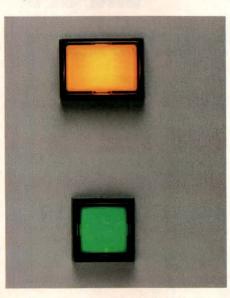


For more information, Circle No 27

International approvals include U/L, LSA, VDE, SEMKO, NEMKO, DEMKO, SEV. Ledex is the exclusive licensee of RAFI of West Germany for the United States.

Write for our catalog today.

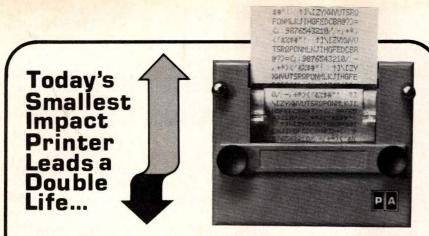Ledex Inc., P.O. Box 427, Vandalia, Ohio 45377. U.S.A. Telephone: 513-898-3621.





Stand our DMPT-3 Miniature Alphanumeric Printer upright for "first line down" data printing, or flip it for "first line up" text. Either way, it not only packs double printing versatility, it comes with its own controller. So you can put it's 120 cps, 20-column capability to work alone as a basic OEM printer, or with its own microprocessor interface and power supply as part of a system. And for more choice, even use it with either parallel or serial ASCII input, at speeds as fast as 1200 baud.

Whichever life the DMPT-3 leads, it keeps your costs down by printing by impact on ordinary adding machine rolls. Saves time by eliminating ribbons. Saves problems, with our unique print-head in 5×7 dot matrix design.See for yourself; call or write for details today.



PRACTICAL AUTOMATION, INC.

Trap Falls Road, Shelton, Conn. 06484/Tel: (203) 929-5381

For more information, Circle No 28



Operate almost anywhere with one power supply

Compare Converter Concepts' switchers and uninterruptible power supplies and you'll know why they're becoming a world standard for design and quality.

WIDE INPUT VOLTAGES Only Converter Concepts produces 15 to 150 watt switchers that operate on any voltage from 90 to 250 VAC or 10 to 40/20 to 60VDC — WITHOUT CHANGING SWITCHES, JUMPERS, TAPS OR OTHER MODIFICATIONS.

LATEST SWITCHER CONCEPTS Wide input ranges are possible through the use of a simple single transistor, single transformer flyback design with soft turn-on and short-circuit protection. Means higher reliability and efficiency at a competitive price.

MANY SWITCHER OPTIONS Single, dual or triple output options in four input power ranges; printed circuit, open frame or RFI-resistant enclosed packages; integral UPS options.

UNINTERRUPTIBLE POWER Automatic, instant transition from AC line to backup battery operation is available either as a separate unit for use with CCI's multiple output DC to DC converters and battery, or as the integral –04 switcher option which features integral battery charger.

NATIONWIDE REPRESENTATIVES Call us today for engineering assistance, our latest catalog, prices and your nearest CCI representative.



435 S. Main St., Pardeeville, WI 53954, (608) 429-2144

For more information, Circle No 29

News

16-pin DIP.

Redundancy fights defects

As memory-device density increases, suppliers are realizing that high defect rates could turn otherwise high-performing parts into financial disasters. As a result, they're adding redundant circuitry to the high-density ICs as a means of keeping yields up and device costs down. While not too important at the sub-16k level, the technique is becoming a virtual necessity above that level.

Session VIII will deal with this subject in the first three of its five papers. Intel, for instance, is applying redundancy techniques to static RAMs and will discuss their impact on a 16k device. According to the company, for a $16k \times 1$ static RAM with 40-nsec typ access time, the additional circuitry increases die area by approximately 6%, access time by 3 nsec and power requirements by only about 3%. Although Intel won't quantify the resulting yield improvements, it does term them "substantial."

Bell Labs is willing to give numbers: It claims a five- to 30-fold yield improvement in a 64k dynamic RAM and will discuss this improvement in session VIII's second paper. Bell, which uses laser programming of redundant circuits in VLSI memories, claims that the improvement calls for less than 4% circuit redundancy.

Emphasis on systems

Although ISSCC 81's memory sessions and their superfast RAMs should drive the "performance" theme home to conference attendees, session IX ("VLSI Microcomputer Systems") should leave visitors with the feeling that the show is also stressing total system integration. And it should leave several jaws hanging, as well. Unlike other sessions, which are set up in one or two sections in the Empire State Ballroom at New York's new Grand Hyatt Hotel, this one has been slated for three large

THE GOLDEN PQUER SUPPLY

We just delivered our one millionth

Why the celebration?

We just delivered our millionth D.C. power supply to a very happy customer. Borrowing a note from the record industry, we presented a special solid gold unit to further honor the occasion.

One million.

An impressive number in itself. But consider what it took to get there.

Electrical Wire - about 475 million feet. That's enough to wrap around the world a few times.

Sheet Metal – an estimated 820,000 sq. ft. Or enough to cover more than 17 football fields.

Transformer Magnetic Steel – around 2,200 tons. This translates into the weight of about 1,250 mid-size automobiles.

Resistors, Capacitors and Semiconductors – approximately 54 million. And each one was individually tested, along with a double in-circuit test.

Assorted Screws, Nuts and Hardware - 45 million pieces or so. Though mostly automated, it's still a lot of turns of the screwdriver.

And on and on it goes. Which leads to the reason we have become, in just a few short years, the world's largest manufacturer of open-frame D.C. power supplies.

We have the experience.

We do all manufacturing in our new 100,000 sq. ft. facility. And we continue to guarantee the service, quality, and reliability you demand.

So now begins the second million. And it won't take long to get there. Not when you see our expanded line of open-frames – plus a new and growing family of switchers. All at our same old low prices!

See for yourself.

Send for our new 1980-81 Catalog and Power-One Tour Guide. You'll know why we reached the first million in record time.





Power-One, Inc. • Power One Drive • Camarillo, CA 93010 Phone: 805/484-2806 • 805/987-3891 • TWX: 910-336-1297

For more information, Circle No 30



WRITE FOR EDN

If you have an idea for an EDN design feature, send us an outline or call the Editor to discuss your proposal. We pay \$30 per magazine page, upon publication, for every contributed feature article. Call Walt Patstone, 221 Columbus Avenue, Boston, MA 02116. Telephone (617) 536-7780.

News

rooms to accommodate an expected heavy turnout.

Although designers from Digital Equipment Corp and Integrated Circuit Systems will coauthor a paper on a 16-bit, 13,000-transistor NMOS microprocessor combining a minicomputer instruction set with a microprocessor bus, the session's really hot items will come from Intel and Hewlett-Packard. Both companies will officially unveil 32-bit processor systems. And although the talk from Intel is expected, the HP disclosure is likely to catch everyone by surprise.

Intel plans four papers describing the basic system philosophy and the three main chips of its iAPX-432 (EDN, November 5, 1980, pgs 103 and 198). With a cost of more than \$30 million and a 5-yr development time, the iAPX-432 utilizes an architecture that's software transparent and accommodates multiprocessing through plug-in devices.

Scheduled for introduction in mid-year, the 32-bit 3-chip set, with a system performance equivalent to that of an IBM 370/158 mainframe (up to 2.5 million instructions per second), will initially cost \$3000. Its price will drop to approximately \$200 by 1984, according to an Intel spokesman.

The set includes a Micromainframe Execution Unit, a Computer Instruction Decoding Unit and an I/O Interface Processor, each treated in a separate session IX paper. The execution unit, a 355-mil-square chip, accepts, decodes and executes the continuous stream of microinstructions received from the microinstruction sequencer in the basic computer. The instruction-decoding unit contains more than 100,000 transistors and measures 320 mils square. It decodes the bit-aligned, variablelength instructions and produces the microinstructions and data necessary to execute them.

To make full use of this system's processing power, Intel has chosen a high-level language rather than assembly-language programming.

ECONO/SWITCH THE SWITCHER COST BREAKTHROUGH **YOU'VE BEEN WAITING FOR!**





nks to a new monolithic chip that contains regulation, modulation and a protective uitry, Power/Mate now offers top quality ching regulated power supplies at a frac-

of the cost of conventional switchers. In ly cases even less than the cost of quality ar supplies.

ypical parts count is reduced 20% for a ch higher MTBF...well over 50,000 hours ... a two year warranty to back it up. Reliity is greatly improved by use of computered "worst-case analysis," individual testing every IC and semiconductor, and a compresive burn-in program.

he new ES Series boasts well over one watt put per cubic inch, 70-80% efficiency and a ns holdup time.

But the big news is dollars per watt, a breakbugh achieved through advanced design manufacturing techniques. Power/Mate's Series switchers set the new standards for ue and performance in switching power oplies for years to come.

Features.

- Brownout protection.
- Overvoltage protection.
- **Overload protection.**
- Short circuit protection.
 - Specifications.
 - AC Input. 85-132 and 170-264 VAC, 47-440Hz. DC Output, See charts
 - DC Output Adjustability. ± 10%

Regulation. Line ±0.1% + 1mV within AC limits specified above. Load ±0.1% + 1mV from no load to full load. Noise and Ripple. 50mV peak-to-peak max., 20Hz to 200KHz.

Efficiency. 70 to 80%.

- Transient Response. Recovery to 1% in 300 microseconds for a 50 to 100% load change. Remote or Local Sensing. Provision included for improved
- overall regulation. Overload and Short Circuit Protection. Solid state short
- verticed and Short Circuit Protection. Solid state short circuit protection. Automatic electronic current limiting circuit limits output current adjustable between 105% and 125% of unit rating, thereby providing protection for the load as well as the supply. Units cannot be damaged by prolonged short circuits.

Overshoot. No voltage spikes on turn-on, turn-off or power failure.

- Reverse polarity protection.
- Soft start protection.
- UL and CSA recognized.
 - Convenient 3-surface mounting.
- Convection cooled.
- Remote sensing.
- **Optional logic inhibit.**
 - Advanced EMI filtering.
 - Logic Inhibit Function Optional. A command signal between 4.5 and 5.5V referenced to (—) negative set terminal will inhibit the DC output. May be used for ense control, sequencing or maintenance. Overvoltage Protection. Built-in, fixed.

Energy Storage Time. The output voltage will remain with-in regulation for a minimum of 16 milliseconds after loss of AC input power (from nominal line voltage).

Polarity. May be either positive, negative or floating up to 300 volts DC.

Soft Start. Provides input current limiting at turn-on. Parallel Operation. Units may be paralleled for increased output current. Consult factory.

Long-Term Stability. 0.1% for 8 hours after 20 minute warm-up.

Ambient Operating Temperature. Continuous duty from 0°C to 71°C. Full rating from 0°C to 50°C, derate linearly to 60% of rating at 71°C.

Storage Temperature. - 20°C to + 85°C. Quality Control. In accordance with MIL-I-45208

S-C Serie	\$\$ \$85. 4.10"	x 3.24" x 1.68"	ES-D Serie	s \$89. 6.12"	x 3.24" x 1.75"	ES-E Serie	s \$99. 4.62"	x 4.88" x 2.00"
IODEL	VOLTAGE	CURRENT	MODEL	VOLTAGE	CURRENT	MODEL	VOLTAGE	CURRENT
S-5C	5 VOLTS	3 AMPS	ES-5D	5 VOLTS	6 AMPS	ES-5E	5 VOLTS	10 AMPS
S-12C	12 VOLTS	1.5 AMPS	ES-12D	12 VOLTS	3 AMPS	ES-12E	12 VOLTS	5 AMPS
S-15C	15 VOLTS	1.2 AMPS	ES-15D	15 VOLTS	2.4 AMPS	ES-15E	15 VOLTS	4 AMPS
S-24C	24 VOLTS	0.75 AMPS	ES-24D	24 VOLTS	1.5 AMPS	ES-24E	24 VOLTS	2.5 AMPS
S-28C	28 VOLTS	0.65 AMPS	ES-28D	28 VOLTS	1.3 AMPS	ES-28E	28 VOLTS	2 AMPS
S-36C	36 VOLTS	0.5 AMPS	ES-36D	36 VOLTS	1.0 AMPS	ES-36E	36 VOLTS	1.5 AMPS
-F Serie	s \$149. 7.10"	x 4.88" x 2.37"	ES-G Serie	s \$189. 8.60"	x 4.88" x 2.37"	ES-H Serie	s \$229. 10.60"	x 4.88" x 2.60"
ODEL	VOLTAGE	CURRENT	MODEL	VOLTAGE	CURRENT	MODEL	VOLTAGE	CURRENT
S-5F	5 VOLTS	20 AMPS	ES-5G	5 VOLTS	30 AMPS	ES-5H	5 VOLTS	45 AMPS
S-12F	12 VOLTS	10 AMPS	ES-12G	12 VOLTS	15 AMPS	ES-12H	12 VOLTS	22 AMPS
S-15F	15 VOLTS	8 AMPS	ES-15G	15 VOLTS	12 AMPS	ES-15H	15 VOLTS	18 AMPS
0.045	24 VOLTS	5 AMPS	ES-24G	24 VOLTS	8 AMPS	ES-24H	24 VOLTS	12 AMPS
5-241	24 VUL13	JUNIO		and the second se				
S-24F S-28F	28 VOLTS	4 AMPS	ES-28G	28 VOLTS	7 AMPS	ES-28H	28 VOLTS	10 AMPS

POWER/MATE. THE SWITCHER COMPANY.

514 S. River St./Hackensack, New Jersey 07601/(201) 440-3100/TWX (710) 990-5023 1400 Coleman Ave., Suite F25/Santa Clara, CA 95050/(408)727-8118/TWX(910)338-0553

The world's largest supplier of quality switching power supplies.

For more information, Circle No 32

ISSCC 81 schedule details

ence is scheduled for February 18 to 20 at New York's Grand Hyatt Hotel. Advance registration fees are \$50 for IEEE members and \$70 for nonmembers; admission prices will be \$60 and \$80, respectively, at the door. All attendees will receive a copy of the 24th evening panel sessions, will take place in the Empire edition of the ISSCC Digest of Technical Papers, containing edited and illustrated condensations of all at \$20 to members, \$30 to nonmembers.

Attendees can register any day during the 8193/8194.

The 1981 International Solid-State Circuits Confer- conference between 8:00 AM and 4:00 PM in the Empire State Ballroom's foyer. Preshow registration, on Tuesday, February 17, will be held between 4:00 and 8:00 PM.

> All 17 technical sessions, as well as the 10 informal State Ballroom.

You can obtain registration forms and additional conference papers. Additional copies will be available information by contacting Lewis Winner, Box 343788, Coral Gables, FL 33134. Phone (305) 446-

				ISSCC 81					
		Empire State			MPIRE STATE BALLRO	OM D	E		
TUE FEB 17	4:00 PM 8:00 PM	Ballroom Foyer Registration	A 	B	с —	_	-		
100-	8:00 AM 4:00 PM	Registration					-		
	9:00 AM 11:45 AM	_	SESSION III Solid-State Devices		SESSIO Static F		SESSION II Consumer Circuits		
	12:00 Noon 1:30 PM Lunch	5 24		-			-		
B 18	1:30 PM 2:10 PM	_			SESSION IV Formal Opening		Star in the second		
AY, FE	2:15 PM 3:00 PM	-			SESSION V Keynote Address	Section and			
WEDNESDAY, FEB 18	3:15 PM 6:00 PM	-	Mem	SION VIII Nories and Sy Techniques	SESSI Data-Acquisi	SESSION VII Microwave Amplifiers			
	6:15 PM 7:15 PM		Author Interviews		-	-	_		
			INFORMAL DISCUSSION SESSIONS						
	8:00 PM	-	WE 1 Power GaAs-FET Amplifiers	WE 2 VLSI Industry/Univer- sity Interaction	WE 3 CMOS vs NMOS for VLSI	WE 4 Speech- Synthesis Techniques	WE 5 ADC for Video Frequencies and Beyond		
	8:00 AM 4:00 PM	Registration	-		-		_		
	9:00 AM 12:15 PM	_	SESSION XI Microwave Circuits		SESSION IX VLSI Microcomputer Systems		SESSION X Analog Filters and Oscillators		
FEB 19	12:15 PM 1:30 PM Lunch	-	-	-	-	-	-		
THRUSDAY, FEB 19	1:30 PM 5:00 PM	-		SESSION XIV Analog Techniques		SESSION XII Memory Techniques			
THRU	5:15 PM 7:00 PM	-		Author erviews	-	-			
			INFORMAL DISCUSSION SESSIONS						
	8:00 PM	-	THE 6 Millimeter-Wave ICs	THE 7 Packaging for VLSI Components	THE 8 Design Methodologies for VLSI	THE 9 The Selection of 16-Bit Micropro- cessor Families	THE 10 Limits of Precision in Analog ICs		
	8:00 AM 11:00 AM	Registration		F	(1)	-	-		
FRIDAY, FEB 20	9:00 AM 12:15 PM	and the second	SESSIC Telecommunic		SESSIOI Advanced Proces	SESSION XVI VLSI Logic			
	12:15 PM 1:15 PM		Auth Interv			-	-		

It uses the object-oriented ADA language (EDN, January 7, pg 171), mapped directly into hardware, as the system's software format.

Density milestone


Not out to steal any of Intel's thunder, HP will nevertheless deliver a bombshell of its own during session IX. Out of the firm's Ft Collins, CO System Technology Operation comes what may be the highest density chip set ever seen in the industry.

Hewlett-Packard designers plan to describe this fully integrated 32-bit VLSI processing system, consisting of six chips housing as many as 600,000 transistors each. The devices include a 32-bit CPU, an I/O processor, a memory controller, a clock driver, a 128k RAM and a record-shattering 528k ROM.

One of the two papers HP will present, emphasizing the CPU chip's processing, will characterize the device's instruction set, performance, internal design and testing—an aspect the company feels is most critical. The second paper will discuss the design of the CPU chip itself as a vehicle for describing the process technology, which HP characterizes as a further advance in NMOS.

Also to be discussed is an outline of the process flow, the design rules and the overall system philosophy. Although HP won't prerelease any more data, a source does reveal that the VLSI devices are fabricated using optical lithography with a $2.5-\mu$ m pitch and double-layer metallization.

However, although the chips definitely constitute a "technological breakthrough," HP is quick to point out that the ISSCC disclosure won't be a new-product announcement. Indeed, no new products, just prototype devices, exist, according to the company. As with most of HP's semiconductor technology, the only way to obtain the fruits of this advance is to buy an HP system incorporating it. Although the company won't say when and if a product employing the 32-bit chip set will appear, it does say that

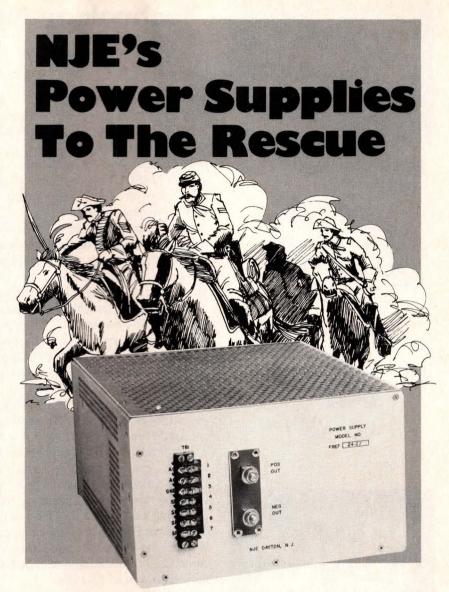

If it's high quality you need, more watt hours per dollar, delivery you can count on and application assistance that is second to none, then it's "NJE to the rescue".

And we've got the industry's most reliable power supplies because we only use the finest components, latest manufacturing techinques and have a series of quality control inspection points that guarantee the quality you need...THAT'S WHY ALL OUR POWER SUPPLIES ARE GUARAN-TEED FOR FIVE YEARS.

We've got a new catalog and a knowledgeable sales engineering team who are anxious to serve you.

Call or write for immediate assistance.

P.O. Box 50, Dayton, N.J. 08810 (201) 329-4611 — TWX 710-480-5674 A DIVISION OF TECHNOLOGY DEVELOPMENT CORP.

For more information, Circle No 33



For more information, Circle No 34



For more information, Circle No 35

Technology News

system implementation is still at least 1 yr away.

Telecomm emphasis remains

One application area continuing to receive increased emphasis from the semiconductor industry is telecommunications, and once again this year the ISSCC program committee has devoted an entire session (XVII) to this subject.

Last year, manufacturers were busy developing monolithic codecs in 1- and 2-chip sets. This year, the emphasis at ISSCC will be on single-chip devices incorporating on-board filters as well. Half of the session XVII papers will describe such devices from Hitachi, Bell Laboratories and NEC/NTT Musashina Electrical Communication Laboratory.

The Bell Labs CMOS chip, containing a codec, filter and trimmed voltage reference, requires only a few nonprecision off-chip capacitors for complete implementation. Power dissipation is a very low 60 mW, reducing the operating cost of the line interface. The chip is currently being sampled within the Bell system and is committed to manufacturing. It has an active area of 23.4 mm².

The Hitachi part, while only slightly larger (30 mm²) than Bell's device, specs twice the dissipation (approximately 130 mW). It, too, is a fully integrated single-chip CMOS-filter/codec with an independent on-chip encoder/decoder, transmit/receive filter and band-gap reference source.

The circuit from NEC/NTT, on the other hand, dissipates a phenomenally low 35 mW. A PCM codec with accompanying filters, it's integrated on a 30.4-mm² chip and also uses CMOS technology. The device consists of an encoder/decoder, switched-capacitor filters and two PLL clock generators.

Applications abound

Another ISSCC session that attendees should find particularly interesting and informative is session XIII, "Advanced Circuit Applications." Of the seven papers to be presented, at least two will report on devices with far-reaching design applications—one in biomedical use and one in communications.

Intersil plans to describe a biomedical microprocessor with analog-I/O capability. Although it was initially designed for use as an implantable pacemaker, coauthors J Berman and J Prak say it can serve in other biomedical applications (such as neurostimulation) requiring monitoring and sensing of the low-level signals present in the body.

The device incorporates two amplifiers capable of sensing 0.5-mV haversine waves and two others with output-drive capability of 1 to 12 mA. The 35,600-mil² CMOS chip contains a 4-bit microprocessor implementing eight programmable modes.

The biggest challenge facing the Intersil designers, say the paper's authors, was the design and integration of the device's low-level sense amps. This accomplishment eliminates the use of separate amplifiers, which heretofore served to boost body-level signals to more usable levels.

Intersil designers consider this circuit the most advanced pacemaker ever developed; it replaces current designs using complex hybrids. Low-power CMOS technology allows the device to operate for 5 yrs on the 1.86V lithium batteries currently used in implantable applications. The part has its own set of built-in diagnostics and can be reprogrammed while implanted to adjust for characteristic patient changes.

Monolithic f-o receiver

IBM's contribution to session XIII will be as impressive as Intersil's: Researcher D L Rogers will report on a single-chip monolithic fiber-optic-receiver circuit capable of 200M-bps operation. The circuit, which generates logic outputs directly from PIN-

The big parade to switching regulators is on! And we've got the capacitors you need.

Everybody's standing up and cheering for the energy efficiency of switching regulator power supplies.

When you switch to switchers, see Mallory for filter capacitors. We can give you a broad selection from which to choose, and the electrical, environmental and reliability performance you need.

 High capacity types up to 320,000 mfd at 3 VDC and 8000 mfd at 100 VDC, for unit chassis power supplies

- Smaller lead-mounted types for PC boards
- Capacitors specifically designed for input sections and output sections, including the new CGO output capacitor with symmetrical ESR and high frequency characteristics
- Medium temperature (85°C) and high temperature (105°C) ratings



EMHART

- High frequency types with low inductance at 20 KHZ
- All of them tested out to exceptionally low ESR values and high ripple current ratings

For complete technical bulletins, contact your nearest Mallory sales office. Or write or call Mallory Capacitor Company, a division of Mallory Components Group, P.O. Box 1284, Indianapolis, IN 46206. (317) 636-5353.

For more information, Circle No 36

photodiode inputs, achieves the broad bandwidth and sensitivity of hybrid designs, says Rogers.

A key element in this circuit's design is the use of current-mode amplification. It permits achievement of greater sensitivity and bandwidth (heretofore unobtainable in monolithic circuits) with today's advanced fiber-optic cables.

New CMOS process

In another anticipated ISSCC development, Intel will use session XV ("Advanced Process Technology") to formally announce its high-performance CMOS process. The firm's paper, titled "HMOS-CMOS Technology," will report on the new bulk-CMOS technology, based on the company's HMOS.

According to Intel, the process affords such features as high resistivity, a p substrate, diffused wells and 2- μ m-channel-length nand p-channel devices. Its high resistivity minimizes parasitic capacitance between the drain and source-to-substrate interface, reducing circuit delays.

Describing a test vehicle for the new technology, the Intel authors will demonstrate its use in a 4k static RAM now under develop-

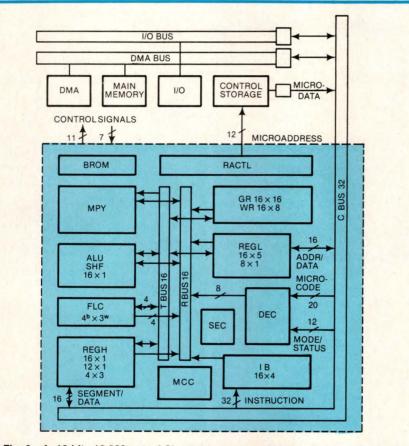


Fig 2—A 16-bit, **12,000-gate LSI processor** from Toshiba employs the firm's CMOS/SOS technology. Scheduled for discussion in ISSCC **session XVI**, the device consists of several subsystems. MCC is a memory-cycle control unit; IB consists of four 16-bit instruction buffers and autonomous instruction-fetch-control circuits; SEC is a sequence-control unit; and DEC consists of a 20-bit microcode register, a 12-bit mode register, a 12-bit status register and microcode decoders. Additionally, REGL consists of a memory-address register, an interface register, current- and advance-location counters, an instruction register and an 8-bit counter; GR/WR is a stores data to distinguish whether an instruction consists of one or more than one microinstruction. Finally, MPY is a 16-bit parallel multiplier; ALU/SHF consists of a binary 16-bit ALU, a decimal adder/subtracter, a 16-bit barrel shifter and a quotient register to implement 32-bit operations; FLC is a flag-control unit; and REGH consists of a memory-data register and segment registers.

ment. The device, which has been fabricated, specs a typical access time of only 25 nsec and microwatt-level standby power. Intel claims the technology presents no major processing problems and is no more complicated than other NMOS processes currently in use. A spokesman maintains that this bulk-CMOS approach could someday become the dominant VLSI processing technology.

Although few details are available, one other paper slated for **session XV** appears extremely interesting. In it, researchers at NTT will report on a static bipolar 256×4 ECL RAM with typical access time of only 2.7 nsec, achieved at a power dissipation of only 550 mW. The device is being fabricated with a self-aligned polysilicon base and emitter process. Complete details will be disclosed at the show.

VLSI innovations

Session XVI ("VLSI Logic") will also include some innovative papers. For instance, in addition to applying SOS technology to RAMs (as discussed earlier), Toshiba is applying it to microprocessing. Researchers will report on a 16-bit, 12,000-gate LSI processor using this CMOS/NMOS SOS technology.

The chip features 300-nsec cycle time and 600-mW power dissipation. Architectural features include parallel-pipelined operation with four 16-bit prefetched user instructions, externally placed microprogram storage (resulting in an adaptive architecture), two 16-bit internal data bases and a 32-bitwide interface bus. This bus communicates with external memories and I/O devices in addition to receiving microcode and status/node information.

The device employs a 16-bit barrel shifter, which performs multibit shifting of as many as 15 bits per microcycle. It also incorporates a parallel 16-bit multiplier and a binary ALU with a decimal adder/subtracter (Fig 2).



The program to reduce software costs. Microprocessor Pascal System. New. From Texas Instruments.

Learnability. Transportability. Maintainability.

The features of Pascal, plus the benefits of TI's learning curve experience, are offered in the new Microprocessor Pascal system.

A system designed for microprocessor applications.

A system developed for the 16-bit 9900 Family, including the TM990 microcomputer modules, and 990 minicomputers.

A system to effectively lower your software costs today. And keep them low tomorrow.

At TI, Pascal is the first and only corporate-wide approved high-level programming language. For a lot of good reasons.

Pascal lets you solve your application without getting involved in the intricacies of machine architecture. And, Pascal's block structure results in fewer programming errors, because the code is easier to write, read and modify.

TI's Microprocessor Pascal system consists of six parts and provides the most Pascal capability ever offered:

- Source Editor specifically designed to create/edit Pascal programs and check program syntax.
- Compiler compiles conventional Pascal programs as well as TI's Pascal concurrent extensions into interpretive code, which can then be executed directly, or converted into 9900 native machine code.
- Host Debugger over fifteen options for tracing variables and modifying data.
- Configurator enables the target system to retain only the parts of the runtime support necessary for program execution.

- Native-Code Generator converts Pascal interpretive code into 9900 native machine code.
- Run-Time Support both interpretive and native-code execution provide a speed/memory trade-off.

TI's continuing commitment to innovative, cost-effective 16-bit microprocessor software means an increased applications capability and decreased development time for you.

Find out how you can reduce your present and future software costs. Put the new TI Microprocessor Pascal system to work for you, today.

For more information, call your nearest Texas Instruments field sales

office or authorized distributor, or write to Texas Instruments, P.O. Box 1443, M/S 6404, Houston, Texas 77001.



TEXAS INSTRUMENTS

© 1981 Texas Instruments Incorporated

For more information, Circle No 37

EDN FEBRUARY 4, 1981

855820



For more information, Circle No 38

Power Supply Specifien B or Buyer Should be Should be Should be Uithout It. See It In See It In See It In This Issue. This Issue. Pages 147-Pages 154

Technology News

CHARACTERISTICS OF TOSHIBA'S 16-BIT CMOS/SOS PROCESSOR

CONTROL	MICROPROGRAM		
MACHINE CYCLE	300 nSEC (TYP)		
INSTRUCTION SET	151 INSTRUCTIONS		
ADDRESSABLE MEMORY	16M BYTES		
PREFETCH BUFFER	FOUR 16-BIT INSTRUCTIONS		
TECHNOLOGY	SI-GATE CMOS/NMOS SOS		
CHIP SIZE	6.66 × 7.46 mm		
NUMBER OF GATES	12,000		
POWER DISSIPATION	0.6W (TYP)		
PACKAGE	64-PIN DIP		
INSTRUCTION	TYPICAL EXECUTION TIME (µSEC)		
REGISTER TO REGISTER	•		
ADD/SUBTRACT	0.3		
MULTIPLY	1.2		
DIVIDE	10.5		
SHIFT (0 TO 15 BITS)	0.3		
BRANCH	0.3/1.35		
FLOATING POINT ADD	11.55-22.5		
SUBTRACT	11.85-22.8		
MULTIPLY	6.0-14.7		
DIVIDE	32.85-35.25		
MEMORY TO REGISTER (INDEXE	D)		
ADD/SUBTRACT	1.05		

The instruction set consists of 151 commands, including 12 floatingpoint and 16 decimal ones, and the device can address as much as 16M bytes. Additional specifications appear in the **table**, which also provides instruction-execution times.

Toshiba's fabrication process fully utilizes ion implantation for threshold - voltage control and source/drain formations. A single n-type polysilicon gate structure serves in both n- and p-channel transistors with a $3.5-\mu$ m channel length. Gate-oxide thickness equals 700Å, and the device employs a highly resistive p-type 0.6- μ m-thick silicon film on sapphire.

Convolver in monolithic form

Following the Toshiba paper will be one that describes a noteworthy device from TRW. In "One Micron Bipolar VLSI Convolver," the firm will describe a 16-stage unit, consisting of 16,200 devices, that operates at 30 MHz while consuming only 700 mW. It can perform 96 million additions and subtractions per second.

Convolution principles apply to many digital-signal-processing requirements, but convolver circuitry to date has been primarily fabricated with discrete devices. Typical applications for such devices have centered on military hardware, including sonar, radar and guidance systems. Although pricing information for the TRW device is not yet available, the high cost of traditional convolution circuitry now in use, in addition to the design's space-saving factors, should make it very attractive to the military establishment at any price.

Although this preview has discussed only a handful of ISSCC 81 papers, don't think they're the only important ones. Other sessions will report on advances in consumer and microwave circuits, dataacquisition systems, analog filters and oscillators. And all should prove useful to attending engineers, because the focus is on practice, not theory. EDN



A Schlumberger Company

You like what you've heard about the FAST family of Advanced TTL Logic, but you want to know more, right? That's easy. Just sign up.

Announcing the new, expanded FAST Technology Seminar. Applications, comparisons, reliability, delivery, ordering information - everything you need to know, at no cost, from the people who know it best-the Fairchild **FAST** Marketing Application Team.

You get a FAST data book, a workbook containing all of the materials presented in the seminar, samples and availability information.

And you get all the latest input on the technology that's delivering up to 40% more speed than Schottky, with a reduction in power of up to 75%! And up to 75% more speed than low-power Schottky.

The Fairchild FAST Application Seminar. Just check the listing for the city and date most convenient for you, fill out the coupon and mail it in. We'll send you a confirmation with the F. 74 FOO 3ns 74 F194 120 MHz 74 F241 64 mA 74 F241 64 mA

seminar location and a seating guarantee. FAST.

Where and when.

Feb. 4, 1981-Santa Clara, CA (408) 987-9530 Feb. 5. 1981 -Seattle, WA (503) 641-7871 Feb. 6, 1981 Portland, OR (503) 641-7871 Feb. 9, 1981-San Fernando Valley, CA (213) 990-9800 Feb. 10, 1981 Los Angeles, CA (213) 990-9800 Feb. 11, 1981 -Anaheim, CA (714) 557-7350 Feb. 12, 1981 -Irvine, CA (714) 557-7350 Feb. 13, 1981 San Diego, CA (714) 557-7350 Feb. 16, 1981 -Phoenix, AZ (602) 864-1000 Feb. 17, 1981 -Salt Lake City, UT (801) 566-3691 Feb. 18, 1981 Denver, CO (303) 794-8381 Feb. 19, 1981 -Minneapolis, MN (612) 835-3322 Feb. 20, 1981 -Chicago, IL (312) 640-1000 Feb. 23, 1981 -Dallas, TX (214) 234-3391 Feb. 25, 1981 -Houston, TX (713) 771-3547

Feb. 26, 1981 -Huntsville, AL (205) 837-8960 Feb. 27, 1981 -Atlanta, GA (205) 837-8960 March 2, 1981 -Detroit, MI (313) 478-7400 March 3, 1981 -Cleveland, OH (216) 587-3600 (Pioneer Electronics) March 4, 1981 Dayton, OH (513) 236-9900 (Pioneer Electronics) March 5, 1981 Indianapolis, IN (317) 849-5412 March 6, 1981 Tulsa, OK (214) 234-3391 March 9, 1981 -Boston, MA (617) 237-3400 March 10, 1981 -Stamford, CT (516) 293-2900 March 11, 1981 New York, NY Area (516) 293-2900 March 12, 1981 Philadelphia, PA (215) 657-2711 March 13, 1981 -Baltimore, MD (301) 730-1510 March 16, 1981 Orlando, FL (305) 834-7000 March 17, 1981 -Fort Lauderdale, FL (305) 771-0320

And how:

Fill out and mail FAST to guarantee your reservation. Or call the local number in your area.

> Title_ Company

Name_

Address_

City_

State Seminar Location

> Mail to: Fairchild FAST Seminar P.O. Box 7880LSI Mountain View, CA 94042


_____Phone ()_____

___Zip___

For more information, Circle No 39

FAST made easy.

POWER MOSFETs

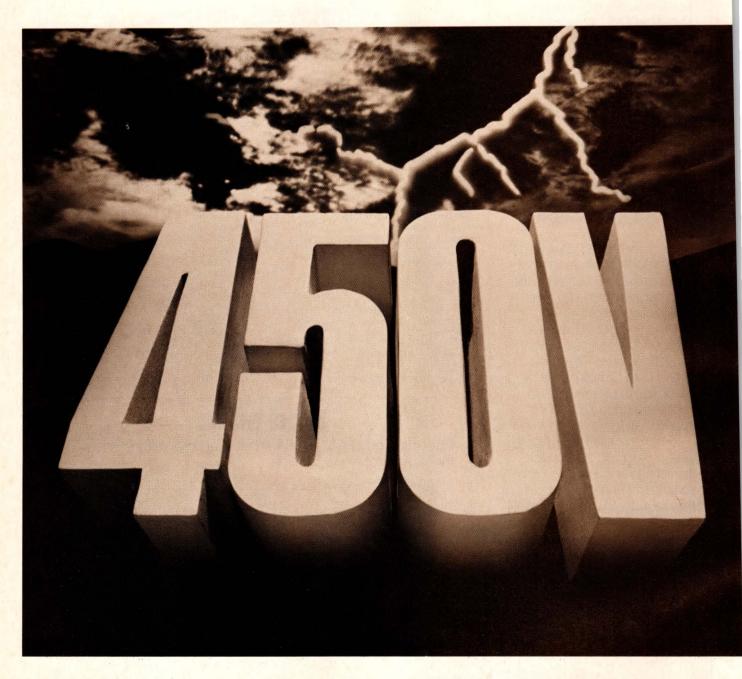

A better power MOSFET.

Announcing a major new family of power MOSFETs: the IVN6000 series. Using an improved DMOS process that provides better transconductance, reliability and high-voltage performance. Now producing a power MOSFET with 450V breakdown voltage and IOns switching speed!

450V—a necessary margin of safety.

If your application operates directly from an ac line, a 400V power transistor can be risky. When you consider the effects of high line voltage, stray inductances, momentary surges and the change in BV_{DSS} with temperature — you need 450V

And that's why the IVN6000 is the answer for a whole spectrum of uses: Switching power supplies, voltage converters and inverters, pulse amplifiers, lighting and motor controls, rf applications, on and on.

FROM INTERSIL.

ioodbye bipolars.

polar power transistors are no nger a good deal. This comparion chart shows why power MOS esigns have fewer parts, smaller price for the 450V IVN6000KNT is only \$10.95.

For the 400V part, it's \$10.25. For the 350V part, it's \$9.50. All in TO-3 packages. Not a bad deal.

	Power MOS	Power Bipolar
Switching Speed	10 ns	l μs
Input Current	100 nA	300 mA
Secondary Breakdown	No	Yes
Drive Circuitry	Simple	Complex
Device Paralleling	Yes	No
ntegral Reverse Diode	Yes	No

Intersil franchised distributors:

Advent (IN, IA) • Alliance • Anthem • Arrow • Bell Industries • Cadence • Cardinal • CESCO • Component Specialties • Components Plus • Diplomat (FL, MD, NJ, UT) • Harvey (upstate NY) • Kierulff • LCOMP • Newark • Parrott • R.A.E. Ind. Elect. Ltd. • RESCO/Raleigh • Schweber • Summit • Western Microtechnology • Wyle • Zentronics

size, less weight, less cooling and nigher overall reliability.

Check these specs:

- Breakdown Voltage: IVN6000KNT = 450V, Min. IVN6000KNS = 400V, Min. IVN6000KNR = 350V, Min.
- Switching Speed: 10ns, Max.
- On Resistance: 3.0Ω at IA, Max.
- Continuous Drain Current: 2.25A, Min.
- Peak Drain Current: 7.5A, Min.

Priced right. Ready to go.

Intersil's DMOS process also provides some significant manufacturing advantages. Its smaller die sizes mean lower prices. So the 100-piece Also, since our DMOS is very manufacturable, you won't have to worry about getting parts. The company that's introducing new highs in power MOSFETs is also introducing new lows in power MOSFET delivery times.

Call us and see.

Intersil sales offices:

CALIFORNIA: Sunnyvale (408) 744-0618, Long Beach (213) 436-9261 • COLORADO: Aurora (303) 750-7004 • FLORIDA: Hollywood (305) 920-2442 • ILLINOIS: Hinsdale (312) 986-5303 • MASSACHUSETTS: Lexington (617) 861-6220 • MINNESOTA: Minneapolis (612) 925-1844 • NEW JERSEY: Englewood Cliffs (201) 567-5585 • OHIO: Miamisburg (513) 866-7328 • TEXAS: Dallas (214) 369-6916 • CANADA: Brampton, Ontario (416) 457-1014



Analog Products – Power MOS 10710 N. Tantau Avenue Cupertino, CA 95014 Tel: (408) 996-5000 TWX: 910-338-0171 Dear Intersil: ______Sounds great! Please send me the details on your new IVN6000 Power MOSFETs, fast. _____Please also include a Ben Franklin poster from your "famous quotations" ad series. Name_______ Company______ Address______ City/State/Zip______ Phone______



climbing to new *POHER PEAKS* in rectifier technology

RSM/Sensitron's new 15 amp axial lead glass rectifiers offer the highest current, highest power, and highest temperature ratings available today...

Our new 15 amp axial lead rectifiers are available in fast recovery and general purpose versions with PIV ratings up to 600 volts. These devices meet, or exceed, all military and aerospace reliability requirements.

Optimum reliability is assured due to the hyper-pure hard glass package and non-cavity metallurgically bonded construction utilized. All lead and die bonding is performed at temperatures in excess of 650°C, no soft solders are used in the manufacture of these devices.

MAXIMUM RATINGS

CHARACTERISTICS	SRSFR605	SRSFR610	SRSFR620	SRSFR640	SRSFR660	UNITS	
DC Blocking Voltage	50	100	200	400	600	Volts	
RMS Reverse Voltage	35	70	140	280	420	Volts	
Peak Non-Repetitive Reverse Voltage (Single Phase, 60 Hz, Resistive Load)	75	150	250	450	650	Volts	
Reverse Recovery Time $I_r = 0.5 \text{ Amps}, I_R = -1.0 \text{ Amps}$ $T_{rr} = \text{Read When } I_R \text{ Recovers}$ to -0.25 Amps		200 MAX					
Average Forward Rectified Current (Single Phase, 60 Hz, Resistive Load)	15A ($T_{L} = 55^{\circ}$ C, $\frac{1}{8}''$ Lead Lengths) 5A ($T_{A} = 55^{\circ}$ C, P.C. Board Mounted)					Amps	
Single Cycle Peak Non-Repetitive Surge Current, 8.3 ms	200					Amps	
Junction Operating and Storage Temperature		-65 to +175					



Sensitron Semiconductor

A DIVISION OF RSM ELECTRON POWER, INC. 221 West Industry Court • Deer Park, N.Y. 11729 Telephone (516) 586-7600 • Telex 96-7737

Technology News

Wavelength multiplex, demultiplex devices emerge from fiber-optic research

Tom Ormond, Senior Editor

Wavelength-division multiplexing for fiber-optic systems is emerging from the laboratory; designers have advanced beyond the feasibilitydemonstration stage and are now developing components that suit specific system requirements. And, points out one expert, they are finding that passive multiplexers and demultiplexers require different design details, even though one device can theoretically perform the two functions.

W John Tomlinson, member of the technical staff at Bell Laboratories (Holmdel, NJ), points out that wavelength-division multiplexing has sparked high interest because it dramatically increases information capacity. And he adds that in addition to the usual factors (cost, availability, reliability), three basic criteria help designers evaluate a multiplexer/demultiplexer pair from a system point of view—insertion loss, channel width and crosstalk.

Designers generally agree that the first quantity must be less than a few decibels at each end of the pair—the lower the better. Additionally, laser diodes' wavelength reproducibility and stability require channel-bandwidth requirements as high as several hundred angstroms; LED sources call for even larger channel widths. Finally, although crosstalk-level specs vary widely, -30 dB usually proves more than adequate.

But Tomlinson observes that in most cases, LED and diode sources don't emit much power outside their peak emission wavelengths, so crosstalk rejection is relatively unimportant for a multiplexer. (It is important, though, to match the source's output-mode pattern to that of the transmission fiber.) A demultiplexer, on the other hand, must meet system-crosstalk requirements because detectors are usually sensitive at each channel's wavelength.

Choose two component classes


Two types of components serve multiplexing and demultiplexing functions: angularly dispersive and filter devices. (Investigators have proposed some multilayer semiconductor detectors, and Tomlinson says that some of these active devices could ultimately prove useful in specialized applications. However, they still require further research.)

Angularly dispersive devices routinely provide crosstalk levels between -20 and -30 dB, and they are well suited to parallel operation, according to Tomlinson. Most basic designs (Fig 1) can separate as many channels as required with one grating or prism. (Although separate lenses are shown for input and output in Fig 1, a single device satisfies both functions in many designs.)


In operation, the input lens collimates the light from the input fiber for passage through the angularly dispersive element to the output lens, which focuses the different-wavelength beams onto the various output fibers. With a monochromatic input signal, this optical system forms an image of the input fiber at some position on the output-fiber array. A wavelength scan of the input signal moves this image along the array; thus, the input and output fibers' mode structures determine the shape of the design's response curves.

Angularly dispersive devices will prove the best choice for demultiplexing applications, claims Tomlinson, because they have low crosstalk and can exhibit relatively wide flat-topped channel bandwidths when used with large-core output fibers. They should demultiplex multimode and single-mode signals equally well.

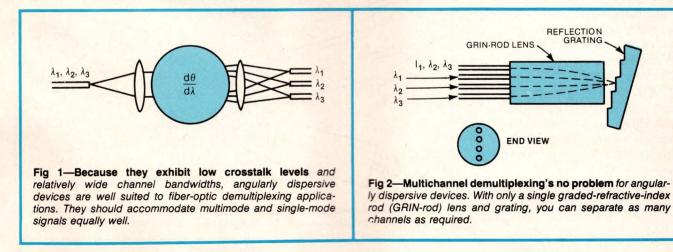These devices will also satisfy multimode-signal multiplexing ap-



Technology News

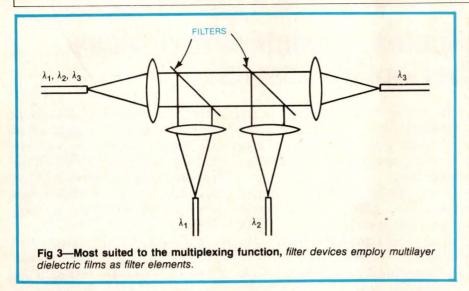

plications, although it will be difficult to attain the necessary channel bandwidths with them. On the other hand, they're unlikely to ever prove useful for multiplexing single-mode signals, says Tomlinson, who reviewed the state of the art in wavelength multiplexing and demultiplexing at the FOC '80 show in San Francisco.

Most angularly dispersive devices use a grating/lens combination (Fig 2) and can be packaged as a solid assembly. Insertion losses are typically in the 1- to 3-dB range, and the grating devices readily adapt for use in any wavelength range. The graded-refractive-index rod (GRIN-rod) lens depicted in Fig 2 is only one design; others use conventional lenses or a concave grating.

Filters suit MUXing

In a basic filter device (**Fig 3**), the elements are multilayer dielectric films with a high reflectivity for one or more channels and a low reflectivity for the rest. Characteristically, says Tomlinson, they are most suited to serial operation: In most cases, each additional channel requires another lens and filter, so multichannel filter-type devices are complex.

Filter-type devices also usually have higher crosstalk levels than angularly dispersive components because fabricating filters with sharp cutoffs remains difficult. On the positive side, their passband shapes don't depend on fiber characteristics—you can use a set of filters providing the desired wavelength characteristic with almost any type of fiber, says Tomlinson.

Considering these characteristics, filter devices are most suited to multiplexing—their crosstalk requirements aren't too stringent, and no channel-bandwidth degradation occurs when matching a filter's output fiber to the transmission fiber.

And in some cases—2-channel systems with widely separated (0.8 and $1.3 \mu m$) channels—filter devices could prove the best choice for both


multiplexing and demultiplexing, according to Tomlinson. In fact, he reports that 2-channel filter devices have already provided simultaneous 2-way transmission over a single fiber. (Additional filtering was necessary to reduce crosstalk to acceptable levels.)

Currently, filter devices also appear to offer the only feasible approach for multiplexing singlemode signals. By mounting all the lenses on axis, one basic design for this purpose (**Fig 4**) eliminates coupling losses from off-axis aberrations.

IC optics still experimental

Examining potential developments, Tomlinson notes that single-mode-signal multiplexing schemes using various integrated optical filters are currently under investigation. However, obtaining wide channel bandwidths in these integrated components remains difficult.

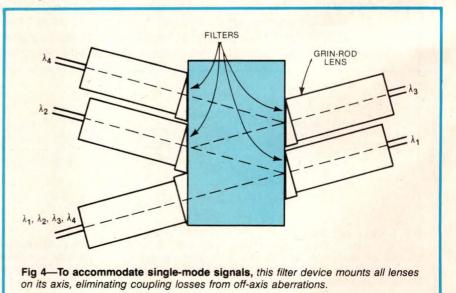Additionally, no technique is yet available to provide low-loss coupling between the planar integrated optics and a single-mode fiber. But modern IC production techniques could readily provide the solution to this coupling problem, says Tomlinson, so the future looks bright for integrated optical-fiber devices. EDN



Digital IC Probe & Logic Pulser

PRB-1 DIGITAL LOGIC PROBE

Compatible with DTL, TTL CMOS, MOS and Microprocessors using a 4 to 15V power supply. Thresholds automatically programmed. Automatic resetting memory. No adjustment required. Visual indication of logic levels, using LED's to show high, low, bad level or open circuit logic and pulses. Highly sophisticated, shirt pocket portable (protective tip cap and removable coil cord).

Automatic threshold resetting • DE to > 50 MHZ

Compatible with all logic families 4-15 VDC • 10Nsec. pulse response

Supply O.V.P. to ± 70 VDC • 120 K Ω impedance

No switches/no calibration • Automatic pulse stretching to 50 Msec.

Open circuit detection • Automatic resetting memory

Range extended to 15-25 VDC with optional PA-1 adapter

PLS-1 LOGIC PULSER

The PLS-1 logic pulser will superimpose a dynamic pulse train (20 pps) or a single pulse onto the circuit node under test. There is no need to unsolder pins or cut printed-circuit traces even when these nodes are being clamped by digital outputs.

PLS-1 is a multi-mode, high current pulse generator packaged in a hand-held shirt pocket portable instrument. It can source or sink sufficient current to force saturated output transistors in digital circuits into the opposite logic state. Signal injection is by means of a pushbutton switch near the probe tip. When the button is depressed, a single high-going or low-going pulse of 2μ sec wide is delivered to the circuit node under test. Pulse polarity is automatic: high nodes are pulsed low and low nodes are pulsed high. Holding the button down delivers a series of pulses of 20 pps to the circuit under test.

High input impedance (off state) 1 meg ohm • Multi mode-single pulses or pulse trains

Low output impedance (active state) 2 ohms • Automatic polarity sensing

Output pulse width 2 µsec nominal • Automatic current limiting; 7 amps nominal

Input over voltage protection + 50 volts • Automatically programmed output level

- Finger tip push button actuated Circuit powered
- Power lead reversal protection No adjustments required

Multi-family RTL, DTL, TTL, CMOS, MOS and Microprocessors.

OK Machine & Tool Corporation 3455 Conner St., Bronx, N.Y. 10475 U.S.A. Tel. (212) 994-6600 Telex 125091

We're High Low on Cost. And



						UIFUI J	UT SUPPLIES			
Sorensen Model No.	Output Current (50°C)	List Price (ea)			Output Current (50 °C)	List Price (ea)			Output Current (50°C)	List Price (ea
SLC5-6B	6A	\$180	12	SLC12-2.5B	2.5A	\$18O	15	SLC15-2B	2A	\$180
SLC5-11B	11A	240	12	SLC12-4.5B	4.5A	240	15	SLC15-3.6B	3.6A	240
SLC5-2OB	20A	345	12	SLC12-8B	8A	345	15	SLC15-6.6B	6.6A	345
SLC5-3OB	3OA	385	12	SLC12-12B	12A	385	15	SLC15-1OB	10A	385
SLC5-4OB	40A	445	12	SLC12-16.7B	16.7A	445	15	SLC15-13.3B	13.3A	445
SLC5-6OB	60A	550	12	SLC12-25B	25A	550				
SLC9-3.3B	3.3A	180			1 1 3 7 1					
SLC9-6B	6A	240								
		and the second	1.			1.27.10				
	Model No. SLC5-6B SLC5-11B SLC5-20B SLC5-30B SLC5-40B SLC5-60B SLC9-3.3B	Model No. (50 °C) SLC5-6B 6A SLC5-11B 11A SLC5-20B 20A SLC5-30B 30A SLC5-40B 40A SLC5-60B 60A SLC9-3.3B 3.3A	Model No. (50 °C) Price (ea) SLC5-6B 6A \$180 SLC5-11B 11A 240 SLC5-20B 20A 345 SLC5-30B 30A 385 SLC5-40B 40A 445 SLC5-60B 60A 550 SLC9-3.3B 3.3A 180	Model No. (50 °C) Price (ea) Voltage SLC5-6B 6A \$180 12 SLC5-11B 11A 240 12 SLC5-20B 20A 345 12 SLC5-30B 30A 385 12 SLC5-40B 40A 445 12 SLC5-60B 60A 550 12 SLC9-3.3B 33A 180 180	Model No. (50 °C) Price (ed) Voltage Model No. SLC5-6B 6A \$180 12 SLC12-2.5B SLC5-11B 11A 240 12 SLC12-4.5B SLC5-20B 20A 345 12 SLC12-4.5B SLC5-30B 30A 385 12 SLC12-12B SLC5-40B 40A 445 12 SLC12-16.7B SLC5-60B 60A 550 12 SLC12-25B SLC9-3.3B 3.3A 180 180 180	Model No. (50 °C) Price (ea) Voltage Model No. (50 °C) SLC5-6B 6A \$180 12 SLC12-2.5B 2.5A SLC5-11B 11A 240 12 SLC12-4.5B 4.5A SLC5-20B 20A 345 12 SLC12-4.5B 8A SLC5-30B 30A 385 12 SLC12-12B 12A SLC5-40B 40A 445 12 SLC12-16.7B 16.7A SLC5-60B 60A 550 12 SLC12-25B 25A SLC9-3.3B 3.3A 180 180 180 180	Model No. (50 °C) Price (ea) Voltage Model No. (50 °C) Price (ea) SLC5-6B 6A \$180 12 SLC12-2.5B 2.5A \$180 SLC5-11B 11A 240 12 SLC12-4.5B 4.5A 240 SLC5-20B 20A 345 12 SLC12-4.5B 8A 345 SLC5-30B 30A 385 12 SLC12-12B 12A 385 SLC5-40B 40A 445 12 SLC12-16.7B 16.7A 445 SLC5-60B 60A 550 12 SLC12-25B 25A 550 SLC9-3.3B 3.3A 180 180 180 180 180	Model No. (50 °C) Price (ea) Voltage Model No. (50 °C) Price (ea) Voltage SLC5-6B 6A \$180 12 SLC12-2.5B 2.5A \$180 15 SLC5-11B 11A 240 12 SLC12-4.5B 4.5A 240 15 SLC5-20B 20A 345 12 SLC12-8B 8A 345 15 SLC5-30B 30A 385 12 SLC12-12B 12A 385 15 SLC5-40B 40A 445 12 SLC12-16.7B 16.7A 445 15 SLC5-60B 60A 550 12 SLC12-25B 25A 550 15 SLC9-3.3B 3.3A 180 12 SLC12-16.7B 16.7A 445 15	Model No. (50 °C) Price (ea) Voltage Model No. (50 °C) Price (ea) Voltage Model No. SLC5-6B 6A \$180 12 SLC12-2.5B 2.5A \$180 15 SLC15-2B SLC5-11B 11A 240 12 SLC12-4.5B 4.5A 240 15 SLC15-3.6B SLC5-20B 20A 345 12 SLC12-4.5B 8A 345 15 SLC15-6.6B SLC5-30B 30A 385 12 SLC12-12B 12A 385 15 SLC15-10B SLC5-40B 40A 445 12 SLC12-16.7B 16.7A 445 15 SLC15-13.3B SLC5-60B 60A 550 12 SLC12-25B 25A 550 15 SLC15-13.3B SLC9-3.3B 3.3A 180 180 12 SLC12-25B 25A 550	Model No. (50 °C) Price (ea) Voltage Model No. (50 °C) Price (ea) Voltage Model No. (50 °C) SLC5-6B 6A \$180 12 SLC12-2.5B 2.5A \$180 15 SLC15-2B 2A SLC5-11B 11A 240 12 SLC12-4.5B 4.5A 240 15 SLC15-3.6B 3.6A SLC5-20B 20A 345 12 SLC12-4.5B 8A 345 15 SLC15-3.6B 3.6A SLC5-30B 30A 385 12 SLC12-12B 12A 385 15 SLC15-10B 10A SLC5-40B 40A 445 12 SLC12-16.7B 16.7A 445 15 SLC15-13.3B 13.3A SLC5-60B 60A 550 12 SLC12-25B 25A 550 550 SLC15-13.3B 13.3A SLC9-3.3B 3.3A 180 16 172 SLC12-25B 25A 550 SLC15-13.3B 13.3A

SPECIFICATIONS:

Input Voltage: Single Output Units and 40W Triple Output Units: 90-127V AC and 180-254V AC 80W Triple Output Units: 103-127V AC

Input Frequency: 47-440 Hz Efficiency: Up to 77%

Output Line Regulation: 0.2% max. for input variations of input voltage specifications. 0.1% max. for 300W unit. 0.5% max. for triple output.

Load Regulation: O.2% max. for load variations from full load to no load. O.3% max. for 300W unit. 1% max. for triple output units. **Ripple and Noise:** 50 mV p-p max. for 5V models; 100 mV p-p for 9V to 48V models. **Temperature Coefficient:** Less than $\pm 0.02\%/°C$ for


all outputs.

Transient Response: Recovery to 0.5% regulation bandwidth within 1 ms typical.

FEATURES:

Remote Sensing Overload Protection Overvoltage Protection EMI Suppression 5 Year Warranty

on Efficiency. .ong on Warranty.

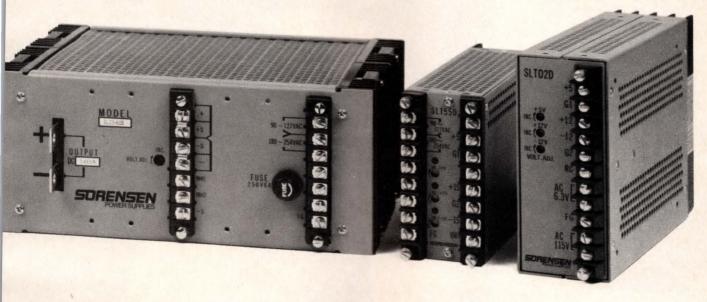

and the second s	Sorensen Model No.	Output Current (50°C)	List Price (ea)	And the second second	Sorensen Model No.	Output Current (50°C)	List Price (ea)	*Output Voltage	Sorensen Model No.	Output Current (50 °C)	t List Price (ea)
	SLC2O-1.5B SLC2O-2.75B	1.5A 2.75A	\$18O 24O	24 24	SLC24-1.2B SLC24-2.2B	1.2A 2.2A	\$180 240	+5V, +12V, -12V	SLT-52D	5A, O.5A, O.5A	\$310
	SLC2O-5B SLC2O-7.5B	5A 7.5A	345 385	24 24	SLC24-4B SLC24-6B	4A 6A	345 385	+5V, +12V, -5V +5V, +15V,	SLT-525	5A, O.5A, O.5A	310
20	SLC2O-1OB	. 10A	445	24 24	SLC24-8.3B SLC24-12.5B	8.3A 12.5A	445 550	-15V +5V. +12V.	SLT-55D	5A, O.5A, O.5A	310
				28 28	SLC28-7B SLC28-1OB	7A 10A	445 550	-12V +5V, +12V,	SLT-O2D	10A, 1A, 1A	380
				48	SLC48-6B	6A	550	-5V +5V, +15V, -15V	SLT-O25 SLT-O5D	10A, 1A, 1A 10A, 1A, 1A	380 380

If you're looking for the high efficiency of a switching power supply at the cost of most linears, look to the Sorensen SLC-B series. With up to two watts per cubic inch power density and two mounting surfaces, it's the ideal series for economical, high density electronic packages. You'll also find our delivery is faster than you thought possible. But most important: when you install an SLC-B or SLT unit from Sorensen, you can depend on it. All 39 models are backed by a comprehensive five year warranty, because Sorensen knows they will last. *Output Voltage Adjustment: ±10%

Call 603/668-4500 to order one of these dependable low cost switchers. From Sorensen, *the Source*,



What the world has been waiting for in high performance micros. <u>Immediate delivery</u>.

114

and the

Digital is changing the way you get your products to market.

We're making it faster.

Because right now our basic LSI-11 product family is available with off-the-shelf delivery. So you don't have to wait around to get your product started.

And once you have our micros, you can do more with them. Our unique buildingblock approach lets you design whatever system you need.

Start with your choice of microcomputer terminals. Either the VT103-AA—a specially configured VT100 with an LSI backplane that accepts up to 8 double-height modules. Or the VT103-BA, featuring a backplane and a TU58 dual-drive cartridge tape.

Then you add our KD11-HA LSĬ-11/2 CPU Board, a low-cost 16-bit processor with the power to drive virtually any small to medium-sized system.

Plus you can choose either one of these powerful modules.

- The MXV11 LSI-11 Multifunction Module. Featuring 8 or 32Kb of RAM, up to 8Kb of PROM (user supplied), 2 asynchronous serial I/O ports and real-time clock.
- 2. The MSV11-DD 64Kb RAM Board. Complete with on-board refresh.

These boards, plus the VT103, are available immediately. To give you all the flexibility and performance you need to develop a great micro product. Or a great micro development system. Or both.

Of course, once you get started with an LSI-11, there's no telling where you might want to go. So we offer lots of other modules for you to plug into your VT103: 9 different memory boards, 11 I/O modules, 9 communications options, even kits for designing your own custom interfacing.

And if you need more, there are also 8 different peripherals, all running on Digital's industry-standard LSI-11 Bus, the most widely used bus structure in micros.

Great flexibility in software, too.

Our RT-11 development and applications software gives you a wealth of high level languages and development aids. Its capabilities range from multitasking, multiterminal support for larger configurations, to a very small kernel for single-task applications. There's also SIMRT, a subset of RT-11 designed for PROM applications that's an integral part of FORTRAN IV.

And because your development software has the same RT-11 software as your target system, you can debug your programs with complete confidence.

The total approach to micros.


Helping you get your product to market quickly is just one of the ways we make micros easier to work with.

We also back all our boards with over 14,000 service people worldwide, technical consultation and training. Plus a range of support agreements to meet your needs.

It's the total approach to micros, only from Digital.

For more information call our toll-free LSI-11 Hotline at **800-225-9220.** (In MA, HI, AK and Canada, call 617-467-7000.) Or send the coupon.

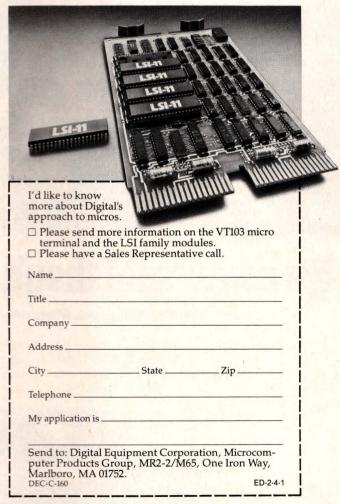Digital Equipment Corporation, MR2-2/ M65, One Iron Way, Marlboro, MA 01752. In Europe: Digital Equipment Co. Limited, Acre Rd., Reading, RG2 OSU, England. In Canada: Digital Equipment of Canada, Ltd. Or contact your local Hamilton/Avnet distributor.



digital We change the way the world thinks.



We never said they'd be good-looking.

ELPAC's Switching Power Supplies, where reliability at an affordable price came first.

When we set out to design and produce a line of switching power supplies, looks were not important. Performance and cost were. ELPAC's goal was to deliver high quality switchers at a good price. And we've done it!

Now you can select from standard ELPAC switchers in 100, 175, 180 or 250 watt series. They are available at your local distributor. Open or closed frame. Dual input. Single or multiple output. Truly measured to be greater than 70% efficient. Fully rated for 0°C to 40°C operation with convection cooling.

The design is state of the art yet simple. A low component count offers high reliability.

All models feature a 20 KHz switching frequency which is pulse width modulated for minimum line noise, EMI and RFI. Line and load regulation are $\pm 0.1\%$ with soft start and overvoltage protection standard on all units.

So specify an ELPAC Switcher.It's reliable. It's priced right.It's an UGLY.tm But that's no surprise.

Write or call for complete specifications today, We've got local, national, and international distribution. Ask about our custom capabilities. GET UGLY!!!



ELPAC POWER SYSTEMS A DIVISION OF ELPAC ELECTRONICS, INC.

3131 South Standard Avenue Santa Ana, California 92705 (714) 979-4440 TWX 910-595-1513

For more information, Circle No 45

Editor's Choice: New Products

Low-capacity data logger substitutes bubbles for tapes


Rather than record data on tape cassettes, Model MBM-1 stores it in two 64k-bit, 4-page Fujitsu FMB31CA bubble-memory cassettes. These devices can be easily removed and transported and reused an unlimited number of times without degradation or loss of data.

The MBM-1 incorporates two input ports: a serial RS-232C unit permitting data rates ranging from 110 to 19,200 baud and an 8-bit parallel port supporting 2k-bytes/sec transfer rates. Its recording format permits writing of special control characters differentiable from other 8-bit binary inputs because each byte is recorded in a 9-bit code.

CMOS logic

The data logger employs CMOS logic that supports control instructions from a host processor or those generated from the front panel. The front-panel functions include Write (sets the Record mode), Read (sets the Read mode), Read Off (stops a read operation), Erase (removes all data from cassette memory and puts a start mark at the first available location), Start (initializes a cassette at prerecorded start mark for either reading or writing), File (puts a byte in a cassette to identify a specific file for later search), Page (moves the memory pointer to the next logical page in the 64k-bit memory map) and Reset (reinitializes the system).

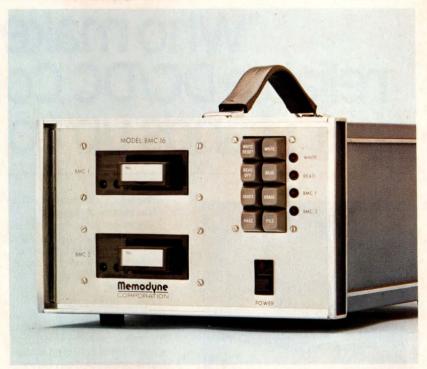The unit suits industrialcontrol applications requiring



Using two 64k-bit bubble-memory cassettes, Model MBM-1 solves data-logger reliability problems in harsh environments.

small amounts of memory but high reliability. According to the manufacturer, it finds use in environments subject to dust, chemicals or drastic temperature changes.

Because the bubble module incorporates no moving parts,

nothing can fail as a result of mechanical stress caused by temperature variations, \$1995.

Memodyne Corp, 220 Reservoir St, Needham Heights, MA 02194. Phone (617) 444-7000. Circle No 454

Look for a Special Report on highfrequency instruments in EDN's February 18 issue. You'll also find articles on


- The use of S/H amplifiers as circuit components
- The design of effective EMI and RFI shielding
- The role of digital simulation in increasing your design expertise
 The computerized analysis of
- transient response

NEXT TIME

• The use of a digital storage scope's Envelope mode to catch short-lived glitches on long sweeps.

... and much more. Also look for news stories on the latest benchtop testers and on "standards" that sometimes aren't, plus our regular μ C Design Techniques, Design Ideas and A Question of Law departments. You can't afford to miss this issue!

EDN: Everything Designers Need

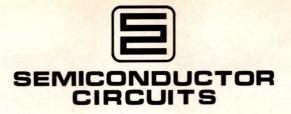

NOISE! TEMPERATURE! TRANSIENTS!

"Who makes a reliable DC/DC Converter that stands up to all of it?"



CU chassis mount



We do... because we know what you're up against!

We know your operational problems are complex. That's why we combined a host of innovations into our U and CU series of 25W dc/dc converters.

A 4:1 input range — unique in the industry — is standard in this line. So is the special filter that isolates the input source from reflected spikes. Input protective circuitry can sustain a minimum of 40% overvoltage, making transient suppression simple. Protective circuitry safeguards the input source and the output load. Remote shutdown conserves power and offers sequencing capability, and the self-resetting shutdown system ensures continuous operation. That's reliability!

Great innovations. Great choices. Both series are available with single, triple, or quadruple outputs. The shielded cases are designed for mounting convenience and noise-free operation. And like *all* the power supplies we make, our U and CU lines require *no derating from* -25° to $+71^{\circ}$ C. Converters are 10-piece-priced at \$157 for single output (5V or 12V), \$228 for triple outputs (±5V, +12V, or +5V, ±15V), and \$228 for quadruple outputs (±5V, ±12V).

For process control, telecommunications, any application where reliability and noise control are vital in a dc/dc converter, depend on us for the answer. We are Semiconductor Circuits. Call on us for problem solving. Look to us for innovation. See our product listings in EEM and Gold Book and ask for a free wall chart of our products.

Problem Solving Through Innovation



49 Range Road Windham, NH 03087 (603) 893-2330

© Semiconductor Circuits, Inc. 1980

SALES OFFICES: AL., Huntsville (205)882-0827; AZ., Scottsdale (602)994-3230; CA., Santa Ana (714)557-9780; Milpitas (408)946-8300; CO., Denver (303)759-1666; CT., Guilford (203)453-5424; FL., Meibourne (305)259-2711; GA., Atlanta (404)252-6609; IA., Cedar Rapids (319)365-8071; IL., La Grange Park (312)354-5100; IN., Indianapolis (317)21-1621; KS., Derby (316)788-0621; Mission (913)831-0555; KY., Louisville (502)451-1860; MA., Wellesley Hills (617)235-2330; MD., Baltimore (301)247-0400; MI., Farmington Hills (313)553-9800; MN., Minneapolis (612)553-1886; MO., Hazelwood (314)895-4577; NC., Greensboro (919)294-4783; NJ., Ho-Ho-Kus (201)447-1770; Livingston (201)992-5331; NY., Clark Mills (315)853-6126; Pittsford (716)381-8350; Plainview (516)681-3163; Syracuse (315)458-5241; OH., Dayton (513)890-2150; Shaker Heights (216)491-9177; Columbus (614)888-0483; OR., Tigard (503)641-4463; PA., Allison Park (412)487-4300; Harleysuille (215)643-5560; TX., Addison (214)887-2489; Austin (512)452-9459; Houston (713)988-0991; UT., Salt Lake City (801)484-4222; VA., Lynchburg (804)237-6221; WA., Bellevue (206)451-8223; WA., Yakima (509)248-9114; WI., Elm Grove (414)784-5212.

Editor's Choice: New Products

5×8×11-in. switching supply delivers 1500W

Model PM 2501 provides as much as 1500W in a standard $5 \times$ 8×11 -in. package: 2V at 400A, 5V at 300A, 12V at 120A, 15V at 100A, 18V at 90A, 24V at 66A, 28V at 54A or 48V at 32A. And the voltage you specify stays solid as the ac input varies from 182 to 262V (47 to 63 Hz); the switcher is even protected from line dips down to 160V ac.

Throughout, the supply's worst-case error band never exceeds $\pm 2\%$ or ± 100 mV, whichever is greater. This band includes variations caused by

- Input-power fluctuations over the specified range
- Static loads from 0 to 100%
- Dynamic load steps (10µsec rise) of 25% or 50A, whichever is smaller
- Ripple and switching spikes
- Temperature variations from 0 to 50°C
- Drift for an 8-hr period following initial warmup.

Foldback current limiting

The supply's current-limiting circuitry initiates foldback when the switcher delivers 100 to 120% of its full load current. The output recovers automatically from overcurrent shutdown after you remove the load fault. Overvoltage-protection circuits ensure that your system will never see more than 125% $(\pm 10\%)$ of the rated output voltage.

If the input power quits completely, the PM 2501 provides 20 msec of hold-up time. An optional power-fail



In a package that formerly provided 1000W, Model PM 2501 delivers 1500W. The 20-lb switcher comes with foldback and current limiting and furnishes a 20-msec hold-up period.

circuit allows the supply to notify the system immediately.

Other options include logic inhibit and enable, crowbar, remote programming, automatic paralleling and a Power Good signal. And if necessary, the manufacturer can tailor the supply to meet unusual requirements.

The standard supply weighs

20 lbs and comes with an LC EMI-suppression filter. Adding an external filter allows the unit to meet VDE 0871B specs.

A 5V, 300A model costs \$1000. Delivery, 6 to 8 wks ARO.


Pioneer Magnetics, 1745 Berkeley St, Santa Monica, CA 90404. Phone (213) 829-6751. Circle No 453

Insert this preassembled card edge connector in one step, and forget it.

Preassembled to cut backplane production time. Designed for mother board insertion without damage to plated-through holes.

The one-step AMP PACE Connector does a lot to make your production simpler—and free from worry.

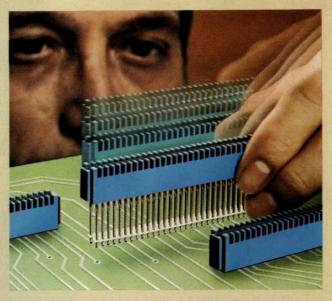Using our unique ACTION PIN contact compliant design, just press the connector into place. Assembly is



complete. There's no solder or costly, time-wasting rejects.

Even our Accu-plate precision plating avoids waste. By pinpointing gold only on the final contact area and using nickel and tin elsewhere, you don't pay for what you don't need.

The AMP PACE Connector. It's good enough to forget.

AMP Facts

Description: preassembled card edge connectors for .100" x .100," .100" x .200," and .125" x .250" centerlines; size 15 to 61, dual position. Contact Rating: 3 Amp Contact Resistance: Spring contact to test board-8 milliohms Total circuit resistance-9 milliohms Operating Temperature: -55°C to +85°C Voltage Rating (Sea Level): .100' centerline spacing-1000 VAC Insulation Resistance: 5,000 Megohms Durability: 100 cycles Salt Spray: MIL-STD-1344, Method 1001 Thermal Shock: MIL-STD-1344, Method 1003 Physical Shock: MIL-STD-1344, Method 2004 Humidity: MIL-STD-1344, Method 1002, Type II Vibration: MIL-STD-1344, Method 2005

For more information, call the AMP PACE Connector Desk at (717) 780-8400. AMP Incorporated, Harrisburg, PA 17105.


AMP, AMP PACE and ACTION PIN are trademarks of AMP Incorporated.

Accu-plate precision plating puts the gold where it does the most good, for superior electrical contact at a reasonable cost.

The contact's unique beam design accommodates and compensates for daughter board ____ warp and stress, assuring long-term, reliable performance.


Spring sections of ACTION PIN contacts compress in opposite directions, maintaining a gas-tight fit with pc board.

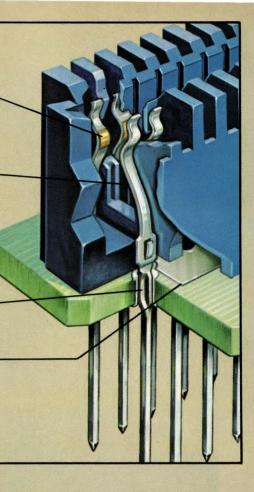Mylar strip assures straight and stable pin alignment.



CIRCLE



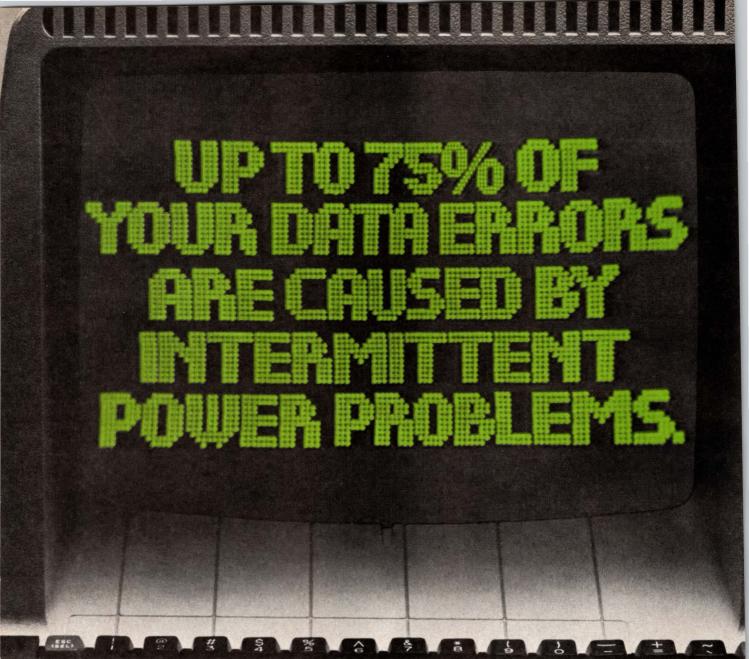

Stabiline[®] power conditioners slash data loss and errors.

Most data loss and errors are caused by electrical noise and line voltage fluctuations. Not by your hardware or software, as many people think.

Stabiline[®] Automatic Voltage Regulators intercept these power irregularities before they can cause problems in microprocessors and computers. They virtually eliminate powerline variations before they create erratic operations, damage components or shorten equipment life.

Let us show you how to condition your power input with one of Superior Electric's many power conditioners. All designed with state-ofthe-art technology to provide smooth, dependable power, in lightweight, low cost units. Call Richard Pettey 203-582-9561 or write The Superior Electric Company, Bristol, CT 06010 today for a FREE problem power troubleshooting manual and complete product information.



© 1980 The Superior Electric Company Stabiline® Automatic Voltage Regulators is a Reg. TM of The Superior Electric Company For more information. Circle No 47

µC Design Techniques

Program calculates stock-options tax

Ed Oxner

Siliconix Inc, Santa Clara, CA

If your company's stock-purchase plan offers you the opportunity to buy shares at less than the fair market price, you could be subject to a preferential tax. But whether or not you were aware that purchasing shares under either a qualified or restricted stock-option plan poses a potential tax liability, you might find this program for the HP-67 calculator useful.

Under current IRS rulings, the preferential tax is based on a simple formula: If the total cost of the shares purchased at your option price is more than \$10,000 under the fair market price for a like number of shares at the time of your purchase, you must pay a tax on the amount exceeding \$10,000. The tax rate is now 15%. (Remember, too, that when you sell the stock you must also consider your tax liability.)

The program (figure) offers two types of solutions: You can ask how many shares you can buy to avoid liability for the tax, or you can ask how much tax you'll owe on the number of shares you wish to purchase. Of course, the input figures you use might not be the final figures your company uses when it gets around to placing your order, but they should be close. Should the IRS modify its tax structure, the program will still prove useful because both the allowable amount and the tax rate are variables.

To use the program, enter:

- A=Your option price in decimal dollars; for example: \$3.75
- B=Government allowance, currently \$10,000
- C=Preferential-tax rate in percent, currently 15%
- D=Fair market price per share in decimal dollars; for example: \$16.375 (16% per share)
- E=If you're asking how many tax-free shares you can purchase, just hit the key. On the other hand, if you want to know your tax liability, enter the number of shares you wish to buy.

The program produces one of two types of answers. If you're asking how many shares you can buy without incurring a tax, a whole number will appear. For instance, the example figures lead to an answer of 791 tax-free shares. If you're asking for your tax liability on a specified number of shares, on the other hand, one of two numbers will appear. For a number of shares less than the maximum (791 in this example), you'll get the number of shares allowable with no tax liability. For a request greater than what is tax free, a decimal-dollar figure results. For example, the tax liability on 900 shares using the example figures is \$204.38.

1.1			and the second second						
	STEP	KEY ENTRY	KEY CODE	STEP	KEY ENTRY	KEY CODE	STEP	KEY ENTRY	KEY CODE
	001	f LBL A	31 25 11	025	RCL 8	34 08	049	STO+3	33 61 03
	002	STO A	33 11	026	h RTN	35 22	050	GTO (i)	22 24
	003	h RTN	35 22	027	f LBL 1	31 25 01	051	f LBL 4	31 25 04
	004	f LBL B	31 25 12	028	f GSB 2	31 22 02	052	RCL 3	34 03
	005	STO B	33 12	029	h RTN	35 22	053	h RTN	35 22
	006	h RTN	35 22	030	f LBL 2	31 25 02	054	f LBL 6	31 25 06
	007	f LBL C	31 25 13	031	1	01	055	RCL D	34 14
	008	STO C	33 13	032	5	05	056	RCL 9	34 09
	009	h RTN	35 22	033	CHS	42	057	Х	71
	010	f LBL D	31 25 14	034	h ST I	35 33	058	STO 8	33 08
	011	STO D	33 14	035	RCL 3	34 03	059	RCL A	34 11
	012	h RTN	35 22	036	RCL A	34 11	060	RCL 9	34 09
	013	f LBL E	31 25 15	037	Х	71	061	Х	71
	014	STO 3	33 03	038	RCL B	34 12	062	STO-8	35 51 08
	015	STO 9	33 09	039	+	61	063	RCL 8	34 08
	016	f x=Ø ?	31 51	040	RCL D	34 14	064	RCL B	34 12
	017	GTO 1	22 01	041	÷	81	065	-	51
	018	f GSB 2	31 22 02	042	f INT	31 83	066	ENTER	41
	019	STO 8	33 08	043	RCL 3	34 03	067	RCL C	34 13
	020	RCL 9	34 09	044	-	51	068	f %	31 82
	021	-	51	045	STO 5	33 05	069	DSP 2	23 02
	022	f x Ø ?	31 71	046	f x=Ø ?	31 51	070	h RTN	35 22
	023	GTO 6	22 06	047	GTO 4	22 04	071	R/S	84
	024	DSP Ø	23 00	048	RCL 5	34 05			

Use your HP-67 to calculate the tax liability when you take advantage of your company's stock-option plan.

µC Design Techniques

Interrogation tells µP which boards are present

N D Mackintosh

Burroughs Corp, Westlake Village, CA


One of the microprocessor's greatest assets is its versatility. And to take advantage of this feature, more and more systems are being designed in a rack format, in which several card positions suit any number of different cards. As a result, the μP must be able to determine which cards are plugged in and which positions they occupy.

The simple answer to this problem centers on switches mounted on a subpanel. But this approach ignores situations in which a board is removed for repair while the rest of the system keeps running. A more elegant solution provides the μP with the ability to interrogate each board to determine its type. Because all boards already have address decoding, the task proves simple and might require adding no hardware at all. The required added function consists of one extra address—a board address (rather than the function address already used).

At power-on or at regular intervals, the μP performs an attendance check, sending out the address reserved for each board position and determining what comes back on the data bus. When the μP addresses a given board and no board is present, the data bus's pull-up resistors cause the bus to read all ONEs.

If a board is in a slot, it must impose a ZERO on one or more of the data-bus lines to indicate its presence. Each board should have a unique pattern that indicates its type; by toggling only one bit, your system can identify as many as eight types, and using all eight bits provides identification of 255.

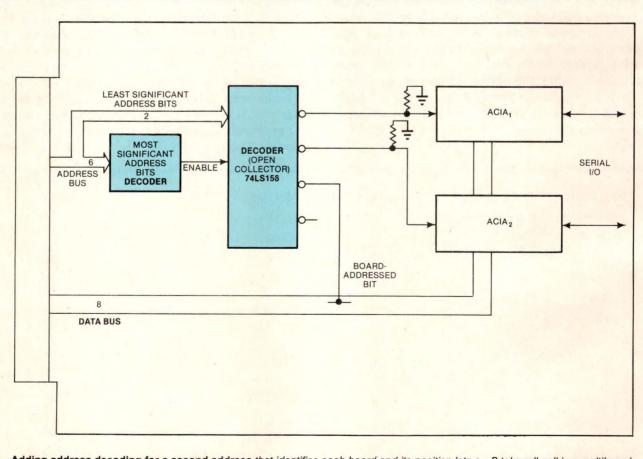The **figure** illustrates a simple open-collector decoder that can directly indicate a board's presence by manipulating a bit on the data bus. **EDN**



Adding address decoding for a second address that identifies each board and its position lets a µP take roll call in a multiboard system.

The World's Largest, Best-Attended Electronics Manufacturing Exposition



FEBRUARY 24-26, 1981 Anaheim Convention Center, California

Presenting solutions to manufacturing problems in **PWB** fabrication, circuit assembly, hybrid microelectronics, semiconductor processing and electronic testing

Plan NOW to Participate

SUPPLIERS: For information on exhibiting, telephone (312) 263-4866, or write The Kiver Organization, 222 W. Adams St., Chicago, IL 60606. Telex 256148

SHOW VISITORS:

Use the coupon below

SPONSORED BY

Electronic Packaging and Production magazine Semiconductor International magazine The International Electronics Packaging Society American Society for Quality Control, **Electronics Division** The California Circuits Association The Arizona Printed Circuits Association

ORGANIZED BY The

Kiver Organization

222 W. Adams Street, Chicago, Illinois 60606 Telex 256148 (312) 263-4866



A Cahners Exposition Group Company

OVER 1,400 DISPLAYS

including a separate area on the exhibit floor devoted exclusively to the

"Electronics Testing Center"

PRODUCTIVE TECHNICAL PROGRAM

PWB Fabrication/Production Artwork Design & Generation, Etching, Screen Printing, Cleaning (aqueous and solvent), Materials (flex circuits and multilayers)

Hybrid Microelectronics and Semiconductor Processing

Vacuum Deposition, Laminar Flow, Wafer Processing, Micro Lithography, Laser Trimming and Marking

Automated Assembly/Packaging Component Insertion Machinery, Soldering, Component Trimmers, Lead Cutters, Connector Technology

Electronic Testing **ATE Systems** Wire Harness Cable Testers, QC/QA Inspection, Microcircuit IC Testing

Management Workshop "Managing Human Resources"

FREE ADMISSION TO THE EXHIBITION

SAVE \$1000

Bring this coupon to Registration Desks at NEPCON WEST '81

(Make copies for your associates)

*µ***C Design Techniques**

EDN Software Note #62 Program tests 9900 system's memory

Ralph Tenney

George Goode & Associates Inc, Dallas, TX

The program shown in the **figure** helps maintain several TM 990/302 software-development systems. Produced with the 302's resident assembler, the procedure begins with a simple functional test clear all memory under test. A walking-ONEs test follows; this procedure involves successively writing a ONE to each bit in a 16-bit memory word, beginning with $8000_{\rm H}$, then leaving the value $0001_{\rm H}$ in each word. The program tests the write operation at each bit location before moving to the next one. The final test writes all ONEs (FFFF) to a location, then checks the remaining locations for possible changes.

The procedure involves three error flags and error messages. An error stops the test; you must then check the offending location with the debugging monitor to determine whether the error is soft or hard. For a hard error, you must change the test boundaries to exclude the affected location; a soft error only requires starting the test from scratch.

The test isn't rapid; you'll need approximately 5 min to perform one iteration over $3000_{\rm H}$ locations. Each successful pass prints "OK" on the terminal. Thus, you can leave the system in the Test mode for long periods of time and know how many iterations it has made. At the end of a complete test, one "OK" will have been printed for each program iteration, followed by "AA." Failure to pass the memory-clear test produces only "AA," while failure of the walking-ONEs test produces "BB." If the all-ONEs test fails, you'll see "FF."

Share your experiences

Can you provide any hints that will help EDN's readers better utilize their own μ Cs and more thoroughly enjoy experimenting with those systems? Have you developed hardware that expands development-system capabilities? How about software (even games you've programmed for a specific system)? Hobby applications such as ham radio or robot-construction projects make interesting reading, too, and we solicit your inputs.

EDN pays \$25 for every article we publish in μ C Design Techniques. Send your ideas (or call to discuss any suggestions) to:

EDN μC Design Techniques 221 Columbus Ave Boston, MA 02116 (617) 536-7780

009		0000		EQU EQU	0 1	
011)	0002	R2	EQU	2 3	
013	1	0004	R4	EQU	4	1
014)	0005	R6	EQU	5 6 7	
016)].	0007		EQU	7	
018	1	0009		EQU	9 10	
020	0	0008	R11	EOU	11	
021		0000	R13	EQU	12	
0231		000E	P15	E0U EQU	14 15	
0250	0000)	+THIS	PROG	RAM IS A MEME	DRY TEST WHICH CLEARS THE MEMORY
0271	0000)	+BIT	TEST	IS PERFORMED,	DRY TEST WHICH CLEARS THE MEMORY HECKS THE RESULT. THEN A WALKING FOLLOWED BY WRITING ALL ONES TO THE WHOLE MEMORY. THEN WRITING
0291	0000)	+IU I	HE ME	XI LUCHIIUN.	ENTER THE STHRTING ADDRESS IN
030	0000		+F1.	THE E	NDING ADDRESS S IN R7.	IN R2, AND THE NUMBER OF TEST
0321)) 3E00			IDT	MTST/ >BE00	
) 3E00	0350 (LUPI		
0351	3E04	2 3E90 C101	ST	MOV	P1.R4	GET STARTING ADDRESS SET UP STARTING PATTERN
0361) 3E06) 3E08	0405		CLR	R5 R8,1	SET UP STARTING PATTERN SET UP A TEST PATTERN
0381	3E 0A	0001	DUT1		R5. +R4	AND WRITE IT TO MEMORY
0391) 3E ()E	8084		C	R4, P2	TEST FOR END ADDRESS
0401	3E18	8174		JEO	TST2 ◆R4++R5	IF END, START NEXT TEST CORRECT MEMORY ENTRY?
		1626		JHE	ERRÓ R4+R2	REPORT THE ERROR LAST LOCATION?
0440		12F9 C101		JLE	DUT1 R1,R4	IF NDT. GD AGAIN GET STARTING ADDRESS
0460	3E10	0205		LI	R5,>8000	SET UP WALKING BIT START PATTERN
0470	3E20	C505	DUT2	MOV	P5. +R4	AND WRITE IT TO MEMORY
0490	3E24			CUER	R4+R2 TST3	TEST FOR END ADDRESS IF END, START NEXT TEST
0500		8154 161F		C JINE	+R4+R5 ERR1	CHECK FOR CORRECT MEMORY CONTENTS REPORT ERROR
0520	3E20	0B15		SRC	R5,1 R5,>8000	WALK THE BIT TEST FOR FULL SHIFT
	3ESE	8000				
	3E35	0504		JNE		IF NOT DONE, FINISH UP BEGIN TESTING
		10F5 C101		JMP MOV	DUT2 R1,R4	DN NEXT LOCATION GET STARTING ADDRESS AGAIN
0580	3E38	0705 0505		SETD	R5 R5.+R4	SET PATTERN TO ALL ONES
06.00	3E3C	C182	uora.	MOV	R2+R6	WRITE IT IN MEMORY SAVE END ADDRESS
0620	SESE SE40	C186		MOV	R4,R6 R6,R6	FIND OUT HOW MANY LOCATIONS LEFT ANY UNTESTED LOCATION?
0630	3E42 3E44	1309 8154		UE0 C	REPT +R4,R5	IF NOT, CLEAN UP AND GD HOME TEST FOR CORPENT MEMORY ENTRY
	3E46 3E48			JNE MOV	ERRF P4+R9	REPORT ANY ERRORS SAVE CURRENT TEST POINTER
0670	3E4A	8219	CPAT	C	*R9,R8	TEST FOR CHANGED PATTERN
0690	3E4E	1BFD		JH	CPAT	BUMP TO NEXT LOCATION TO BE CHECKE CONTINUE TESTING UNTIL DONE
0710	3E52	8084		INCT C	R4. P2	BUMP POINTER TO NEXT LOCATION LAST LOCATION?
0720		12F2 0200	REPT	JLE	DUT3 R0,MSDK	REPEAT UNTIL DONE
0740	3E58 3E5A	3E7C			₽>E01C	AND OUTPUT IT
0750	3E5C	E01C		DEC	R7	BUMP THE COUNTER
0760	3E6.0	1BD1	EDDO	JH	ST	AND REPEAT TESTS UNTIL DONE
	3E64	3E81	ERRO	LI	ROIMSSA	GET FIRST ERROR FLAG
0780 0790	3E68		ERP1	JMP	EXIT R0.MSSB	AND PRINT IT GET SECOND ERROR FLAG
0800	3E6A 3E60	3E86 1003			EXIT	AND PRINT IT
0810	3E6E	0200 3E8B	ERRF		ROIMSSE	GET THIRD ERROR FLAG
0820	3E72	1000		JMP		AND PRINT IT
	3E76	E01C	EXIT		⊋>E01C	ISSUE STATUS
	3E78 3E78	E000		BLWP	<pre>\$>€000</pre>	AND GO HOME
0850	3E7C	4F4B 0D0A	MSOK	BYTE	>4F.>4B.>0D.	OA
0860	3E80		MSSO	BYTE	0 >41,>41,>0D,>	
	3E83	ODOA	Heen			WH I I I I I I I I I I I I I I I I I I I
0890	3E85 3E86	4242	MSSR	BYTE	0 >42,>42,>0D,)	0A
0900	3E88 3E8A	0000		BYTE	0	
0910	3E8B	4646 0D0A	MSSF	BYTE	>46,>46,>0D,>	OA
	3E8F	0000	us.	BYTE		
0940		3E 0 0	m2	BSS	STO	STOP ASSEMBLY AND LOAD PC
ERPOR	<2=0					

Make three specific memory checks on a TM 990/302 system with this diagnostic program.

MINIATURIZED POWER SUPPLIES





Nominal Output Voltage	0	Regulation		Dimula			dian and
	Output Current Amps.	Load ±%	Line ±%	Ripple mv RMS	Price	Model	Case Size
55555	.500 1.0 1.5 2.0 2.5	.15 .25 .35 .25 .25	.05 .05 .1 .05 .05	1 1 1 1	\$ 55 75 105 115 130	5EB50 5EB100 5EB150 5EB200 5EB250	EB-10 EB-13 EB-13 EB-20 EB-20
±12	.100	.05	.05	1	55	DB12-10	EB-10
±12	.150	.05	.05	1	65	DB12-15	EB-10
±12	.200	.05	:05	1	75	DB12-20	EB-10
±12	.300	.05	.05	1	105	DB12-30	EB-13
±12	.350	.05	.05	1	110	DB12-35	EB-13
±12	.500	.1	.05	1	135	DB12-50	EB-20
±15	.100	.05	.05	1	55	DB15-10	EB-10
±15	.150	.05	.05	1	65	DB15-15	EB-10
±15	.200	.05	.05	1	75	DB15-20	EB-10
±15	.300	.05	.05	1	105	DB15-30	EB-13
±15	.350	.05	.05	1	110	DB15-35	EB-13
±15	.500	.1	.05	1	135	DB15-50	EB-20

PCB Mounting

With Screw Terminals

Nominal	Quitaut	Regu	lation	Dinula			
Output Voltage	Output Current Amps.	Load ±%	Line ±%	Ripple mv RMS	Price	Model	Case Size
555555	.250 .500 1.0 1.5 2.0 2.5	.05 .1 .2 .3 .15 .15	.05 .05 .05 .1 .05 .05	0.5 1 1 1 1	\$ 39 49 69 98 110 125	5E25 5E50A 5E100 5E150 5E200 5E250	ES-10 EL-10 EL-13 EL-13 EL-20 EL-20
$\pm 12 \\ \pm 12 \\ $.025 .050 .100 .150	.1 .1 .05 .05	.05 .05 .05 .05	1 1 1 1	24 39 49 59	D12-03 D12-05 D12-10A D12-15A	ES-10 ES-10 EL-10 EL-10
±12 ±12 ±12 ±12 ±12	.200 .300 .350 .500	.05 .05 .05 .1	.05 .05 .05 .05	1 1 1 1	69 98 105 130	D12-20 D12-30 D12-35 D12-50	EL-10 EL-13 EL-13 EL-20
±15 ±15 ±15 ±15	.025 .050 .100 .150	.1 .1 .05 .05	.05 .05 .05 .05	1 1 1 1	24 39 49 59	D15-03 D15-05 D15-10A D15-15A	ES-10 ES-10 EL-10 EL-10
+15 +15 +15 +15 +15	.200 .300 .350 .500	.05 .05 .05 .1	.05 .05 .05 .05	1 1 1 1	69 98 105 130	D15-20 D15-30 D15-35 D15-50	EL-10 EL-13 EL-13 EL-20

Input Voltage: 105-125 Vac, 47 to 420 Hz, single phase.

Output Voltage Setting: Single output models are factory preset to within $\pm 2\%$ of nominal output voltage, and may be more precisely trimmed to the nominal voltage rating with an external trim resistor. Dual models are set to within $\pm 1\%$ of their nominal ratings, and are not trimable.

gcopian

MINIATURE AC to DC POWER MODULE

Polarity: Either positive or negative terminal of a single output module may be grounded. Dual output modules have a positive/common/negative output terminal configuration.

Ambient Operating Temperature: -20 to $+71^{\circ}$ C. (Model 5E150 and 5EB150, 0 to $+71^{\circ}$ C.) No derating required.

Temperature Coefficient: 5-volt models, .03%/°C; dual output models, .015%/°C.

Impedance: 0.07 ohm at 1 kHz, 0.2 ohm at 10 kHz (approx.).

Optional 230 Volt Input: To order, add suffix "-230" to model number and \$10.00 to price.

Case Sizes and Weight:


EB-10: 3.5" x 2.5" x 1.375" (1 lb) EB-13: 3.5" x 2.5" x 1.625" (1 lb 5 oz) EB-20: 3.5" x 2.5" x 2.375" (2 lb 1 oz) EL-10: 3.5" x 2.5" x 1" (15 oz) EL-13: 3.5" x 2.5" x 1.25" (1 lb 3 oz) EL-20: 3.5" x 2.5" x 2" (2 lb) ES-10: 2.3" x 1.8" x 1" (7 oz)


Other models available from 1 to 75 volts. Send for complete information.



Corp., Easton, Pa. 18042 Tel: (215) 258-5441

For more information, Circle No 49

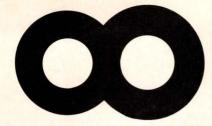

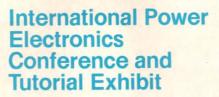

April 27 - 30, 1981 Loews Anatole Hotel Dallas, Texas


Some facts about POWERCON...

Over 85% of the registered attendees at a POWERCON conference are practicing power electronics engineers and engineering managers.

POWERCON conferences, seminars and tutorial exhibits are designed by practicing power electronics technologists, like you. That means we know what you need most.

A POWERCON must be *experienced*, for the value of even the most exemplary technical presentation cannot begin to compare with the catalytic effect of being among, and comparing notes and experiences with, the hundreds of your contemporaries who attend.

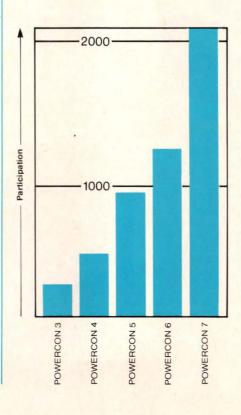The participation in POWERCON has increased phenomenally over the past 5 years (see for yourself, below). And we frequently sell out.



POWERCON. Once a technical luxury. Now a professional and practical necessity.

The Conference

Eighth in a series of annual technical conferences devoted exclusively to the practical design and application of solid-state power electronics equipment and components. Emphasizing the modern trend to switched-mode and other "non-dissipative" technologies, POWERCON conferences offer a comprehensive and intensive examination of the latest and most important developments in the power electronics field.

- Three full days of technical presentations.
- Over 50 papers, presented by outstanding power electronics authorities.
- New MOSFET "know-how"... important new inverter and converter topologies...microprocessor-based power systems... controlled-resonant conversion... power electronics circuit modelling...reliability...computer-aided design and evaluation techniques ...dynamic performance...

Plus a new program expansion devoted to the specialist in high voltage, high power, and motor control.

The Tutorial Exhibit.

Over a hundred informal tutorial and "hands-on" (fully instrumented and working) demonstration exhibit booths presented by technologists representing significant suppliers in and to the power electronics field. Each exhibit is specially configured to enhance your technical expertise through improvement of your detailed knowledge of the supplier's technology and processes.

- Investigate working circuits and waveforms.
- See new devices in action.
- See working demonstrations of exciting new converter topologies.
- See new instrumentation and test equipment for power electronics.
- Magnetics. Capacitors. EMI. Heat transfer. IC's and hybrids. Complete power supplies, inverters and systems.
- And much, much more.

EDN FEBRUARY 4, 1981

Plus...an expanded Professional Advancement Seminar Program

Designed to provide in-depth treatment of those topics most essential to the power electronics specialist, POWERCON 8 Professional Advancement Seminars offer designers, managers and users a comprehensive selection of invaluable learning opportunities under the direction of some of the world's leading authorities. Topics to be presented include:

- Designing power electronics circuits for extremely high frequencies.
- Designing compact aerospace high-voltage converters.
- Measuring, assessing and controlling converter dynamic properties.
- Using computer-aided design methods in power electronics.
- Using power MOSFET's in high frequency power circuits.
- · Power converter noise measurement and assessment.
- Controlling motor drive dynamic properties.

... and for those in the "business end" of the business, our third annual power electronics marketing seminar.

In the interest of providing a quality learning experience, seminar registrations will be limited, and may not be available to last-minute registrants.

POWERCON is a registered service mark of Power Concepts, Inc. (Ronald I. Birdsall, President), an independent consulting and educa-tional firm dedicated to the advancement and dissemination of power electronics technology.

Hotel Headquarters for POWERCON 8

Loews ANATOLE Dallas

Only 5 minutes from downtown Dallas, this world-famous premiere resort hotel is located in a peaceful and out-of-town area just 20 minutes from Dallas/Ft. Worth International Airport. Combining the ultimate in pleasant surroundings with swimming, racquetball,

sophisticated conference facilities. and the full amenities of a world-class resort, the Loews Anatole promises a memorable POWERCON 8 experience.

As always, special room rates will be available to registered POWERCON 8 attendees.

For further information concerning POWERCON 8, please call: (805) 985-6978 or (805) 656-3948

Power Concepts, Inc	c., PO Box 5226, Ventura, CA 93003
	ush complete POWERCON 8 program and
Name	
Title	
Company	
Div./Dept	
Address	
City, State, Zip	
	ues may be interested in attending see send them invitations:
Name	Title
Name	Title
Power Concepts Inc. 1981	

For more information, Circle No 50

Switching power supplies

Tailoring a switching power supply to meet your special needs is one option today's product choices provide. (Photo courtesy Boschert Inc) The latest switchers allow you to take advantage of their low cost and small size in a wider variety of applications than ever.

Edward R Teja, Associate Editor

Whether or not switchers will eventually replace linear power supplies for all applications remains to be seen; but even now, they have changed the way you must think about powering your designs.

The latest switchers don't necessarily provide more features or a higher level of sophistication than linear supplies. Their significance comes from more basic values: They provide a system with all the power it needs while occupying less space and producing less heat than equivalent linear units—all at lower prices than linears for units supplying more than 50W. (Although one switcher advance—higher-than-100-kHz switching frequencies—will ultimately enhance these benefits, it hasn't appeared in products as rapidly as anticipated and might not prove as great a boon as some designers expect.)

To take advantage of switchers' benefits, however, you must avoid designing your system first and then allocating the leftover space to the power supply; if you follow this approach, you lose the flexibility to make advantageous tradeoffs among switchers' wide selection of packages, features, power levels and voltages. Instead, consider the supply at the beginning of the design procedure.

An efficient operation

The advantage of switching power supplies lies in their ability to operate inside your system with only convection cooling. Although all switchers can't work this way—some high-power units do employ fans open-frame supplies, at least, carry on the tradition.

Switchers don't care for high-temperature operation any more than linear units do, but the more efficient switchers generate less heat for any given task than linears do. It isn't unusual to see data sheets claiming 70 to 85% efficiency as a matter of course, with the more exotic switchers operating at more than 90% efficiency.

Note, however, that because efficiency is a widely touted specification, you must understand the many different ways manufacturers measure it. Although the definition of efficiency makes its calculation seem straightforward—divide the output power by the input power—actually measuring the input power can be a problem, according to RO Associates marketing vice president Richard Okada.

Why? Most power supplies employ a capacitive input filter. Thus, their input currents aren't sinusoidal, and conventional power-factor formulas don't apply. And if you try to measure the power with an integrating wattmeter, you probably won't get a valid reading, because some meters assume sinusoidal waveforms and others don't integrate quickly enough to measure the actual current.

Okada suggests applying dc to the supply's input for power measurements. (If your supply has an input transformer, you'll have to measure the transformer's losses separately.) The dc input lets you measure input and output power accurately and accounts for all losses except those in the input rectifier, which shouldn't affect accuracy by more than 1%.

If you doubt such a measurement's results, you can cross check them by measuring the actual heat loss in the supply—performing a calorimetric measurement.


High efficiency permits tiny size

One exciting aspect of switchers' cool operation comes in the form of small dc/dc converters that mount on pc boards. Tecnetics Inc, for example, sells a 1W hybrid unit that measures $1.05 \times 0.94 \times 0.32$ in. and fits in a DIP socket. It provides power conversion and isolation on cards where heat sinking isn't available. The supply accepts 5 to 28V and furnishes 5 to 300V; if you need dual outputs, they can each supply 5 to 24V.

Efficient switcher technology puts supplies on pc boards

Because these encapsulated units (either hermetically sealed or potted) cost \$75 apiece, though, they primarily suit less cost-conscious military applications.

Another small unit—a cube measuring $\frac{1}{2}$ in. on a side—provides 40 mW of unregulated dc from a 90 to 255V ac supply. Suitable for driving LCD panel meters and other low-power devices, the Microsource costs only \$3.55 (100). Higher power costs more, of course: A 100-mW $\frac{1}{2} \times \frac{3}{4} \times \frac{3}{4}$ -in. version runs \$3.57, and with regulation on all outputs, it's priced at \$5.07 (100). And a recently introduced $\frac{3}{4} \times \frac{3}{4} \times \frac{3}{4}$ -in. member of this miniature family produces a whopping $\frac{3}{4}$ W for approximately \$22.

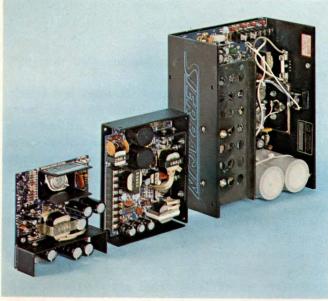


Providing dc power from 40 to 500W, Sierracin/Power Systems' switching-supply family members furnish a broad choice.



Modular power supplies from Intronics convert ac to dc right on a circuit card.

Stevens-Arnold has applied switcher technology in developing its wide-input-range, single-output dc/dc Switchpak modules. These 88%-efficient supplies provide 15 to 50W on pc cards. Intronics also offers modular power supplies. The SME Series, for example, converts ac to dc, delivering 2.5W and more. Various packages provide one 5V output at 500 mA (\$41) and triple outputs of 5V and either $\pm 12V$ or $\pm 15V$ (\$114). And the firm's recently introduced DCS Series meets dc/dc-conversion requirements for 30 to 100W.

Note that the modular approach allows you to standardize at least part of your power-supply design. You can utilize dc/dc converters from firms such as Endicott Research Group to transform the voltage from standard power supplies to nonstandard values as needed. Thus, you can buy one single-voltage supply and convert its output to any level between 5 and 1000V at 3, 6, 12 or 25W for about \$1 per watt.

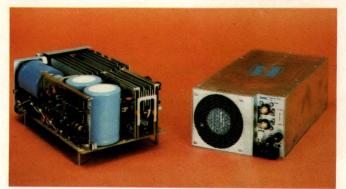

The first switcher to break the 1000W barrier in a 5×8 -in. box came from Boschert Inc. This Model HL1500 provides 5V at 300A.



For 1000W delivered as 5V at 200A, try Pioneer Magnetics' Model PM 2500A.



Switching regulators, such as Technology Dynamics' Model SR50P, can deliver 50W in a small package.

The selection doesn't stop here, either. Power/Mate sells encapsulated supplies, the Mini/Mate Series, that convert ac to dc on circuit boards (units priced at \$35 to \$102), provide higher power from a chassis-mounted device (\$69 to \$130) or convert dc to dc in 5 to 6W and 10 to 12W packages (\$94 to \$99). And offering a 25W board-mountable switcher that competes in price with 5W encapsulated linear supplies, Power General sells its Series 325 units for \$89. These off-line switchers measure $2.75 \times 4 \times 1.375$ in. and furnish 80% efficiency.


With yet another alternative, Powercube's Cirkitblock Modules furnish the means for creating a custom supply for your application at any power rating between 50 and 100W. You select the appropriately spec'd switching preregulator, high-frequency generator and transformer-isolated output modules. For high-power applications, the Cirkitblocks mount inside heat sinks.

Keep the supply in the open

Although such modules and modular supplies are important because they let you take advantage of switcher technology in a custom manner, they don't represent the mainstream of switcher technology. The switchers that have really made inroads into the linear-power-supply market are open-frame supplies in the 50 to 500W range.

Open-frame switchers have broken the price barriers between switchers and linear supplies apparent over the last couple of years and typically provide the lowest cost solutions to medium-power, multiple-output needs. The classic application for switchers—EDP equipment—exemplifies these requirements; it also requires the small dimensions associated with switchers.

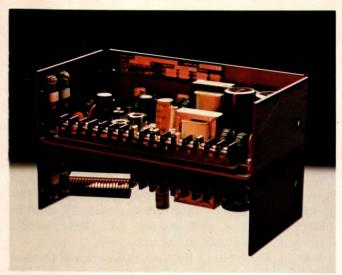Open-frame switchers don't usually come as single catalog items; each model actually represents a variety of versions. In this sense, most open-frame supplies are customized for specific applications. Note that each manufacturer offers products in a range of power levels and that low-power units operate according to flyback principles unlike those of higher power supplies. And



Operating at 40 kHz, LH Research's Teeny Tiny-Mite Series supplies provide power to 100W. The μ P in the foreground provides a size comparison.

because open-frame supplies generally demand different manufacturing talents than do enclosed units, the products a manufacturer chooses to offer tell you something about the areas of its expertise. Only the largest firms can afford continuing development of every switcher power rating and configuration.

One manufacturer, Sierracin/Power Systems, produces a fairly comprehensive line of switchers. This family covers power levels from 40 to 500W in a variety of output-voltage levels. Another firm, Boschert, markets open-frame units well down in the low-power range. Its standard 25W Model OL-25, for instance, suits small μ P systems, desktop calculators and mini CRT displays. The \$80 (100) unit measures only $2.5 \times 4 \times 6$ in.

Powertec keeps expanding its Valuswitcher 19 open-frame line, which now includes units providing four voltage outputs at six power levels from 50 to 400W. You can order all auxiliary outputs with either partial or full regulation. In the latter case, all outputs stay within 0.2% over 20 to 100% of rated load.

For low-power applications, LH Research has introduced the 40-kHz Teeny Tiny-Mite (TTM) Series; it includes 16 basic models that output combinations of dc levels up to 100W total. Prices range from \$205 (5V at 12A and 12V at 1.5A) to \$275 (5V at 12A, 15V at 3A, -15V at 1.5A, -5V at 0.5A and 24V at 2A). These supplies exhibit an extended hold-up time (the time a switcher's output takes to drop after the ac input drops out) of 20 msec, compared with the standard 16-msec spec most switchers provide. Error-proof voltage sequencing and power-fail detection come standard.

If you need only 75W, consider Condor Inc's \$150 Model MDS-75. This 75%-efficient (at 75W) supply restricts inrush current to 25A max and holds output ripple to 2% p-p on all outputs.


Another alternative, the Econoswitch Series from Power/Mate, gives you a choice of two broad lines—one featuring single-output units, the other offering multiple voltages. A monolithic chip containing the

Open-frame supplies furnish an alternative to custom units

supplies' regulation, modulation and protection circuitry reduces parts count by as much as 20%. Prices range from \$79 for 18W single-voltage units to \$399 for a multiple-output 300W supply.

Lambda Electronics—one of the pioneers in switchers—offers supplies that suit the same applications as open-frame units, yet are completely enclosed. Members of the LU Series, for instance, provide 5V at 3A in $3.82 \times 1.38 \times 3.54$ -in. packages for \$46. Other models furnish 12, 15 and 24V at the same price.

Finally, Elpac Power Systems makes one of the few switching supplies advertised as a convertible. Although most open-frame units require relayout and perhaps redesign to operate enclosed, you can get Elpac's ES130 switchers in either configuration. The 4-output supplies cost \$182 (250) as open-frame units and \$189 (250) enclosed. Designated the Ugly switchers, they produce 5V at 20A; auxiliaries are available for 12V at 1.5A, 15V at 1.2A and 5V at 0.5A.

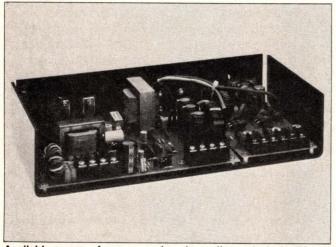

Available as open-frame or enclosed supplies, units in the ES 130 line come from Elpac Power Systems. The open-frame versions cost \$182 (250); enclosed units, \$189 (250).


The choice is yours

Open-frame supplies provide you with a multitude of features; output power, dc voltages, regulation, logic signals such as power-fail detect and other options all enter into a design decision. But except for supplies such as those in Power/Mate's Econoswitch Series, open-frame switchers aren't merely enclosed supplies with their lids removed; they tend to be designed for simplicity, both in their operation and manufacture.


Most open-frame units, for example, use only one pc card and are laid out much like their block diagrams indicate. In the case of the National Power Technology (NPT) switchers, for instance, you could confuse the circuit's board-layout plan with its block diagram; you can start at one end of the circuit board and trace the power flow from the ac input through the line filters and soft-start circuits to the control circuits and out the regulators.

This type of layout helps hold prices down because the manufacturer doesn't have to consume time and money dealing with the interaction of inputs and outputs—they never come close to each other. NPT's 200W switchers cost \$239 (100).

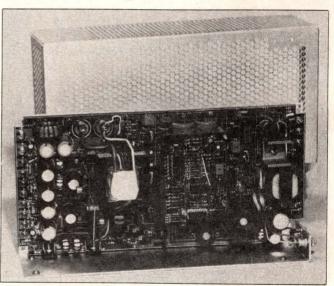
Another manufacturer, Kepco, exemplifies the drive



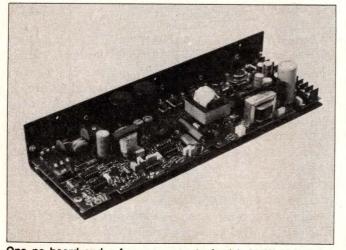Five independent dc outputs produce a total of 300W in Power/Mate's ESM 300 Series.



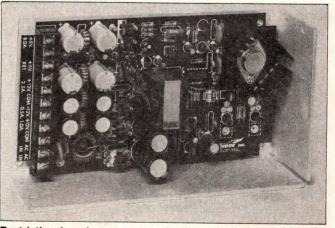One pc board and a few components furnish 200W in National Power Technology's open-frame switcher.




Restricting inrush current to 25A, Condor Inc's Model MDS-75 costs only \$150.

to bring costs down by using a different approach. In a joint effort with TDK, it has built a plant in Japan dedicated to building its EFX power supplies as inexpensively as possible. The plant began operation last year with 65% of the assembly procedures automated; by the end of this year, Kepco expects to have automated 85% of the processes involved in transforming bare circuit boards into finished power supplies. The firm feels that this approach produces supplies in large quantities while maintaining their reliability and reproducability.


A typical EFX model provides multiple outputs, is rated at 50W and suits EDP applications; it costs \$84 in OEM quantities. Other EFX-family members extend the range to 300W.

Custom-made versatility

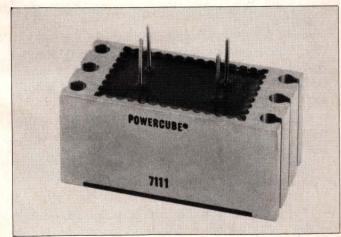The myriad versions of each manufacturer's openframe units exist because a certain degree of uniformity, combined with the right amount of versatility, produces power supplies exactly tailored to an application—without the premium charged for truly custom supplies. If you envision large production runs, though, you might well decide that a true custom supply is an



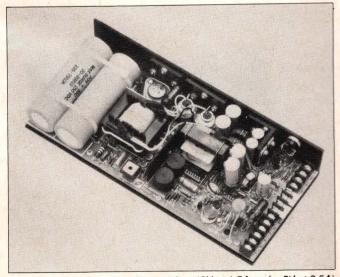Build a custom switching supply using Powercube's Cirkitblock modules.



Four common voltages (5V at 15A, \pm 12V at 1.5A and -5V at 0.5A) provide 111W from RO Associates' \$225 Model 912.


item your design can't live without. Space limitations or special power requirements sometimes preclude using even one of the tailored open-frame units, and custom-switcher prices can be reasonable in highvolume applications (but see **box**, "Buy or build?").

If, for example, you're designing a system for the Space Shuttle, cost becomes less of a factor than getting exactly the power supply you need—in terms of reliability and durability as well as the proper voltages and currents. And you might choose to do exactly what the Shuttle's equipment designers did: approach a modular-switcher house such as Arnold Magnetics.


Prices for custom switchers run a bit higher than those for conventional industrial units (a typical 4-output, 200W Arnold supply costs \$1100), but you get a unit that exceeds the rugged MIL-STD-810C and have it delivered within 8 wks. Not bad for a custom order.

Check out the subtle design factors

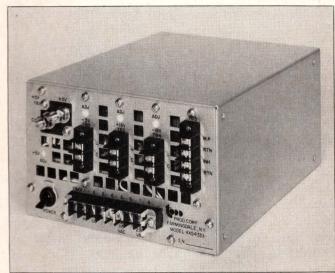How do you find the right unit for your application among the many different switchers discussed here? For one thing, examine such subtle factors as the way switchers would mount in your design. Additionally,



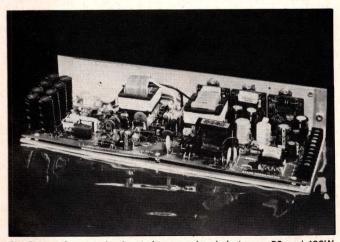High-power switchers usually provide a single voltage, but Todd Products Corp's SM3 brings 750W to the party in four outputs.



Get four voltage outputs at six power levels between 50 and 400W from Powertec's Valuswitcher 19 Series.

Ordering only the regulation required can save money

Power/Mate marketing VP Joe Geronimo suggests that you consider other parameters:

- Input-voltage range—A considerable price difference exists between a 90 to 130V ac-input supply and a 105 to 125V unit.
- Separate ground returns—Requiring a separate ground return for each supply output can reduce crosstalk.
- **Ripple and noise**—Specs can vary substantially, but a good switcher exhibits 50 to 75 mV p-p.

One last factor you must consider is whether you need regulation on all outputs. Each manufacturer provides a different regulation solution.

A great deal of effort has been required to convince system designers that every application doesn't need the 0.005% regulation linears offer so effortlessly. In this respect, Boschert Inc engineering VP Bob Boschert was a prime mover in pointing out that open-frame switchers with quasiregulation on auxiliary outputs suit many applications. In doing so, he opened the flood gates for the widespread use of this type of unit.

The argument against demanding regulation on every output is simple: If you manufacture a highvolume product, you can save a great deal of money by not paying for regulation where it isn't needed.

All switcher outputs do provide some regulation, though; a feedback loop stabilizes the primary output voltage, furnishing both line and load regulation. All auxiliary outputs benefit from such line regulation, too, but they don't have load regulation unless it's specifically added. These outputs' regulation can vary from 20 to 100%, according to ACDC Electronics's head of new-product development, Walter Hirschberg. He adds that you must also deal with some interaction between the main and auxiliary outputs.

Buy or build?

Jeff Shepard, LH Research Inc

(Ed note—The biggest competition faced by power-supply manufacturers comes from firms that design their own supplies. But many of these OEMs don't really understand the problems involved in such an undertaking. Here's one expert's look at what the task entails.)


If your company produces power supplies strictly for internal consumption, you'll encounter inflexibilities in the use of materials, parts or supplies compared with the situation of buying the complete unit outside. Purchasing another manufacturer's power supplies, however, permits you to buy from whatever source offers the best combination of price, quality and service. And you're then free to substitute items, shift vendors or split orders among competitors.

Additionally, companies that produce their own supplies can rarely afford the research-anddevelopment effort available to firms that make power supplies their primary business. Manufacturing power supplies for internal use involves new equipment, new skills, new technology and new personnel.


And if you intend to sell large numbers of units, you must ensure that your supply-production operation can meet the demand. Your designs must be flexible enough to meet all your system needs, too.

Unfortunately for designers, switchers involve high-power, nonlinear analog feedback circuits requiring production techniques that differ from most of those used in host digital systems. Thus, think twice before designing your own switchers.

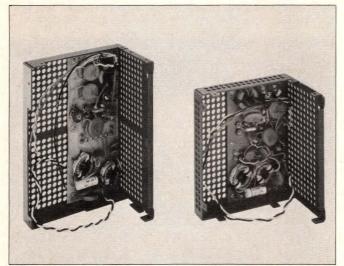(The author is manager of marketing operations at the Tustin, CA-based firm.)



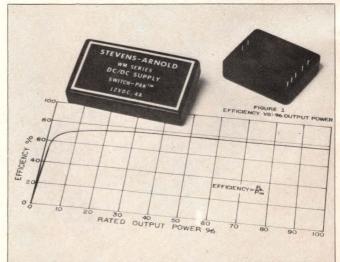EMI-suppression covers for Lambda switchers include filters to reduce conducted emissions.



Highly efficient switch-mode operation suits Stevens-Arnold's dc/dc supplies for use on pc boards.

MODEL	REGULATION (LINE OR LOAD)	RIPPLE (RMS)	VOLT VDC		OUTP MAX CUR 50°C	RENT AMP	S AT 71°C	PKG SIZE	DIMENSIONS ⁽²⁾ (INCHES)	PRIC
5 VOLTS ±	5% ADJ., 9V-1	2V AD	J.				and the second	-	(
ND-X-MPU(3)	0.1%	1.5	5±5%	7.0(5.95)	6.0(5.11		3.2(2.72)	х	7 x 4-7/8 x 2-7/8	\$172
ND-P-MPU(3)	0.1%	1.5	9-12	1.2(1.02)	1.110.94					
ND-P-MPU.	0.1%	1.5	5±5% 9—12	14.0 ^(13.3) 2.5 ^(2.38)	2.2(2.09		7.5 ^(7,13) 1.35 ^(1,28)	Р	11 x 4-7/8 x 4-13/32	245
de te de		Sec. 1		DUAL T	RACK	ING		1		
15 VOLTS	TO ±12 VOLT	S ADJ				1.2.2.4			and the second second second	
ND-Z-152	0.15%	1.5	±15 to ±12	0.6 ^(0.54) 0.6 ^(0.54)	0.55(0.5) 0.55(0.5)	0.45(0.41)	0.3(0.27)	Z	4-7/8 x 4 x 1-3/4	85
ND-Y-152	0.1%	1.5	±15 to	1.4(1.20)	1.2(1.02)	0.9(0.77)	0.6(0.51)	Y	5-5/8 x 4-7/8 x 2-5/8	120
ND-X-152	0.1%	1.5	±12 ±15 to	1.2 ^(1.02) 2.5 ^(2.13)	1.1(0.94) 2.1(1.79)	0.8(0.68)	0.5(0.43)	х	7 x 4-7/8 x 2-7/8	150
ND-W-152	0.1%	1.5	±12 ±15 to	2.3 ^(1.96) 3.3 ^(3.0)	1.9 ^(1.62) 3.1 ^(2.8)	1.4(1.2) 2.6(2.34)	0.9 ^(0.77) 2.0 ^(1.8)	w	9 x 5 x 2-7/8	
			±12	3.1(2.8)	2.8(2.52)	2.3(2.07)	1.6(1.44)			170
ND-P-152	0.1%	1.5	±15 to ±12	5.3 ^(5.04) 4.6 ^(4.37)	4.7(4.47) 4.0(3.80)	3.9 ^(3.71) 3.3 ^(3.14)	2.9 ^(2.76) 2.5 ^(2.38)	P	11 x 4-7/8 x 4-13/32	240
				SINGLE	OUTR	UT				
	REGULATION	RIPPLE		(1) MAX	CURREN	T AMPS AT		PKG	DIMENSIONS(2)	
MODEL	(LINE OR LOAD)	(RMS)	40° C	50°	C	60° C	71° C	SIZE	(INCHES)	PRIC
5 VOLTS ±										
NS-Z-5-OV	0.15%	1.5 1.5	3,0 ^(2.7) 6.0 ^(5.4)	2.74		2.3 ^(2.1) 4.2 ^(3.8)	1.7 ^(1.5) 3.1 ^(2.8)	Z	4-7/8 x 4 x 1-3/4	\$ 80
NS-X-5-OV	0.1%	1.5	10.0(8.5)	8.90		7.3(6.2)	5.3(4.5)	Y X	5-5/8 x 4-7/8 x 2-5/8 7 x 4-7/8 x 2-7/8	115
NS-W-5-OV	0.1%	1.5	14.0(11.9)			0.0(8.5)	7.5(6.4)	ŵ	9 x 5 x 2-7/8	175
NS-P-5-OV	0.1%	1.5	22.0(20.9)			6.5(15.68)	13.0(12.35)	P	11 x 4-7/8 x 4-13/32	220
S VOLTS ±	5% ADJ.									
NS-Z-6	0.15%	1.5	2.512.25			1.9(1.7)	1.4(1.3)	Z	4-7/8 x 4 x 1-3/4	75
NS-Y-6	0.1%	1.5	5.6(5.0)	4.9		4.0(3.6)	2.9(2.61)	Y	5-5/8 x 4-7/8 x 2-5/8	110
NS-X-6	0.1%	1.5	9.5(8.1)	8.4		7.1(6.0)	5.0(4.25)	×	7 x 4-7/8 x 2-7/8	130
NS-W-6	0.1% 0.1%	1.5 1.5	13.0(11.0) 20.5(19.4)			9.3 ^(7.9) 5.3 ^(14.54)	6.8 ^(5.9) 12.0 ^(11.4)	W P	9 x 5 x 2-7/8 11 x 4-7/8 x 4-13/32	165
2 VOLTS	-5% ADJ.					1.57				
NS-Z-12	0.15%	1.5	1.7(1.55)	1.6	1.45)	1.5(1.4)	1.3(1.2)	Z	4-7/8 x 4 x 1-3/4	75
NS-Y-12	0.1%	1.5	4.0(3.6)	3.50	3.15)	2.9(2.6)	2.2(2.0)	Y	5-5/8 x 4-7/8 x 2-5/8	110
NS-X-12	0.1%	1.5	6.5(5.5)	5.5		4.5(3.8)	3.3(2.8)	х	7 x 4-7/8 x 2-7/8	130
NS-W-12	0.1%	1.5 1.5	8.5 ^(7.2) 14.0 ^(13.3)	7.2		5.9 ^(5.0) 0.0 ^(9.5)	4.2 ^(3.6) 7.3 ^(6.94)	W	9 x 5 x 2-7/8	165
NS-P-12	0.1%	1.5	14.0000	12.4		0.013.37	7.3.0.047	P	11 x 4-7/8 x 4-13/32	200
IS VOLTS	± 5% ADJ. 0.15%	1.5	1.4(1.3)	1.3	1.62)	.2(1.1)	1.0(0.9)	z	4-7/8 x 4 x 1-3/4	75
NS-Y-15	0.1%	1.5	3.4(3.1)	3.14		.6(2.35)	2.0(1.8)	Y	5-5/8 x 4-7/8 x 2-5/8	110
NS-X-15	0.1%	1.5	5.5(4.7)	4.8		9(3.35)	2.8(2.4)	X	7 x 4-7/8 x 2-7/8	130
NS-W-15	0.1%	1.5	7.7 6 55			5.5(4.7)	3.8(3.15)	W	9 x 5 x 2-7/8	165
NS-P-15	0.1%	1.5	12.0(11.4)	10.6	10.1) 8	1.5(8.1)	6.3(6 0)	Ρ	11 x 4-7/8 x 4-13/32	200
20 VOLTS										
NS-Z-20	0.15%	1.5	1.010.69			0(1.08)	0.45(0.41)	Z	4-7/8 x 4 x 1-3/4	75
NS-Y-20	0.1% 0.1%	1.5 1.5	2.7(2.45)			6(2.2)	1.3 ^(1.2) 1.6 ^(1.4)	Y X	5-5/8 x 4-7/8 x 2-5/8 7 x 4-7/8 x 2-7/8	110
NS-W-20	0.1%	1.5	6.1(5.2)	5.24		2(3.6)	3.0(2.6)	ŵ	9 x 5 x 2-7/8	165
NS-P-20	0.1%	1.5	10.0(9.5)	8.918		.5(7 13)	5.5(5.23)	Ρ	11 x 4-7/8 x 4-13/32	200
4 VOLTS	±5% ADJ.	1.1.1.1.1			1		1.17		1.	5.
NS-Z-24	0.15%	1.5	0.9(0.81)	0.75		0.6(0.55)	0.4(0.36)	Ζ	4-7/8 x 4 x 1-3/4	75
NS-Y-24	0.1%	1.5	2.3(2.1)	2.103		.7(1.5)	1.1(1.0)	Y	5-5/8 x 4-7/8 x 2-5/8	110
NS-X-24	0.1%	1.5	3.8(3.25)	3.212		4(2.0)	1.4(1.2)	X	7 x 4-7/8 x 2-7/8	130
NS-W-24 NS-P-24	0.1% 0.1%	1.5 1.5	5.4 ^(4.6) 9.0 ^(8.55)	4.6(3)		3.7 ^(3.1)	2.5 ^(2,1) 5.0 ^(4,75)	W P	9 x 5 x 2-7/8 11 x 4-7/8 x 4-13/32	165
8 VOLTS	and the second sec	14.2			12.1.25				and the second	
NS-Z-28	0.15%	1.5	0.810 75)	0.65	0.6) (1.510 451	0.35(0.32)	Z	4-7/8 x 4 x 1-3/4	75
NS-Y-28	0.1%	1.5	2.0(1.8)	1.811		.5(1.35)	1.0(0.9)	Y	5-5/8 x 4-7/8 x 2-5/8	110
NS-X-28	0.1%	1.5	3.4(2.9)	2.912		2.2(1.5)	1.2(1.0)	x	7 x 4-7/8 x 2-7/8	130
NS-W-28	0.1%	1.5	4.7(4.0)	4.013		3.2(2.75)	2.2(1.9)	W	9 x 5 x 2-7/8	165
NS-P-28	0.1%	1.5	8.0(7.6)	7.116	(5) (5.0(5.7)	4.5(4 28)	Ρ	11 x 4-7/8 x 4-13/32	20
18 VOLTS	5% ADJ.									
		1.5	4.5(4 28)	4.013		3.4(3.2)	2.5(2.38)	P	11 x 4-7/8 x 4-13/32	25

VOLTAGE & CURRENT RATINGS

NOTE: 1. Rating in Parenthesis or LNSeries when cover is used.

Dimensions include cover.
 Includes OV protection on both outputs (5V OV trip point is 6.6 ±.2V fixed; 9–12V OV trip points is 13.7 ±.4V fixed).


A typical open-frame-switcher data sheet-in this case, for Lambda's LN Series-indicates the wide range of specs you can choose from.

Boxed switchers provide up to 1500W


As an example of switcher regulation, consider the block diagram of Adtech Power's patented 1-transistor, pulse-width-modulated Univerter design (**Fig 1**). This circuit provides one semiregulated output (line regulation only) along with a tightly regulated primary and one fully regulated secondary. Notice that a post regulator furnishes the secondary's regulation.

Some manufacturers choose to offer regulation on all outputs and sell supplies without this feature only on a custom basis. National Power Technology designers, for example, feel that a supply with unregulated outputs is vulnerable to damage if its host system's loads aren't what the system designer expects them to be. Thus, putting regulators on all outputs prevents catastrophic failures.


Sierracin/Power Systems contends that although you might find applications (such as daisy-wheel printers) that do allow use of unregulated auxiliary outputs, the approach isn't generally a good idea. According to the firm's VP for engineering, Ken Lauchner, the typical $\pm 5\%$ of line and load regulation combines with another $\pm 3\%$ of cross regulation, $\pm 2\%$ of thermal drift and 200 mV of distribution losses to introduce a worst-case output variation exceeding 10%. You can make sure a

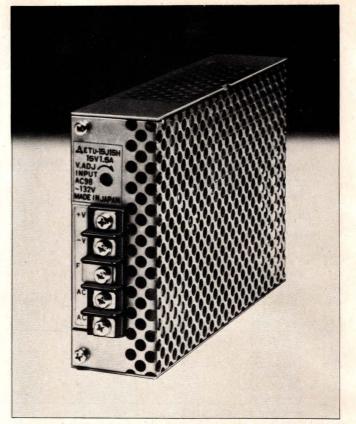

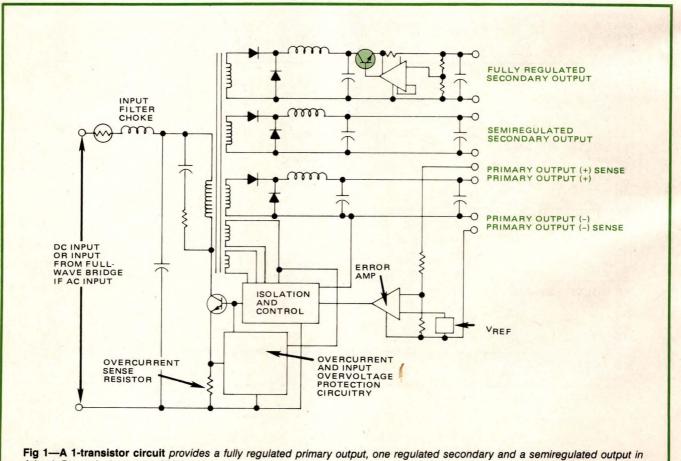Measuring 5.35×3.82×1.18 in., Panasonic's J Series 20W switchers come in 5V/4A, 12V/1.8A, 15V/1.5A and 24V/1A versions and operate to full rating at 50°C with normal convection cooling. The manufacturer warrants them for 3 yrs.



Adtech Power Inc's patented Univerter.

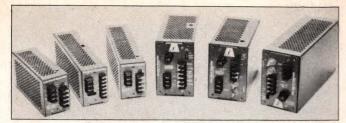

Thirty-nine models in the AMS Series from Acme Electric Corp furnish output voltages from 2 to 28V dc and power capability of 100 to 625W.



\$46 buys a variety of low-power options in Lambda's LU Series.

given output variation won't affect your system adversely only by testing a supply under all of the system's static and dynamic load conditions. If the variation might cause damage, you can't use the supply without adding at least some regulation.

Put more power in the box

With or without regulation, switchers have now moved into applications previously in the domain of linears, as well as opening up new applications themselves. And product development continues at all power levels.

Examining switchers' inroads into linear territory, Sierracin's Lauchner believes that the switcher-vslinear crossover-pricing curve shown in Fig 2 tells the story. Yet others feel that the curve might prove misleading. Bob Boschert, for instance, insists that no such curve exists at all. The market for switchers, he argues, encompasses a set of discrete-power-level requirements for which available switchers are more cost effective than equivalent linear supplies.

Even if power-supply pricing does follow the curve, the chart erroneously implies that above 600W switchers cost less than linear supplies. The graph, however, begins at 600W because the first switchers to compete in price with linears were 600W units.

Switching supplies have made selective inroads in the high-power region, though. Most of these units come in $5 \times 8 \times 10$ (or 11)-in. cases and furnish only one output

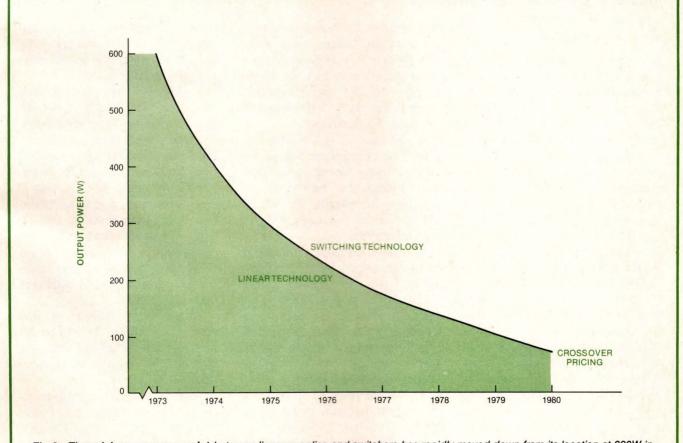


Fig 2—The pricing-crossover point between linear supplies and switchers has rapidly moved down from its location at 600W in 1973. (Courtesy Sierracin/Power Systems)

High-frequency switching permits smaller supplies

voltage. They use their cases as heat sinks and employ fans to help stay cool.

Pioneer Magnetics' Model PM 2500A, for example, provides 1000W, delivering 5V at 200A. You don't get the flexibility provided by low-power open-frame supplies, but you do receive a reliable unit that the manufacturer terms a workhorse. (The Editor's Choice on pg 83 illustrates the next evolutionary step in this line.)

Boschert also packs a lot of power in a 5×8 -in. box. Members of the HL Series introduced last year, for example, furnish 1500W. One model, the HL1500, delivers 5V at 300A. All the \$960 (100) switcher's critical components—including the power bridge, diode assembly, control electronics and input and output capacitors—are field-replaceable plug-in modules. The control electronics permits remote sensing, $\pm 10\%$ output programming and remote on/off switching.

Another 1500W 5×8-in. box comes from Qualidyne systems. Model 9010 delivers one dc output, ranging from 5V at 275A to 28V at 55A. The unit's transient response limits output deviation to 3% of peak output for a $\pm 25\%$ load change; output recovers to within 1% of



Taking advantage of the efficiencies available at higher frequencies, Abbott Transistor Labs' Model Z switcher runs at 38 kHz.

Incompatible MTBF specifications

Dan Ketcham and Dave Newton, Abbott Transistor Labs

Because the costs of a switcher failure go far beyond powersupply replacement cost, OEMs always look for ways to compare estimates of supply reliability.

The most often cited spec is the mean time between failures (MTBF), but you might have problems using this measurement. Incompatibilities can arise if you compare MTBF specs calculated using different versions of the Military Handbook 217 (MIL-HDBK-217) reliability standard.

Now in its third revision (C), this handbook identifies individual component-failure rates. However, any one of the four handbook versions (the original and three revisions) could have supplied the failure rates used to calculate a specific product's MTBF. To properly interpret the reliability value, then, you must know which handbook version was used. In general, each new version of the standard utilizes more accurate models for component-failure mechanisms and has shortened inflated MTBFs based on the original standard and preceding versions. For example:

• Revision C is the only version that recognizes the weakness of using nonhermetic ICs. It also recognizes the impact of package complexity on MTBF rather than circuit complexity or part-failure rate.

• Rev C penalizes the use of plastic packages, raising the basic failure rate for plastic power transistors, in particular. This version changes temperaturederating rules and decreases quantitative estimates of the effects of applied voltage and quality levels on failure rates.

• Failure rates of commercial metal-film resistors spec 300% higher in Rev C than in B; carbon-film and military metal-film rates are halved. Wire-woundresistor rates increase by 50%, and all trimming-pot failure rates are substantially lower.

• Dielectric-film-capacitor failure rates rise 1000% in Rev C. Mica parts are considered 500% more prone to failure than before, but the standard lists ceramic units as 90% more reliable. Tantalum failure rates fall 60%. Rev C also provides a capacitancedependent failure-rate multiplier.

• The latest standard increases all types of magnetics' failure rates 100% and tags commercial-grade parts with an additional 50% increase.

These rating differences can vary a switcher's MTBF by as much as a factor of two, depending on the handbook revision used.

(The authors are managers of corporate marketing and engineering, respectively, at the Burbank, CA-based company.) Better, in that you can now realize all the attributes you've wanted for your power supply requirements – all from the reliable single-source – KEC, the most cost-attractive and complete switcher family around.

Take open-frames. Ours come in all sizes – from the newest 15, 25 and 40-Watt SKFs and 65-Watt SCF – all the way up to 300-Watt SCBs. Their trim and rugged lightweight structures afford optimum mounting flexibility and durability. What's more, they provide tight line/load regulation, multiple outputs, overload and overvoltage protection, and have the widest brownout protection ranges to be had. If modulars are your thing, be sure to take a good look at our UL recognized SAs, dual-input SBs, or multivoltage SAM/SBMs. And when you need high power types, your best bets are our 375-Watt SDs and 750-Watt SEs.

So, since we're not able to give you all the details about the over 100 member KEC family – the biggest in the switching field – in this limited space, contact us.

KEC ELECTRONICS, INC. 19300 S. Vermont Avenue, Gardena, CA 90248. Phone: (213) 515-2561.

KEC, the First Family in Switchers, just added two new beauties. Good for us. Even better for you.



Military will provide the spur for high-frequency designs

however; it measures 61/8×91/8 in.

Generally, the higher you make a supply's switching frequency, the smaller you can make its transformers a fact that has prompted much research into higher switching frequencies. Such frequencies also reduce problems with radiated noise and help eliminate heat from the magnetics. Today's commercial switchers operate at 20 to 40 kHz, with a few (such as Hewlett-Packard's 50W supply) going up to the 200-kHz stratosphere. But most manufacturers don't feel any pressure to rush into frequencies above 100 kHz.

its nominal value within 300 μ sec. The 16-lb unit costs \$875.

If you want a lot of power in one package but need it divided up among several voltages, try the units in Todd Products Corp's SM Series. They furnish 750W, parceled out to as many as four dc voltages. One such supply, the SME, occupies a bit more than 5×8 in.,

Switching-power-supply manufacturers

For more information on switching power supplies, contact the following manufacturers directly or circle the appropriate numbers on the Information Retrieval Service card.

AAK 11 Villa St Haverhill, MA 01830 (617) 373-3769 Circle No 371

Abbott Transistor Laboratories Inc 639 S Glenwood PI Burbank, CA 91506 (213) 842-7150 Circle No 372

ACDC Electronics 401 Jones Rd Oceanside, CA 92504 (714) 757-1880 Circle No 373

Acme Electric Corp 49 Water St Cuba, NY 14727 (716) 968-2400 Circle No 374

Adtech Power Inc 1621 S Sinclair Anaheim, CA 92806 (714) 634-9211 Circle No 375

Advanced Electronics Design 440 Potrero Ave Sunnyvale, CA 94088 (408) 733-3555 Circle No 376

Advanced High Voltage Co Inc 14532 Arminta Ave Van Nuys, CA 91402 (213) 997-7222 Circle No 377

Arnold Magnetics 11520 W Jefferson Culver City, CA 90230 (213) 559-0103 Circle No 378

Ault Inc 1600 H Freeway Blvd Minneapolis, MN 55430 (612) 560-9300 Circle No 379

Berkleonics Inc 1 Aerovista Park San Luis Obispo, CA 93401 (805) 544-5454 Circle No 380 Bikor Corp 1504 W 228th St Torrance, CA 90501 (213) 539-6320 Circle No 381

Boschert Inc 384 Santa Trinita Ave Sunnyvale, CA 94086 (408) 732-2440 Circle No 382

Calex Manufacturing Co Inc 3355 Vincent Rd Pleasant Hill, CA 94523 (415) 932-3911 Circle No 383

California DC 2150 Anchor Ct Newbury Park, CA 91320 (213) 991-1168 Circle No 384

CEI Corp Box 501 Londonderry, NH 03053 (603) 623-8885 Circle No 385

Century Electronics 5965 Washington Blvd Culver City, CA 90230 (213) 870-1083 Circle No 386

Computer Power Systems 18150 S Figuero St Carson, CA 90248 (213) 515-6566 Circle No 387

Condor Inc 4880 Adohr Lane Camarillo, CA 93010 (805) 484-2851 Circle No 388

Conver Corp 10629 Bandley Dr Cupertino, CA 95014 (408) 255-0151 Circle No 389

Converter Concepts Inc 435 S Main St Pardeeville, WI 53954 (608) 429-2144 Circle No 390 Datel-Intersil 11 Cabot Blvd Mansfield, MA 02048 (617) 339-9341 Circle No 391

Deltron Inc Box 1369 North Wales, PA 19454 (213) 699-9261 Circle No 392

Digital Power 686 E Gish Rd San Jose, CA 95112 (408) 288-5000 Circle No 393

Dynage Inc 1331 Blue Hills Ave Bloomfield, CT 06002 (203) 243-0315 Circle No 394

Electro-Module Inc 3501 Harbor Blvd Costa Mesa, CA 92626 (714) 540-1234 Circle No 395

Electronic Measurements Inc 405 Essex Rd Neptune, NJ 07753 (201) 922-9300 Circle No 396

Elpac Power Systems 3131 S Standard Ave Santa Ana, CA 92705 (714) 979-4440 Circle No 397

Emco High Voltage Co 556 Weddell Dr Sunnyvale, CA 94086 (408) 734-9123 Circle No 398

Endicott Research Group Inc Box 128, Westview Stn Binghamton, NY 13905 (607) 798-7846 Circle No 399

ERA Transpac Corp 311 E Park St Moonachie, NJ 07074 (201) 641-3650 Circle No 400 Frequency Technology Inc 410 Great Rd Littleton, MA 01460 (617) 486-3539 Circle No 401

Glassman High Voltage Box 551 Whitehouse Stn, NJ 08889 (201) 534-2226 Circle No 402

GM Research 1048 E Burgrove Carson, CA 90746 (213) 639-4663 Circle No 403

Gould Inc 4323 Arden Dr El Monte, CA 91731 (213) 575-4777 Circle No 404

Hewlett-Packard Co 1507 Page Mill Rd Palo Alto, CA 94304 Phone local office Circle No 405

Intronics 57 Chapel St Newton, MA 02158 (617) 332-7350 Circle No 406

KEC Electronics Inc 19300 Vermont Ave Gardena, CA 90248 (213) 515-2561 Circle No 407

Keltec Florida Drawer 2917 Ft Walton Beach, FL 32549 (904) 862-3107 Circle No 408

Kepco Inc 131-38 Sanford Ave Flushing, NY 11352 (212) 461-7000 Circle No 409

Lambda Electronics 515 Broad Hollow Rd Melville, NY 11747 (516) 694-4200 Circle No 410 At Abbott Transistor Laboratories, for instance, a development team started out to design a 30-kHz switcher and moved up to 38 kHz before becoming satisfied with its performance. The resulting \$215 Model Z measures $6 \times 4 \times 2.25$ in. and comes in 14 versions that furnish 100W at 3 to 30V dc. Abbott applies the catch phrase "2W per cubic in." to the units.

Because power density is the name of the game for switchers, what's holding back even higher frequencies? The magnetics pose one problem. Although transformers characterized at 200 kHz have been specified for more than 2 yrs, few transformer manufacturers will carry them in stock until demand increases; the parts thus sell at premium prices.

Power-loss problems also affect the move to higher switching frequencies. If a supply's transistor switching losses (including its voltage-control circuits) remain constant in every cycle, as you raise the switching frequency, the losses increase also. Thus, Sierracin's Lauchner estimates that raising the switching frequency by an order of magnitude reduces a unit's size and weight by only 10 to 20%, and the cost goes up, too. ACDC's Hirschberg agrees and remarks that such a price increase completely offsets the size benefit.

LH Research 14402 Franklin Ave Tustin, CA 92680 (714) 730-0162 Circle No 411

Lorain Products 1122 F St Lorain, OH 44052 (216) 288-1122 Circle No 412

Microcomputer Power Inc 2272 Calle De Luna Santa Clara, CA 95050 (408) 988-0265 Circle No 413

Microsource Corp 7330 Rogers Ave Chicago, IL 60626 (312) 465-8419 Circle No 414

MIL Electronics Inc 176 Walker St Lowell, MA 01854 (617) 458-4535 Circle No 415

National Power Technology 2111 Howell Ave Anaheim, CA 92806 (714) 937-1301 Circle No 416

Nortel Ltd 31149 Via Colinas Bldg 608 Westlake Village, CA 91361 (213) 707-0120 Circle No 417

Novatronics 500 SW 12 Ave Pompano Beach, FL 33061 (305) 942-5200 Circle No 418

Optimal Systems Corp 44755 Grimmer Blvd Fremont, CA 94538 (415) 657-9256 Circle No 419

Panasonic Co 1 Panasonic Way Secaucus, NJ 07094 (201) 348-7276 Circle No 420 Philips* TQ III-4 Eindhoven, The Netherlands Circle No 421 *European sales only

Pioneer Magnetics 1745 Berkeley St Santa Monica, CA 90404 (213) 829-6751 Circle No 422

Power Design 1700 Shames Dr Westbury, NY 11590 (516) 333-6200 Circle No 423

Power Dynamics Corp 9421 Telfair Ave Sun Valley, CA 91352 (213) 767-9640 Circle No 424

Power General 152 Will Dr Canton, MA 02021 (617) 828-6216 Circle No 425

Power/Mate 514 S River St Hackensack, NJ 07601 (201) 440-3100 Circle No 426

Power-Matic Inc 7667 Vickers St San Diego, CA 92111 (714) 292-4422 Circle No 427

Power-One Inc Power-One Dr Camarillo, CA 93010 (805) 484-2806 Circle No 428

Powercube Corp 8 Suburban Park Dr Billerica, MA 01821 (617) 667-9500 Circle No 429

Powertec 20550 Nordhoff St Chatsworth, CA 91311 (213) 882-0004 Circle No 440 Qualidyne Systems Inc 2256 Main St Chula Vista, CA 92011 (714) 429-7440 Circle No 431

Reliability Inc Box 37409 Houston, TX 77036 (713) 492-0550 Circle No 432

RO Associates Inc 246 Caspian Dr Sunnyvale, CA 94088 (408) 744-1450 **Circle No 433**

Semiconductor Circuits Inc 218 River St Haverhill, MA 01830 (617) 373-9104 Circle No 434

Sierracin/Power Systems 20500 Plummer St Chatsworth, CA 91311 (213) 988-9873 Circle No 435

Sola Electric 1717 Busse Rd Elk Grove Village, IL 60007 (312) 439-2800 Circle No 436

Sorenson Co 676 Island Pond Rd Manchester, NH 03103 (603) 668-4500 Circle No 437

Spellman High-Voltage Electronics 7 Fairchild Ave Plainview, NY 11803 (516) 349-8686 Circle No 438

Standard Power Inc 1400 S Village Way Santa Ana, CA 92705 (714) 558-8512 Circle No 439

Stevens-Arnold Inc 7 Elkins St South Boston, MA 02127 (617) 268-1170 Circle No 430 Switching Power Inc 4835 Veterans Hwy Holbrook, NY 11741 (516) 981-5353 Circle No 441

Technipower Inc Box 222 Commerce Park Danbury, CT 06810 (203) 748-7001 Circle No 442

Technology Dynamics Inc 415 Rte 303 Tappan, NY 10983 (914) 359-4000 Circle No 443

Tecnetics Inc 1625 Range St Boulder, CO 80306 (303) 442-3837 Circle No 444

Todd Products Corp 50 Emjay Blvd Brentwood, NY 11717 (516) 231-3366 Circle No 445

Trio Laboratories Inc 80 Dupont St Plainview, NY 11803 (516) 349-0400 Circle No 446

Velonix 560 Robert Ave Santa Clara, CA 95050 (408) 727-7370 Circle No 447

Wall Industries Inc 2 Franklin St Lawrence, MA 01846 (617) 688-1287 Circle No 448

NOW, a small-size, small-price resettable protector

The Re-Cirk-It® protector. Looks like a conventional 5/8" fuseholder. Even installs in the same panel space, with a simple push-on clip. But it puts an end to fuses. No more expensive service calls when a fuse can't handle normal starting surges. No chance ever that the wrong fuse will be installed. With Re-Cirk-It, the white band signals when it's tripped. To reset, just push a button. UL-recognized as a supplementary protector for electrical equipment, CSA-certified, SEVapproved. Current ratings from 0.25A through 15A, 250 Vac and 32 Vdc. Request bulletin KD4001. Heinemann Electric Company, Trenton, NJ 08650.

7370

HEINEMANN We serve you better

C Heinemann

For more information, Circle No 52

YOU LIKE TO WRITE, RIGHT?

Then EDN wants you, providing you also have an EE degree and at least two years' circuit-design experience. We seek individuals who want to be Boston-based technical editors for this top electronics publication.

To qualified individuals, EDN offers an attractive salary, industry-wide recognition, high job satisfaction, and the ability to keep abreast of ...

- Advanced Technology
- Exciting New Products
- State-of-the-art circuit and system-design techniques.

If you thrive on meeting challenges head-on...

If you are an effective, technical communicator . . . then send your resume and salary requirements in strict confidence to: Roy Forsberg, Editorial Director, EDN, 221 Columbus Avenue, Boston, MA 02116.

An Equal Opportunity Employer

Keep FCC EMI rules in mind when shopping for a switcher

Because of the pricing drawback and because a supply's switching frequency doesn't directly affect a host system, there's no demand for switchers with frequencies above 100 kHz—except perhaps for military applications. And in the long run, military money will provide the push that makes high-frequency units economically feasible.

Beware radiated-noise pollution

One area in which switching supplies *have* made great strides is noise control. Switchers used to get a black eye from many OEMs because of the noise they delivered with the dc voltage. Switcher design has come a long way, however, and units such as Powertec's Valuswitcher restrict ripple and noise to 2% p-p.

Today, concern with switcher noise centers on their radiated signals. You'll see many supplies billed as meeting some combination of FCC, UL or VDE specifications. But because this claim is inherently ambiguous and carries many shades of meaning, check with manufacturers to determine its exact meaning for each power supply. Bear in mind that "designed to" doesn't necessarily mean "meets," and "meets" doesn't necessarily mean "approved by."

The problem becomes particularly nasty in the case of the VDE specifications. They cover two types of requirements: those relating to EMI and RFI and those relating to safety. And the safety considerations prove tougher to meet than those of Underwriters Laboratories. If your products never leave the US, though, you needn't bother about VDE specs.


One set of specs that you *should* bear in mind, however, is the FCC rules governing EMI emissions, which go into effect in October. Make sure that when a manufacturer says a supply meets FCC specs, those specs comply with these new rules.

To meet the new FCC requirements, Sierracin has recently redesigned its entire switcher line. If you buy modules or open-frame supplies, however, you'll probably have to tackle the FCC-approval chore yourself. Some power-supply manufacturers can assist more than others, but vendors should at least supply you with a radiation profile for a supply and any assistance needed in designing EMI and RFI filters.

Some manufacturers, such as Lambda, can provide EMI-suppression options for their switchers. The firm's \$110 Model M-YXX-1 EMI-suppressing cover, for example, includes filters that permit LY Series switchers to meet MIL-1-6181D conducted-emissions specs; the perforated cover itself minimizes radiated emissions.

> Article Interest Quotient (Circle One) High 485 Medium 486 Low 487

Introducing SwitchTron® Plastic Power:

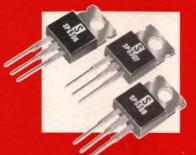

16 Amp* High Voltage, Fast Switching TO-220 Transistors!

TO-220 Type Number	V _{CE} (sus) Volts	V _{CEX} Volts	Ic (cont)* Amps	hFE @ Min/Max	Ic Amps	VCE(sat) Volts Max	<pre>@ Ic Amps</pre>	fT MHz Min	tf μsec Max
SP 6306	250	500	8	15/75	3	0.8	3	5	0.4
SP 6307	300	600	8	15/75	3	1.0	3	5	0.4
SP 6308	350	700	8	12/60	4	1.5	3	5	0.4
SP 13006	300	600**	8	8/40	2	1.0	2	5	0.4
SP 13007	400	700**	8	6/30	5	1.5	5	5	0.4


*Peak I_C = 16 amps @ 5ms PW, Duty Cycle ≤ 10% **VCEV, V_{bE} = -1.5V

Voltages up to 700V...peak IC's of 16 A*...switching speed of 400 nsec at 3 A... that's the performance you can expect from Solitron's new TO-220 transistors. They're part of our SwitchTron® family and it means that this unique fast switching family is now available to you in plastic power configurations. Solitron TO-220 transistors are triple-diffused, high reliability devices that can solve switching problems when cost and size are a criteria.

Competitively priced, these devices are available now for high voltage inverters, switching regulators, power amplifiers and power supplies. Look over our specification chart. Then call toll-free 800-327-8462 for more information.



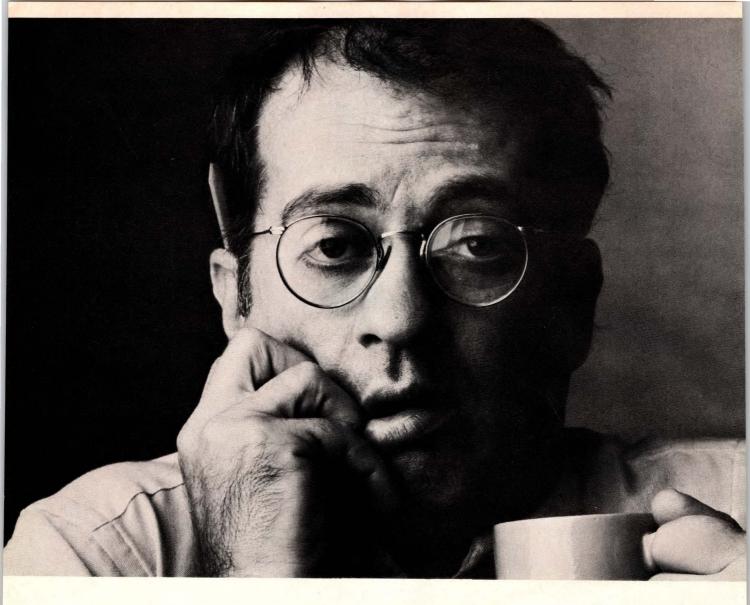1177 Blue Heron Blvd., Riviera Beach, Florida 33404 (305) 848-4311/TWX: (510) 952-7610/TELEX: 51-3435



SOFT ERRORS CAN BE HARD ON YOUR SYSTEM.

Your RAMs are getting denser. Your soft error rate is getting higher. And you're getting a headache.

Soft errors, alpha particles, system crashes, hard errors. Take it easy. Relax. There's a simple solution.

Introducing the Am2960 Error Detection and Correction (EDC) Unit.

The Am2960 EDC corrects single-bit errors and detects double-bit errors. It's easily expandable from 16-bits wide to 32 or 64 bits. Its worst case speed is an amazing 34ns detect, 64ns detect and correct! And best of all, it's available right now.

You want byte operations? You got 'em. You need initialization, error logging and diagnostic capabilities? No problem. The Am2960 gives you all the functions of 25 to 50 TTL packages on one chip.


And if you're worried about the data path, don't be. Our slim 24-pin Am2961 and Am2962 EDC Bus Buffers solve the complete interface problem between the RAM, the EDC unit and the system data bus. There's just no easier, cheaper, faster way to find and fix errors than the Am2960.

Bipolar LSI: The Simple Solution.

Our new Am2960 family of bipolar LSI and interface dynamic memory support devices will help you maximize your system's performance and reliability, minimize its chip count and cost.

And you won't find higher quality parts. Since the day we opened for business we've given every single part we make MIL-STD-883. For free.

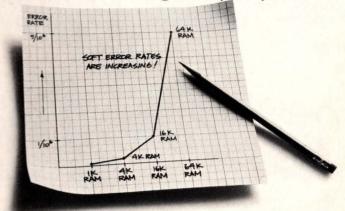
Get the Am2960 Error Detection and Correction Unit. It'll be good for your system.





901 Thompson Place, Sunnyvale, CA 94086 · (408) 732-2400 Right, From The Start.

People are switching to Boschert

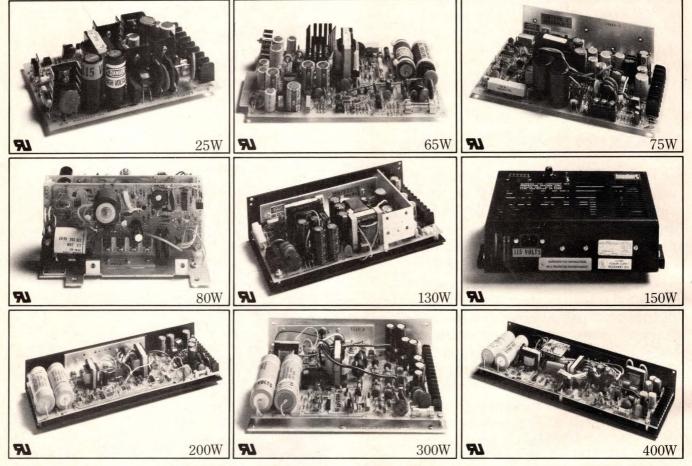

because only Boschert offers a complete line of 25-400 watt switching power supplies.

When you want power, come to Boschert. We're the power leader with more standard 25-400 watt switching power supplies in production and in stock than any other manufacturer. Every one is ULrecognized. Each meets international input voltage requirements. And we offer the multiple output voltages you need to meet your particular system requirements. Plus, when you switch to Boschert, you enjoy advantages only a leader can offer. Like high volume automated production capabilities to support your volume requirements. Off-the-shelf delivery when you need product fast. Custom tailoring. An up-todate understanding of VDE requirements. Boschert even offers you an extensive European distribution network to support you overseas.

At Boschert we've been building off-line switching power supplies for almost a decade. Over 200,000 of For more information, Circle No 56 our multiple output power systems are now in operation. Isn't it time you made the switch to Boschert?

For more information on our full line of switching power supplies, contact your local Boschert representative, or write: Boschert Inc., 384

> Santa Trinita Ave., Sunnyvale, CA 94086. Or call us direct, (408) 732-2440.

Simple guidelines for gatherings help you meet with success

If your meetings are boring and unproductive, turn them around. As group leader or participant, you can maximize time spent with colleagues and transform dull meetings into effective forums.

H Kent Baker, The American University

As a technical-staff member, you probably spend many hours each week in meetings with your coworkers discussing the progress you've made on a project or planning the next project phase. When you glance at your calendar and see "meeting, 10 AM," what flashes through your mind? If you envision a boring, fruitless gathering, you're not alone.

Meetings can be a bane of professional life unproductive, frustrating time wasters—but they *needn't* be. Your meetings can come alive and be effective and even enjoyable if you follow a few basic guidelines.

To begin with, face the fact that when you join an organization, you're sentenced to be a "meeting lifer." You'll probably spend a year or more of your working life in meetings—time worth a staggering sum of money. But you needn't serve your entire sentence. You can grant yourself a parole for good behavior; the choice is yours.

Why do meetings fail?

To get the most out of meetings, understand their purpose. Although they come in all shapes and sizes, meetings generally fall into three goal categories: educational, informational and decision-making. Managers, for example, hold meetings to train people, develop teamwork, disseminate information and solve problems—laudable goals, but seldom achieved.

Meetings fail to meet their objectives when the leader and participants don't recognize their roles or understand how to conduct effective meetings. Such problems stem from the lack of a good meeting model. For example, engineers promoted to managerial positions typically base the way they conduct their meetings on those they have attended. If they've never been exposed to a good meeting model, they probably

won't conduct productive meetings.

If you've been to more unproductive meetings than useful ones, you, too, must develop an effective meeting model. To do this, recognize how misconceptions about meetings hinder their success.

Dispelling meeting myths

Five myths influence the way people conduct meetings:

• The success of a meeting depends solely on its leader—a half-truth at best. A meeting's success is a shared responsibility, as is its leadership. In fact, the leadership role can change hands several times during a meeting. Without cooperation and teamwork, a meeting can degenerate into a wasted effort, a merry-goround of activity accomplishing little.

All attendees can play a variety of roles to help the group achieve its goals and work together productively. They can perform many task functions, such as seeking and offering opinions and information, clarifying and elaborating on material presented, and summarizing. Additionally, participants perform maintenance functions, including encouraging others to participate, setting and testing standards, limiting conflict, and compromising and negotiating to reduce destructive disagreement. These functions are too numerous and varied for the leader to carry out; all participants must share them.

• The leader must maintain tight control another false assumption. When the leader assumes the role of traffic cop—setting the structure, directing who will speak and limiting discussion—he gets into trouble. That type of "it's my meeting" attitude inhibits dialog and stifles the vitality of free-flowing interaction. This type of leader reduces attendees' functions to reporting only and engages in one-on-one communication without allowing group discussion. Consequently, viewpoints that could be helpful are repressed; a frustrating,

Properly handled conflict is a positive meeting force

unproductive meeting results. Yet such a leader is likely to announce proudly, "I certainly got through that agenda in a hurry."

• Group participation is necessary in every meeting. The current emphasis on participation is an overreaction to the very autocratic approach formerly used. For two decades people have heard that truly enlightened managers encourage staff participation. Thus, people tend to believe that participating is productive while observing quietly is harmful. Managers who accept this doctrine without considering the situation often adopt a weak, ineffective management style. On the other hand, the nondirective leader who gives participants free rein almost ensures meeting failure from the start.

A high level of participation is important to some meetings, however. But the leader must be sensitive to the situation, then adopt the most appropriate style; no one leadership style works for all meetings. Sometimes, such as in decision-making meetings, for example, participation is crucial; for others, such as informational meetings, a more directive approach works. Whether the meeting leader prefers a directive, nondirective or something-in-between style, he must recognize that he is the major session catalyst.

• Avoid conflict at all costs. Contrary to popular belief, conflict can be a positive force in a meeting if handled properly. For instance, conflict can broaden the understanding of certain problems. Encouraging conflict in problem-solving meetings can help uncover a variety of solutions. Conflict can also stimulate interaction and involvement of meeting participants (see **box**, "How to encourage *constructive* conflict").

• Everyone should be invited. Because a large group often slows a meeting's pace, limit the number of people you ask to attend. Touching base with interested parties is a sound idea, but a meeting might not be the place to do so. Don't invite people to a meeting unless you really need them. And if you only require their presence for part of the meeting, schedule a specific time for their arrival. You'll thus avoid having an uninterested person sit through your meeting waiting to be called on.

Follow guidelines selectively

Once you debunk the myths surrounding meetings, you're ready to apply a few meeting guidelines. But consider them selectively to avoid taking a stilted, cookbook approach. Then, when you're asked to lead a meeting, remember these suggestions:

• Don't hold unnecessary meetings. The easiest way to reduce the number of meetings you hold is to find other ways to communicate. Reports, memos, telephone conversations and face-to-face discussions, for instance, can serve the same purpose in less time. Because regularly held meetings often become rituals, consider their value carefully. Sometimes the only reason for holding a staff meeting is because it's Monday. Regularly schedule certain gatherings such as staff meetings only when they will provide a forum for worthwhile communication.

• Set realistic goals. Before you call a meeting, know exactly what you want to accomplish. If you don't, the meeting is likely to wander aimlessly from one issue to another. If you're unsure of your objectives, certainly others will also be lost.

Furthermore, make sure that you can accomplish the meeting's objectives within a reasonable amount of time. Meetings tend to diminish in productivity after 1½ hrs. Participants get restless, enthusiasm wanes and the meetings become endurance tests. Lengthy meetings also encourage people to babble on without accomplishing anything worthwhile. When your meeting goals appear too ambitious, hold two meetings separated by at least one day.

• Don't spring surprises. Try to circulate a copy of your objectives and agenda before the meeting; if you want people to study background material, send that too. Advance information helps participants come prepared.

• Avoid catching people off guard. If you save a touchy subject for the meeting and spring it unannounced on your colleagues, they might resent your tactics, and their hostility could diminish your effectiveness as a leader. Therefore, if you expect your group to contribute its best efforts, provide it with a sufficiently detailed agenda a few days before you meet. And to

How to encourage constructive conflict

Conflict can actually make a meeting more productive when the leader ensures that it helps develop solutions and doesn't just fuel disagreements for the sake of arguing. To monitor conflicts at your next meeting, heed some simple advice:

• Agree to disagree—Emphasize that it's acceptable to express views contrary to the prevailing opinion. Encourage those with differing opinions or original ideas to speak up.

• Stress noncombative disagreement— Remind the meeting participants that disagreement isn't intended to produce winners or losers but rather to improve their understanding of the problem at hand.

• Create a supportive atmosphere—Support each participant's right to disagree and express his opinion. Because a strong faction might attempt to intimidate an individual with an unpopular opinion, ensure that anyone who wishes to speak gets the group's attention.

• Focus on issues, not personalities— Establish the ground rule that participants can disagree on an issue, but they can't attack the people who express opinions on it. further avoid surprises, you can make notations next to each agenda item to alert participants about how you expect them to contribute to the meeting.

• Set the proper climate. A good meeting environment won't ensure that the meeting will run smoothly, but uncomfortable surroundings, poor lighting and interruptions will certainly make concentration difficult. Monitor the participants' feelings during a session. When their interest and energy have dissipated, don't drone on just to cover the agenda; if you do, you'll accomplish little. Notice signs that indicate changing energy levels—tone of voice, loudness of speech, body posture, fidgeting and doodling. Recognize them and act appropriately—take a short break, change the pace or just tell a joke.

You can also foster a supportive atmosphere by encouraging cooperation rather than competition among participants. And try to prevent anyone from monopolizing the discussion. One of your responsibilities as leader is to ensure that each member has the opportunity to speak. A useful technique is to seek the opinions of junior members before those with senior status speak. By drawing junior members into the discussion, you emphasize their right to contribute and might hear ideas that would not otherwise be offered.

• Summarize. By making frequent summaries during the session, you can note the meeting's progress and point out any disagreements that the group should straighten out. At the meeting's close, review conclusions reached, major disagreements still unresolved and steps to be taken so that participants clearly understand what the meeting has accomplished.

• Finally, follow up. As a leader, you carry a responsibility that extends beyond the actual meeting. To fulfill it, send a written summary to the meeting attendees and others who need to know what the group decided and what action it will take. Because attendees tend to forget what happened at a meeting, send the minutes the day of the meeting if possible. Lastly, ensure that those who have agreed to take action carry it out as the group mandated.

Participants have a job, too

These guidelines demonstrate how a group leader can set a meeting's tone and influence its productivity. Yet participants, too, can contribute to a meeting's success. As a participant, consider these guidelines:

• Be prepared. Lack of preparation wastes time and leads to confusion and frustration. People who prepare or rehearse their reports during a meeting distract and annoy others and minimize their own potential contributions.

• Insist on starting and ending on time. Question a leader who wants to postpone the meeting's start for latecomers. Point out that such action penalizes those who come on time and actually rewards those who arrive late. And if the meeting runs on for an unreasonably long time, remind the leader that the participants have other commitments, and suggest adjourning.

• Don't bring a hidden agenda. Try not to digress too far from the scheduled agenda. And if others do, try to refocus the group's attention to the items it has met to discuss.

• Demand excellence. If you are tired of attending ineffective meetings, constructively make your feelings known. Propose a meeting audit where participants record suggestions for improvement. Collect their lists and discuss them. You might find that you aren't the only one who's disappointed in the way the group has been conducting meetings.

Finally, remember that the guidelines offered here are useless until you apply them. If you've been tolerating unproductive meetings, you are part of the problem. But if you follow these simple suggestions, you can lift your meetings out of the doldrums.

Incidentally, it's time for that 10 AM meeting. Are you ready for it?

Author's biography

H Kent Baker is a professor of finance at The American University, Kogod College of Business Administration, Washington, DC, where he teaches at the graduate level and conducts management research. He previously taught at the University of Maryland and served as assistant dean of Georgetown University's School of Business Adminis-



tration. Professor Baker earned a BSBA at Georgetown University, an MBA, MEd and DBA at the University of Maryland and an MS from The American University. A member of the American Finance Association and the Washington Society of Investment Analysts, he enjoys music and writing in his spare time.

> Article Interest Quotient (Circle One) High 470 Medium 471 Low 472

NEXT TIME

Look for a Special Report on high-frequency instruments in EDN's February 18 issue. You'll also find articles on

- The use of S/H amplifiers as circuit components
- The design of effective EMI and RFI shielding

... and much more. Also look for news stories on the latest benchtop testers and on "standards" that sometimes aren't, plus our regular μ C Design Techniques, Design Ideas and A Question of Law departments. You can't afford to miss this issue!

EDN: Everything Designers Need

YOUR GOOD DESIGN BECOMES EVEN BETTER.



With the Best **Power Supply** Behind it.

Power Products offers more than 150 precision power supplies from one-half watt to 25 watts that'll make that good design a great one.

We give you everything you need in a power supply. And more of what you want...

like brand-name components. Conservative specs. Field-proven reliability. And warranteed performance. At a fair price.

Like quick delivery. Small quantities shipped directly from stock within three days ARO.


Like technical support. A partnership approach to problem solving that eliminates your power supply headaches. We let you concentrate on the other aspects of your designs. The aspects that your customers deem most important.

Find out what power supplies from the Low-Power Giant can do for your designs. Solve that power problem on the very first call by calling Power Products first.

FIND US IN EEM!

116

EDN FEBRUARY 4, 1981

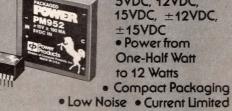

Power Products Division of Computer Products, Inc.

1400 N.W. 70th Street • Fort Lauderdale, Fla. 33309 • (305) 974-2442 • TWX 510-956-3098 For more information, Circle No 57

New Application Technology

Extend your design options with a new comparator IC

More than an over/undervoltage protector, a recently introduced multicomparator IC combines programmable hysteresis with dual high-current outputs. Applications range from ac-mains-loss monitoring to dual-channel proportional control.

William F Davis, Motorola Inc

Circuit designers familiar with ICs employed in power-supply-type voltage-monitoring and faultdetection applications usually cite lack of versatility as those devices' major limitation. The MC3424, a monolithic dual-channel high-output-current voltage comparator, overcomes this lack of flexibility in monitoring and fault-detection designs. And it's versatile enough to meet many of your other design needs, too. The device achieves this capability by incorporating features and options not usually found in other comparator ICs (see **box**, "An uncommon comparator").

The problems with conventional ICs

Traditional fault-monitoring ICs often provide only the inverting or noninverting input of a comparator, with perhaps a small amount of internal hysteresis. And what's worse, that comparator might be referenced to Text continues on pg 120

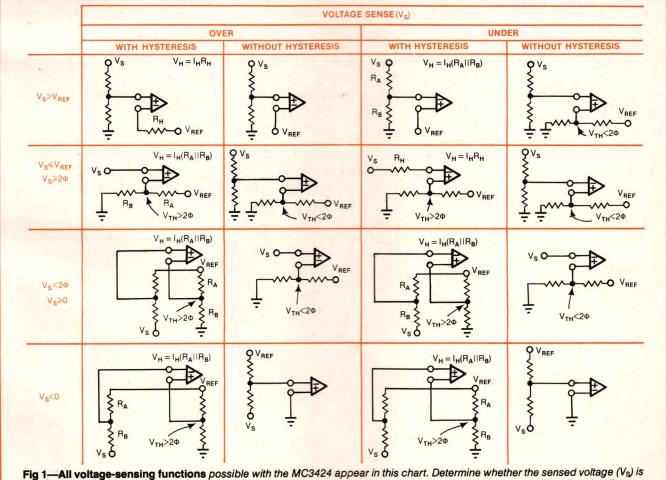


Fig 1—All voltage-sensing functions possible with the MC3424 appear in this chart. Determine whether the sensed voltage (v_{s}) is positive or negative, whether it's greater or less than the reference (V_{REF}) and whether hysteresis is required. Then find the diagram satisfying these constraints and apply the indicated resistor ratios.

An uncommon comparator

The MC3424—a high-current dual-channel voltage comparator incorporates the two separate and independent channels shown in **Fig A.** Capable of operating over a 4.5 to 40V supply range and over -55 to +125°C, each channel includes a fully differential input voltage comparator (comparators 1 and 2) with programmable hysteresis capability and a delay filter terminal (DLY) at its output.

The voltage at this filter point goes to an output comparator internally referenced to the 2.5V reference (V_{REF}). This comparator drives the output power devices to a source-current limit of 300 mA at the DRV pin and an indicator-output current sink of 30 mA at the IO pin.

A TTL LOW at the remote activation (RA) input overrides the input comparator and its associated time delay at any time and turns the output power devices on. A similar LOW at the Input Enable (IE) pin disables one or both of the input comparators. Under these conditions, inputcomparator outputs can't occur, regardless of the input state. You can disable both channels when the noninverting input (C_1^+) of input comparator 1 is less than $0.9V_{\text{REF}}$ and the IE voltage is LOW. Otherwise, IE disables only input comparator 2.

The device's laser-trimmed voltage reference (V_{REF}) is adjusted to within $\pm 1\%$ of 2.5V, has a temperature coefficient of approximately 50 ppm/°C and can deliver load currents up to 10 mA.

Note several important points regarding the MC3424's inputcomparator circuitry, shown in **Fig B**. In both of the input comparators, the differential inputs are externally available and can handle a common-mode range of V_{cc} -1.4V including ground. Thus, you can reference these comparators to virtually any reference voltage within the common-mode range.

Whenever the noninverting input (C⁺) exceeds the inverting input (C⁻), an internally generated hysteresis sink current (I_H) appears at the inverting input. Placing any resistance R in series with the inverting input then produces a hysteresis voltage equal to $I_H R$ volts (I_H is typically 12 μA).

If, however, the inverting-input voltage is less than two forwardbiased diode drops ($2\Phi \approx 1V$ at 25° C), the internally activated hysteresis current can't appear at the inverting input because it can't flow through diodes biased below their conduction level. Thus, for this particular case, hysteresis isn't generated with resistance in the inverting input.

Because of the inherent highvoltage junctions incorporated in this comparator, an input-voltage differential of $\pm 40V$ is permissible. The diodes placed within the comparator also allow both inputs to exceed the supply voltage without detrimental effects on the adjacent channel. Furthermore, they aid in reducing the comparator's large-signal delay to less than 200 nsec.

By attaching a capacitor to the comparator-output Delay pin (DLY), you can obtain a fixed time delay before the capacitor is charged by the internally generated current (I_0) to the output comparator's reference voltage.

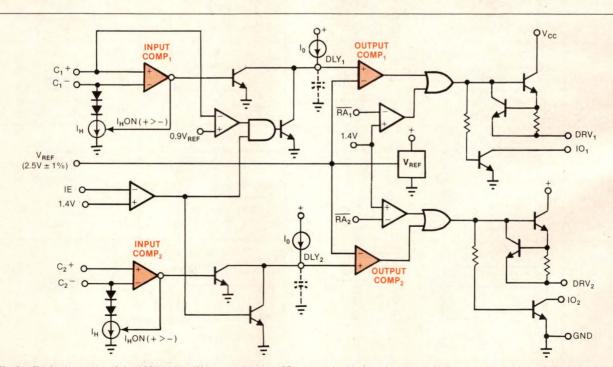


Fig A—Both channels of the MC3424 voltage-comparator IC appear in this functional circuit diagram. The device incorporates such extra functions as Input Enable (IE), Remote Activation (\overline{RA}), Delay (DLY) and hysteresis control on the input comparators' inverting inputs. The dual outputs (DRV) can each source as much as 300 mA, and the indicator outputs (I0) each can sink up to 30 mA.

This delay time is given by $T_d=CV_{REF}/I_0$, where I_0 is approximately 200 μ A.

The MC3424's modified bandgap voltage reference (Fig C) employs one additional smallvalue resistor (R_A) in the unit-area device's emitter. This construction reduces the amplifier's transconductance (g_m) without lowering its current. Large-value resistors for R_B and R_C would normally be required for g_m reduction by a more classical approach.

This g_m reduction allows you to capacitively load the band-gap reference with a wide range of values. You can thus improve the regulator's high-frequencytransient performance without degrading its stability.

Resistors R_A and R_B are laser trimmed to provide the reference voltage's initial $\pm 1\%$ tolerance and ensure a typical TC of 50 ppm/°C. This precision allows you to more accurately define your voltage-sense limits in production without tweaking.

The basic MC3424 output circuitry shown in **Fig D** demonstrates the solution to a problem that other circuits of this type suffer. Although you would like the output drive to be OFF (ie, the output comparator holding transistors Q_2 and Q_3 OFF), a rapid V_{CC} rise can cause the parasitic capacitance at Q_1 's base and Q_5 's collector-base junction to generate displacement currents (I_B and I_{CB}), which then enter node A.

If transistor Q_4 is OFF, this parasitic current drives the base of the Darlington output device and creates a spurious output. In the MC3424, though, transistor Q_4 is turned on through resistor R, sinking the displacement current when the supply has risen above approximately 0.7V. This technique permits supply turn-on voltage dv/dt to exceed 200V/µsec before 1 mA of parasitic output drive current is generated.

For a data sheet on the MC3424, Circle No 449.





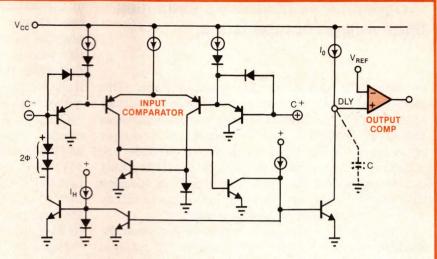


Fig B—Programmable input hysteresis results from controlling the current flow through the MC3424's inverting inputs' diodes. Tying an external resistor (R_H) to each inverting input generates a hysteresis voltage equal to the diode current (typically 12 μ A) times the resistance value.

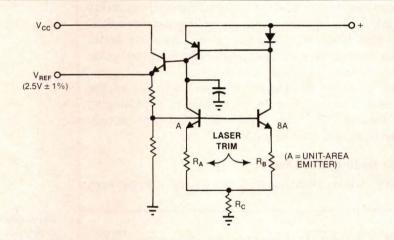

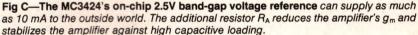

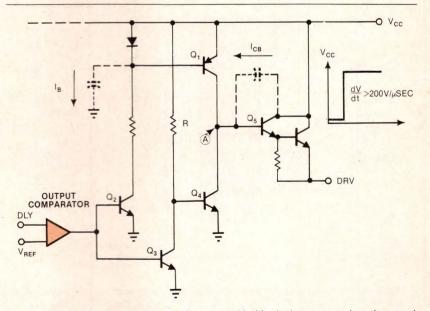

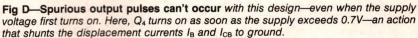

Programmable hysteresis simplifies tight voltage comparisons

an internally generated untrimmed voltage. This arrangement tends to constrain usage to one particular application type; ie, always sensing over/undervoltages above the reference. And for single-positive-supply operation, this limitation automatically excludes all negative voltages. You might also be unable to easily disable any one of the input functions for a specified time interval or adjust the input hysteresis to satisfy some particular input-noise requirement.

An especially troublesome situation occurs when the on-chip reference voltage isn't available for external use; you can't employ this voltage as a system reference throughout your design. And if it's available but untrimmed, you often must trim all of the design's level-shifting resistors. Additionally, some powersupply-monitoring ICs have output-current capability too low to directly drive high-power transistors or SCR crowbars. Conversely, it's not unusual for some device types to produce a spurious high-current output pulse when the supply voltage first turns on.

All of these drawbacks are designed out of the MC3424. The result? A device capable of wide-ranging applications, not the least of which are supply monitoring and fault detection.

Fault finding made easy

Even when operating with one supply voltage, each



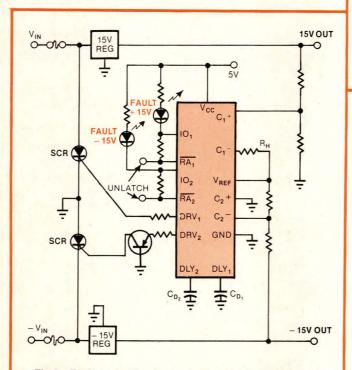


Fig 2—Fault-protecting two separate supplies is easy with the MC3424. If either 15V supply faults, the IC senses the condition and crowbars the appropriate SCR and fuse. The 5V supply is necessary only if continuous LED fault indication is important. of the MC3424's input comparators can sense either overvoltages or undervoltages for all positive and negative values greater or less than the reference. And this sensing can occur with or without programmable hysteresis. Hence, you can implement all of the possible input-comparator configurations depicted in **Fig 1** without using additional devices.

Consider a power-supply supervisory function, for example. Assume you want to monitor two separate and independent supplies for overvoltage faults: one at 15V with hysteresis, the other at -15V without hysteresis. You can arrange the supervisory circuitry so that when either supply reaches an overvoltage level for more than a specified time, an SCR crowbar blows its fuse and the appropriate indicator turns on.

However, because both supplies can shut down

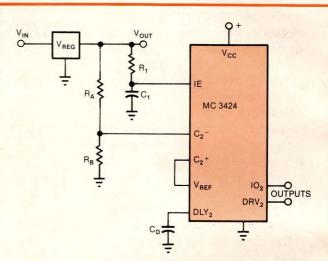

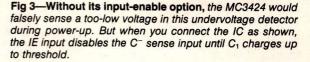

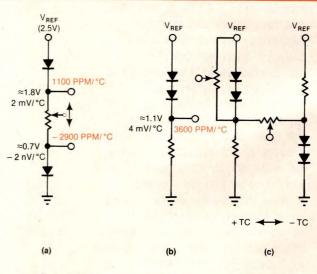


Fig 4—Obtain positive and negative TCs from the MC3424's sense-reference level with the scheme shown in (a). A larger (but fixed) positive TC results with the circuit in (b), and (c) provides a method of achieving variable positive or negative values.

simultaneously, in this case you should power the MC3424 from a third supply to activate the desired indication. Also, you must latch the appropriate output ON once the overvoltage occurs, because the crowbar removes the overvoltage condition. Achieve this latching capability merely by connecting the IC's Indicator Output pin (IO) to the Remote Activation input (\overline{RA}) through a resistor (Fig 2). Then, during an overvoltage, the IO pin is pulled to ground, holding \overline{RA} below the TTL threshold and latching both outputs of that channel ON, regardless of subsequent input conditions. You can unlatch the output by pulling \overline{RA} above the TTL input threshold.

Adjust the input hysteresis for the positive-voltage sensing by varying the $I_H R_H$ product, and select the delay capacitors (C_{D_1} and C_{D_2}) to meet your specified time-delay requirements. The gate and indicator output resistors serve to force the high-current outputs into

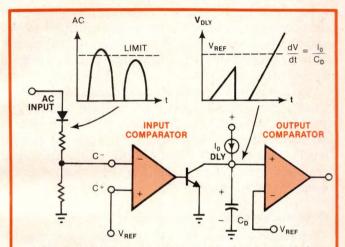


Fig 5—AC-power-line monitoring can occur on a cycle-bycycle basis with the MC3424. If the peak ac input doesn't exceed a predetermined limit, capacitor C_D charges to the output comparator's reference level, and a fault output results.

saturation, minimizing chip power dissipation in the Output Latched mode.

Fig 3 demonstrates how you can employ input comparator 2 of the MC3424 to sense undervoltage conditions with hysteresis. Choose the R_1C_1 product to ensure that the sensed supply's undervoltage condition during power-up is not reported; to accomplish this function, C_1 holds the high-impedance Input Enable pin (IE) below its TTL threshold. Resistor R_1 subsequently charges C_1 past the IE threshold and permits undervoltage monitoring of the sensed supply after that supply reaches its normal operating range.

Hysteresis magnitude is determined by the $I_{\rm H}(R_{\rm A}||R_{\rm B})$ product, and internal charge current I_0 and capacitor $C_{\rm D}$ control comparator output delay. Note that input comparator 1 isn't disabled when input comparator 2 is unless the noninverting input (C_1^+) is less than $0.9V_{\rm REF}$. Because the comparators have an input common-mode range spanning $V_{\rm CC}$ -1.4V, you can easily monitor *relative* voltages. Voltage V₁, for example, can be checked to see whether it's always greater than V₂; likewise for V₃ greater than V₄. Similarly, you can sense whether $V_1 > V_2 > V_3$. And should a voltage lie outside the IC's common-mode range, you can use resistive scaling to bring it within that range.

Track the sensed voltages' TC

Sometimes a sensed voltage has a well-defined temperature coefficient that you'd like to track. Several possibilities exist for generating both positive and negative TCs when you use the MC3424's reference voltage in conjunction with some external forwardbiased silicon diodes.

Such diodes—with a TC of approximately -2 mV/°C—can connect to the IC's zero-TC V_{REF} pin to achieve an overall positive TC, a technique depicted in

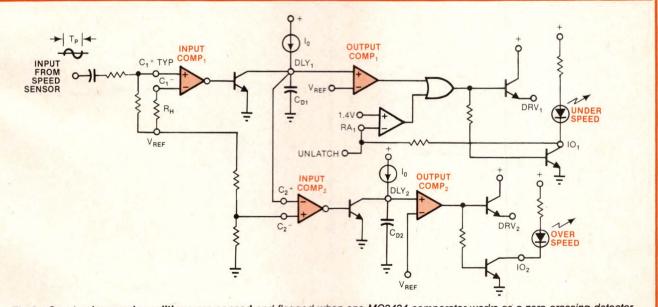


Fig 6—Over/underspeed conditions are sensed and flagged when one MC3424 comparator works as a zero-crossing detector and the second functions as a variable-threshold detector. So long as the input-signal period (T_P) falls within the time windows set by C_{D_1} and C_{D_2} , neither LED lights.

Dual 300-mA output stages drive SCR crowbars directly

Fig 4a. And you can realize larger positive TCs by using the scheme shown in Fig 4b, incrementally adjusting those TCs with the method detailed in Fig 4c. Finally, you can easily realize negative TCs by connecting the off-chip diodes to ground.

Monitor the mains

The MC3424-based ac-mains monitor shown in Fig 5 can sense a low ac-mains voltage occurring for any specified number of cycles. When the ac voltage is below the defined limit for that number of cycles, the MC3424's input comparator allows the delay capacitor to charge at a dv/dt determined by I_0/C_D .

If the next cycle's most positive peak exceeds the limit, the comparator's output pulls the capacitor's accumulated voltage back toward ground. However, if the next cycle's peak doesn't exceed the limit, C_D continues to ramp up at the same uninterrupted rate. By selecting the appropriate value for C_D , you can determine how many cycles the circuit can miss before C_D 's voltage reaches the output comparator's V_{REF} threshold and triggers an output response.

Sequential turn-ons are possible

In another MC3424 application, you can interconnect one channel's IO pin with the other's RA or Delay (DLY) terminal and realize a sequential activation sequence. For example, if you hook up channel 1's IO pin to channel 2's RA input, channel 1 triggers channel 2's output, but 2 won't activate 1's output. Alternatively, if you couple channel 1's IO to channel 2's DLY input so that 1's output holds DLY LOW, a channel 1 output inhibits a channel 2 output without the converse condition being possible. Consider what other possibilities exist if you permit interaction to occur with the IE pin.

You can also generate sequential time delays. Connect the input comparators to a common input signal; by selecting different delay-capacitor values, you can then produce different time delays for each channel—with repeatability limited only by the capacitors' tolerances and TCs. Independent high-current outputs then occur after a fixed time interval from the input's transition.


Try a 2-input, variable-threshold AND

By connecting channels 1 and 2's DLY pins together, you can obtain a 2-input, variable-threshold AND function, with or without delay. If you also connect the drive and indicator outputs together, you double the minimum drive and indicator output currents to 600 and 60 mA, respectively. Furthermore, by making use of the IE function's TTL threshold, you can create a 3-input AND gate.

You can also realize an OR gate. Connecting channel 2's indicator outputs together accomplishes half the job; you must also OR the drive outputs with a pair of off-chip diodes capable of handling the 300-mA current levels. Connect each diode's anode to the individual channel's outputs and obtain the ORed output at the common-cathode point.

Over/underspeed indicator works continuously

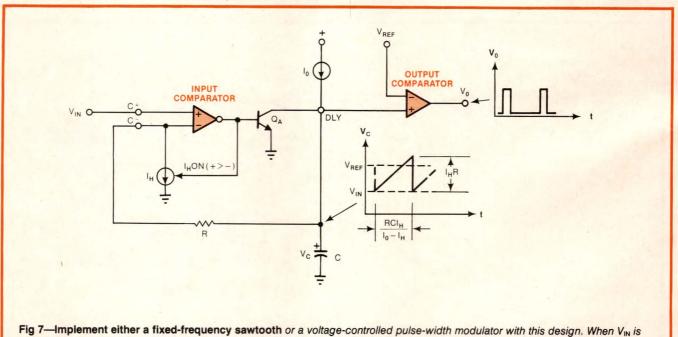The indicator depicted in **Fig 6** demonstrates how you can use one comparator in the MC3424 as a zerocrossing detector with hysteresis while the other acts as a variable-threshold detector. Here the object is to



rig 7—Implement either a fixed-frequency sawtooth or a voltage-controlled pulse-width modulator with this design. When V_{IN} is constant, the sawtooth's period is determined only by the relationship shown. But when you modulate V_{IN} , the varying point at which the sawtooth's peak exceeds the reference voltage determines the output pulse's width.

latch an indicator ON when an underspeed situation occurs and continuously indicate overspeed conditions.

Assume the ac input (with period T_P) comes from a speed sensor. Set input comparator 1 to switch with a hysteresis voltage of I_HR_H for any positive-input zero crossings. Under these constraints, C_{D_1} ramps to a voltage of $I_0T_P/2C_{D_1}$ before the negative-going input cycle pulls the capacitor back toward ground. At speeds below the desired limit, the capacitor's voltage exceeds not only output comparator 1's threshold, but also input comparator 2's during the positive-going input interval $(T_P/2)$.

This action clamps the DLY_2 voltage to ground and turns channel 1's outputs on. And because channel 1's IO pin connects to the \overline{RA} pin, the output latches up and indicates that an underspeed condition has occurred. During the negative-going input cycle, DLY_1 's voltage clamps to ground, and DLY_2 's voltage is allowed to rise. Choose C_{D_2} for worst-case minimum speed, however, so that DLY_2 's voltage can't reach output comparator 2's V_{REF} threshold before the next positive input occurs.


When the speed increases to the design range, DLY₁'s voltage doesn't reach output comparator 1's threshold but does continue to exceed input comparator 2's, thereby always resetting C_{D_2} . This action allows channel 1 to unlatch if \overline{RA}_1 's input voltage gets pulled above the TTL threshold. Thus, both outputs remain OFF when the input speed lies within range. At speeds above the design limit, C_{D_1} 's voltage remains below the thresholds of both input comparator 2 and output comparator 1. Channel 1's output is OFF and C_{D_2} charges beyond output comparator 2's threshold,

producing a continuous channel 2 output so long as the input frequency (speed) exceeds the upper limit.

RC oscillators are simple and stable

Fig 7 shows an interesting method for using an MC3424 to create an RC relaxation oscillator. The design employs one resistor, one capacitor and an input comparator. Assume that the delay capacitor's voltage has just decreased past the input voltage V_{IN} (due to the IC's pull-down current of transistor QA). This action activates the hysteresis current and produces an I_HR voltage differential at the comparator's input. The internal pull-down current switches off, and the delay-capacitor voltage begins to rise at dv/dt equal to $(I_0 - I_H)/C$. When this voltage reaches $I_H R$, the input comparator's voltage changes sign and switches the hysteresis current off. The internal pull-down current again switches on, causing the capacitor's voltage to decrease until the comparator again switches and repeats the cycle. Thus, the sawtooth waveform's magnitude is I_HR , and its period equals $RCI_H/(I_0 - I_H)$. Note that because I_H/I₀ is reasonably constant over temperature, supply-voltage and processing variations, you can tightly control the oscillator's frequency through RC selection alone.

Fig 7's design lends itself to pulse-width-modulation schemes, too. In those cases, an analog input signal (V_{IN}) modulates the output pulse's width but not its oscillation frequency. The output pulse is ON for the time during which the sawtooth's peak exceeds the output comparator's threshold. Applications for this class of proportional controller include switching regulators, motor controllers and thermal regulators.

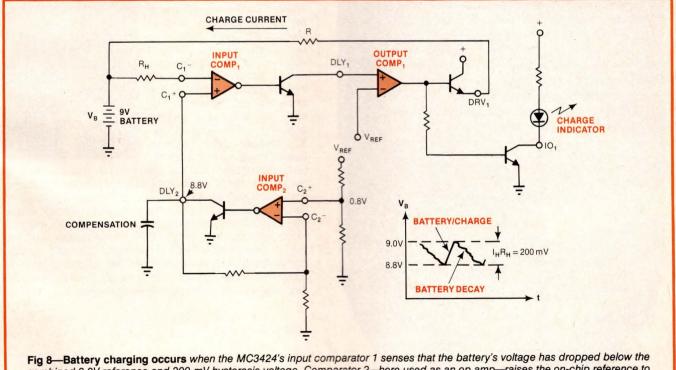

combined 8.8V reference and 200-mV hysteresis voltage. Comparator 2—here used as an op amp—raises the on-chip reference to 8.8V. Because the IC can use any supply voltage between 4.5 and 40V, you can adapt this design to any requirement so long as the 300-mA max charge-current limit isn't exceeded.



LECTRO-QUIP.

THE NOW GENERATION OF SWITCH LOCKS FOR ADVANCED ELECTRONICS AND COMMUNICATIONS APPLICATIONS

Every component and feature in this field-proven line has been designed to deliver top performance. Example: solderable faston type terminals made of silver plated copper alloy, rotary slide and wafer design switches and die cast "Zamak 3" zinc alloy bodies. Small wonder more and more manufacturers of computer terminals, data storage systems, test and measurement instruments and medical electronic equipment are specifying LECTRO—QUIP.

> Write Or Call Today

Ilinois Lock Company

A Division of The Eastern Co. 301 West Hintz Road • Wheeling, Illinois 60090 Phone 312-537-1800

Built in delay functions suppress power-up false triggering

Charge a battery with one IC

As a final example, the battery-sense and-charger design detailed in Fig 8 exploits the MC3424's input comparators as op amps. Here, you scale up the on-chip reference voltage to 8.8V by applying feedback around comparator 2. (Note that you must keep the input voltage to the op amp below the hysteresis-threshold level to eliminate the positive-hysteresis loop's oscillatory tendencies.)

Comparator 1 uses this 8.8V level as the reference on its noninverting input and senses the battery's voltage through its inverting input. The base current of the input pnp transistor associated with the inverting input, although small, actually tries to charge the battery in the Sense mode rather than discharge it. Hence, this design (unlike others) offers true "no-load" battery-monitoring capability.

When the battery voltage falls below the 8.8V reference, comparator 1 turns the hysteresis current and outputs on. The output charges the battery at a current rate limited by resistor R until the battery's voltage equals 8.8V plus the 200 mV $I_{\rm H}R$ hysteresis voltage. (Eliminating R allows you to achieve a 300-mA rate.) Then comparator 1 again switches and turns off the charge cycle and LED indicator.

Author's biography

William Davis, a senior member of the technical staff at Motorola's Semiconductor Div, Mesa, AZ, has made a specialty of integrated-circuit design. Within a year of earning his BSEE degree at the University of Arizona (Tucson), he became a project engineer in the firm's Linear-IC Research and Development Group. In this position,



he concentrated on the design and development of medium-power ICs, with special emphasis on monolithic voltage regulators. From there, he became engineering design manager of a consumer-oriented IC group, where he worked on automotive-IC designs and initiated Motorola's linear-I²L efforts. Bill's interests now lie in the design and development of industrial ICs, and he has completed the course work for an MS degree at Arizona State University (Tempe). He holds 27 patents in the IC field and has authored several related papers.

> Article Interest Quotient (Circle One) High 476 Medium 477 Low 478

NOW! TANTALUMS WORTH WAITING FOR ...WITH LITTLE OR NO WAITING.

Sprague Tantalex[®] Solid-Tantalum Capacitors <u>Shipped 4 to 8 Weeks ARO</u> ... Popular Ratings Available Off-the-Shelf from Sprague Distributors.



- Meet stringent performance requirements of industrial and allied applications.
- Lowest guaranteed d-c leakage currents available.
 Guaranteed high-frequency impedance limits.
- High stability, little capacitance change over temperature range of -55°C to +125°C.
- High-quality epoxy-dipped coating provides excellent electrical and mechanical protection.
- Available in popular values over the range of 0.1 to 330 μF. Voltage ratings from 4 to 50 volts d-c.
- Also available as CX02 and CX12 to MIL-C-49137.

Call your Sprague sales representative or district office for competitive prices. Sprague Electric Company, 491 Marshall St., North Adams, Mass. 01247.

- Ideal for entertainment and commercial equipment.
- Priced competitively with other capacitors of this sort, domestic or offshore.
- Lower d-c leakage currents and lower dissipation factor than other capacitors of this type.
- Superior, flame-retardant, moisture-resistant epoxy encapsulant.
- Available in popular values between 0.1 and 680 μF.
 Voltage ratings from 3 to 50 volts d-c. Capacitance tolerances, ±10%, ±20%.
- Four lead configurations for easy plug-in mounting on printed wiring boards.

SPRAGUE® THE MARK OF RELIABILITY

THE BROAD-LINE PRODUCER OF ELECTRONIC PARTS

a subsidiary of GK Technologies

Network-analysis program runs on small computer system

Edward Niemeyer, Intel Corp

You can analyze a large number of network-element types by running the program discussed in this article on a Hewlett-Packard HP 9825 desktop computer. With memory requirements of approximately 13k bytes, it favors network-data storage over program-memory requirements—a plus in small computer systems. Based on Schnider's algorithm (**Ref 1**), which uses the indefinite admittance matrix to solve network problems, the program (**Fig 1**) handles both passive and active network elements and even accommodates transmission-line analysis. It's written in HPL, but if an HP 9825 is not available, you can easily translate this BASIC-like language into forms suitable for use on alternative computers.

```
0: "NET*80":dim A[10,10], B[10,10], P[10,10], Q[10,10], R[10,10]
      1: dim S[10,10],I[20]
2: dim T[20],M[20],N[20],O[20],L[20],Z[20]
      3: 1+1
       4: 1+I
    4: 1+1

5: 0+P[I,J]

6: 0+Q[I,J]

7: 0+R[I,J]

8: 0+S[I,J]

9: if I<10;I+1+I;gto 5
9: if I<10; H1+I;I; gto 5
10: J1+J; fi J<11; gto 4
11: 1+X; 0+T[X]
12: 0+N
13: ptt "1 RESISTOR"
14: ptt "2 CAPACITOR"
14: ptt "3 INDUCTOR"
15: ptt "3 INDUCTOR"
16: ptt "4 TRANS LINE"
17: ptt "5 OPEN STUB"
19: ptt "7 OP-AMP"
20: ptt "8 NPN TRANS"
21: ptt "9 FET"
22: ptt "10 STOP"
23: ptt "11 ANALY2E"
24: ptt "
25: ptt "
26: 0+C6; ent "SELECT FROM LIST++++++, r6; ptt "
27: if r6=1; ptt "(1) RES "; gto "res"
28: if r6=2; ptt "(2) CAP "; gto "cap"
29: if r6=3; ptt "(3) IND"; gto "ind"
30: if r6=4; ptt "(4) T-LINE"; gto "o, stub"
31: if r6=7; ptt "(7) OP-AMP"; gto "o, stub"
32: if r6=7; ptt "(7) OP-AMP"; gto "o, stub"
33: if r6=7; ptt "(8) NPN"; gto "non"
35: if r6=9; ptt "(9) FET"; gto "fet"
36: if r6=1; ptt "(1) ANALYSIS'; gto "anal"
36: gto 26
39: "t, line": 1+T[X]; enp "SHIELD-IN", M[X]
40: enp "CENTER-IN", I[X]; "CENTER-OUT", O[X]
41: enp "NODE A", M[X]
43: enp "QUARTER WAVE FREQ(Hz)?", L[X]
45: enp "QUARTER WAVE FREQ(Hz)?", L[X]
46: if [X] NX; M[X] +N
48: if N[X] NX; N[X] +N
44: if N[X] NX; N[X] +N
45: if N[X] NX; N[
      10: J+1+J; if J<11;gto 4
11: 1+X;0+T[X]
    46: 11 1 [X] >N; 1 [X] +N
47: 1f M[X] >N; M[X] +N
48: 1f N[X] >N; N[X] +N
49: 1f O[X] >N; O[X] +N
50: X+1+X; 0+T[X]
    51: gto 26
52: "s.stub": 3+T[X]
    53: gto 42
54: "o.stub":2+T[X]
    55: gto 42
56: "res":enp "NODE A",I,"NODE B",J,"RES(OHMS)",V
     57: 1/V+V
      58: gsb "resl"
    59: gto 26
60: "ind":enp "NODE A",I,"NODE B",J,"IND(Hy)",V
 60: "Inc":eng

61: 1/V+V

62: gsb "indl"

63: gto 26

64: "cap":enp "NODE A",I,"NODE B",J,"CAP(FARADS)",V

65: gsb "capl"

7 "SOURCE",J,"DRAIN",I,"GAIN(A/
    66: gto 26
67: "fet":enp "GATE", K, "SOURCE", J, "DRAIN", I, "GAIN (A/V) ", V
    68: J+L
69: gsb "trans"
70: qto 26
```

```
71: "npn":enp "BASE",K,"EMITTER",J,"COLLECTOR",I,"BETA",r5
72: enp "Rbe(OHMS)",V
73: 1/V+V
   74: I+L
75: K+I
   76: gsb "resl"
77: L+I
   78: J+L
  /8: J+L
79: f5*V+V
80: gsb "trans"
81: gto 26
82: "op.amp":enp "+IN",K,"-IN",L,"-OUT",I
83: enp "+OUT",J,"GAIN (V/V)",r5,"OUTPUT RES (OHMS) ",V
84: 1/V+V
85: gcb "rcol"
 84: 1/V+V

85: gsb "resl"

86: r5*V+V

87: gsb "trans"

88: gto 26

89: "anal":enp "INPUT NODE", E, "OUTPUT NODE", F;N-1+N

90: enp "START FREQ-Hz", G, "STOP FREQ(Hz)", H

91: enp "# DATA POINTS", M

92: enp "FREQ SWEEP-LOG=0(LIN=1)", r6

93: (H-G)/(M-1)+D

94: 10<sup>°</sup>(log(H/G)/(M-1))+r4

95: G+r0;0+r9;fxd 4
   96: r9+1+r9
  97: 2*π*r0+W;rad
98: E+O;F+Z
 99: gsb "t.load"
100: gsb "det"
101: r5+V;Z+U
102: if (E+F)/2=int((E+F)/2);gto 104
103: U-180+U
 104: E+0;E+Z
105: gsb "det
104: E+0;E+2
105: gsb "det"
106: U-2+U
107: if V=0;-9999+r7;gto 110
108: if r5=0;9999+r7;gto 110
109: V/r5-V;20*log(V)+r7
110: if U>180;U-360+U
111: if U<-180;U-360+U
112: prt "FREO",r0;prt "AMPL",V;prt "20LOG",r7
113: prt "PHASE",U;prt "
114: if r6=0;r0*r4+r0
115: if r6=0;r0*r4+r0
115: if r6=0;r0+D+D+O
116: if r9#M;gto 96
117: N+1+N
118: qto 26
  118: gto 26
119: "indl":R[I,I]+V+R[I,I]
  120: R[J,J]+V+R[J,J]
121: R[I,J]-V+R[I,J]
 122: R[J,I]-V+R[J,I]
123: if I>N;I+N
124: if J>N;J+N
124: if J>N;J+N

125: ret

126: "resl":P[I,I]+V+P[I,I]

127: P[J,J]+V+P[J,J]

128: P[I,J]-V+P[J,J]

129: P[J,I]-V+P[J,I]

130: gto 123

131: "capl":Q[I,I]+V+Q[I,I]

132: Q[J,J]+V+Q[J,J]

133: Q[I,J]-V+Q[J,J]

134: Q[J,I]-V+Q[J,I]

135: gto 123

136: "trans":P[I,K]+V+P[I,K]

137: P[J,L]+V+P[J,K]
 138: P[J,K] -V+P[J,K
 139: P[I,L]-V+P[I,L]
 140: if K>N:K+N
 141: if L>N;L+N
```

Without sacrificing speed, an easy-to-use program for a desktop computer lets you take full advantage of circuit-analysis techniques without the problems associated with large-scale time-shared computers.

Getting the program started

After loading the program, you start the analysis by pressing the 9825's Run key; the printer then displays a command list (Fig 2a). The first nine entries catalog the types of elements that the program accommodates; items 10 and 11 are Stop and Analyze commands.

To illustrate program syntax and internal software functions, consider a simple RLC analysis problem (Fig 3a). As a first step in this analysis, you must start at 1 and consecutively number each node in the network, ensuring that at least one element connects to each node.

Although the program interprets the highest node number as network common, you can assign any numbers you want to the input and output nodes. However, network excitation (an ideal voltage source of

142:	gto 123		1+I
143:	"comp":if N>1;gto 146		0+J;0+L
144:	A[1,1]+0;B[1,1]+2		L+1+L
145:			if L#Z;gto 214
146:			
147:			P[K+I,L+J] +A[K,L]
148:			W*Q[K+I,L+J]-R[K+I,L+J]/W+S[K+I,L+J]+B[K,L]
149:			if L#N;gto 211
	abs(A[K,K])+abs(B[K,K])+S		if K#N;gto 207 gsb "comp"
	K-l+I		r5+N
	I+1+I		√(0*0+Z*Z)+r5
	abs(A[I,K])+abs(B[I,K])+T		2+Y
	if S>=T;gto 156		if O=0;gto 228
	I+L;T+S		$180/\pi * atn(Z/O) * Z$
	if I#N;gto 152		if O>0;ret
	if L=K;gto 163		: Z+sgn(Y)*180+Z
158:	0+5 J+1+J		if Y=0;180+Z
			ret
	-A[K,J] +S;A[L,J] +A[K,J];S+A[L,J]		90*sgn(Y)+Z
	-B[K,J]+A;B[L,J]+B[K,J];A+B[L,J] if J#N;gto 159		ret
	K+1+L;L-1+I		: "t.load":if T[1]=0;ret
	I+1+I		: 0+X
	A[K,K] * A[K,K] + B[K,K] * B[K,K] + A		: 0+rl
	(A[I,K]*A[K,K]+B[I,K]*B[K,K])/A+S		: rl+l+rl;0+r2
	(A[K,K] *B[I,K] - A[I,K] *B[K,K]) / A + B[I,K]		: r2+1+r2
	S+A[I,K]	235:	: 0+S[r1,r2]
	if I#N;gto 164	236:	: if r2#N+1;gto 234
	K-1+C	237:	: if rl#N+1;gto 233
	if C=0;gto 179		: X+l+X
	L-1+J	239:	: if X>20; ret
	J+1+J;0+I	240	: if T[X]=0;ret
	I+1+I	241	: if T[X]=1;gto 247
	A[K,J] - A[K,I] * A[I,J] + B[K,I] * B[I,J] + A[K,J]	242	: if T[X]=2;gto 266
	B[K,J] - B[K,I] * A[I,J] - A[K,I] * B[I,J] + B[K,J]	243	: -1/(Z[X] *tan(.25*W/L[X]))+r1
	11 C#1;gto 174		M[X] + Q; N[X] + R
178:	if J#N;gto 173		: gsb 270
179:	K+C		: gto 238
180:	K+1+K;K-1+I		: -1/(Z[X]*tan(.25*W/L[X]))+r1
	I+1+I;0+J		: M[X] +Q; I[X] +R
	J+1+J		: gsb 270
	A[I,K] - A[I,J] * A[J,K] + B[I,J] * B[J,K] + A[I,K]		: N[X] +Q;O[X] +R;gsb 270
	B[I,K]-B[I,J]*A[J,K]-A[I,J]*B[J,K]+B[I,K]		: 1/(Z[X]*sin(.25*W/L[X]))+r1
	if J#C;gto 182		: I[X]+P
	if I#N;gto 181		N[X] +R
	if K#N;gto 149		: S[R,P]-rl+S[R,P]
188:			: S[P,R]-rl+S[P,R]
	int(N/2) +C		: O[X]+R
	if N=2*C;gto 193		: S[R,P]+rl+S[R,P] : S[P,R]+rl+S[P,R]
	0+L		: M[X] +P
	A [N, N] +O; B [N, N] +Z O+I		: S[R,P]-r1+S[R,P]
	I+1+I		: S[P,R]-rl+S[P,R]
	N-I+L+J		: N[X] +R
	A[I,I]*A[J,J]-B[I,I]*B[J,J]+S		: S[R,P]+r1+S[R,P]
	A[I,I]*B[J,J]+A[J,J]*B[I,I]+A		: S[P,R]+r1+S[P,R]
	0*S-Z*A+T		: gto 238
	Z*S+O*A+Z		: 1/(Z[X]*tan(.25*W/L[X]))+r2
	T+0		: 1/(Z[X]*sin(.25*W/L[X]))+r3
	if I#C;gto 194		: r3*r3/r2-r2+r1
	ret		: gto 244
	"det":N+r5		: S[Q,Q] + r1 + S[Q,Q]
	N-1+N		: S[R,R]+r1+S[R,R]
	0+I	272	: S[Q,R]-r1+S[Q,R]
	0+K		: S[R,Q] - r1 + S[R,Q]
	K+1+K	274	: ret
	if K#O;qto 210	*39	9

Fig 1—High transportability characterizes this network-analysis program. The BASIC-like HPL language in which it's written easily translates for use on computers other than the HP 9825.

Program places no restrictions on input/output-node numbering

unit magnitude) is always between input and common, and output readings are presented in relation to the common terminal. Order of network-element entry is not critical because the analysis doesn't start until you select item 11 on the command list.

To initiate program data entry for this example, enter a number from the command list and press the Continue key. (This key provides the same function as Carriage Return on a larger system, reactivating the computer at the end of data entry.) The program prints the selected network element and then branches to one of the subroutines shown in the command-list flow diagram (Fig 2b).

As the program accesses each subroutine (Fig 3b), it places each element value and related topology information into the appropriate P (resistive), Q (capacitive) or R (inductive) matrix and prints a permanent record of both the questions and the data. It continues this data-collection process until it has entered data describing the complete network. Fig 3c represents the final state of the P, Q and R matrices,

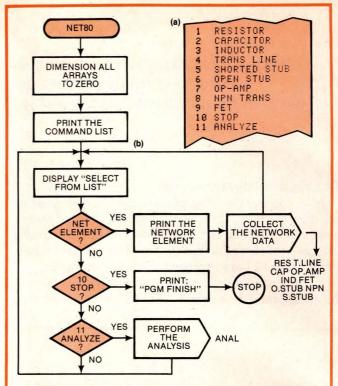


Fig 2—The program accommodates a wide variety of network elements (a). A flowchart (b) illustrates the element-value collection sequence.

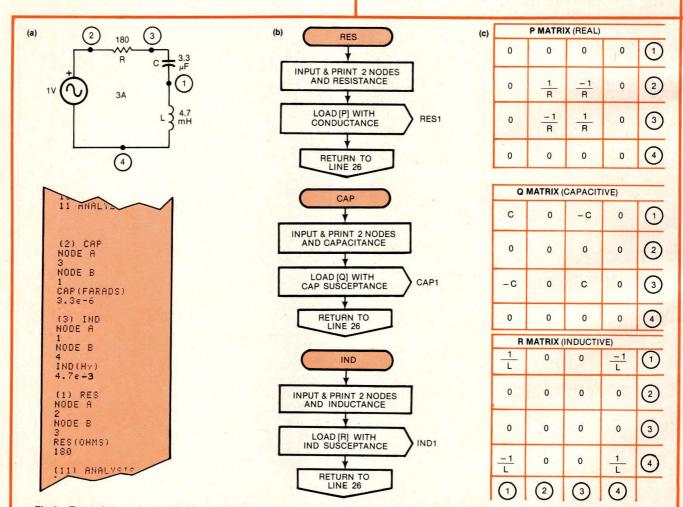


Fig 3—To analyze a simple RLC network (a), the program uses similar subroutines (b) to add the resistive, capacitive and inductive components to their respective matrices (c).

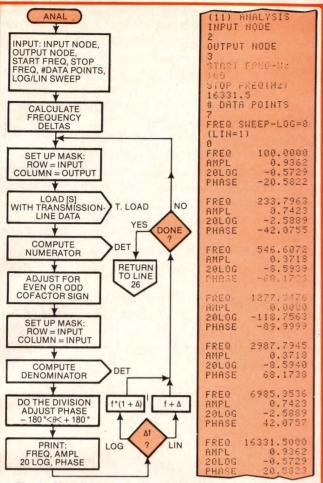


Fig 4—Magnitude and phase calculations at each new frequency occur in the main analysis loop. The 20log value adds dynamic range to the program.

respectively, for this example.

Justifying matrix construction

Note that data for each passive element appears, in a perfectly symmetric manner, at the corners of a square in the appropriate matrix. Furthermore, this data is centered on a diagonal, with the node numbers defining both row and column position. To show why this appearance results, write the current equations in terms of the node voltages. For nodes 1 through 4,

$$sC(V_1 - V_3) + \left(\frac{1}{sL}\right)(V_1 - V_4) = 0$$

$$\left(\frac{1}{R}\right)(V_2 - V_3) = I_2$$

$$\left(\frac{1}{R}\right)(V_3 - V_2) + sC(V_3 - V_1) = 0$$

$$\left(\frac{1}{sL}\right)(V_4 - V_1) = -I_2.$$

Collecting the terms by the various node voltages gives all of the coefficients for each respective nodal expression the dimensions of admittance:

$$\left(sC + \frac{1}{sL} \right) V_1 + (0)V_2 + (-sC)V_3 + \left(-\frac{1}{sL} \right) V_4 = 0$$

$$(0)V_1 + \left(\frac{1}{R} \right) V_2 + \left(-\frac{1}{R} \right) V_3 + (0)V_4 = I_2$$

$$(-sC)V_1 + \left(-\frac{1}{R} \right) V_2 + \left(sC + \frac{1}{R} \right) V_3 + (0)V_4 = 0$$

$$\left(-\frac{1}{sL} \right) V_1 + (0)V_2 + (0)V_3 + \left(\frac{1}{sL} \right) V_4 = -I_2.$$

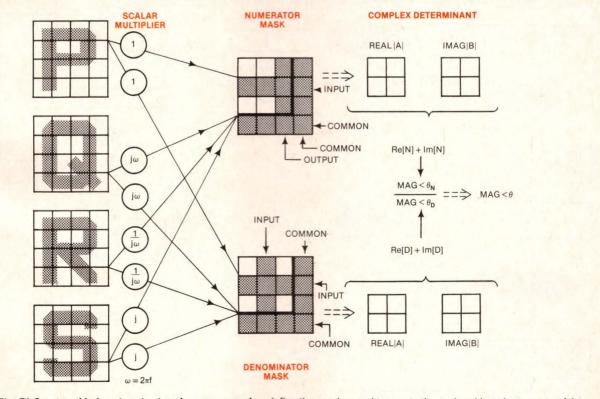


Fig 5—The RLC network's input, output and common nodes define the masks used to create the real and imaginary parts of the complex determinants for the numerator and denominator. The quotient of the complex vectors prints as a magnitude and phase.

Active-device modeling approach parallels that for passive units


Then, separating these coefficients into resistive, capacitive and inductive components shows that the complex-frequency terms containing s and 1/s represent the only difference between those components and the P, Q and R matrices. But these frequency terms factor out because they are scalar multipliers in both the Q and R matrices.

Getting down to cases

With this justification of the program's data-entryphase operation, you're ready to begin the network analysis. Enter 11 from the command list. After collecting input and output node numbers, start and stop frequencies and the number of data points for the frequency sweep (including starting frequency), the HP 9825 runs through the program and provides a printout. This data is actually the quotient of two values returned from the DET subroutine (Fig 4). At every frequency, each element of the P matrix passes through its corresponding position in the numerator-blockout mask to form the real part of the matrix's complex determinant (Fig 5). With appropriate frequency adjustments, the Q, R and S matrices receive similar treatment for summing into the determinant's imaginary part. After similar treatment of the denominator, the program then evaluates the determinants and converts the information into polar coordinates to present as final output data.

The numerator mask suppresses the rows representing the input and common nodes and the columns representing the output and common nodes. Suppression of rows and columns representing the input and common nodes occurs in the denominator mask. Fig 6 illustrates the details of this function, and Ref 2 offers the underlying theory and a treatment of the analysis method.

When the computer finishes printing the frequencyanalysis data, the program returns to the command-list entry point. If necessary, you can then enter negative passive elements to modify various network values for further analysis.

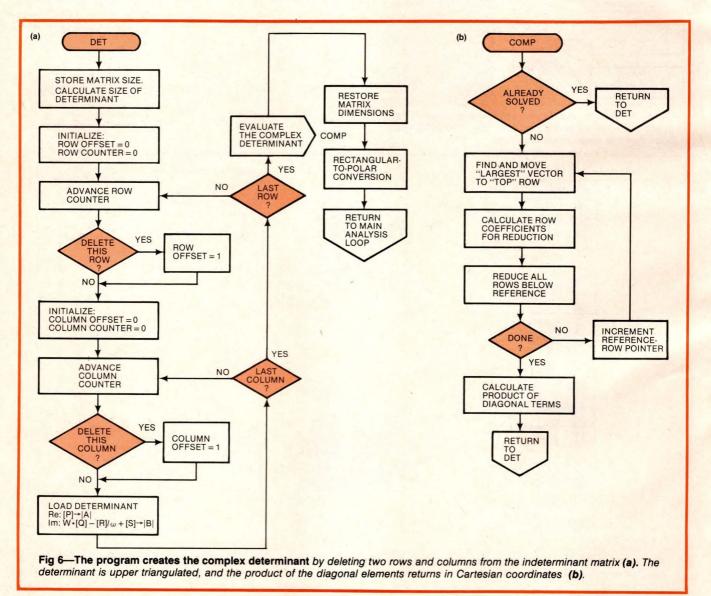

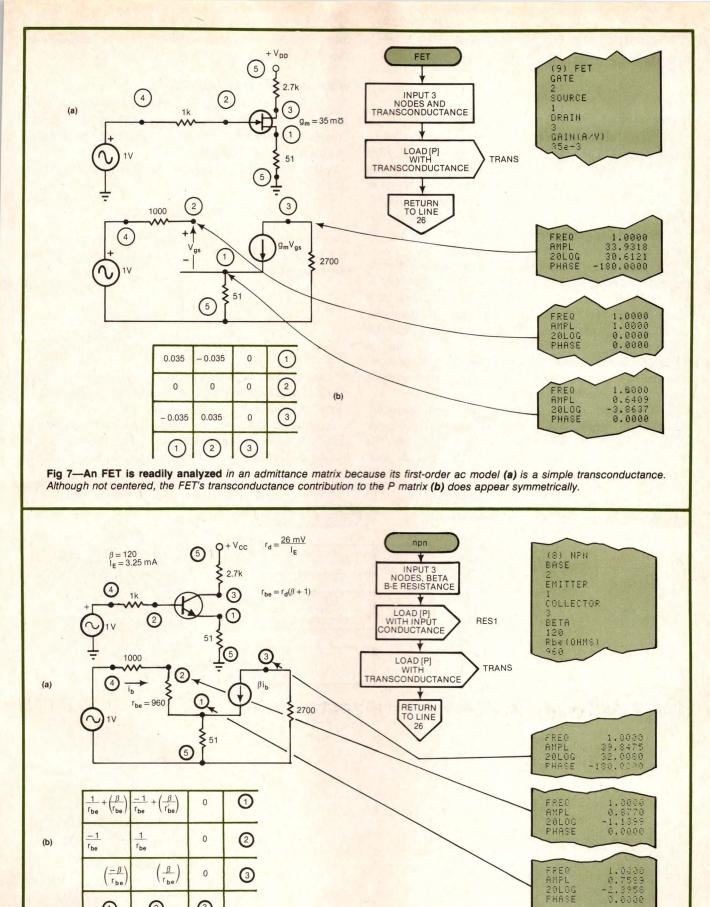


Fig 8-For network analysis, the program models an npn transistor as a resistance and a transconductance (a). It then loads these elements separately into the P matrix (b).

3

2

Z-mismatched transmission lines appear to contain active devices

Active devices present no problems

The approach to active-device modeling is similar to that for passive devices. Because an FET's first-order ac model is merely a transconductance (Fig 7), this type of active device is the simplest one for analysis in an admittance matrix. Note that interelectrode components (such as capacitance) between existing nodes require no additional memory space—you can handle them as you would any passive component.

You can model any other type of transistor as a simple extension of the FET by calculating the equivalent of its input voltage from the values of input current and base-emitter resistance (**Fig** 8). For this circuit model, P-matrix loading requires two separate steps: First the program loads the resistive component r_{be} ; then it calculates the transconductance (using the transistor's base-emitter resistance and current gain β) and loads that quantity into the P matrix.

Op-amp modeling usually utilizes a differentialvoltage-gain block with a defined output impedance (Fig 9). With the same subroutines used for the transistor, the program calculates the block's lowfrequency Norton output equivalent and loads it into the P matrix as a resistance and transconductance.

What about transmission lines?

The program also accommodates transmission-line analysis, but this type of passive network element presents an interesting problem—you must model it as an active device (Fig 10).

A transmission-line analysis starts with this equation (Ref 3):


$$E_1 = E_2 \cosh \gamma x + I_2 Z_0 \sinh \gamma x.$$

Limiting the model to lossless lines and assuming implied line reciprocity, applying hyperbolic-to-circular identities yields


$$\begin{split} \mathbf{I}_{1} &= \left(\frac{-\mathbf{j}}{\mathbf{Z}_{0} \tan \theta}\right) \mathbf{E}_{1} + \left(\frac{\mathbf{j}}{\mathbf{Z}_{0} \sin \theta}\right) \mathbf{E}_{2} \\ \mathbf{I}_{2} &= \left(\frac{-\mathbf{j}}{\mathbf{Z}_{0} \tan \theta}\right) \mathbf{E}_{2} + \left(\frac{\mathbf{j}}{\mathbf{Z}_{0} \sin \theta}\right) \mathbf{E}_{1}. \end{split}$$

In each of these equations, the first and second voltage coefficients are admittance and transadmittance components, respectively.

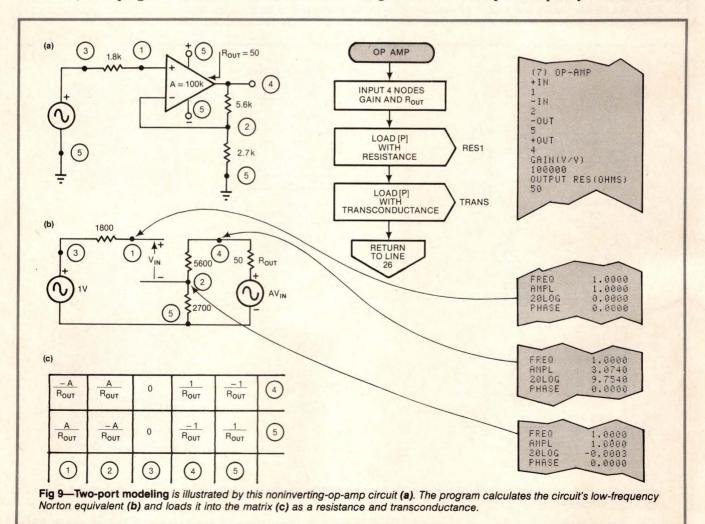A significant difference exists between this transmission-line model and the models cited earlier—you can no longer factor the complex frequency term out of the



EDN FEBRUARY 4, 1981

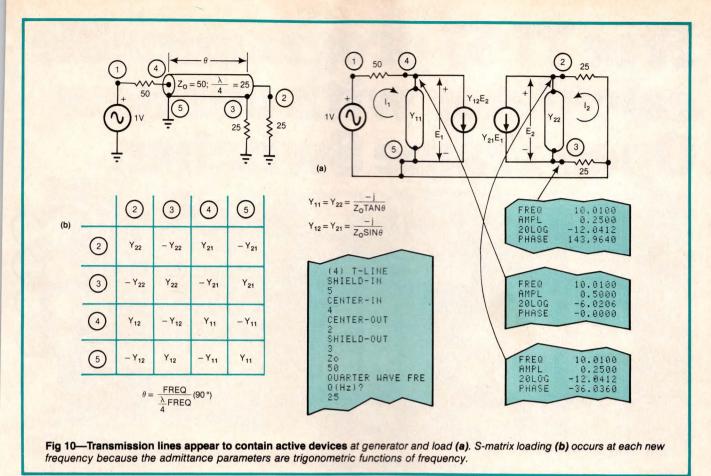

matrix. Thus, you'll now require an additional $n \times n$ matrix and a network list for lines. Execution time also increases, because the program now must load the new matrix at each new frequency. However, an IF statement does save execution time when the transmission-line list is empty by bypassing transmission-line-subprogram operations.

You can derive the line's open- and short-circuit stubs by opening $(I_2=0)$ or shorting $(E_2=0)$ the transmissionline model's output end and solving for the input admittance. Both exercises yield a circular-function 2-terminal admittance for loading into the S matrix like transmission-line data at each new frequency. To minimize memory requirements, these elements use a subset of the data-acquisition- and transmission-linematrix loader routines.

NEXT TIME

Look for a Special Report on high-frequency instruments in EDN's February 18 issue. You'll also find articles on

- The use of S/H amplifiers as circuit components
- The use of a digital storage scope's Envelope mode to catch short-lived glitches on long sweeps.

... and much more. You can't afford to miss this issue!

EDN: Everything Designers Need

References

1. Schnider, W A, "Verify network frequency response with this simple BASIC program," *EDN*, October 5, 1977, pg 87.

2. Mason, S, and Zimmerman, H, *Electronic Circuits, Signals and Systems*, John Wiley and Sons Inc, New York, 1960.

3. ITT Editorial Board, *Reference Data for Radio Engineers* (fifth edition), Howard W Sams and Co, Indianapolis, IN, March 1970.


Author's biography

Edward Niemeyer is testengineering manager at Intel Corp's Telecomm-Automotive-Military Operation (TAMO), Santa Clara, CA. His duties include optimization of IC production testing and development of production-test hardware and software for future telecommunications products. A pilot, Ed dabbles in amateur radio and photography in his spare time.



Article Interest Quotient (Circle One) High 482 Medium 483 Low 484

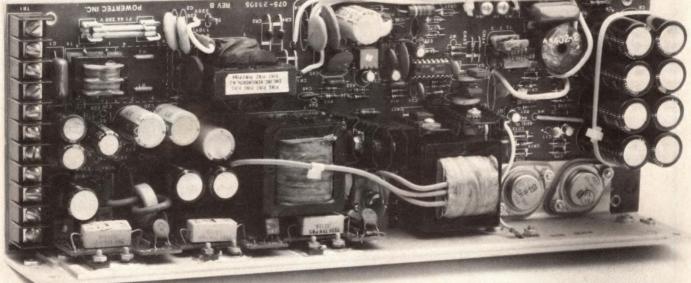Free TI-57 programmable calculator with our new n Frame Switcher.



Powertec new 150W quad output open frame ValuSwitchers™ +5V @ 20A, ±12V @ 4A, -5V @ 4A 19C-A01-A + 5V @ 20A, ± 12V @ 4A, + 24V @ 2A + 5V @ 20A, ± 15V @ 4A, - 5V @ 4A 19C-B01-A 19C-C01-A +5V @ 20A, ±15V @ 4A, +24V @ 2A 19C-D01-A



MAIL COUPON WITH PURCHASE ORDER FOR POWERTEC'S SPECIAL OFFER AND GET YOUR PROGRAMMABLE CALCULATOR FREE!

(One to a customer, limited time offer.)

Yes, I'd like to make my own evaluation. My company purchase order is enclosed listing the desired 150W Valu-Switcher at \$245 and free TI-57 Programmable Calculator.

> 19C-A01-A 19C-C01-A 19C-B01-A 19C-D01-A

Send me complete information on your new full line of Series 19 ValuSwitchers.

The figures are all in your favor - simply buy a new Powertec 150W guad output fully-regulated ValuSwitcher for only \$245 (our 100 unit price) and get a free TI-57 programmable calculator (\$75.00 value) for use on your job.

We're making this special offer so you can test and compare Powertec features, dependability, quality and cost with what you're using now. We figure the ValuSwitcher will prove it has more of what you're looking for - in the same space.

These ValuSwitchers feature: DC Outputs: Fully regulated, OVP on all outputs. Size: 2.5" x 4.8" x 13.6" (OL-150 replacement). Widest AC Input Range: 90-132/180-264 VAC. Tight Load **Regulation:** All outputs $\pm 0.2\%$ except -5V, $\pm 1\%$. Brownout: 85 VAC or 170 VAC. Holdup: 20 ms minimum from nominal line. Safety: Designed to UL478, VDE 804, CSA 22.2 and IEC 435-Basic. EMI: Designed to meet FCC requirements. Field strappable: 115/230 VAC.

Need power fail module or cover? These options and a lot more are yours in Powertec's full line of new Series 19 ValuSwitchers - your choice of semi-regulated or fully regulated models in four standard voltage combinations at power levels of 50, 150 and 300 watts. For more information. Circle No 60

Name	
Company Name	The state of the state
Address	MS No.
City/State/Zip	
Phone/Area Code/Number	EDN-2
DORSZ	NUMB

D.C. Power Supplies

POWERTEC, INC., DEPT. VS. 20550 Nordhoff Street, Chatsworth, California 91311 (213) 882-0004 TWX 910-494-2092

AFTER YEARS OF WORLDWIDE SUCCESS ELMA SWITCHES COME TO AMERICA!

SUPERIOR QUALITY, PRECISION MADE IN SWITZERLAND, BY MAJOR EUROPEAN MANUFACTURER, ELMA SWITCHES ARE NOW AVAILABLE IN U.S.A....AND WE, AT TRANSTEK TAKE THE PLEASURE TO MAKE THIS INTRODUCTION TO THE AMERICAN ELECTRONIC INDUSTRY!

TRANSTEK, INC., SOLE U.S. AGENT AND DISTRIBUTOR FOR THIS LEADING MANUFACTURER OFFERS SHIPMENTS FROM LOCAL STOCK OF ELMA'S MOST EXTENSIVE LINE OF ROTARY SWITCHES.

The ingenuous and uniquely adaptable design of each one of Elma's seven basic types offers literally hundreds of configurations in standard versions alone. Together with practically limitless number of possibilities for custom designs, to suit even the most uncommon requirements, Elma switches cover the widest variety of switching applications.

EXCLUSIVE FEATURES COMMON TO ALL ELMA SWITCHES:

ALL SWITCHES ARE AVAILABLE IN EITHER ONE OF THE THREE COLOR CODED VERSIONS OF GOLD TREATED CONTACT MATERIALS:

0.2 MICRON GOLD FLASHED CONTACTS (BLUE) 3 MICRON HARD GOLD PLATED CONTACTS (RED) 5 MICRON HARD GOLD PLATED CONTACTS (BLACK) ALSO, ALL HAVE USER ADJUSTABLE POSITION STOPS - OR ALTERNATIVELY EACH CAN BE ORDERED WITH FACTORY PRESET NUMBER OF POSITIONS, DUST PROOF CONSTRUCTION - OR REMOVABLE TRANSPARENT DUST COVERS, SPRING LOADED BALL/GROOVE INDEXING MECHANISM (EXCEPT 05 TYPE USING STARWHEEL MECHANISM)

TYPE 04P (CIRCLE 120)

Derived from type 04, this model is basically of the same construction and features, ec ceramic wafers are replaced with printed circuit board wafers made of glass epoxyde. Tinned solder tabs (standard 01" spacing) are directly insertable on PC boards. ures, except Standard 04P versions are only available with 3 micron gold plated contacts, with all other mechanical/electrical specs being the same as for type 04.

In addition to the standard option, BCD 10 position wafer design, 04P printed wafers offer the best media for "special" internal connections according to the customer's design.

Another ELMA exclusive – unique combination of top quality switch with top security lock! All the outstanding features of 01 and 06 type switches are now complemented by the features most wanted by entire security, communications, computer, cash register, surveillance, access control and associated industries.

To be used wherever only the highest level of security is required – ELMA lock switches offer most revolutionary, newly-developed lock with: springless tumblers, flat but uncopiable keys, (by any standard RCLF 124) equipment) and most importantly – up to 4 different key **TYPE 01/06L** (CIRCLE 124) combinations per each lock.

> Furthermore, the total number of either "key removable" or "key unremovable" positions (up to 12) can vary with each individual key-according to user's requirements.

> > NEW!

TYPE 01

(CIRCLE 125)

High performance and quality in

alate (PBTB)

compact size at economy price.

36° indexing angle – 12 (shorting)
 36° indexing angle – 10 (shorting)
 60° indexing angle – 6 (nonshorting)

num positions

Maximum poles per wafer – 4 Maximum wafers per switch – 2

rotor of polybutyleneterephthalate (P Maximum contact rating 3 A @ 20°C

Wafers made of HF ceramic

Maxin

5 (CIRCLE 121) r in performance, sturdy in construction, is a "natural" for all heavy tions and where high number per wafer is a require m positio indexing angle-26

a) indexing angle -13

ting) ım poles per wafer – 13 ım wafers per switch—3 rd versions) nade of HF ceramic/ polycarbonate (PC) um contact rating 20°C

EWI

TYPE 04

(CIRCLE 122)

"backbone" of ELMA line with t standard features and most ptability to custom requirements. imum positions @ 15° indexing angle—24 (shorting) imum positions @ 30° indexing angle—12 (nonsho imum poles per wafer—6 imum waters per switch – 4 (standard versions) ers made of HF ceramic/rotor of polyacetal (POM) dmum contact rating 5 A @ 20°C

TYPE 06 (CIRCLE 123)

Mini in size, maxi in performance and midi in price. Maximum positions $@\ 30^\circ$ indexing angle -12 (shorting and nonshorting (including 12 positions BCD code switch) Maximum poles per wafer – 4 Maximum wafers per switch – 4 (standard versions) Wafers made of diallylphthalate (DAP)/rotor of polyacetal (POM) Maximum contact rating 3 A @ 20°C

TYPE 08 (CIRCLE 126)

1

131

Most unique low profile switch specifically designed for direct mounting on PC boards. Another unique feature of this switch – is its availability in 2 versions: as a kit – in separate components or as an assembled unit. Maximum positions @ 30° indexing angle – 12 (shorting and nonshorting) (including 12 position BCD code switch) Maximum poles per wafer – 4 (standard versions) Wafers made of polyetrafluoraethylen (PTFE/PE)/rotor of polyacetal (POM) Spring loaded ball/groove indexing mechanism with means for direct fastening to the PC board. Standard D. 12' sonce in hetween contracts Standard 0.1" spacing between contacts. In kit form, mechanism, wafers and shaft (in 4 standard lengths) are supplied separately with color coded (white and black) rotors for shorting/nonshorting recognition. m contact rating 5 A @ 20°C.

T ORDER FULFILLMENT!

DUCTION ORDERS SHIPPED FROM FACTORY TYPICALLY IN 4-5 WEEKS IN 1000 UNIT QUANTITIES

SHAFTS CUT TO ANY DESIRED LENGTHS AT NO EXTRA CHARGE-WITH CUSTOM ASSEMBLY ON PREMISES (WITHIN STANDARD VERSIONS) AND QUICK DELIVERIES FROM LARGE LOCAL STOCK. ALSO, UTMOST SPEED AND FLEXIBILITY FROM THE DESIGN TO THE DELIVERY OF CUSTOM MODELS.

TIONS

CONCENTRIC SHAFTS, WATERPROOF BUSHINGS, MOUNTING PLATES, SPECIAL WAFER SPACING, SHORTENED BUSHINGS, BUSHING SPACERS/EXTENDERS, PC INCLUDE: BOARD SOLDER TABS, DUMMY WAFERS, SUPPORT BRACKETS, SPECIAL TORQUES, SPECIAL INDEXING ANGLES, SPECIAL SHAFT DIAMETERS AND LENGTHS, ETC...

IF YOUR PRODUCT DEMANDS TOP QUALITY SWITCH, AT AN ADEQUATE PRICE, WITH A PROMPT DELIVERY-

YOU SHOULD DEMAND ELMASWITCH!

TO GET ELMA-JUST CALL, WRITE OR TELEX FOR IMMEDIATE ACTION! ... AND ACT WE WILL! ... WITH OUR 52 PAGE FULL COLOR SWITCH CATALOGUE—to get you complete specifications WITH OUR COLLECTION OF OUTSTANDING SWITCH SAMPLES—to convince you of the top quality WITH OUR SWITCH SPECIALIST- to help you design-it-in

AND OUR COMPETITIVE SWITCH QUOTE—to make you...MAKE THE SWITCH TO ELMA

Transtek Inc.

3100 Airway Dr. Suite 130 Costa Mesa, Calif. 92626 Tel: 714/556-6210

or Toll free 800/854-2003 Ext. 928

Tix: 681396 (worldmart csma)

(CIRCLE 127)

Three Interconnecting modules, no hard wiring and you get the Switching Power Supply of the 80's

Customer: What's the significance of the 3 modules?

ACDC Salesman: In the past, everybody including ACDC produced specific switchers for given applications. You know, assemble the components in a box, wire them and then tweak and test and trim, etc. In our RS/RT switchers, we produce large quantities of three basic modules, and then test the daylights out of them, followed by full load, high temp burn-in.

Customer: What modules are you talking about and how do they work?

ACDC Salesman: O.K., we produce input modules, converter modules and output modules. We have 16 different board modules that make up 50 different power supplies. We take various combinations out of stock and assemble them in a chassis, interconnecting them through a mother board. It's fast, reliable, and it eliminates hard wiring.

Customer: I see, you can make up most

any switcher I could want right out of stock. You say no hard wiring...what's wrong with wiring?

ACDC Salesman: Harnesses are a point of potential failure. There are possible cold solder joints vulnerable to everything including shipping vibration, not to mention noise considerations in how the harnesses are placed throughout. No one has ever successfully introduced a switching supply without hard wiring until our RS/RT Series.

Customer: When you say you test the daylights out of them, give me some details.


ACDC Salesman: O.K. First, all of our active devices are 100% screened. We stable bake, temperature cycle, and then 100% electrical test. All to MIL-STD-883B. The modules themselves are computer tested. When we assemble them into the final unit, we first Auto-Test, then burn-in for 48 hours at 50°C under full load, cycled, Auto-Test again with computer print out- serialized. You get one copy of the hard test data and we keep a copy. In other words we all know exactly what you're getting.

Customer: Everything sounds good, but what about the cost?

ACDC Salesman: Simple. We save you money because instead of building a hundred of these and fifty of those, etc., we continuously build thousands of the same modules each month. That saves us, and you, money. We test everything thoroughly and that eliminates warranty returns, reworks and all those costly problems. Believe me, if you've ever seen the production of power supplies, you'd know we have a uniquely superior product here...and, at a fantastically low price.

Customer: It sounds to me like you've brought power supply technology up to date.

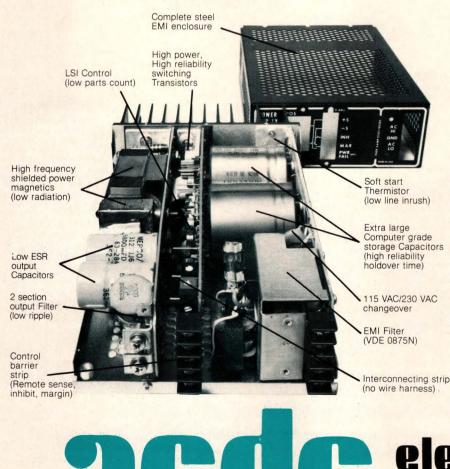ACDC Salesman: Thanks...we think our RS/RT Series are the switchers of the 80's.



RS Series/Single Output

SINGLE OUTPUT							
OUTPUT	OUTPUT CURRENT						
VOLTS	RS50	RS100	RS150	RS300	RSF375		
2	10.0	20.0	30.0	60.0	_		
5	10.0	20.0	30.0	60.0	75		
6	8.0	9.0	25.0	50.0			
12	4.5	9.0	13.5	27.0	31		
15	3.6	7.2	10.8	21.0	25		
18	3.0	6.0	9.0	18.0			
24	2.5	4.5	7.0	13.0	15		
28	2.0	4.0	6.0	11.5	-		

RT Series/Triple Output

N	IULTIPL	E OUTPL	JT	- The second
	Sec.	QUAD		
	RT100	RT150	RT300	RQ300
MAIN OUTPUT	5V 20A	5V 30A	5V 60A	5V 30A
AUXILIARY OUTPUTS	Contraction of the	12V 5A 15V 4A 5V 5A	Prove Statistics	15V 4A 5V 5A
MAX. POWER	100W	150W	300W	300W

These Power Supplies are shipped with the industries most complete instruction manual.



401 Jones Road, Oceanside, California 92054 Telephone 714/757-1880 211 West Clay Avenue, Roselle Park, New Jersey 07204 Telephone 201/241-6077

etron

Low-cost instrument measures 4-decade power

Using standard parts, a watt/watt-hour meter calculates power consumption for line-powered devices over an extremely wide measurement range—2W to 2 kW FS. And its multiple analog and digital outputs allow both direct and time-related power readings.


Jim Williams, National Semiconductor Corp

If you must monitor the usage of costly electricity in commercial, industrial or consumer equipment designs, build the inexpensive but versatile watt/watt-hour meter described in this article. It resolves power measurements to as low as 0.1W, achieving 2% accuracy over $25\pm5^{\circ}$ C. And it can determine the power consumption of any 115V ac unit, from large factory machines to small hand-held tools. The instrument requires only about \$175 worth of off-the-shelf parts, whereas many conventional power meters cost much more and provide lower performance.

To handle a wide variety of power measurements, mostly in cases where energy conservation has high priority, the instrument provides three analog and two digital power-related outputs. One analog output serving a 200-µA FS meter—displays power values in watts. Another furnishes 0 to 5V for driving strip-chart recorders, while the third supplies instantaneouspower-output levels for use in external-tracking applications. One of the digital outputs—a readout indicates time-based or watt-hour readings; the second supplies watt-hour data for use by external equipment.

A look at the overall approach

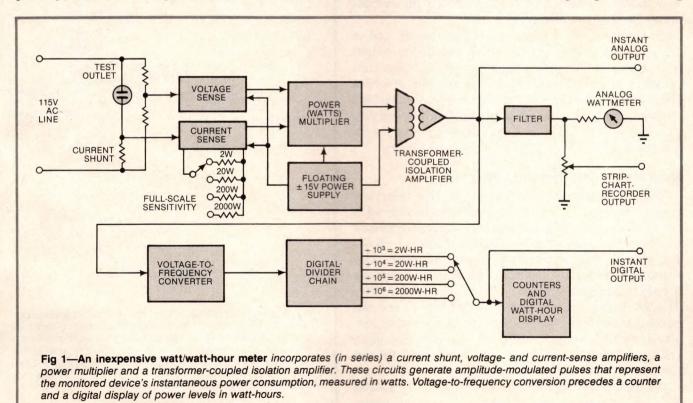The watt/watt-hour meter's design is straightforward (Fig 1). The device under measurement plugs into a standard 115V ac outlet mounted on the instrument's front panel. With line power applied, the ac voltage across the monitored load passes through a resistor divider and feeds (via an op amp) to an analog



Single low-resistance shunt handles all four power ranges

power multiplier.

The voltage across a low-resistance shunt represents the current through the load. Even when measuring a 20A max flow, this shunt needs only 133 mV—a feature that eliminates high-resistance-current-shunt inaccuracies. Additionally, by accommodating all four power ranges—2, 20, 200 and 2000W FS—the single shunt eliminates the need to switch-in high-impedance shunts for high-sensitivity scales.

The instrument's measurement technique utilizes the low input error in a current-sense amplifier, whose output also goes to a power multiplier. Switchable gain within the amplifier makes possible the 4-decade sensitivity setting. A 4-quadrant configuration, the power multiplier produces an output representing the test load's true instantaneous-power product $(E \times I)$, regardless of the load's relative voltage and current phases.

Because the multiplier and its associated voltage- and current-sense amplifiers connect directly to the ac line, though, they require a floating $\pm 15V$ power supply. Consequently, you can't safely monitor their outputs with grounded test equipment, such as strip-chart recorders. To deal with this problem, the multiplier's output drives an isolation amplifier that operates at unity gain but has no galvanic connection between its input and output terminals. The amplifier employs pulse-amplitude-modulation techniques in conjunction with a small transformer. By grounding its output, you can safely connect test equipment to all circuits following the transformer.

In addition to driving an analog meter and a strip-chart recorder, the isolation amplifier's output also biases a voltage-to-frequency (V/F) converter, which in turn combines with digital counters to form a digital integrator. This circuit translates the amplifier's analog outputs into time-related power levels. Varying the counters' divide ratio (and thus the power levels) produces the instrument's four watt-hour ranges.

Multiplier portrays instant power

The hardware implementation of this overview appears in **Fig 2.** At the ac-line input, voltage division occurs in the 100- and 4.4-k Ω resistor string. Connected to this string, A_{2A} serves as a buffer amplifier and feeds the voltage-sense input to the power multiplier. Also working off the line input, A_1 monitors the voltage across the current shunt at a fixed gain of 100. Two 1N1195 diodes and two 20A fuses protect A_1 and the current shunt from shorts across the load's test socket. Receiving A_1 's output, amplifier A_{2B} provides gain, calibrated wattage switching from 2 to 2000W FS and the power multiplier's current-sense input.


Composed of amplifiers A_{3C} and A_{3D} and an LM394 IC's dual transistors, the multiplier—a variable trans-


conductance type—uses its current-sense input to vary a 2N2222 transistor amplifier's gain. This amplifier receives A_{2A} 's voltage-sense output as its input.


At the multiplier's output, A_{3C} produces an output representing the load's instantaneous power consumption (Fig 3, trace A). This output in turn biases a pulse-amplitude-modulating isolation amplifier (A_{3A} and A_{3B}) and three transistors (Q_1 to Q_3).

Generating an oscillator output (trace B), A_{3A} biases the Q_1/Q_2 switch connected across the transformer's primary. Meanwhile, A_{3B} 's negative input measures the pulses' amplitude at the transformer's primary. A_{3B} then servo-controls the pulses to the same amplitude as those received at its positive input (biased by the multiplier's output). Transistor Q_3 provides currentdrive capability and completes A_{3B} 's feedback path.

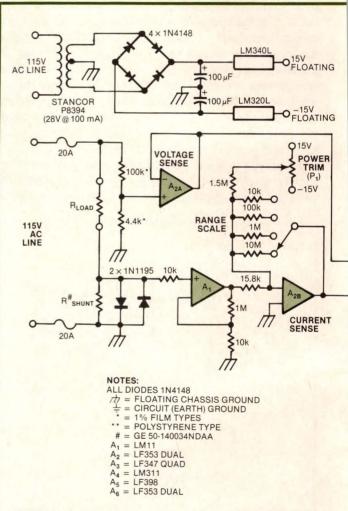Trace C in **Fig 3** illustrates how Q_3 's emitter voltage changes to meet the servo-loop requirements. Trace D shows the pulses applied to the transformer. Note that these pulses' amplitudes form an envelope whose amplitude equals the multiplier's output.




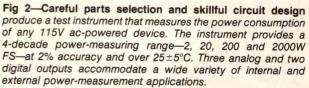

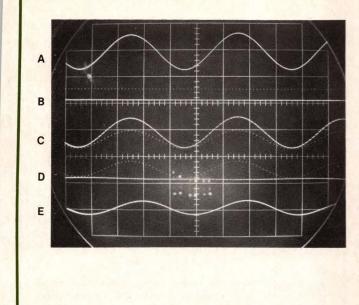

TRACE	VERTICAL	HORIZONTAL
Α	5V/DIV	1. A Contraction of
В	50V/DIV	
С	5V/DIV	2 mSEC/DIV
D	10V/DIV	
E	10V/DIV	

Fig 3—During instrument operation, the power multiplier's output (trace A) represents the monitored device's instantaneous power consumption. Biased by this output, A_{3A} 's oscillator output (refer to **Fig 2**) biases the Q_1/Q_2 switch (trace B). Completing the feedback path to A_{3B} , Q_3 changes its emitter voltage to maintain servo-loop needs. Via Q_1 , Q_2 , Q_3 , A_{3A} and A_{3B} , amplitude-modulated pulses arrive at the isolation transformer's primary (trace D). Connected to this transformer's secondary, A_5 's output represents a sampled version of the monitored device's power consumption (E).

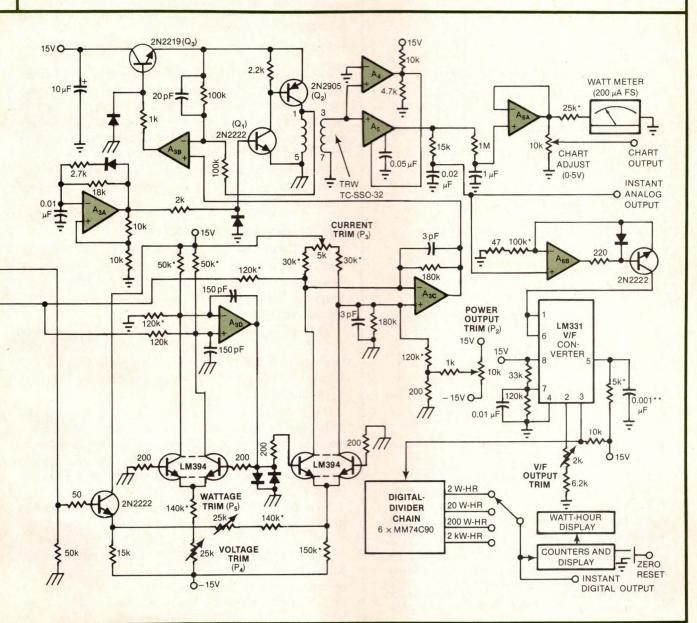

Pulse sampling and filtering smooth out power-signal levels

The amplitude-modulated pulses appear at the transformer's secondary, which is referenced to the instrument's earth ground. Each pulse's amplitude gets measured by a sample/hold amplifier (A_5) whenever A_4 generates a Sample command. Lightly filtered by the 15-k Ω , 0.02- μ F network, A_5 's output provides a sampled version of the load's instantaneous power consumption (trace E). Heavy filtering by the 1-M Ω , 1- μ F network's time constant produces a smoother version of the sampled power signal. This signal drives the watts analog-meter and strip-chart-recorder outputs via the A_{6A} buffer.


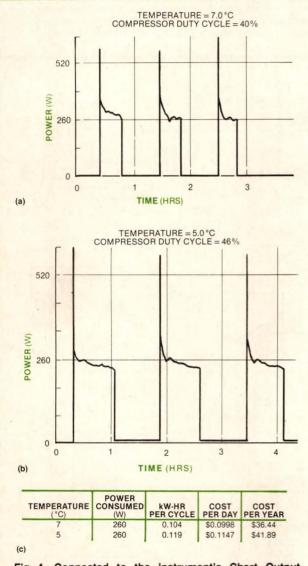


Fig 4—Connected to the instrument's Chart Output terminal, a strip-chart recorder logs a refrigerator compressor's power consumption at 260W for several hours. At a 7°C temperature setpoint, the compressor functions at a 40% duty cycle (a); lowering the temperature to 5°C increases this duty cycle to 46% (b). Extrapolated data (c) shows that the lower temperature results in increased kilowatt-hour consumption per cycle and therefore in higher operating cost.

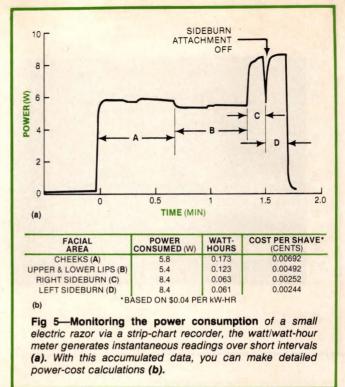

In conjunction with a digital-divider chain, an LM331 V/F converter forms a digital time integrator. To bias the V/F converter, A_5 's lightly filtered output goes to A_{6B} . Driven by the V/F converter's output, the divider chain sets the integrator's time constant and switches the scale factor for watt-hour measurements. Additional counters drive a digital readout that shows the actual measurements. Pressing the Zero Reset pushbutton resets the watt-hour readout.

Use this procedure for calibration


To calibrate the watt/watt-hour meter, shut off the instrument's ac line power and remove the two 20A fuses. Set the Range Scale switch to 2. Then apply power and adjust the Power Trim pot (P_1) so 0.00V appears at A_{2B} 's output.

Turn off the ac line power. Then disconnect the power multiplier's two input lines and connect them to the instrument's floating ground. Turn on line power and adjust the Power Output Trim pot (P₂) for 0.00V at A_{6A} 's output.

Once more, turn off ac line power. Unground the multiplier's current-sense input but leave the voltagesense input grounded. Then turn on line power and apply a 10V p-p 60-Hz signal to the multiplier's current-sense input lead. Adjust the Current Trim pot (P_3) for 0.00V at A_{6A} 's output.

Now turn off ac line power yet again, ground the multiplier's current-sense input and unground the voltage-sense input. Turn on the power and adjust P_4 (the Voltage Trim pot) for 0.00V at A_{6A} 's output. Then turn off the power and reconnect the multiplier's current-sense input into the circuit.

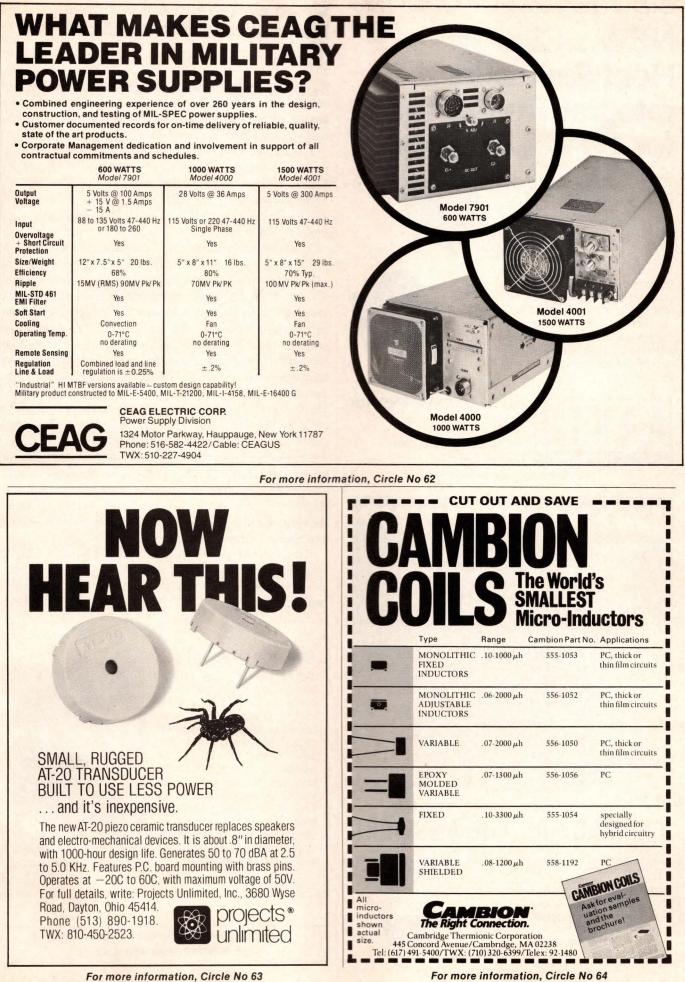
Next, turn on the line power and read ac line voltage with a precision digital voltmeter. Plug a known load



EDN FEBRUARY 4, 1981


CUT THE COST OF COOLING NEW...Clip-On **Heat Sink with Integral Tinned Tabs** for TO-220 Devices

Save time, save money, save on accessory hardware with Aavid's new, patented, Clip-On heat sink designed specifically for TO-220 packages. May be mounted vertically or horizontally. Supplied complete with integral tinned tabs for direct soldering to your PC board, Our Series 5743 provides excellent retention and maximum heat dissipation. No need for special or separate mounting hardware. Samples for engineering evaluation and complete catalog available by writing to:

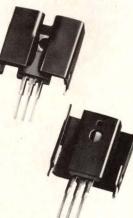



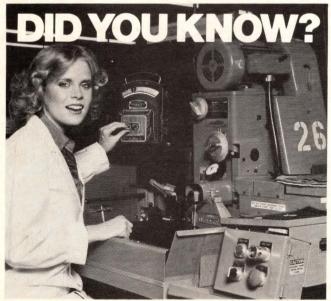AAVID ENGINEERING, INC. 30 Cook Court, Laconia, New Hampshire 03246 Tel. 603/524-4443 For more information, Circle No 65



When you need special magnet fabrication, PERMAG HAS THE ANSW

PERMAG grinds, cuts and fabricates all of its products to your needs. PERMAG's special equipment can make countless kinds of modifications on all kinds of magnetic materials, precisely and promptly. Close tolerances are our specialty. Our 9 modern plants are stocked, staffed and equipped to meet your every requirement.

"In the magnetic field, PERMAG is No. 1" ALL ACROSS THE COUNTRY NEW YORK . BOSTON . ATLANTA . TOLEDO CHICAGO • DALLAS • LOS ANGELES • SAN FRANCISCO MINNEAPOLIS/ST. PAUL

Consult Yellow Pages for address & phone number of PERMAG near you

For more information, Circle No 66

PERM

V/F converter and divider chain form a digital integrator circuit

(eg. a 1% power resistor) into the instrument's test outlet. Adjust the Wattage Trim pot (P5) until the analog meter reads the correct wattage (watts equals line voltage times load resistance).

Finally, turn off line power and disconnect A_{6B}'s positive input line. Then turn on the power and apply 5.00V to A_{6B}'s positive line. Adjust the V/F Output Trim pot (P₆) until the LM331's output at pin 3 runs at 27.77 kHz. Then turn off line power and reconnect A_{6B}'s positive input line.

A watt/watt-hour meter calibrated in this manner can accurately measure the power consumption of any 115V ac-powered device, large or small. Connecting the instrument to a home refrigerator demonstrates its prowess with large equipment: In one test, the refrigerator operated for 31/2 hrs at a temperature setpoint of 7°C (Fig 4), and each time its compressor turned on, it consumed approximately 260W. As the compressor warmed up, power consumption actually decreased slightly. Changing the refrigerator's temperature control to 5°C increased the compressor's duty cycle by 15%. This power change reflects directly in the unit's per-cycle kilowatt-hour consumption.

Connecting the watt/watt-hour meter to an electric razor demonstrates its ability to monitor small equipment. In this setup, the meter recorded the electric razor's power consumption during a faceshaving exercise (Fig 5). Note that various facial areas cost more to shave than others.

Time-related power computations revealed that a complete daily shave costs about \$0.09 per year. If this is excessive, a user could economize by growing a beard. EDN

Author's biography

Jim Williams is a design engineer with National Semiconductor Corp's Linear Applications Group, Santa Clara, CA, specializing in analogcircuit and instrumentation development. Previously, he worked as an analog-systems and -circuit consultant at Arthur D Little Inc and directed the Instrumentation Development Lab at the Massachu-



setts Institute of Technology. Jim studied psychology at Wayne State University and in his spare time enjoys skiing, art and collecting antique scientific instruments.

> Article Interest Quotient (Circle One) High 479 Medium 480 Low 481

EXEMPLARY PERFORMANCE

NO ONE DELIVERS CUSTOM POWER SUPPLIES WHICH PERFORM BETTER THAN CIRKITBLOCK[®] MODULES.

LOAD

EFFICIENC

10

EFFICIENCY


For over 10 years, custom power supplies from Powercube® have met or exceeded the severe performance requirements of major military and space programs.

PERFORMANCE: RS SERIES SPECIFICATIONS: RS SERIES

Today, custom power supplies configured from proven Cirkitblock[®] modules continue to provide the high performance and long term reliability needed in critical applications.

Their small size, light weight, and rugged construction permit designers to fit or retrofit Powercube power supplies into tight configurations or harsh environments. And because Cirkitblock modules have been qualified on major military programs and are easily assembled into custom configurations, a prototype can very quickly be upgraded to an operating hi-rel unit. In addition to being the performance leader in MIL-qualified custom power supplies, Powercube can also supply single or multifunction modules for inclusion in your own power supply design.

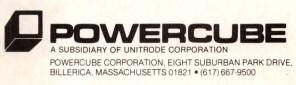If you have a requirement for a MIL-qualified power supply (or any other tough power supply problem) which needs to be filled fast, call Powercube at (617) 667-9500.



For more information, Circle No 67



DON'T LET DRIVING YOUR MEMORY DRIVE YOU CRAZY.

You're trying to drive a large, highperformance memory array using 16K or 64K RAMs. And it's driving you nuts.

What with the undershoot, the skew problems, the large number of packages, the boss expecting a faster system than last year's – what's a designer to do?

Introducing the Am2964B: The Simple Solution.

Now Advanced Micro Devices has a bipolar dynamic memory controller for use with 16K and 64K RAMs. It's easy to use. It's flexible. And it takes care of all your RAS, CAS and address problems on one chip.

The Am2964B replaces about a dozen high-speed, high-power Schottky parts. And it not only does the job faster, it uses less power.

But what about the interface to the RAM? We thought you'd never ask.

Meet our Am2965/66 RAM drivers.

The faster you drive your memory, the faster your system. And that's where our new Am2965/66 come in. Together with our Am2964B, they achieve maximum performance and completely eliminate undershoot. The speed is specified up to 500 pf. Min's and max's, too.

And if you need to upgrade your system, no problem. Our new RAM drivers have the same pin-outs as the S240 and 244, so it's easy to convert your existing system.

The Am2964B and Am2965/66 are the newest members of AMD's dynamic memory support family — the family that makes implementing dynamic RAM systems easier, cheaper, simpler, faster. Like all our parts, they're MIL-STD-883 for free, the highest quality parts you can buy.

Don't let driving your memory drive you up a wall. Send for all the facts on AMD's Dynamic Memory Support Family.

Bipolar LSI: The Simple Solution.

ADDRESS



901 Thompson Place, Sunnyvale, CA 94086 · (408) 732-2400 Right, from the start. For more information, Circle No 68

If There's a Fan Specify	and the second se	DON'T MISS OUT!!
IMCcol® 12 Why use a cluster of three or more fans to flush out heat when it can be done with a single unit more economi- cally and efficiently? IMC's 60 HZ, 12-inch Tubeaxial Fan made to your exact specifi- cations can be your answer. Literature on request! For further information please call E.V. Lauria, Sales Manager at 516/334-7070 or write:		If you're reading a borrower copy of EDN, don't gamble on missing the next issue EDN publishes valuable, up to-date information at the forefront of electronics tech nology; the person whe loaned this issue to you might not want to part with his copy next time. To re- ceive your own subscription to EDN, take a few moment to fill out the reader qualifi- cation card at the front of the magazine; if the card if missing, request one from
		EDN Subscription Office, 27 Saint Paul St, Denver, CC 80206. Phone (303) 388-4511
	URY, NEW YORK 11590	EVerything Designers Need
570 MAIN STREET, WESTBU For more information For more information For more information If Sierracin's new 1981 short form can then someone else has itbut you can This catalog features the widest line linear power supplies in the industry. buyer should be without it. FEATURING 7 new Switching Power Supplies 40 to 500 watt Switching Line 10 Industry standard OEM Linears 11 Floppy Disc Supplies 11 f you want your own copy fast them below. If you can wait 10 days then cu line, fill in the information requested a	ALIANCE AND	Everything Designers Need
570 MAIN STREET, WESTBU For more information For more informatio	Ation, Circle No 69 Ation, Circle No 69	Ites
570 MAIN STREET, WESTBU For more information For more information For more information If Sierracin's new 1981 short form can then someone else has itbut you can This catalog features the widest line inear power supplies in the industry. buyer should be without it. FEATURING 1 A0 to 500 watt Switching Line 2 A0 to 500 watt Switching Line 3 Floppy Disc Supplies 4 you want your own copy fast them below. If you can wait 10 days then cu line, fill in the information requested an have more time than that, then circle to NAME COMPANY NAME & DIV.	Ation, Circle No 69	<section-header></section-header>
570 MAIN STREET, WESTBURGER For more information For more information And a	Ation, Circle No 69	<section-header></section-header>

Analyze size, maintenance factors to ensure memory reliability

By analyzing the effects of RAM size and error-maintenance techniques, you can determine how to design-in the memory-system reliability you require.

Steven Grossman and Fred Jones, Mostek Corp

Utilizing the computerized reliability model described in Part 1 (EDN, January 21, pg 131), this 2-part series concludes by examining graphical presentations of memory-system reliability and the effects of various maintenance schedules. Although the system-reliability model described in these articles doesn't establish a minimum acceptable reliability level for you, it can help determine the tradeoffs involved in designing for the level you choose.

Over extended time periods, for example, the model can determine how you can change major performance parameters and maintenance techniques to keep a single-error-correcting system's failure (double-bit-hit) probability lower than a target value. When using this procedure, you vary one system characteristic while holding all others constant. Then, at specific time intervals, the computerized model calculates the system failure probability to determine the characteristic's influence on system reliability.

Data accumulated from implementing this scheme shows that performance parameters and maintenance techniques generally affect memory-system reliability in several ways:


- Increasing memory size by increasing the total number of storage devices degrades reliability.
- Although larger word sizes require proportionately fewer error check bits, elongating word length decreases reliability.
- Higher density storage devices can have higher per-device soft- and hard-error rates without degrading reliability, so long as per-bit error rates don't increase.
- Without hard- or soft-error maintenance, an increase in the device error rate results in downgraded reliability.
- An increase in the average percentage of device lost from a hard error decreases reliability.
- By choosing the appropriate maintenance intervals, you can compensate for the effects of degraded reliability.


To place this information in perspective, the graphical plots presented here summarize memory-system reliability factors clearly and simply. Each plot's vertical axis indicates double-bit-hit probability—the reliability measure assumed in Part 1. The horizontal axis tracks system operation time in days.

Larger systems lead to lower reliability

The first system-parameter analysis focuses on how memory size affects reliability. In **Fig 1**, the 256k-word curve represents the reference memory system introduced in Part 1. Observe that the two larger memory systems included in the graph yield a greater number of double-bit hits than does the smallest system. In fact, without error maintenance, the 64k-word system takes 16 times longer to accumulate as many hits as the 1024k-word system. And the double-bit-hit probability of the 64k-word system always stays much lower than those for the two larger systems.

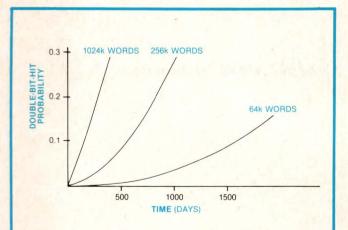The next parameter analysis considers word-size effects on memory-system reliability. Fig 2 shows plots for three systems that each contain 512k usable storage



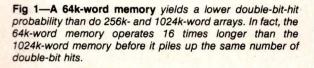

Large memory and word sizes downgrade system reliability

bytes. The $64k \times 72$ -bit system comprises a 64-bit data word plus eight check bits to accomplish single-error correction and double-error detection. Similarly, the $128k \times 39$ -bit system contains a 32-bit data word with seven check bits, and the $256k \times 22$ -bit reference memory system includes 16 data bits and six check bits.

As the curves for the systems illustrate, even if you decrease system size to compensate for a word-length increase, that increase boosts the double-bit-hit probability and decreases system reliability.

On the other hand, if you scale down the number of system words in proportion to the change in total word length—rather than in proportion to the number of information bits—total memory size will be larger than 64k and 128k. Because large memory systems perform less reliably than small ones (all other parameters being equal), the 72- and 39-bit reliability curves would shift farther to the left than shown in **Fig 2**.

Fewer errors come from denser devices

Next, consider component-density effects on memory-system reliability (Fig 3). The 16k-RAM curve models the reference memory system, which contains $16k \times 1$ -bit dynamic RAMs.

Because the soft- and hard-error rates per device in Fig 3 are held constant relative to all the component densities, the systems with denser components yield proportionally fewer errors. Consequently, systems using denser devices achieve higher reliability levels than do systems with a larger number of less dense devices—so long as all the devices are subject to the same total error rate.

Thus, when you upgrade a system with denser devices, it can tolerate higher per-device soft- and hard-error rates. In fact, the per-bit error rates

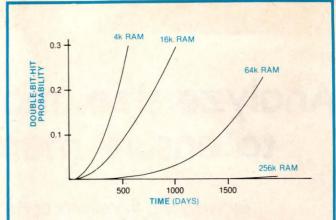


Fig 3—When subjected to the same per-device hard- and soft-error rates, memory systems containing dense memory devices (eg, 64k and 256k RAMs) experience fewer total errors than do those with less dense devices (eg, 4k and 16k RAMs). Thus, use of denser devices with equal per-device error rates results in memory systems having higher reliabilities.


become more significant than the per-device rates in determining system reliability. For example, when you substitute $64k \times 1$ -bit devices for $16k \times 1$ -bit parts, the denser system can tolerate four times as many soft errors and failed bits per device per unit time than the less dense system, without affecting system reliability.

Soft errors add up to trouble

Needless to say, not all memory devices are subject to the same soft- and hard-error rates. You could reasonably expect 64k dynamic RAMs, for example, to be more susceptible to alpha radiation, and hence exhibit more soft errors, than 16k RAMs.

In this regard, Fig 4 shows soft-error-rate effects on system reliability. The 0.1%/1k-hrs curve models the reference memory system. The other four curves illustrate other system soft-error rates ranging from 0 to 1% per 1000 hrs.

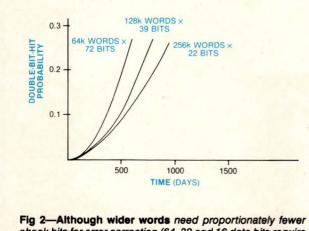Not surprisingly, the systems with higher soft-error



check bits for error correction (64, 32 and 16 data bits require eight, seven and six bits for single-error correction with double-error detection, respectively), systems employing them run the risk of higher double-bit-hit probabilities.

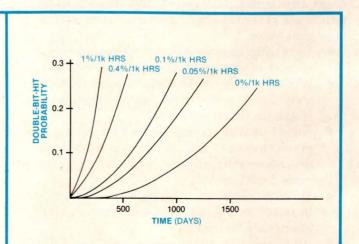


Fig 4—High soft-error rates (eg, 1% per 1000 hrs) have a relatively strong effect on memory-system reliability. Of particular interest, the 0%/1k-hr curve represents a memory system that experiences only hard errors.

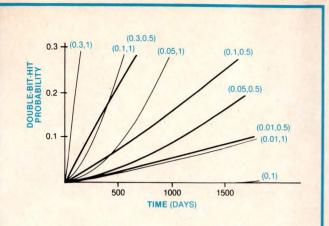


Fig 5—Curves show the effects of varying hard-failure rates on memory-system reliability. The two terms in parentheses for each curve represent the Weibull distribution's 100/ α and β characteristics. As the 100/ α (first) term increases, the overall hard failure rate also increases and in turn decreases system reliability. The β (second) term affects the curve's shape.

rates are less reliable than otherwise identical systems with lower rates. For comparison, the 0%/1k-hrs curve represents a system with no soft errors; its double-bithit probability results entirely from hard errors.

To analyze another key parameter, Fig 5 exhibits a host of curves that monitor the effects of hard-error rates on memory system reliability. A set of two Weibull-distribution terms in parentheses accompanies each curve. The first term—which corresponds to the Weibull distribution's 100/ α characteristic—is the A value given in Part 1's computer program. When the hard-error rate is constant, this term expresses the hard-error rate in percent per 1000 hrs.

The set's second term stands for the Weibull distribution's β (or B in the computer program) characteristic. When β equals 1, for example, the hard-error rate stays constant over time. When β equals 0.5—a common value for memory devices—the distribution reflects an infant-mortality mechanism.

All the Fig 5 curves show the effects of varying both α and β . The bold-line curves represent the β -equals-0.5 cases, whereas the fine-line curves indicate the β -equals-1 cases. The reference (0.05, 1) curve represents a constant 0.05%-per-1000-hr hard-error rate.

Note from these curves that increasing the Weibull set's first term increases the overall system hard-error rate and shifts the curves to the left. Note, too, that varying the second term (β) changes the curves' shapes. Specifically, the β -equals-0.5 curves tend to be flatter than the β -equals-1 curves because their hard-error rates decrease with time. In fact, for a constant α , the β curves cross eventually, just as do the instantaneous hard-error-rate curves.

The (0,1) curve represents a system with no hard errors; its double-bit-hit probability originates from soft errors alone. This probability remains near zero because of the relatively small number of total bits lost due to soft errors. In contrast, the relatively large number of bits lost per hard error would cause the 0%/1k-hrs curve in Fig 4 to yield a somewhat higher double-bit-hit probability, where only hard errors exist.


Reliability goes down as device loss goes up


Another parameter analysis covers the effects of different percentages of device lost due to a hard error (Fig 6). The 10% curve stands for the reference memory system. Obviously, with an increase in loss percentage, the total number of bits affected by hard errors increases and system reliability decreases.

To simplify the foregoing parameter analyses, the system-reliability calculations assume that a memory system has received no periodic maintenance. Fig 7, however, illustrates the effects of adding hard-error maintenance and soft-error scrubs to the reference memory system. The smooth reference-system curve shows system reliability without soft-error scrubs or hard-error maintenance. The other three jagged curves illustrate the effects of adding periodic hard- and soft-error maintenance individually and in combination.

Consider first the effects of adding soft-error scrubs only. Write cycles and read/modify/write cycles associated with normal memory activities accomplish some nonperiodic soft-error maintenance in many systems. In fact, a virtual memory system that allows paging can be modeled as having an inherent soft-error scrub, whose rate depends on the interval in which all pages are swapped. For simplicity here, however, soft-error maintenance refers to scheduled periodic soft scrubs only.

The 90-day-soft-scrub-only curve in Fig 7 outlines the effects of performing a soft-error scrub on the reference memory system. The curve's jagged nature results from the decrease in double-bit-hit probability every 90 days when the scrub occurs. Note that after each scrub, the lower points on this curve track the corresponding points on the 0%/1k-hrs curve in Fig 4, which models a memory system with no soft errors. The slight difference between the two curves results

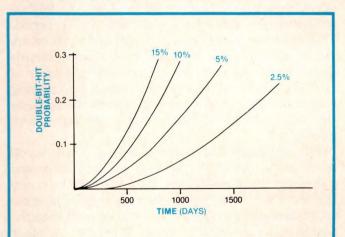

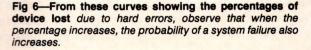

Dense storage devices yield fewer total errors

from the small probability of one or more soft errors occurring within the 90-day period between scrubs. Because the mean time between soft errors in the reference memory system equals 118 days (as calculated in Part 1), using shorter scrub intervals achieves only modest reliability gains—a few percentage points at best.

Hard-error maintenance helps even more

The foregoing analysis examines soft-error-scrub effects without hard-error maintenance. But because you must perform a rewrite after replacing failed devices, soft-error scrubs usually occur whenever hard-error maintenance is performed.

On the other hand, a memory-deallocation maintenance technique eliminates all hard errors but relatively few soft errors. Although this article doesn't present separate data for a memory-deallocation maintenance example, those results closely resemble that of a system with simple hard-error maintenance. Any differences could be traced to total available memorysize changes resulting from the use of the memorydeallocation technique.

The 90-day-maintenance-only curve shown in **Fig 7** presents the effects of performing hard-error maintenance every 90 days. The curve is jagged like the soft-scrub-only curve because the double-bit-hit probability decreases after you remove hard failures from the system. The sawtooth shape becomes even more pronounced with hard-error maintenance because you repair more bits when eliminating hard failures than you do correcting single-bit soft errors. After each maintenance, the lower points on this curve track **Fig** 5's (0, 1) curve, which models a system with no hard errors.

Note in Fig 7 that the 90-day-maintenance-only curve rises proportionately higher than the 90-daysoft-scrub-only curve after each maintenance period. This difference arises because a hard error that occurs within the 90 days between maintenance periods generally affects a proportionately larger number of bits than does a soft error. Carefully choosing hard-error-maintenance periods appears to be more significant, therefore, than choosing soft-error-scrub intervals.

The 90-day-maintenance-plus-90-day-soft-scrub curve shows the effects of applying both hard- and soft-error maintenance to the reference memory system. Even when you perform both types of error maintenance only every 90 days, you can still keep the double-bit-hit probability below 1 or 2%. In other words, you can preserve the high reliability of memory arrays that employ error correction by choosing appropriate soft- and hard-error maintenance intervals.

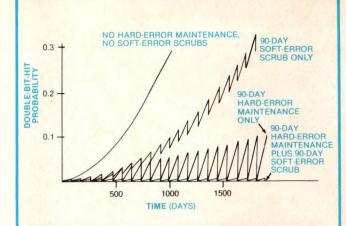


Fig 7—Adding error-maintenance capabilities and employing them on a periodic basis changes the reference memory system's double-bit-hit probability from a smooth curve to a set of lower value sawtooth-shaped ones exhibiting improved reliability.



Short maintenance intervals aid large systems


How do you determine the appropriate maintenance parameters for a memory system? Running Part 1's computer program with a variety of parameters to explore their reliability effects provides a good start.

With regard to shortening the hard- or soft-error maintenance intervals, however, the best reliability improvement you can obtain corresponds to approximately a memory system's lowest double-bit-hit curve with no hard or soft errors, respectively. You can smooth the curves' jagged nature with short and ultimately continuous maintenance intervals, though. Fig 8 illustrates these effects in a general sense.

For a given memory system, though, a surprisingly long soft-error-scrub or hard-error-maintenance interval might achieve an acceptable system-reliability level. And note that additional or shorter-interval maintenance proves most valuable in large memory systems—those composed of storage devices with high error rates—and in systems requiring a high reliability level.

> Article Interest Quotient (Circle One) High 473 Medium 474 Low 475

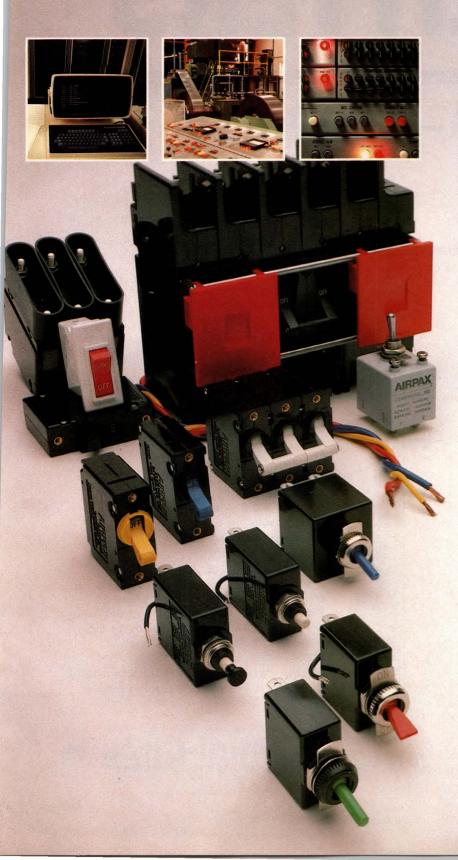The challenge...positive, reliable circuit switching and protection




AIRPAX engineers have designed a complete line of circuit breakers with full awareness of your needs and requirements. Reliability of circuit protection is mandatory. High temperatures and other harsh environmental factors are carefully considered.

AIRPAX Circuit Breakers are made strong enough to withstand stresses of system assembly, connection and operation. They are qualified and recognized under applicable military, (IL, CSA and SEV specifications. "Hotline" delivery (2 weeks or less) is assured for prototype requirements. Find out how we can help you meet the challenge of positive, reliable circuit switching and protection.


Specifications are available in our new short form catalog. Write or call AIRPAX/North American Philips Controls Corp., Cambridge Division, Woods Road, Cambridge, MD 21613, telephone (301) 228-4600.



90° POWER SPLITTERS

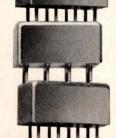

1.4-450 MHz

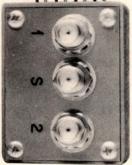




Model No.	Freq. Range MHz	ange tion dB		Inser- tion Loss dB*		Phase Unbalance Degrees	Amplitude Unbalance dB	Price	
		Тур.	Min.	Тур.	Max.	Max.	Max.	Each	Qty.
PSCQ-2-1.5	1.4-1.7	29	25	0.4	0.7	3.0	1.2	12.95	(5-49
PSCQ-2-3.4	3.0-3.8	30	25	0.4	0.7	3.0	1.2	16.95	(5-49)
PSCQ-2-6.4	5.8-7.0	30	25	0.4	0.7	3.0	1.2	12.95	(5-49)
PSCQ-2-7.5	7.0-8.0	35	25	0.4	0.7	3.0	1.2	12.95	(5-49
PSCQ-2-10.5	9.0-11.0	25	20	0.4	0.7	3.0	1.2	12.95	(5-49
PSCQ-2-13	12-14	29	25	0.4	0.7	3.0	1.2	12.95	(5-49
PSCQ-2-14	12-16	30	25	0.3	0.6	3.0	1.8	16.95	(5-49
PSCQ-2-21.4	20-23	30	25	0.4	0.7	3.0	1.2	12.95	(5-49)
PSCQ-2-50	25-50	30	20	0.3	0.7	3.0	1.5	19.95	(5-49
PSCQ-2-70	40-70	25	20	0.3	0.7	3.0	1.2	19.95	(5-49
PSCQ-2-90	55-90	30	20	0.3	0.7	3.0	1.2	19.95	(5-49
PSCQ-2-120	80-120	25	18	0.3	0.7	3.0	1.5	19.95	(5-49
PSCQ-2-180	120-180	23	15	0.3	0.7	4.0	1.2	19.95	(5-49
PSCQ-2-250	150-250	23	18	0.4	0.8	4.0	1.5	19.95	(5-49
PSCQ-2-400	250-400	22	16	0.4	0.9	4.0	1.5	19.95	(5-49
PSCQ-2-450	350-450	22	16	0.4	0.9	4.0	1.5	19.95	(5-49
ZSCQ-2-50	25-50	30	20	0.3	0.7	3.0	1.5	39.95	(4-24
ZSCQ-2-90	55-90	30	20	0.3	0.7	3.0	1.2	39.95	(4-24
ZSCQ-2-180	120-180	23	15	0.3	0.7	4.0	1.2	39.95	(4-24
ZMSCQ-2-50	25-50	30	20	0.3	0.7	3.0	1.5	49.95	(4-24
ZMSCQ-2-90	55-90	30	20	0.3	0.7	3.0	1.2	49.95	(4-24
ZMSCQ-2-180	120-180	23	15	0.3	0.7	4.0	1.2	49.95	(4-24

*Average of coupled outputs less 3 dB Impedance 50 ohms all models

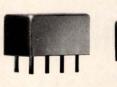2625 East 14th St. Brooklyn, NY 11235 (212) 769-0200 Domestic and International Telex 125460 International Telex 620156





FROM \$ 40.95 5-49 atv

- Over 20 models available
- Compact PC. . . 0.4" × 0.8" × 0.4" H
- High isolation...
 better than 0.3 dB
- Low insertion loss. . . less than 0.3 dB

2-way, 90°, pin or connector models... Mini-Circuits offers a wide variety of Power Spitters/Combiners to chose fromwith immediate delivery. But there are always "special" needs for "special applications"... We can supply them at your request...with rapid turnaround time... and at standard catalog prices!



49 Rev Orig.

EDN FEBRUARY 4, 1981

Design Ideas

Parallel-to-serial scheme increases ROM speed

Marian Stofka

Bratislava, Czechoslovakia

When your design's speed performance is bound by ROM access time, consider the concept depicted in Fig 1. If the design employs successive ROM addressing—as is the case in waveform-generation equipment—a parallel-to-serial ROM organization can improve speed by at least a factor of two.

Fig 1's block diagram illustrates the paralleladdressing scheme employed in this concept. In addition to being addressed in parallel, the ROMs' outputs are also sampled in parallel by fast, edge-triggered memory registers just before new data is required. These registers have 3-state or open-collector outputs to simplify the parallel-toserial conversion. (The appropriate outputs are wire-ORed to create the output lines.)

K words stored in the registers thus emerge at a rate K times that of the address generator. You provide the register's output-enable control (OC) by decoding the divide-by-mod-K counter's output; the

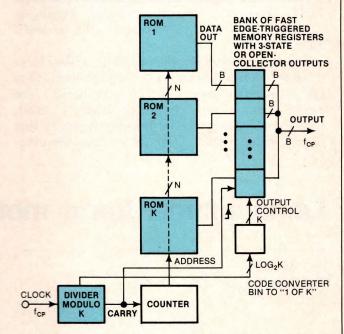


Fig 1—Parallel-addressing K ROMs increases their apparent speed by a factor of K. The 3-state output registers are output enabled by decoding the divide-by-K counter's output.

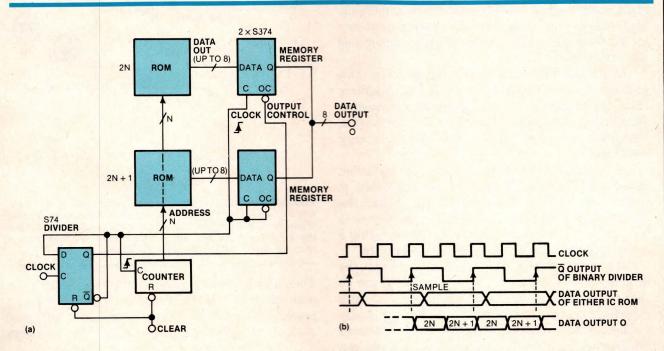


Fig 2—A hardware realization of a ROM-speed-up concept (a) can at least double your data's throughput rate. With this technique, you can reduce the ROM system's effective address time (and therefore data-output time) by a factor of K. In the example shown, the divide-by-2 approach results in the alternating ROM outputs defined in (b).

Design Ideas

ROM's address generator/counter comes from the divider's Carry output.

The ROM system's data is organized so that at any address location, each ROM contains one word of a group of K succeeding words. As a result, the array has an effective address time only 1/K that of a single ROM. Total ROM capacity remains unchanged, though: K ROMs with a $2^N \times B$ organization become a $K2^N \times B$ format.

The configuration shown in Fig 2 uses these ideas to achieve a factor-of-two speed improvement. (You can extend the concept to suit your needs.) The ROMs' data outputs go to the inputs of 8-bit, high-speed, edge-triggered memory registers that have 3-state outputs. ROM 2N contains the evennumbered words; ROM 2N+1, the odd-numbered ones. The ROMs' output data transfers to the memory registers as a result of the LOW-to-HIGH transitions appearing at the divider's inverting output.

The clock-driven divider drives the ROM address generator and simultaneously enables the memory registers in an alternating mode. (Note that the data output at point O is delayed by two clock cycles with respect to the start of addressing.) The organization resulting from a $2^N \times 8$ format is $2^{N+1} \times 8$.

To Vote For This Design, Circle No 450

Lamp dimmer forms motor controller

HO Winters

IBM Corp, Boulder, CO


Common household devices such as fans and furnace blowers load ac induction motors fairly constantly once they're up to speed. However, these devices aren't really very efficient—in terms of necessary input power—when running under these conditions. And designs that increase their running efficiency are apt to be costly and complex when they must also start the motor.

The design illustrated in the **figure** solves this problem at a very reasonable cost. The lamp dimmer costs approximately \$5; the additional components, \$2. Employed in conjunction with a furnace blower, the circuit has saved 11.5% of the blower's energy consumption.

The modified lamp dimmer starts the induction motor at full power. Then, after a time delay, it reduces the motor's input power. As shown, the circuit can directly control motors rated as high as ¹/₃ hp. And you can increase this level by employing a higher current triac as the prime control device.

Capacitor C presents a low-impedance shunt to the level-set potentiometer R_1 , supplying full power to the motor during the start-up phase. As this capacitor charges, the applied power gradually reduces to the level set by R_1 . When the power turns off, bleeder resistor R_2 discharges C, and you can restart the motor in approximately 5 sec.

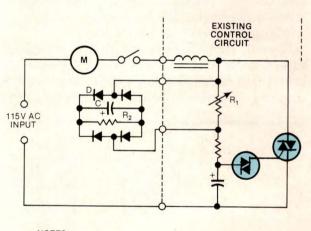To set up a motor using this controller, first start the motor R_1 set fully clockwise for maximum power.



NOTES $C = 10 \ \mu\text{F}, \ 200 \ \text{V DC}$ $R_2 = 500 \ \text{k}, \ \emph{y}_2 \ \text{W}$ D = ANY SUITABLE BRIDGE $M = \ \emph{y}_4 \ \text{+P MOTOR}$

Economical motor control results when you make these low-cost additions to a standard triac-controlled lamp dimmer. Capacitor C effectively shorts out the speed-control pot (R_1) until the induction motor has fully started. Then the motor runs at reduced speed but with increased efficiency.

Then slowly reduce power until the motor slows noticeably but keeps running. Finally, increase power until the motor resumes running at full speed at a smooth, quiet level.

To Vote For This Design, Circle No 451

THE TO-5 IS A TERRIFIC RELAY. WHEN YOU CAN GET IT & AFFORD IT.

Introducing the new generation of miniature hermetically-sealed metal case relays, the Hi-G MM-5. We made them simpler than the TO-5—just 5 integral parts instead of 11—for more reliability and a substantially longer life. They still give you equivalent TO-5 performance, ideal for non-military commercial applications, but at a remarkably lower price.

If you're a designer of microcomputers, μ P systems or industrial, test and communications equipment, you already know the advantages our hermetically-sealed metal case relays have over plastic devices. Even in tough atmospheres, harsh solvents, heavy



shock and vibration, our miniature MM-5 relays will last and last—up to 10 million operations. They'll often outlast the equipment they're installed in. How do we know? Because they employ the same basic design principles proven in military applications except with fewer mechanical parts for exceptional reliability.

And while you're waiting for the other guys to fill their TO-5 backorders, you can get rapid delivery on our longerlasting, more reliable, less costly MM-5 equivalents. For prices and catalog, write or call: Hi-G, Inc., Relay Division, 580 Spring St., Windsor Locks, CT 06096; (203) 623-2481.

For more information, Circle No 72

CONSIDER THE MM-5 COMMERCIAL RELAY. SIMILAR PACKAGE, SIMPLER DESIGN, LOWER PRICES, AVAILABLE NOW.



Design Ideas

Battery charger snaps from full to trickle

Kennan C Herrick

ESI Electronics Corp, San Francisco, CA

The best way to manage lead-acid-battery charging is to supply a constant current until you reach a prescribed cell voltage, then lower the voltage to maintain "float" charging. As a rule of thumb, the charging current should be no more than one-fourth of the battery's ampere-hour rating. Additionally, the battery's fully charged voltage is about 2.4V/cell; the float voltage should be approximately 90% of that value.

The circuit shown in Fig 1a, simpler than most, provides these functions adequately. Although designed for a 12V, 5-Ahr lead-acid battery, it adapts to batteries with other voltage and current ratings. The programmable IC regulator (IC₁) and transistor Q_1 provide a relatively constant current until the battery voltage reaches the fully charged value. Transistor Q_2 then senses this condition and drops the regulator's output voltage to the float value.

IC₁'s output voltage is set by the ratio of R_3 to R_5+R_6 , where R_6 adjusts for the exact output voltage desired. You can find this output voltage by using

 $V_{REG} = V_{REF}(1 + ((R_5 + R_6)/R_3)) + I_{ADJ}(R_5 + R_6)$ where V_{REG} is Q_2 's emitter-node voltage and V_{REF} is the nominal 1.25V reference voltage maintained by IC₁ across R_3 . IC₁'s Adj pin supplies I_{ADJ} , a nominal 100 μ A. Note that the R_3 used in the equation can be either R_3 's value alone or the effective value of R_3 paralleled by R_4 .

In the Charging mode, Q_2 is ON, thanks to the emitter-to-base charging current. R_4 thus parallels R_3 , and IC₁'s V_{REG} equals 16V (with nominal circuit values and R_6 set near mid-resistance). Subtracting a typical D₁ drop of 0.7V and Q₂ emitter-base drop of 0.7V provides 14.6V. When the battery voltage rises to this value—signifying full charge—Q₂ starts to turn off (**Fig 2**, point A). At this time, with Q₂'s base current approaching zero, the remaining charging current (through R_7) is approximately 30 mA.

As Q_2 turns off, R_4 becomes disconnected from R_3 , the R_5/R_6 current decreases, V_{REG} (at Q_2 's emitter) falls and Q_2 turns off further. This transition to the float voltage is regenerative and abrupt (Fig 2, point A to point B, then point B to point C as the battery voltage declines to the float value).

Float V_{REG} is 14.5V with Q_2 OFF. Subtracting 0.6V for D_1 's drop (at low current) and a few tenths


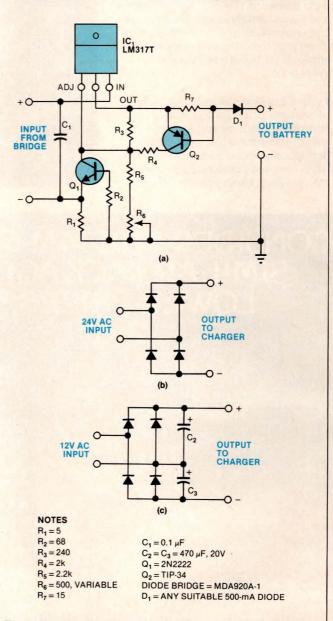


Fig 1—Battery charging switches from full to float when the combined D_1 and $Q_2 V_{BE}$ voltage drops are reduced as the battery reaches its fully charged potential. At this time, Q_2 turns off and R_4 no longer parallels R_3 , an action that reduces the charging-current rate. Depending on the transformer type you use, one of the bridge circuits ((b) or (c)) provides the required input voltage.

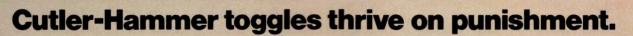of a volt across R_7 yields a float battery voltage of about 13.7V. The circuit maintains this voltage until the battery voltage drops the several additional tenths of a volt necessary to cause Q_2 to turn on (Fig 2, point D). Q_2 stays ON (Fig 2, point E), and charging continues until the battery's voltage again reaches 14.6V.



Meet the toggles that can really take it. Our environmentally-sealed toggles meet MIL-S-3950 standards for toughness and durability. And you can order them with standard lever or lever lock action; 1, 2, or 4 pole. You'll find just the switch you need in our complete line of dependable toggles.

pendable toggles. For more information on any product in our full line, contact your Cutler-Hammer Aerospace Products Specialist or distributor—they know your business. And, write for our free catalog. Eaton Corporation, Aerospace Control/Systems Division, 4201 N. 27th St., Milwaukee, WI 53216.



Design Ideas

Design Entry Blank

\$25 Cash Award for all entries selected by editors. An additional \$50 U.S. Savings Bond Award for winning design each issue, determined by vote of readers. Additional \$1000 Bond Award for annual Grand Prize Design, selected among semimonthly winners by vote of editors.

To:	Design Ideas Editor
	EDN
	Cahners Publishing Co.
	221 Columbus Ave., Boston, MA 02116
I he	reby submit my entry for
	's DESIGN IDEAS PROGRAM.

	The second second second		
Title		Phone	
Company			-
Division (if any)			_
Street			3
City	State	Zip	
Design Title			_
		1	

Print full name (no initials) and home address on lines below for mailing of your bond if chosen monthly issue winner. Also, please include your Social Security number.

Social Security No.

Entry blank must accompany all entries. Design entered must be submitted exclusively to EDN, must be original with author(s), must not have been previously published (limited-distribution house organs excepted), and must have been constructed and tested.

Exclusive publishing rights remain with Cahners Publishing Co. unless entry is returned to author or editor gives written permission for publication elsewhere.

In submitting my entry, I agree to abide by the rules of the Design Ideas Program.

Signed.

Name

Date_

Your vote determines this issue's winner. All designs published win \$25 cash. All issue winners receive an additional \$50 U.S. Savings Bond and become eligible for the annual \$1000 U.S. Savings Bond Grand Prize.

Vote now, by circling the appropriate number on the reader inquiry card.

Submit your own design, too. Mail entries to Design Ideas Editor, EDN, 221 Columbus Ave., Boston, MA 02116.

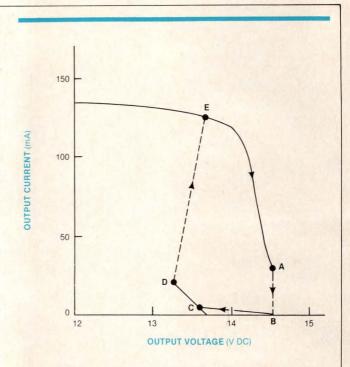


Fig 2—Full charging continues until the battery's voltage reaches the "topped-up" level (A). At this point, **Fig 1a**'s circuit rapidly reverts to a trickle-charge mode (points B through D) until the battery is sufficiently discharged. Full charging again occurs when the circuit switches back to point E operation.

Nominal constant-current charging is Q_1 's function. Charging current through R_1 tends to turn Q_1 on at a value of about 600 mA, in turn causing IC₁'s output voltage to diminish to maintain that current. (This procedure works because IC₁'s adjustment node is pulled toward ground.)

You can modify the design for a different battery voltage merely by changing the ratio of R_3 to R_5/R_6 . Select R_4 to provide the desired float-vs-chargingvoltage differential. R_7 determines the minimum charging current; the charging current itself—up to near the full battery charge—is set by R_1 .

Because this design works just as well with a pulsating input from the diode bridges shown (Figs 1b and 1c), you probably won't need to employ any additional filter capacitors. However, National Semiconductor (IC₁'s manufacturer) does recommend using a large-value capacitor to absorb possible ac-mains transients. You can adjust a pulsating charging current upward to compensate for the less-than-100% duty cycle by choosing the proper value for R_1 . Note that if you adapt this design for higher charging currents, Q_2 's base must be able to handle the full charging current safely.

To Vote For This Design, Circle No 452

THE MOST POWERFUL BENCHTOP TEST SYSTEM IN THE WORLD.

BIG SYSTEM PERFORMANCE AT A BENCHTOP PRICE.

The LTS-2000 is a lot more than a simple tester. It's a powerful instrument you can use anywhere in your plant for almost any kind of test from basic go/no-go to full-blown Discrepant Material Reports. And it can not only test DAC's and ADC's but a wide variety of linear components, including Op Amps, regulators, comparators, bifets, etc. Test results are immediately displayed and printed, and full reports including statistical analysis, data log and summary sheets are available through the integral 20 column printer.

Interface to peripherals, like line printers, CRT terminals or a HOST computer are easily accomplished via the IEEE-488 interface or either of the RS232 ports. The LTS-2000 gives you true big system" performance, like system measurement accuracy to greater than 16 bits, \pm 1LSB; selfcalibration and diagnostics, 16 bit microcomputer with 64K bytes of memory and more all at 1/4 the "big system" price.

EASY-TO-PROGRAM, EASY-TO-USE.

The unique design also allows for easy use. You can set up a

program in minutes either with a program from the device library or with the complete test menu of fill-in-the-blanks software. Just snap in the appropriate family board mod-



IT'S THE MOST VERSATILE BENCHTOP YOU CAN BUY.

You can not only use the LTS-2000 for incoming inspection, but component selection and grading engineering analysis

ing, engineering analysis, quality control, final test, qualification test, and even as a diagnostic tool for component evaluation.

Never before has a compact benchtop linear test system offered so much versatility for so little. For more information on the LTS-2000, or the LTS-2010 which lets you program in BASIC, contact Greg LaBonte at (617) 329-4700, Analog Devices, P.O. Box 280, Norwood, MA 02062.

AND WE CAN

DELIVER

ule and socket module, plug in the device and press "GO" – the LTS-2000 does the rest. There's even a full-edit capability, so test parameters can be changed quickly and easily.



WAYOUT IN FRONT.

Analog Devices, Inc., Box 280, Norwood, MA 02062; East Coast: (617) 329-4700; Midwest: (312) 894-3300; West Coast: (714) 842-1717; Texas: (214) 231-5094; Belgium: 031/37 48 03; Denmark: 02/84 58 00; England: 01/941 0466; France: 01/687 3411; Germany: 089/53 03 19; Japan: 03/263 6826; Netherlands: 076/87 92 51; Switzerland: 022/31 57 60; and representatives around the world See the all new

1981

EDN CARAVAN

Western Show Tour

Signetics Corporation Harris Semiconductor Unitrode Corporation Centralab, Inc. **Teledyne Relays** Mepco/Electra, Inc. Brand-Rex Co., Electronic Products Div. **Mupac Corporation** Sorensen Company **Berg Electronics** Multiwire Div., Kollmorgen Corporation **B&K Precision Div., Dynascan Corporation** Belden Corporation, Electronic Div. **Garry Manufacturing Company** Ferroxcube Div., Amperex Electronic Corp. Slatersville Div., Amperex Electronic Corp. E.F. Johnson Co. Components Div.

CHECK THE ITINERARY FOR DATE WE VISIT YOU.




1981 EDN CARAVAN ELECTRONIC SHOW TOUR February 16 to March 27 (first half)

DATE	TIME	SITE	DATE	TIME	SITE
2/16	9-12	ROCKWELL INT'L AUTONETICS	3/11	8:30-10	GM DELCO ELECTRONICS
Monday	AM	3370 Miraloma Ave., Anaheim, CA	Wednesday	AM	6767 Hollister Ave., Goleta, CA
2/16	2-4	NORTHROP CORPORATION	3/11	10:30-12	BURROUGHS CORPORATION
Monday	PM	500 East Orangethorpe, Anaheim, CA	Wednesday	AM	6300 Hollister Ave., Goleta, CA
2/17	8:30-11:30	HUGHES AIRCRAFT Company	3/11	2:30-4	BURROUGHS CORPORATION
Tuesday	AM	1901 W. Malvern Ave., Fullerton, CA	Wednesday	PM	5411 N. Lindero Canyon, Westlake Village, CA
2/17	1-3	BECKMAN INSTRUMENTS, INC.	3/12	9-11:30	HUGHES AIRCRAFT COMPANY
Tuesday	PM	2400 Harbor Blvd., Fullerton, CA	Thursday	AM	8433 Fallbrook Ave., Canoga Park, CA
2/17	3:30-4:30	BECKMAN INSTRUMENTS, INC.	3/12	1:30-4	LITTON GUIDANCE & CONTROL SYSTEMS
Tuesday	PM	200 So. Kraemer Blvd., Brea, CA	Thursday	PM	5500 Canoga Ave., Woodland Hills, CA
2/18	8:30-10	INTERSTATE ELECTRONICS CORPORATION	3/13	8:30-9:45	DATA PRODUCTS CORPORATION
Wednesday	AM	707 E. Vermont Ave., Anaheim, CA	Friday	AM	6200 Canoga Ave., Woodland Hills, CA
2/18	10:30-12	INTERSTATE ELECTRONICS CORPORATION	3/13	10:45-12	TELEDYNE SYSTEMS COMPANY
Wednesday	AM	1001 Ball Rd., Anaheim, CA	Friday	AM	19601 Nordhoff St., Northridge, CA
2/18	2-3:30	CALIFORNIA COMPUTER PRODUCTS	3/13	2-4	LITTON DATA SYSTEMS
Wednesday	PM	2411 W. La Palma, Anaheim, CA	Friday	PM	8000 Woodley St., Van Nuys, CA
2/19	8:30-9:30	COMPUTER AUTOMATION	3/16	8:30-10	BURROUGHS CORPORATION
Thursday	AM	18551 Von Karman Ave., Irvine, CA	Monday	AM	460 Sierra Madre Villa, Pasadena, CA
2/19	10:30-12	MICRODATA CORPORATION	3/16	11-12	GOULD INC.
Thursday	AM	1562 Reynolds Ave., Irvine, CA	Monday	AM	4323 Arden Dr., El Monte, CA
2/19	2-4	SPERRY UNIVAC MINI-COMPUTER	3/16	2-4	NORTHROP CORPORATION
Thursday	PM	16842 Von Karmon Ave., Irvine, CA	Monday	PM	3901 W. Broadway, Hawthorne, CA
2/20	9-11:30	FORD AERO & COMMUNICATIONS CORPORATION	3/17	9-12	HUGHES AIRCRAFT COMPANY
Friday	AM	Ford Rd., Newport Beach, CA	Tuesday	AM	2000 E. Imperial Hwy., El Segundo, CA
2/20	1:30-3:30	ROCKWELL INT'L COLLINS	3/17	1:30-4:40	HUGHES AIRCRAFT COMPANY
Friday	PM	4311 Jamboree Rd., Newport Beach, CA	Tuesday	PM	Centinella & Teale, Culver City, CA
3/2	9-11	HEWLETT-PACKARD COMPANY	3/18	9-11	AMPEX CORPORATION
Monday	AM	1501 Page Mill Rd., Palo Alto, CA	Wednesday	AM	200 N. Nash, El Segundo, CA
3/3 Tuesday	1-2 PM	DIGITAL TELEPHONE SYSTEMS 1 Commerce Blvd., Novato, CA AMPEX CORPORATION	3/18 Wednesday	1:30-4 PM	XEROX CORPORATION 701 So. Aviation Blvd., El Segundo, CA
3/2 Monday 3/3	1-3 PM 9-11:30	401 Broadway, Redwood City, CA HEWLETT-PACKARD COMPANY	3/19 Thursday	8:30-10 AM	BURROUGHS CORPORATION 25725 Jeronimo Rd., Mission Viejo, CA
Tuesday	AM	1400 Fountain Grove, Santa Rosa, CA	3/19	11-12	HUGHES AIRCRAFT COMPANY
3/3 Tuesday	3:30-4:30 PM	DIABLO SYSTEMS INC. 24500 Industrial Blvd., Hayward, CA	Thursday 3/19	AM 2:30-4:30 PM	6155 El Camino Real, Carlsbad, CA CUBIC CORPORATION 9233 Balboa Ave., San Diego, CA
3/4 Wednesday	8:30-11:30 AM	LOCKHEED MISSILES & SPACE CO. 1111 Lockheed Way, Sunnyvale, CA	Thursday 3/20	8:30-9:30	HEWLETT-PACKARD COMPANY
3/4	1-2	ATARI INC.	Friday	AM	16399 W. Bernardo Dr., San Diego, CA
Wednesday	PM	1272 Borregas Ave., Sunnyvale, CA	3/20	10-12	NCR CORPORATION
3/4	2:45-4:30	AMDAHL CORPORATION	Friday	AM	16550 W. Bernardo Dr., San Diego, CA
Wednesday	PM	1250 E. Arques Ave., Sunnyvale, CA	3/20	2-4	GENERAL DYNAMICS ELECTRONICS
3/5 Thursday	9-11:30 AM	HEWLETT-PACKARD COMPANY 11000 Wolfe Rd., Cupertino, CA	Friday	РМ	5011 Kearney Villa Rd., San Diego, CA
3/5	1-2	APPLE COMPUTER CORPORATION	3/23	8-9	HONEYWELL PROCESS CONTROL
Thursday	PM	10460 Banley Dr., Cupertino, CA	Monday	AM	16404 N. Black Canyon Hwy., Phoenix, AZ
3/5	3-4:30	SHUGART ASSOCIATES INC.	3/23	9:30-12	HONEYWELL INFORMATION SYSTEMS
Thursday	PM	475 Oakmead Pkwy, Sunnyvale, CA	Monday	AM	13430 N. Black Canyon Hwy., Phoenix, AZ
3/6	8:30-10	FOUR PHASE SYSTEMS INC.	3/23	2-4:30	SPERRY FLIGHT SYSTEMS
Friday	AM	10700 N. De Anza Blvd., Cupertino, CA	Monday	PM	21111 N. 19th Ave., Phoenix, AZ
3/6	11-12	MEMOREX CORPORATION	3/24	9-12	MOTOROLA GOV'T ELECTRONICS
Friday	AM	18922 Forge Drive, Cupertino, CA	Tuesday	AM	8201 E. McDowell Rd., Scottsdale, AZ
3/6	2-4	ROLM CORPORATION	3/24	2-3:30	ITT COURIER
Friday	PM	4900 Old Ironsides Dr., Santa Clara, CA	Tuesday	PM	1515 W. 14th St., Tempe, AZ
3/9	9-11	HEWLETT-PACKARD COMPANY	3/25	9-11:30	IBM CORPORATION
Monday	AM	5301 Stevens Creek Blvd., Santa Clara, CA	Wednesday	AM	Tucson, AZ
3/9	1-3:30	MEMOREX CORPORATION	3/25	1:30-4	HUGHES AIRCRAFT COMPANY
Monday	PM	San Tomas & Central Xway, Santa Clara, CA	Wednesday	PM	Nogales Hwy., Tucson, AZ
3/10	8:30-1	IBM CORPORATION	3/27	1:30-4	SPERRY UNIVAC
Tuesday	AM/PM	5600 Cottle Rd., San Jose, CA	Friday	PM	322 N. 2200 West, Salt Lake City, UT

Let Mini-Circuits' RF TRANSFORMERS Do Your Matching! 10 kHz - 800 MHz

...from \$2.95

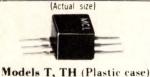

(0.300" sq. × 0.230" high) (Actual size)

(Act

Model TMO (Metal case) (.500" L * .230" w * .255" h)

CENTER-TAPPED DC ISOLATED

Model No. T1-1T TM01-1T	Imped. ratio	Freq. (MHz) .05-200 .05-200	Price (10-49) \$3.95 \$6.45	UNBALAN & SECON		IMARY	i.
T2-1T TM02-1T T2.5-6T	2 2 2.5	.07-200 .07-200 .01-100	\$4.25 \$6.75 \$4.25	Model No.	Imped. ratio	Freq. (MHz)	Price (10-49)
TM02.5-6T	2.5	.01-100	\$6.75	T2-1	223	.025-600	\$3.45
T3-1T	3	.05-250	\$3.95	TM02-1		.025-600	\$5.95
TM03-1T	3	.05-250	\$6.45	T3-1		.5-800	\$4.25
T4-1	4	.2-350	\$2.95	TM03-1	3	.5-800	\$6.95
TM04-1	4	.2-350	\$4.95	T4-2	4	.2-600	\$3.45
• T4-1H	5	8-350	\$4.95	TM04-2	4	.2-600	\$5.95
15-11	5	.3-300	\$4.25	T8-1	8	.15-250	\$3.45
TM05-11	5	.3-300	\$6.75	TM08-1	3	.15-250	\$5.95
T13-11	13	.3-120	\$4.25	T14-1	14	.2-150	\$4.25
TM013-11	13	.3-120	\$6.75	TM014-1	14	.2-150	\$6.75

50

DC ISOLATED PRIMARY

Imped.

ratio

1.5 1.5 2.5 2.5

4

9

à

9

16

16

16

• Up to 100mA DC without saturation

Freq

& SECONDARY

Model

T1-1 TM01-1

No.

• T1-1H

T1 5.1

19-1

•T9-1H T16-1

•T16-1H

TM09-1

TM016-1

TM01.5-1

T2.5-6 TM02.5-6 T4-6 TM04-6 ç.

i

Price

FOR ADDITIONAL INFORMATION. COMPLETE SPECIFICATIONS, AND PERFORMANCE CURVES. REFER TO 1979-80 MICROWAVES' PRODUCT DATA DIRECTORY Dgs. 161 to 368 or 1979 EEM 2770 to 2974.

(MHz) (10-49) \$2.95 \$4.95 \$4.95 \$3.95 \$6.75 \$3.95 \$6.45 \$6.45 .15-400 8-300 .1-300 .01-100 .02.200 \$3.95 .02.200 \$6.45 \$3.45 \$6.45 .15.200 \$5.45 2.90 .3-120 \$3.95 \$6.45 .3-120 7-85 \$5 95

It's easy to transform impedance and reduce VSWR.

Chose from 40 models, 12.5 to 800 ohms, 10 kHz to 800 MHz, ultra- low distortion (H models) balanced, unbalanced and center-tapped . . . immediate delivery . . . at prices that can't be matched, starting at \$ 2.95



2625 East 14th Street Bklyn, New York 11235 (212) 769-0200 Domestic and International Telex 125460 International Telex 620156

R 42/Rev/A

INSTRUMENTATION & POWER SOURCES



TEST SET. Model 8903-E85 semiautomatic transceiver test set makes in-channel tests from AM, FM and PM communication transceivers from 150 kHz to 990 MHz, either automatically under control of an HP 85F controller or manually using instrument frontpanel keyboard entry.

Its measurement capabilities range from simple tests such as frequency and distortion through complex measurements including usable sensitivity and audio flatness.

Providing an HP 8903A audio analyzer, HP 8901A modulation analyzer, HP 8656A synthesized signal generator, a switching module and a relay actuator, the μ P-controlled unit is fully programmable and includes an HP-IB (GPIB) interface for remote control by the instrument controller.

The modulation analyzer can measure AM depth or FM deviation to 1% accuracy in <2 sec with one keystroke or instruction and furnishes selectable FM de-emphasis filters; post-detection audio filters; and peak, peak-hold and average detectors. The audio analyzer similarly performs a SINAD measurement with typical residual noise and distortion of <0.003%.

The HP 11723A Application Pac software tape can be used to make 14 transceiver tests. \$28,500. Delivery, 24 wks ARO. Hewlett-Packard Co, 1507 Page Mill Rd, Palo Alto, CA 94304. Phone (415) 857-1501. Circle No 172


INTERFERENCE ANALYZER.

Conforming to the guasi-peakmeasurement standards of CISPR, VDE and ANSI Standard C63.2-1980, Model CPR-25 measures EMI utilizing LCDs that represent attenuation setting and show tuned frequency to an accuracy of ±0.1% over a 10-kHz to 1000-MHz range. It also incorporates circuits for detecting peak, average and rms levels and ratios that can be displayed on an 80-dB frontpanel meter or tracked by singleor dual-pen X-Y plotting. Additionally, video response over each octave-range band can be presented on any conventional or storage-type oscilloscope, implementing a tuned - front - end spectrumanalyzer capability. \$27,900. Delivery, 90 to 120 days ARO. Penril Corp, 5520 Randolph Rd, Rockville, MD 20852. Phone (301) 881-8151. TWX 710-828-Circle No 173 0522.



POWER SUPPLIES. For precision laboratory high-voltage applications, these solid-state benchtop $5 \times 7\% \times 71$ /4-in. units feature digital voltage controls with a resolution of 200 mV, a front-panel voltage meter, regulation and ripple of 0.001%, TCs of 50 ppm/°C, plug-in pc boards and encapsulated high-voltage circuitry. They are arc protected, self restoring and claimed to be

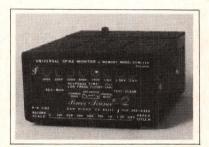short-circuit proof. Model 214 has a floating output and can serve as a positive or negative source delivering 0 to 1000V at 15 mA. Model 215 provides a polarity switch with LED polarity indicators and an output of 0 to \pm 3000V at 5 mA. \$485 for either model. **Bertan Associates Inc,** 3 Aerial Way, Syosset, NY 11791. Phone (516) 433-3110. **Circle No 174**



SPIKE MONITOR. Measuring peak amplitude of normal- and common-mode power-line spikes in eight discrete levels of 100V to 2 kV, the Universal Spike Monitor stores the result in a voltage-sensitive shift register and displays it on eight corresponding LEDs on its front panel. Measurement response time equals 25 nsec, and a 1-kHz cutoff network rejects low-frequency disturbances such as surges, sags or dropouts, forming an effective spike-monitor window of approximately 1 kHz to 10 MHz. The unit provides two modes of operation. In the Monitor mode, memory is instantly updated to hold (and display) the worstcase spike amplitude indefinitely until cleared by a front-panel pushbutton. In Recording mode, the memory produces a proportional dc current for a strip-chart recorder, clearing itself automatically after 1 min when a spike has been registered. \$445; strip-chart recorder, \$685. Power-Science Inc, 7667 Vickers St, San Diego, CA 92111. Phone (714) 292-4322. Circle No 175




BER INDICATOR. Providing bit-error-rate measurements to 325 MHz, the modular BERTS-325C includes a clock source, transmitter and receiver that generate pseudorandom or fixed-word patterns for stimulating the system under test and measure the bit-by-bit errors received. BER or total errors can be measured on continuous or burst data for applications such as TDMA testing. Data and delayed-data outputs are furnished for QPSK-test applica-

No Supply Power Supply Specifien Specifien Specifien Buyer Buyer Buyer Buyer Buyer Should be Should fit. Without It. See It In See It In See I fiel Should fit. Dages 147-Pages 154

tions. A printer output is standard, and an optional GPIB interface permits automated-test applications. The transmitter provides four pseudorandom test patterns (27-1, 215-1 and 2²³-1 bits) and four 16-bit words, including alternating ONE/ZERO. Errors can be injected internally at a 2×10-2 BER or at an externally controlled rate. For measurements on nonpseudorandom 16-bit patterns, an external reference-data input is provided. \$17,195. Delivery, 8 to 10 wks ARO. Tau-Tron Inc. 27 Industrial Ave, Chelmsford, MA 01824. Phone (617) 256-9013. TWX 710-343-6781. Circle No 176

TEST SYSTEM. A minicomputer-controlled wafer-level parametric test system, System 300 can also be configured to test discrete semiconductor devices or functional circuits. It includes a PDP-11/23 minicomputer with 128k bytes of memory, dual floppy disks, a CRT or printing terminal and plug-in instrumentation modules for forcing dc current from 25 pA to 100 mA (to 250V) and dc voltage from 0.25 mV to 300V (to 1A). Standard modules provide voltage measurements from 100 µV to 250V and current measurements from 5 pA to 1A (0.01 pA with low-current matrix option). Capacitance measurement from 0.01 to 3000 pF FS is also available. Maximum matrix size is 144 pins, and the pins can be multiplexed to as many as four device test stations. A single measurement can be made in <3 msec; typical floating-pointcalculation time equals 100 usec. From \$49,000. Delivery, 90 to 120 days ARO. Keithley Instruments Inc, 28775 Aurora Rd, Cleveland, OH 44139. Phone (216) 248-0400. TLX 985469. Circle No 177

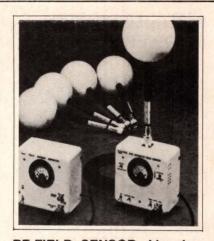

RF-FIELD SENSOR. Manufactured by the Italian firm Aeritalia, this system uses balanced isotropic probes responding to any incident field (regardless of polarization) to provide a true reading of all incident electric or magnetic fields in the 1- to 500-MHz range. It comprises a shielded metering instrument with separate sensor probes and a field-sensor repeater connected to the metering device via fiber-optic cable. Three sensor probes cover electric field strengths from 10 to 100 V/m FS: two cover magnetic fields of 1 and 10 A/m FS. The repeater unit can be isolated from the incident field for remote-location readout. \$7650 for metering instrument, repeater, fiber-optic link and five probes. Delivery, 60 to 90 days ARO. Amplifier Research, 160 School House Rd, Souderton, PA 18964. Phone (215) 723-8181. TWX 510-661-6094. Circle No 178

EPROM PROGRAMMER. For 25XX and 27XX Series EP-ROMs, the ROMMR erases, tests, programs and verifies 2708/58/16/32/64, 2516/32/64 and 68764 devices. It's available as an option to the maufacturer's Sprint 68 microcomputer/development system. \$299. Wintek Corp, 1801 South St, Lafayette, IN 47904. Phone (317) 742-8428. Circle No 179



SATELLITE-VIDEO RECEIVER. You can receive any of the 24 video channels broadcast from SATCOM, WESTAR, COMSTAR or ANIK satellites with the Model AR1000 Simulchannel satelliteearth-station video receiving system. Equipped with an orthomode antenna feed, two LNA/down converters and separate horizontal and vertical feed lines, it can automatically select the correct feed line for a given transponder channel number (entered on a front-panel pad) to provide simultaneous access to six video channels. Other key features include PLL demodulation with threshold extension. automatic frequency control, digital channel selection and modular construction. Four receivers can be cascaded to provided simultaneous demodulation of 24 channels. Approximately \$15,000 for 6-channel, 19-in,-rack-mounting unit with two LNA/down converters. Delivery, starting in May. Avantek, 3175 Bowers Ave, Santa Clara, CA 95051. Phone (408) 727-0700. Circle No 180

LINEAR SUPPLIES. Q Series UL-recognized open-frame devices furnish output voltages of 5, 12, 15 or 24V dc and output currents of 1.2 to 12A for 5V models, 1.2 to 4.8A for 24V versions. Overvoltage protection is standard on all 5V outputs and optional for the others. Dual- and triple-output models are also available. All units incorporate a grounded shield for 2500V isolation between the primary and secondary windings, and outputs supply either positive or negative voltages. Other features include 115/230V ac inputs, full-output ratings over 0 to 50°C, short-circuit and overcurrent protection and terminals for remote-sensing leads. Line regulation specs at $<\pm 0.05\%$ for 10% line change; load regulation, $<\pm 0.05\%$ for 50% load change. \$25.70 to \$89.55 for 5V single-output models with overvoltage protection; \$25.70 to \$83.95 for 12, 15 or 25V versions without OVP. **Dynage Inc,** 1331 Blue Hills Ave, Bloomfield, CT 06002. Phone (203) 243-0315.

Circle No 181




Dripproof Pushbutton Switches

NEW...Series 50 Dripproof Lighted Display Pushbutton Switches and Indicators are designed for those problem installations that may be exposed to rain, open deck spray, condensation on the panel surfaces, or similar applications where moisture may be encountered. The display pushbuttons' captive rubber seal, precisely seated in the switch body, effectively closes all possible paths that moisture might follow into the switch. All units meet or exceed the requirements of MIL-S-22885 and MIL-STD-108E.

Switches are available as individually mounted or matrix mounted units with choice of 2PDT or 4PDT circuitry, solder, PC, wire wrap, or crimp pin receptacle termination, and either alternate or momentary switch action. Matching indicators provide look-alike appearance. Four-lamp illuminated display pushbuttons provide one to four message areas, with a wide choice of legend style and colors.

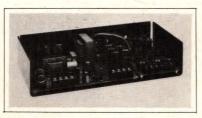FREE...Design Catalog GC-6/7. Write today for fully illustrated catalog giving complete descriptions, dimensions, and specifications.





SWITCHER. An addition to the Ualy line, the ES130 Series furnishes a main output of 5V/20A and auxiliary outputs of $\pm 12V/1.5A$, $\pm 15V/1.2A$ and 5V/0.5A. Overvoltage protection is standard on the main output and optional on the others. You can select inputs from 90 to 125 or 180 to 250V, 47 to 63 Hz. Other features of the 10.76× 5.25×2.375-in. supply include tight regulation, low noise, convection cooling without additional heat sinking and full rating to 40°C. Open configuration, \$182; enclosed, \$189 (250). Elpac Power Systems, 3131 S Standard Ave, Santa Ana, CA 92705. Phone (714) 979-4440. TWX 910-595-1513.


Circle No 182



DIGITAL VOM. A 6-function, 24-range unit, Model 3410 features a 1000V ac/dc range, overload protection to 600V on all current ranges (with 2A/250V and 3A/600V fuses), protection to 1000V on resistance and voltage ranges and typical 9V-alkaline-battery life of 500 hrs. Its 3½-digit, 0.5-in.-high LCD has overrange blanking indication plus autopolarity and autozero capability. The unit comes with 36-in. test leads. screw-on insulated alligator clips, 9V battery, spare 2A fuse, wire tilt stand and instruction manual. Model 3410 kit adds a clamp-on ac ammeter, line separator, 6-kV ac and dc high-voltage probe and carrying case. \$140; \$208 kit (including VOM). **Triplett Corp**, 1 Triplett Dr, Bluffton, OH 45817. Phone (419) 358-5015. TWX 810-490-2400. **Circle No** 183

DEVELOPMENT SYSTEM. The microprogramming Model DS500 features a 4-MHz Z80-based computer system with 64k bytes of memory, two dual-density floppy-disk drives and a CRT terminal. A 2901-based PROM emulator/ logic-state analyzer ties to the computer as well as the CRT terminal. The logic-state analyzer furnishes a 20-MHz trace (1023 words deep), expandable to 80 channels wide. An unlimited break/trigger feature provides simultaneous and independent arming, conditional break/trigger and unconditional break/trigger of any number of addresses within the 8192location addressing space. Two external-event break/trigger inputs can capture glitches as short as 8 nsec. Other features include single-step capability and PROM-emulator output enable/disable. From \$15,900. Hilevel Technology Inc. 14661C Myford Rd, Tustin, CA 92680. Phone (714) 731-9477. Circle No 184

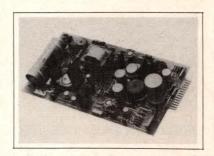SWITCHER. An open-frame 50 to 65W unit furnished in pc-board form, the 5×9 -in. Etatech Series provides as many as five outputs. The primary output is rated at 5V to 8A; the others at ± 12 to $\pm 15V$ to 12W, -12 to -15V to 12W and 5 to 15V (either polarity) to 18W.



Input-voltage range specs at 85 to 135V rms, 47 to 440 Hz single-phase or 115 to 185V dc. Regulation on primary output equals ±15 mV (line) and 10 mV (load), 10% to full load. Total line, load and interaction regulation (secondary outputs) equals ±10%. Ripple and noise on the primary output are held to 100 mV p-p; on the secondary outputs, 2% or 200 mV p-p. Short-circuit and overload protection come standard. \$132.20 (100). Adtech Power Inc, 1621 S Sinclair St, Anaheim, CA 92806. Phone (714) 634-9211. Circle No 185

DATA-ACQUISITION SYSTEM. Storing 600M bits on an ANSI-compatible 1/4-in. tape cartridge, this system operates with dual µPs to selectively receive, format, record and reproduce data from as many as four 0 to 200k-bps serialasynchronous data channels. It records for nearly 1 hr at 200k bps and for more than 6 days at an input rate of 1000 bps. Data bursts of 128k bits can be accommodated at megabit rates. Recording format is 7200 bpi: data records in serpentine fashion on 10 tracks. Total tape length equals 700 ft. The tape drive uses a 10,000-hr brushless dc motor with a proprietary digital servo. \$16,000 to \$29,000. Delivery, 6 months ARO. Peripherals Development Associates Inc, 3303-B1 Harbor Blvd, Costa Mesa, CA 92626. Phone (714) 546-9640. Circle No 186

COMPONENTS & PACKAGING



DATACOMM NETWORK. Model 6010 Datanet can replace fiber-optic or hardwired data links, telephone lines and modems connecting terminals, process-control transducers, computers and controllers.

All solid state (including light sources), the optical system uses infrared energy to transmit serial binary data over line-ofsight paths. The receiver circuitry compensates for changes in atmospheric conditions such as fog, dust, strong sunlight or smoke, allowing system use outdoors or in harsh industrial environments.

All full-duplex channels are operable simultaneously at 0 to 2400, 4800 and 9600 bps without requiring user adjustment, and the remote transceiver station can be placed as far as 35 ft from the central transceiver (up to 328 ft with Model 5010 transceiver).

Plug compatible with most μ Cs and peripherals, the system comes with standard RS-232 or current-loop interfaces; others are available. \$2750 for 5-channel system. Scientific Radiation Corp, 1201 San Antonio Rd, Mt View, CA 94043. Phone (415) 965-0910. TLX 345506. Circle No 225

COMPUTER CHASSIS. Packaging disk-based-computer and µP systems, the rack-mountable Model Q MFR-1 can house nine pc-board or Scotchflex-type wiring modules, one or two 5.25-in. floppy-disk drives, a linear or switching power supply and ac line filtering. The 10.5×19 -in. unit can be remotely turned on and off via a solid-state relay for use with modems or multiple-processor networks and accommodates pc

cards on 0.1-in. centers with dual 40-pin card-edge connectors. The enclosure is constructed of black anodized aluminum with extruded cross members. \$250 to \$500, depending on options. **Q Computers**, 134 Water St, Wakefield, MA 01880. Phone (617) 245-7323. **Circle No 226**

Technipower The High Reliability Power Conversion Source



MIL-QUAL 24 or 28 VDC SINE WAVE INVERTERS

A new, high reliability Series of Inverters that delivers Mil-Quality performance and dependability for any industrial UPS system. Operates from any nominal 24 VDC (20 to 28) or 28 VDC (24 to 32) source with less than 5% distortion. Choice of 8 open frame models, all with 70% efficiency rating and equipped with 115 or 220 VAC outputs, 50/60 Hz or 400 Hz input. Regulation is $\pm 1\%$ source and load; temperature rating -71° C and better; load power factor -0.8, leading or lagging. Automatic short circuit and source reverse polarity protection. Send for Technical Data Bulletin.



HARSH ENVIRONMENT, SEALED AC-DC/DC-DC SWITCHERS

Advanced IC technology, epoxy sealed packages made to meet 35,000 hours MTBF stress levels at 80°C base, outputs from 2.8V to 250 VDC and power ratings to 100 Watts — all contribute to the "Mil-Qual" performance of these new, modular V-80 Switchers. The 25 KHz switching frequency helps achieve 80% efficiency and high reliability from a small package. Regulation is $\pm 0.05\% + 5mV$ line; ripple is 0.2% + 10mV; load effect is $\pm 0.1\%$ + 5mV; overvoltage, short circuit protection, slow start, remote sensing and floating output are included. Send for Technical Data Bulletin.

Backed by 5 year Warranty.

VARIAC[®]

Variac[®] Autotransformers and Voltage Regulators are now solely manufactured and sold in the U.S. and Canada by Technipower.[®]



P. O. Box 222 Commerce Park, Danbury, Conn. 06810 Tel: (203) 748-7001 TWX: 710-456-9280

F-O RCVRS, XTMRS. Epoxy encapsulated in SMA-type brass connectors, these units mate with any SMA-terminated fiberoptic system. Model 9824.01.A is a silicon-phototransistor receiver; Model 9824.02.A, a silicon PIN-photodiode unit with a rise time of 25 nsec. Models 9823.01.A and 9823.02.A IR LED transmitters operate at 940 nm, while Model 9823.03.A produces an 890-nm output. The units operate between -55 and +100°C. Model 9824.01A, <\$14; Model 9824.02.A, approximately \$40; Model 9823.01.A, \$20; Model 9823.02.A, \$30; Model 9823.03.A, \$22 (100). Opti-Cal Inc, Box 10362, Glendale, CA 91209. Phone (213) 246-3901. Circle No 227

PRESSURE TRANSDUCER. A general-purpose unit packaged in a stainless-steel diaphragm and case, Model AB measures from 0 to 6 and 0 to 20,000 psi and comes in gauge, absolute and sealed versions. Suiting industrial, oil-drilling, oceanographic, medical, aerospace and process-control applications, it features accuracy to 0.5% (including nonlinearity, repeatability and hysteresis). Output equals 100 mV at rated pressure. \$100 (100). Data Instruments Inc, 4 Hartwell PI, Lexington, MA 02173. Phone (617) 861-7450. TWX 710-326-0672. Circle No 228

LED STICK DISPLAY. The multidigit 0.3-in.-high MMN-30000 Series display uses a GaAsP-on-GaP-substrate die, comes in 2- and 4-digit end-stackable packages and provides orange, yellow, green and high-efficiency-red outputs, prematched for brightness and hue. Lens-color options can tailor the display to a particular application. Viewable in sunlight under normal conditions, it operates over -40°C to +85°C and comes in multiplexed or direct-drive configurations. \$2.75 for 2-digit unit (1000); \$5.60 for 4-digit version (500). **General Instrument Corp**, 3400 Hillview Ave, Palo Alto, CA 94304. Phone (415) 493-0400. **Circle No** 229



THERMOCOUPLE WIRE, Containing 12 spools of calibrated thermocouple wire, these kits can be used to form thermocouples that meet the ANSI Limits of Error for Thermocouples standard (MC96.1, 1975) if produced using standard manufacturing practices. Four kits are available: Kit E, Chromel and Constantan: Kit J. iron and Constantan; Kit K, Chromel and alumel: and Kit T. copper and Constantan. You get six wire sizes in each kit, ranging from 0.001 to 0.015 in. in diameter. Each spool contains 50 ft of wire, protected with snap-on covers. \$89. Temperature Co Inc, Box 686, Metuchen, NJ 08840. Phone (201) 287-3490. Circle No 230

SOCKET STRIPS. Providing a double row of contacts on a 0.1-in. grid, Socket Strips have terminals of one row bused to terminals of the other row to provide a commoned 1-row pinout. The terminals can also be left unbused for use as an LED-array socket. You can

connect any number of strips side by side, maintaining the 0.1-in. grid pattern. Both square-wrap and solder-pin terminals are standard in tin or gold plate. Solder-pin styles plug into themselves, permitting stacking for breadboarding or vertical packaging. \$1.45 (100) for a 16-contact commoned 2-row assembly. **Samtec Inc,** 810 Progress Blvd, New Albany, IN 47150. Phone (812) 944-6733. **Circle No 231**

OPTICAL FIBER. For short-tointermediate-distance and medium-bandwidth applications, this moderate-loss fiber consists of a silica core, plastic optical cladding and a protective jacket. It comes in standard diameters of 200, 300, 400 and 600 µm; other sizes are also available. Attenuation specs at <50 dB/km at 790 nm. Features include NA of 0.3, a 1.46 core index of refraction, 20-MHz-km bandwidth, short-gauge-length tensile strength >60 kg/mm² and claimed low radiation sensitivity. From \$0.50 per metre (small gty) for 200-µm-core fiber. EOTec Corp, 200 Frontage Rd, West Haven, CT 06516. Phone (203) 934-7961. Circle No 232

ISOLATOR. Model 60A2051 covers a frequency range of 8 to 18 GHz and, excluding connectors and termination, occupies only 0.125 in.3 16-dB min isolation is guaranteed, as are 0.7-dB max insertion loss and 1.5 max VSWR over -45 to +85°C. Designed for airborne and missile environments, the unit sports SMA female connectors. \$138 (small qty). Trak Microwave Corp, 4726 Eisenhower Blvd, Tampa, FL 33614. Phone (813) 884-1411. TLX 52827. Circle No 233

We Pioneered The Industry

The Autotest UTS-3000[™] — the acknowledged leader in power supply testing systems. For over four years, Autotest has had systems, a service staff and policies that are the envy of its competition.

Autotest has more power supply testing systems in use than anyone else in the field. And, we have the most experience in testing switching supplies and high power applications utilizing our own hardware.

Our AUTOSOFT[®] software is the most advanced in the industry, and is totally integrated with Autotest's hardware. On the UTS-3000, over 90% of its components are designed and manufactured in-house . . . competitive units purchase many of their

AUTOTESTen

components from outside suppliers, causing service and repair problems.

Autotest also supplies multi-station test head capability. No matter how complex your power supply testing requirements might be, Autotest can meet the challenge with system reliability and integrity undreamed of before. Best of all, the best is affordable.

Call today and find out why you should have an Autotest UTS-3000 system in your plant.

- A Comprehensive Support Plan to optimize uptime
- On-site spare parts kits to minimize any repair time that might occur
- Proven capability and predictable delivery at known cost
- Easy to program and operate

To SAVE time, to CUT labor costs, to obtain CONSISTENT results and product QUALITY, write or call us today.







LARGE-AREA LCDs. Standard Model 740 (6-digit) and 742 (8-digit) displays feature bonded pin connectors. Both offer 0.5-in. character heights and include colons and decimal points. The displays operate over a 3 to 20V rms range and furnish low dissipation (50 µW typ for Model 740). Package sizes measure 2.75×1.2 and 3.7×1.2 in. for the 740 and 742, respectively. Connectorless versions are optional. Beckman Instruments Inc, Box 3579, Scottsdale, AZ 85257. Phone (602) 947-8371. Circle No 248

WIRE-WRAPPING BOARDS.

Model 2-8010 comes in two connector configurations (-A. with 296 I/O locations; -B, with 272 I/O pins) for direct installation into the SBC 80/10 card cage. Both feature a universal-style pattern with 62 rows of 52 plated-through holes on 0.1-in. centers. The boards accommodate DIP-pin spacings of 0.3 to 0.9 in. Bypass capability is provided for all independent planes, and power, ground and I/O locations come prepinned. \$93.50 for 2-8010A version. Hybricon Corp. 410 Great Rd. Littleton, MA 01460. Phone (617) 486-3174. Circle No 234

PROCESS METER. The CM-35X requires no external supply, drawing its operating power directly from a 4- to 20- or 10- to 50-mA current loop. You can scale the 31/2-digit device to display data in almost any

engineering unit. The 0.48-in. LCD provides a user-selectable trailing zero or a choice of °F or °C descriptors. You can also access other segments of the inactive last digit to display A, E, N or 1. Stackable cases are available (no extra charge) for multiple-meter-array applications. \$75. **Texmate Inc**, 348 S Cedros Ave, Solana Beach, CA 92075. Phone (714) 481-7177. **Circle No 235**



DIVIDER/COMBINER. Model D412M resistor-isolated power divider operates over 8 to 18 GHz with minimum isolation of 18 dB. Insertion loss equals 1 dB max, insertion phase is within $\pm 5^{\circ}$ port to port and amplitude balance is within ±0.2 dB. In power-divider mode, input VSWR measures 1.7 max. In 4-way power-combiner usage. input VSWR to each port equals 1.5 max. Internal resistors have a power rating of 0.25W cw, 1 kW pk. \$175. Delivery, 60 days ARO. Engelmann Microwave Co, Skyline Dr, Montville, NJ 07045. Phone (201) 334-5700. Circle No 236

DIP DELAY LINES. DP14 Series units are available in MIL and commercial versions, both TTL compatible. They are fully encapsulated and come with delay ranges of 10 to 1000 nsec, delay/rise-time ratios of 5:1 and impedances of 50 to 500Ω . Taps are spaced at 10% intervals, and package heights of 0.187, 0.225 and 0.3 in. are available. Operating range spans -30 to +85°C for commercial versions. Approximately \$5 and \$6 (1000) for commercial and MIL units, respectively. Delivery, 10 to 12 wks ARO. **Kappa Networks Inc**, 165 Roosevelt Ave, Carteret, NJ 07008. Phone (201) 541-1600. **Circle No** 237

ISOLATOR CARD. In the presence of 250V commonmode voltages, Model 722 analog-to-analog isolator handles inputs of 25 mV to 100V dc in four ranges with continuous zero and span (gain) adjustments. It provides either a process-current (4 to 20 mA) or dc-voltage (1 to 5, 0 to 1, 0 to 5 or 0 to 10V dc) output. The Span pot has a 10:1 adjustment range. and the Zero pot adjusts from 0 to 25% of maximum input span. Two response options are available: dc to 10 and dc to 100 Hz. From \$160. Delivery, 6 wks ARO. Acromag Inc, 30765 Wixom Rd, Wixom, MI 48096. Phone (313) 624-1541.


Circle No 238

PRESSURE TRANSDUCERS.


Models 204 and 204E feature 5V outputs, <1 msec response, 0.02% repeatability, 0.05% hysteresis and 0.1% nonlinearity. In addition, they have full-scale gauge and absolute pressure ranges of 25 to 10.000 psi and 0 to 14.7 psi vacuum, 10 Ω output impedance and 0.01% max output noise. Model 204 is compensated for both zero and sensitivity shifts arising from temperature variations. Model 204E, from \$320; Model 204, from \$505. Setra Systems Inc, 1 Strathmore Rd, Natick, MA 01760. Phone (617) 655-4645. Circle No 239



CARD FILE. The Micro-File features standard 4-connector backplanes, with all interconnections, ready to go in Multibus systems. It includes aluminum end plates and mounting bars and nylon self-lubricating guides that ease card insertion. Standard files have a 4-card add-on capability; custom units are available with variable card counts and spacings. \$187 for a typical unit. Delivery, 8 to 10 wks ARO. Scanbe Div/Zero Corp, 3445 Fletcher Ave, El Monte, CA 9173l. Phone (213) 579-2300. Circle No 240

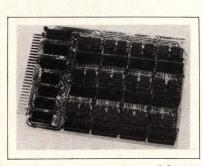

SWITCH CARD. The CS8901 BCD switch panel provides an array of 24 rotary switches (rated for 10,000 detent operations) on a STD Bus-compatible card. Rotors are slotted to permit digit-value selection with a small screwdriver. The card functions like a 12-byte ROM: Each of the 12 address codes selects a pair of digits for reading by the system processor. The -8901 can be I/O mapped via jumpers (with 8-bit addressing) or memory mapped (with full 16-bit addressing). \$275 (10). Circuits & Systems Inc, 2 Main St, Hollis, NH 03049. Phone (603) 465-7063. Circle No 241

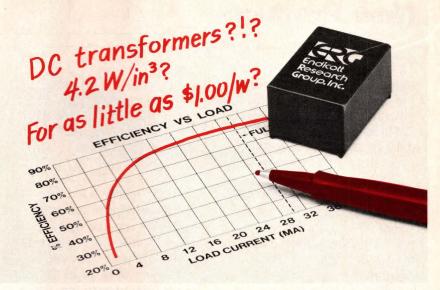

That's right! ERG's DC-to-DC converters power any application up to 25 W, at efficiencies up to 85%. Standard units: 3 W, 6 W, 12 W and 25 W, unregulated. Input range 5-48 V. Output range 5-1,000 V. Others to spec.

Originally designed for gas discharge display activation, ERG converters now find use in a host of applications including high voltage biasing of avalanche diodes, electronic pain killing devices, and miniature lasers for geological study. Send for free data sheet.

Endicott Research Group. Inc. Subsidiary of Endicott Coil Co., Inc. Westview Station, P.O. Box 128 Binghamton, N.Y. 13905 607-798-7846 TWX 510-252-0155

For more information, Circle No 93




THERMOMETERS. This line of panel-mounting thermometers includes Type J and K thermocouple designs (TC-7200) as well as RTD (PT-7600) devices. TC-7200 units have 1° resolution and operate over -180 to +760°C (J) or -50 to +1250°C (K). An optional LED provides °C or °F readout. PT-7600 thermometers work with DIN 100 Ω sensors and offer ranges of -200 to +800°C (1° resolution) or -199.9 to +199.9°C with 0.1° resolution. Readout is in either °C or °F (switch selectable), and both 3and 4-wire sensor connections are accommodated. TC-7200, \$225; PT-7600, \$245. Delivery, stock to 60 days ARO. Caspar Integrated Systems, 541 S Franklin St. Ft Bragg, CA 95437. Phone (707) 964-4109.

Circle No 242

FET AMPLIFIER. Model QCL-5009 operates over 5450 to 5828 MHz and employs three GaAs FETs to achieve 20- to 25-dB gain. Over 0 to 60°C, maximum noise figure equals 3.3 dB. Gain flatness specs at ± 0.5 dB, and input/output VSWR equals 1.35 max. An integral bias regulator is provided, as are input and output isolators to improve matching. The unit measures $3 \times 2 \times 0.76$ in. \$1400 (medium to OEM gty). Raytheon Co, 130 Second Ave, Waltham, MA 02154. Phone (617) 899-8400. Circle No 243

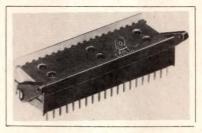ZIF SOCKETS. These zeroinsertion-force DIP sockets are availble in 24-, 28- and 40-pin designs with 0.6-in. centers and with 64 pins on 0.9-in. centers. The normally open contacts are closed with a cam: The last 15° of cam movement provides a wiping action to remove contami-




nation from IC legs. The beryllium-copper contacts are available tin or gold plated. Bodies are 30% glass-filled thermoplastic. Socket height measures 0.45 in. \$2.50 to \$8. **Aries Electronics Inc**, Box 130, Frenchtown, NJ 08825. Phone (201) 996-6841. **Circle No 244**

IR - EMITTING DIODES. MLED93/94/95 Series GaAs units produce a 3- to 7-mW typ infrared output at 9300Å (typ) with a 100-mA input. V_B equals 6V, IF specs at 100 mA, and total power dissipation at T_A=25°C equals 215 mW. The Unibloc TO-92 plastic package facilitates mounting and is compatible with automatic insertion equipment. Suiting industrial processing and control applications such as light modulators, shaft or position encoders, end-of-tape detectors and optical couplers, the diodes, because of their light-dispersion angle, also find use in remotecontrol TV applications. \$0.47 (3-mW output) to \$0.59 (100) (7 mW). Motorola Semiconductor Products Inc, Box 20912, Phoenix, AZ 85036. Phone (602) 244-4556. Circle No 245

DELAY LINES. Units in this family of wide-bandwidth, lowinsertion-loss ultrasonic devices have nominal frequencies ranging from 3.58 to 28.636 MHz. Furnishing delays in the 63- to 128-µsec range, each delay line consists of two proprietary piezoelectric ceramic transducers and a zero-TC glass plate.

As an input electrical signal is applied to the input transducer, its electrical energy is converted into acoustical form. After traveling through the glass plate, it is then converted by the output transducer into an electrical signal with appropriate phase delay. All devices feature approximately 10-dB typ insertion loss, small size (some low-profile units are 0.5 in. high) and -10 to +60°C operatingtemperature range. \$1.50 to \$2.50 (OEM aty). Delivery, stock to 12 wks ARO. Panasonic Co. 1 Panasonic Way, Secaucus, NJ 07094. Phone (201) 348-7282. Circle No 246

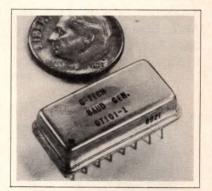

BAUD-RATE GENERATOR. Controlled by a crystal oscillator and suiting modem and datatransmission UART applications. Model QT 101 provides 13 widely used bit rates between 50 and 9600 baud and can control as many as eight transmission channels. Applying the appropriate logic-level signal to the four Rate Select inputs determines its output baud rate. The unit is fully compatible with MIL-spec environmental requirements, and you can specify frequency tolerance to $\pm 0.01\%$ over 0 to 70°C and to ±0.005% over -55 to +125°C. From \$24.19 (100) for ±0.01%, 0 to 70°C units. Delivery, 12 wks ARO. Q-Tech Corp, 2201 Carmelina Ave, Los Angeles, CA 90064. Phone (213) 820-4921. Circle No 247

Two expositions that lead you to improved electronic manufacturing efficiency.

Stressing the fabrication, assembly, production and testing of PWB/PCBs, Multi-Layers and Microelectronic Devices, these exhibitions feature the nation's outstanding suppliers. For the latest cost-saving manufacturing machinery, equipment, tools, hardware, supplies, materials, and test instruments, be sure to see the 175+ displays and exhibits.

The Exhibition The Conference

Among the timely topics presented by industry leaders are:

PWB chemical processes, materials, assembly, repair; soldering materials and techniques; connections and interconnections; fiber optics applications; hybrid technology.

Testing: Bare-board, in-circuit, functional.

Each program is a technological "bonanza" relating specifically to improved productivity.


Plan now to attend!

	Printed Circuits & Printed Circuits & Microelectronics Exposition *81
	April 1 & 2, 1981 Market Hall, Dallas, Texas Orlando, Florida
	ORGANIZED BY Industrial & Scientific Conference Management, Inc. 222 W. Adams Street, Chicago, IL 60606 (312) 263-4866 Telex 256148
	Industrial & Scientific Conference Management, Inc. 222 W. Adams St., Chicago, IL 60606
	I am interested in
	Name
Coupon Details	Title Company Address
	CityStateZip
bany	Telephone () COPY THIS COUPON FOR YOUR ASSOCIATES B

Cahners Exposition Group Com

Mail for

ICs & SEMI-CONDUCTORS

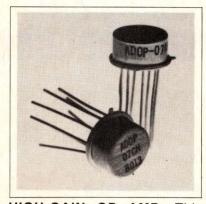

HIGH-GAIN OP AMP. This high-gain version of the standard OP-07 combines a stable offset voltage (as low as $25 \ \mu V \ max$) with an input bias current as low as 2 nA max. Internal frequency compensation and input/output protection eliminate the need for additional components.

The -A version's 3,000,000 (min) open-loop voltage gain is 10 times higher than the standard OP-07's. High input impedance (to 80 M Ω differential and 200 G Ω common mode), a common-mode input-voltage range of ±13.0V min and CMR to 110 dB min fit the unit for noninverting- and differentialamplifier applications.

Five grades are available. The -07A and -07 versions guarantee initial input offset voltages of 25 and 75 μ V max, respectively, and input offset-voltage drifts of 0.6 and 1.3 μ V/°C max over -55 to +125°C. For the E, C, and D grades, the maximum initial input offset-voltage specs are 75, 150 and 150 μ V, respectively. Input offset-voltage drift is pegged at 1.3, 1.8 and 2.5 μ V/°C max, respectively, over 0 to 70°C.

Long-term stability is guaranteed to as low as 1 µV/month max. AD OP-07D, \$4.55 (100). Analog Devices Semiconductor, 804 Woburn St, Wilmington, MA 01887. Phone (617) 935-5565. Circle No 211 EAROM. A 256-bit (64×64) nonvolatile device. Model MN9210 utilizes NOVOL logic and MNOS technology to guarantee 1 yr of data retention in the absence of applied power if temperature is maintained within -40 to +70°C. Additionally, any word can be programmed independently without disturbing the rest of stored data and without removing the circuit. Housed in an 18-pin DIP, the TTL- and CMOS-compatible unit provides latching data and address inputs, 3-state outputs on the data lines, six address inputs, four data I/O lines, a read/write control line, a strobecontrol line, two chip-selectcontrol lines, three power-supply pins and an external capacitor connection. \$28.69 (100). Plessey Semiconductors, 164 Kaiser Ave, Irvine, CA 92714. Phone (714) 540-9979.

Circle No 212




PHASE-CONTROL SCR. A phase-control thyristor that can handle up to 3500V and provide current ratings of 800 to 1200A, Model T9GO minimizes the need for series design in high-voltage circuits. Developed for motor and phase controls, VAR systems, power supplies and fusion systems, it provides guaranteed dv/dt of 300V/µsec. Forward voltage drop specs at 1.7V for the 1200A unit. Other features include gate current of 200A with soft gate control,

0.023°C/W junction-to-case thermal impedance and surgecurrent capability to 27,000A. The device's power disk package allows for single- or double-sided cooling. The unit can be matched for series or parallel operation, and it's available with factory-assembled air- or water-cooled heat exchangers. \$540 (100) for 3500V, 800A unit. Delivery, 10 to 12 wks ARO. Westinghouse Electric Corp, Youngwood, PA 15697. Phone (412) 925-7272. Circle No 213



PAL DEVICES. Additions to the company's programmable-arraylogic Series 20 family, PAL16X4 and -16A4 can perform arithmetic functions such as addition. subtraction, greater than, less than, between limits and equality. Exclusive-OR gates and gated feedback allow the devices to perform counting and logic functions without consuming an excessive number of product terms. The dedicatedparallel-carry feature in the -16A4 permits parallel addition and subtraction. Suiting implementation of 4-bit up/down counters with shift, program counters and between-limits comparators, the units can be programmed on conventional PROM programmers. Propagation delay time equals 40 nsec max, specified over the voltage and temperature range. Clocked-to-output delay time equals 25 nsec. \$39 (100). Monolithic Memories Inc, 1165 E Argues Ave, Sunnyvale, CA 94086. Phone (408) 739-3535. TWX 910-339-9229. Circle No 214

COMPUTER-SYSTEM SUBASSEMBLIES

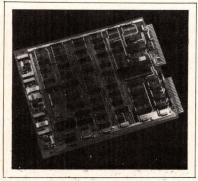


PERIPHERAL BOARDS. Compatible with the Micronova board-computer (MBC) line and the MP/100 and -200 μ Cs, these boards include an analog and digital I/O interface, a video interface, a RAM/EPROM board and an I/O CMOS memory board.

Model 4335-S analog and digital I/O interface board joins with the company's MBC/2 or MBC/3 to form a 2-board intelligent instrument system utilizing FORTRAN or PASCAL and providing the same computing power as a full Nova computer under the MP/OS operating system. It furnishes 16 I/O lines with handshaking signals and operates under programmed-I/O control. The analog input port includes four single-ended channels and four on-board test channels that measure analog signals with 10-bit resolution. One channel of analog output is also provided.

Model 4337-S video interface generates upper- and lowercase alphanumerics on a video monitor and links to an ASCII keyboard.

Extending PROMable capabilities to the MP/200, the RAM/EPROM board comes with 8k bytes of RAM and 32k bytes of EPROM (Model 8688) or with 32k bytes of RAM and 32k bytes of EPROM (Model 8689). Model 8316 I/O CMOS portable memory board furnishes as much as 16k bytes of nonvolatile memory. Model 4335-S, \$800; Model 4337-S, \$750; Model 8688, \$630; Model 8689, \$1260; Model 8316, \$800 (4k bytes) to \$1900 (16k bytes). Delivery, 90 days ARO. **Data General Corp**, Rte 9, Westboro, MA 01581. Phone (617) 366-8911. **Circle No 215**

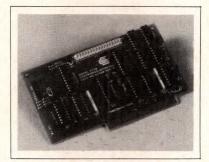


PRINTER INTERFACE. Interfacing Apple II computers to a variety of printers using Centronics-type parallel interfaces, including the Okidata Microline 80, the Microtek MT-80P and the Micro Peripherals 88T, Model 7778 has an on-board 256-byte ROM that provides driver firmware and controls ASCIIcharacter output to the printer. The driver responds to standard Apple II printer commands for selection of command characters, number of characters per line, auto feed and video echo. A **ROM/RAM jumper allows ROM** replacement by RAM. Residing in any Apple II peripheral, the board supports the interrupt daisy chain with arbitration logic (including jumper-selectable IRQ generation) and provides DMA daisy-chain pass-through. An 8-bit data-output bus, four status inputs, Data Strobe and Acknowledge handshake signals and a Reset signal are also provided. \$119.95. California Computer Systems, 250 Caribbean Dr, Sunnyvale, CA 94086. Phone (408) 734-5811. TLX 171959. Circle No 216




A/A CONVERTERS. Series 1800 analog-to-analog signalconversion modules, designed for use as the front ends of analog I/O boards, accept real-world inputs and produce high-level single-ended signals for A/D subsystems. Linearization is standard for RTD inputs and optional for thermocouples. Card cages are available in 4-, 8or 16-model versions with screw terminals for field wiring. All units feature 1500V (breakdown) isolation, 120-dB typ CMR, low-pass-filter options, LED status indicators and 0 to 70°C operation. From \$135. Delivery, 8 wks ARO. Acromag, 30765 Wixom Rd, Wixom, MI 48096. Phone (313) 624-1541. TLX 230505. Circle No 217

MEASUREMENT / CONTROL CARDS. For applications such as batch processing and equipment control with HP 1000 Series uCs. L Series L measurement and control cards are programmable either in the HP 1000 real-time executive operating system or via assembly language. A high-level analog-input card features an 8-channel differential input (expandable to 40 channels) capable of as many as 55,000 readings/sec with 12-bit resolution. Solid-state differential multiplexers permit data acquisition using four programmable

full-scale ranges from ± 1.28 to $\pm 10.24V$. A digital-input card provides 16 fully isolated inputs with resistor-programmable threshold levels, as well as 16 relay outputs (1A at 28V dc or 0.5A at 120V ac). A second digital card furnishes nonisolated 16-bit I/O plus a separate 4-bit control and status register. \$600 to \$1500. **Hewlett-Packard Co**, 1507 Page Mill Rd, Palo Alto, CA 94304. Phone local office. **Circle No** 218

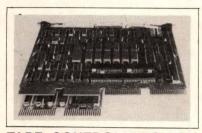

TAPE CONTROLLERS. The T04/T34 family functions with DEC LSI-11 and PDP-11 computers and is TM11/TU10 compatible. Units require one quad board for NRZI mode (PDP-11 or LSI-11); for PE mode, a dual-size PE board is added, drawing 5V and ground from the back panel of the host minicomputer but not using any of the back panel's bus signals. Operating with industry-standard tape drives and providing a 64-byte buffer, the controllers support any combination of 7- or 9-track NRZI or dual-density drives; as many as four drives can be daisy-chained to one controller. 7-track units can operate in NRZI mode at 200, 556 or 800 bpi; 9-track drives, in NRZI mode at 800 bpi or in PE mode at 1600 bpi. Drive speeds to 125 ips are supported. Single-density model, \$2600; dual-density version (quad board plus dual board), \$3300. Dataram Corp, Princeton-Hightstown Rd, Cranbury, NJ 08512. Phone (609) 799-0071. Circle No 219

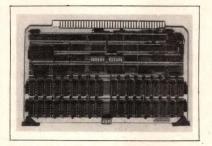


RAM BOARD. Available in 16k. 32k, 48k and 64k versions, Model MM-6800D is a 64k×9 module designed for 2-MHz Exorciser I or II operation. It provides even parity with jumper-selectable outputs and two switch-selectable refresh modes for cycle stealing and hidden refresh. Module selection is decoded in 4k-byte increments by setting the lower and upper limits of a DIP switch. With a write-protect switch to safequard any 8k block or the entire memory, the board uses 5 and 12V supplies and dissipates <7W. \$600 for 64k×9 version. Micro Memory Inc, 9434 Irondale Ave, Chatsworth, CA 91311. Phone (213) 998-0070. Circle No 220



PRINTER INTERFACE. Model 125 single-board interface allows DEC LSI-11 systems to use any of the company's electrostatic plotters or printer/plotters, I/O multiplexers, hard-copy controllers or vector-to-raster converters. Plugging into the computer mainframe or I/O expansion chassis and operating

under direct program control or DMA, the interface is electrically and mechanically compatible with the PDP-11/03 and -11/23 and the LSI-11/2 and -11/23 systems, and with the LP-11 line-printer drive. Supporting all printer/plotter functions, it permits printing speeds to 1000 lpm and plotting speeds to 34 ft²/min and can be located as far as 54 ft from the LSI-11. The package includes an RT-11 print/plot driver that allows transfer of print, plot, SPP, remote-function and vector-to-raster-converter data to the unit and a software-test exerciser. Source and object codes are supplied on an RXO1-compatible diskette. \$1600. Delivery, 90 days, ARO. Versatec, 2805 Bowers Ave. Santa Clara, CA 95051, Phone (408) 988-2800. TWX 910-338-0243. Circle No 221

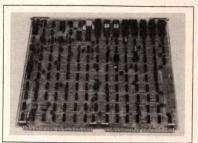

PRINTER CONTROLLER. The μP-based Model VIP-201 plugs into one slot of any Data General minicomputer. Capable of controlling any mix of three Dataproducts- or Centronicsinterface-compatible line printers or the 300-lpm Teletype Model 40 printer, it provides driving capability as great as 2000 ft when used with the Model 40 via its SSI interface. Built-in self tests independent of the CPU furnish line-printer-subsystem diagnostics. \$2400; 1-printer version, \$1900. Delivery, 30 to 60 days ARO. Vetra Systems Corp, Box 714, Melville, NY 11746. Phone (516) 454-6469. Circle No 222




SYNCHRO CONVERTER. Employing Type II servo loops designed to follow input-shaft velocities as high as 1800° /sec (300 rpm), the 16-bit Model 168H100 synchro- or resolver-to-digital unit provides 1.3' accuracy over its full temperature range. It maintains this performance despite $\pm 10\%$ signal- and reference-amplitude


variations, $\pm 10\%$ power-supply variations, input-shaft velocities to 1800°/sec, as much as 10% harmonic distortion and 40° phase shift between reference and input signals. Inputs are balanced to $\pm 1\%$, and 60- or 400-Hz operation requires no external transformers. \$695 for commercial (0 to 70°C) unit; \$795 for military-range (-55 to +105°C) version. **Control Sciences Inc**, 9601-1 Owensmouth Ave, Chatsworth, CA 91311. Phone (213) 709-5510.

Circle No 223

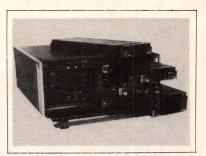A/D CONVERTER. For use in automatic test systems, the multiplexing 8-channel Model 8608 can perform as many as 5000 measurements/sec. Resolution equals 12 bits in three bipolar ranges (100 mV, 1 and



10V), and autoranging is provided. Timing capability allows measurements to be taken continuously or on multiple trigger commands. Fully compatible with the IEEE-488 bus, the module can store high-speed readings for later readout and can be programmed to operate in four different modes (single channel, single channel burst, autoscan and autoscan burst). \$895. Jaycor, Box 370, Del Mar, CA 92014. Phone (714) 453-Circle No 224 6580.

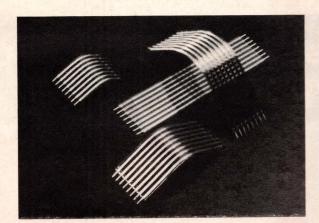

FLEXIBLE HORIZONTAL JUMPERS

- Reduces assembly costs, improves reliability
- Plug-in or solder to PCB
- Many standard sizes on .050" and .100" centers
- Custom sizes and designs at low cost

BUCKBEE-MEARS COMPANY DMC Precision Components Group NASHUA DIVISION 100 NORTHEASTERN BLVD. NASHUA, NEW HAMPSHIRE 03060 (603) 883-5541

For more information, Circle No 96 EDN FEBRUARY 4, 1981



It's only because we've had other important things to talk about—like how our Variable Height Brite-Lites are visibly brighter and how our Super Brite-Lites give you 25 times more brightness.

But now it's time to end the low profile on our Low Profile Brite-Lites. First, you should know they snap into panels as thin as .031 inch without needing snap rings or lock nuts. No hardware is required. They are available in either standard or Super-bright models and designed to last more than ten times longer than incandescents while using half the power.

There's a lot more you should know. For the full story that will end the low profile on our Low Profiles, call today TOLL FREE (800) 421-6815. Within California, call (213) 674-5940.

Proven better and brighter than the rest



303 North Oak Street Inglewood, CA 90302 TWX 910-328-7205

COMPUTERS & PERIPHERALS



HARD-COPY UNITS. Models 4611 (for storage-tube displays) and 4612 (for raster-scan video sources) use a dry carbon toner and an electrostatic process to produce permanent copies on 8½×11-in. dielectric paper. The paper looks and feels like plain bond and permits pen or pencil notations.

Each roll provides approximately 540 hard copies for approximately \$0.02 per sheet and \$0.03 per copy (including toner). Both units deliver vertical-format copies in 24 sec; image size is approximately $7\frac{1}{2} \times 5\frac{3}{4}$ in.

Dot density equals 256 dots/in. horizontally, 171 dots/in. vertically. The dots overlap 67% horizontally and 47% vertically.


Options for the 45-lb, 7.135 \times 20.65 \times 16.75-in. units include a 4-channel multiplexer and foreign-operation capabilities. \$4400. **Tektronix Inc,** Box 500, Beaverton, OR 97077. Phone (503) 644-0161.

Circle No 187

CRT TERMINAL. A blockmode/editing video-display unit, the μ P-based Model 550S provides three operating modes for conversational time sharing, transaction processing or text manipulation/software development. Its 24-line screen acts as a movable window accessing 48 80-column lines of memory. In Transaction Processing mode, the optional second page of scrolling memory can store a second page of a form, called up automatically when an operator tabs off the first page. The standard 83-key keyboard includes a multifunction numeric pad and four (shiftable to eight) program-function keys. Also standard is an ASCII serial printer port and an X-On/X-Off host control over terminal block transmissions and field attributes for half-intensity, blink, nondisplay and protected modes. \$1189. Perkin-Elmer Corp. 360 Rte 206 South. Flanders, NJ 07836, Phone (201) 229-6800. Circle No 188

MODEL MDS-75

STANDARD UNIT PRICES \$15000 1-9

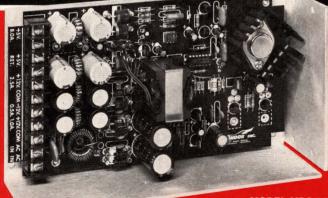

MODEL MDS-75

Key specifications:

Standard outputs: ± 5 VDC 1.6 to 8 A, ± 12 VDC .5 to 2.6A (3.3 A pk), ± 12 VDC .06 to .3 A, ± 12 VDC .2 to 1 A Line Regulation, main output: $\pm .2\%$ for a 10% line change Load Regulation, main output: $\pm .3\%$ at 20% to 100% load OVP: 6.2 $\pm .4$ V on 5 V output See Condor power supplies in Thomcat, EEM and Goldbook.

NOW'S THE TIME TO SWITCH- MOVE YOUR TAIL TO ... 4880 Adohr Lane • Camarillo, California 93010 • (805) 484-2851

Here it is, Condor's new MDS-75 open frame switcher, the switcher that allows you to purchase the equivalent of a custom supply without paying custom supply prices. How do we do it? Simple. A specially designed factory adjustment to standard units allows you to custom specify your output voltages at the time of purchase, within the supply's power range of 75W continuous.

An unusual feature is purchasers can also order the MDS-75 with either standard terminal blocks or Molex connectors at no additional cost.

Order yours now. And ask about the other brand new Condor switchers at comparable prices, 15W to 300W.





CALCULATOR PERIPHER-ALS. Interfacing directly to TI-59 and -58 calculators, these module-selector switching devices hold as many as four TI Solid State Software libraries, enabling a user to select and execute any routine in any module without turning off the calculator and removing a library. The manual-selector version features a 4-position switch that can be rotated to select the desired module. Fitting the battery well of the PC-100 printer, the switch can interface to the 59/58/PC-100 combination or to the calculator alone. The automatic-selector model accesses each library under program control. Capable of running a continuous program of up to 20,000 steps, each unit includes four LED lamps that indicate which module is being accessed. Manual selector, \$99.95; automatic selector, \$199.95. American Micro Products Inc, 705 N Bowser, M/S 107, Richardson, TX 75080. Phone (214) 238-1815. Circle No 189

CRT TERMINAL. The ADM-5 Dumb Terminal provides visual attributes such as reverse video, reduced intensity and reverse video/reduced intensity; limited editing capabilities (erase to end of line or page); and a gated extension port for selective



transmission of data to any serial RS-232C peripheral device. It also features a teletypewriterstyle keyboard, a built-in numeric keypad, separate cursor-control keys and a full upperand lower-case 12-in.-diagonal character display with 2-dot descenders as standard. Characters are displayed as a 5×9 dot matrix in a 7×10 dot-matrix field. A Program-mode key permits writing into the display memory as well as the display of



Introducing LED sockets with built-in resistors

These new sockets eliminate costly re-soldering when changing LEDs. Just pull one out. Plug a new one in. It accepts all T 1³/₄ discrete LEDs, plus our ultra-wide dispersion LEDy-Bug[®]. The price is the same for any voltage from 3.5 to 28 V-dc.


It takes more than brightness to be best. And the socket with a built-in resistor from Data Display Products proves it. We'd like to tell you how we can help brighten up your bottom line. Call today TOLL FREE (800) 421-6815. Within California, call (213) 674-5940.



303 NORTH OAK STREET, INGLEWOOD, CA 90302 TWX 910-328-7205

all control codes. The terminal operates asynchronously in halfor full-duplex modes at any of 11 data rates from 75 to 19.2k bps. \$995. Lear Siegler Inc, 714 N Brookhurst St, Anaheim, CA 92803. Phone (800) 854-3805; in CA, (714) 774-1010.

Circle No 190

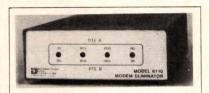

MODEM ELIMINATOR. Permitting the interconnection of data-terminal equipment without modems, Model 6110 can be used in either synchronous or asynchronous mode and with terminals configured for half- or full-duplex operation. Replacing two back-to-back short-range modems, it furnishes internal strap selection of constant or controlled RTS, four selectable RTS/CTS delays, an internal or external clock and nine clock rates ranging from 1200 to 19,200 bps. The DTE interface conforms to RS-232C and CCITT V.24 specifications. Data-terminal equipment can be located as far as 50 ft from the unit (allowing a maximum separation of 100 ft between terminals); a long-distance cable provides maximum separation of 500 ft. \$350. Delivery, 60 days ARO. International Data Sciences Inc, 7 Wellington Rd, Lincoln, RI 02865, Phone (401) 333-6200. TWX 710-384-1911. Circle No 191

FORTRAN IV PACKAGE. FORT/LIFT provides major functional extensions to FOR-TRAN IV. Running on virtually all minicomputers and microprocessors that support FORTRAN, it

FORTRAN-IVincorporates callable subroutines and features character-string and -substring functions, including string comparisons, moves, fills, searches, deletions, insertions and replacements (all functions that operate on variable-length character strings/substrings). plus a disk function that can sort files on up to five variable-length sort keys (numeric or character strings). Universal machine independence is achieved by isolating the few machinedependent functions into usersupplied primitive routines. \$199 on cards or paper or magnetic tape. Software '70, Box 3623, Anaheim, CA 92803. Phone (714) 992-2230. Circle No 192

DISK DRIVE. For the company's 6809 Series Chieftain smallbusiness computers, this double-track, double-density, double-sided 51/4-in. flexible-disk drive provides 1.5M bytes of formatted storage capacity in its standard dual-drive configuration. Recording density specs at 5877 bpi, and the unit provides 80 tracks per side, 96 tpi. Track-to track access time equals 3 msec. \$4075. Smoke Signal Broadcasting, 31336 Via Colinas, Westlake Village, CA 91362. Phone (213) 889-9340. Circle No 193


IMPACT PRINTER. Designed to operate with Apple μ Cs, the IMP2-Apple permits all printer functions to be activated by single commands. Thus, one command can initiate the printing of a screen's contents and control the printing format. Compatible with the PASCAL operating system, the ultralowprofile unit is equipped with both friction and tractor feeds to provide 3-way forms handling:



single sheet, roll paper and fan-fold. It can print 80, 96 or 132 columns of hard copy (throughput, 1 lps). The 7×7 dot matrix furnishes the standard ASCII character sets optional), and the printer can handle user-defined as well as high-resolution graphics under software control. \$895. **Axiom Corp**, 5932 San Fernando Rd, Glendale, CA 91202. Phone (213) 245-9244. TWX 910-497-2283.

Circle No 194

DISPLAY. Providing 79% more active screen area than standard 80-column displays, the 132column Model 5210 large-screen unit serves data-processing, text-editing and communications applications. Its 15-in.-diagonal screen displays 33 lines of 132-column text (4356 characters). An optional screen buffer memory stores an additional 33 lines and provides both up and down scrolling. Other features include 96 upper- and lowercase full-sized 5×8 dot-matrix ASCII characters; character highlighting including dual intensity, blink, reverse video and underscore; direct cursor positioning; seven cursor-control functions; 32 graphics characters; and functions for horizontal and vertical forms ruling. The unit's detached typewriter keyboard has a 15-key data-entry pad and 18 function keys; a datacomm interface provides eight switch-selectable speeds from 300 to 38,400 bps. \$4500. Delivery, 150 days ARO. Data General Corp, Rte 9, Westboro, MA 01581. Phone (617) 366-8911. Circle No 195

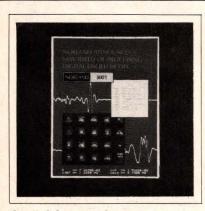

Acquiring and displaying waveforms

A 10-pg brochure details the capabilities of Model 3001 processing digital oscilloscope. Claiming that the firm has increased A/D resolution, improved internal and peripheral storage capability, enhanced output annotation and expanded

diagnostic capability over an earlier model, it outlines the advantages that processing offers in a digital scope. Finally, it provides specs for the scope's acquisition modes, data memory, frequency response, dc offset and trigger functions. Norland Corp, Rte 4, Norland Dr, Ft Atkinson, WI 53538. Circle No 196

Illustrated data on strain gauges

A guide to the theory and application of strain gauges, a 46-pg handbook details the fundamentals of stress and strain, the relationship between strain and resistance, the Wheatstone Bridge, bridge-



sensitivity adjustment and temperature effects. With line drawings, schematics, charts and tables, it provides data on foil strain gauges and gaugesystem selection. BLH Electronics, 42B Fourth Ave, Waltham, MA 02254.

Circle No 197

Write for EDN

Industry recognition and professional satisfaction can both be yours when your work is published in EDN. And there's a financial benefit, too: We pay an honorarium of \$30 per magazine page upon publication of a featurelength article.

Have an idea for an article? Want to share that idea with more than 110,000 of your fellow design engineers? Call Walt Patstone, Editor, at (617) 536-7780 or send an outline/abstract to



Want some tips on how to write for EDN and other technical publications? Circle No. 167 for a free Author's Guide.

EDN: Everything Designers Need

The Two-in-One LEDs Now Come In Ten

Styles

Our popular two-in-one LEDs. that give you two super-bright LEDs in a single enclosure, are now available in ten different styles: bi-pin; midget flanged; discrete; vertical and horizontal printed circuit board types; snap-in; and, basic cartridge style (some styles have more than one variation).

With an installed cost less than two separate lamps, these unique LEDs feature electronic isolation of the LED circuits and allow for different resistor values within the single enclosure. All are available with green or red output in a two terminal package. The cartridge style is available in red/amber, red/ green or amber/green in a four-terminal package.

From Data Display. The world's leader in LED panel lights. Call today TOLL FREE (800) 421-6815. Within California, call (213) 674-5940.



303 North Oak Street, Inglewood, CA 90302 TWX 910-328-7205

For more information, Circle No 101



Investigate cableconnector devices

Specs for components in the Scotchflex cable-connector system for mass termination cable, connectors, assembly equipment and accessories make up an 85-pg catalog. It describes socket, plug, pcboard, DIP, delta, delta-ribbon and card-edge connectors and

No Supply Power Supply Specifier Specifier Buyer Buyer Buyer Buyer Should be Should fit. Uithout It. See It In See I

headers. A cable/connector mating guide is included. In addition, the catalog outlines the Scotchflex breadboard system, which is claimed to enable a user to go from a finished design to operative prototype in half the time required by standard wire-wrapping or hand-soldering methods. **3M Co**, Box 33600, St Paul, MN 55133. **Circle No** 198




Choose from a variety of filters

Catalog 17F presents a line of custom-built LC filters for frequencies from 20 Hz to 400 MHz. It describes bandpass, band-reject, linear phase, highpass and low-pass filters and the VCL Series of delay-equalized NTSC low-pass devices for video use. A glossary of filter terms begins the 24-pg brochure. **Allen Avionics Inc**, 224 E 2nd St, Mineola, NY 11501. **Circle No** 199

Reference data for the communications industry

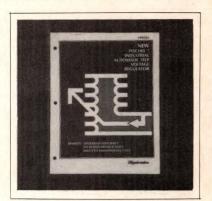The 350-pg "Data Communications Standards Library" describes six EIA RS standards, four EIA industrial bulletins, IBM's Binary Synchronous Communications protocol and ATT's Advanced Communications Service host and terminal functional interface. \$85. **Remark International**, 4 Sycamore Dr, Woodbury, NY 11797. **INQUIRE DIRECT**



Uses for a step voltage regulator

Highlighting the Peschel industrial automatic step voltage regulator, a 12-pg brochure details its operation, sizes, ratings, response speed and reliability. It also outlines applications for the unit, including magnetic devices, motors, distribution equipment, rectifier loads and resistance heating. A spec table lists data on type of connection, voltage, dimensions and weight for 33 standard models. **Hipotronics Inc,** Drawer A, Brewster, NY 10509.

Circle No 200

Customer evaluations of teleprinters

Providing a summary of user experiences with 10.657 installed teleprinter terminals, a 40-pg report contains specs and prices for 125 teleprinter terminals from 50 vendors. It addresses the pros and cons of using teleprinters vs alphanumeric display terminals, the tradeoffs between impact and nonimpact printers, printer types and trends and the anticipated growth of the teleprinter industry. Survey results include ratings for ease of use, keyboard feel, print quality, hardware reliability, maintenance service and overall satisfaction. \$15. Datapro Research Corp, 1805 Underwood Blvd, Delran, NJ 08075. **INQUIRE DIRECT**

EDN Product Mart

This advertising is for new and current products.

Please circle Reader Service number for additional information from manufacturers.


WRITE OR CALL FOR SAMPLE



Put a low cost temperature gauge on everything.

The center spot on a Tempilabel[®] Temperature Monitor turns black when the surface to which it is affixed reaches the specified temperature for that label. Reliable Tempilabel[®] monitors are available with single spots or with multiple spots with pre-determined increments of ratings for monitoring safe operating temperatures. Tempilabels[®] are self-adhesive and may be removed and attached to reports for permanent records. Temperature ranges: 100°F (33°C) to 600°F (316°C). 1% accuracy guaranteed. Monitors with 1, 4, 6 or 8 ratings on each with various increments. Priced as low as 10¢ each. Write or call for free sample. Circle number below for catalog & prices.

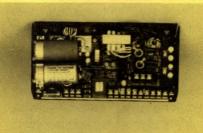Division, Big Three Industries, Inc. So. Plainfield, NJ 07080. (201) 757-8300. Telex 138662. For more information, Circle No 102



200 WATT SWITCHING POWER SUPPLY

New line of 200 watt triple output switching power supplies is already UL recognized. A triple output model $20E5^{+}\pm12$ delivers 5V at 30 amps and ±12 or $\pm15V$ at 1 amp. All units are available from stock. Features include a dual AC input 100-132/200-260VAC, line and load regulation of 0.2% and 0.3% respectively overvoltage protection, and 16ms carryover. Size is 4.92" X 10.5" X 2.25". Prices start at \$240. For applications assistance and Data Sheets call (213) 707-0120. NORTEL, 31149 Via Colinas—Bidg. 608, Westlake Village, CA 91361.

For more information, Circle No 103




To advertise in Product Mart Call Joanne Dorian 212/949-4445




LOW COST AD-MU MAGNETIC SHIELDS. Easily, quickly cut with scissors and shaped by you from AD-MU foil alloys. Available in various widths, lengths, shielding strengths. Time-saving, cost-saving, convenient. No waiting. No designing, tooling or fabricating costs. Ideal for R/D, hard-to-get-at places, or for small quantity or extremely compact applications. One formula (ask us) determines thickness and number of layers. Fully annealed, ready to use. AD-VANCE MAGNETICS, INC., 625 Monroe St., Rochester, Indiana 46975, (219) 223-3158.

For more information, Circle No 106

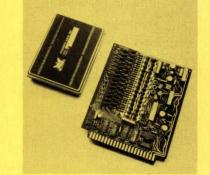

ADC 2000/2100 16-BIT A/D CONVERTERS for airborne, other critical applications. Resolution of ADC 2000/2100 series is 1 part in 65,535—16 binary bits or 2's complement; power consumption only 500 mw; accuracy: ±0.004%; linearity: ±0.002%; output control functions CMOS/TTL-LS compatible with any system. Tested, calibrated, system-ready except for power supply. ADC 2000: P.C. Card; ADC 2100: Encased. PHOENIX DATA, INC., 3384 W. Osborn, Phoenix, AZ 85017. PH 602/278-8528.

For more information, Circle No 104

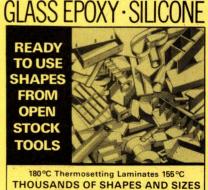

THOUSANDS OF SHAPES AND SIZES Potting Forms • Header Plates • Copper Lined Bobbins • Coil Forms • Tubes • Battery Cases PCB Stiffeners • Rods • CKT Card Holders Excellent Shock Resistance, Machinability, Strength MIL Spec. and UL Certs.

STEVENS TUBING CORP. SUBSIDIARY OF STEVENS PRODUCTS, INC. 128 North Park St., East Orange, N.J. 07019 Established 1937 (201) 672-2140

For more information, Circle No 105

To advertise in Product Mart, call Joanne Dorian, 212/949-4445

EDN Sales

H Victor Drumm Executive Vice President and Publisher Boston, MA 02116 (617) 536-7780

NEW YORK CITY 10017 George Isbell, Regional Manager Bill Segallis, Regional Manager 205 E 42nd St (212) 949-4423

BOSTON 01880 Richard Parker, Regional Manager Hal Short, Regional Manager 1 Lakeside Office Park Wakefield, MA 01880 (617) 246-2293

PHILADELPHIA 19087 Steve Farkas, Regional Manager 999 Old Eagle School Rd Wayne, PA 19087 (215) 293-1212

CHICAGO 60521 Clayton Ryder, Regional Manager Charles Durham, Jr Regional Manager 15 Spinning Wheel Rd Hinsdale, IL 60521 (312) 654-2390

CLEVELAND 44115 Charles Durham, Jr Regional Manager 1621 Euclid Ave (216) 696-1800

DENVER 80206 John Huff, Regional Manager 270 St Paul St (303) 388-4511

SAN FRANCISCO 95008 Hugh R Roome, Vice President, Jack Kompan, Regional Manager Sherman Bldg 3031 Tisch Way, Suite 1000 San Jose, CA 95128 (408) 243-8838

LOS ANGELES 90036 Charles J Stillman, Jr Regional Manager 5670 Wilshire Blvd (213) 933-9525

IRVINE 92715 Ed Schrader, Regional Manager 2021 Business Center, Suite 208 (714) 851-9422

TOKYO 106 JAPAN Tomoyuki Inatsuki TRADE MEDIA JAPAN INC R212, Azabu Heights 1-5-10 Roppongi, Minato-ku Tel: (03) 585-0581 Telex: J28208 MEDIAHS

CAREER OPPORTUNITIES Eastern US Kathy Huestis 221 Columbus Ave Boston, MA 02116 (617) 536-7780 Western US Diane Smith 5670 Wilshire Blvd Los Angeles, CA 90036 (213) 933-9525

Literature



Select data-processing supplies and services

"The Easy Reference to Essential Data Processing Supplies" is a guide for specifiers of diskettes, disk packs, printer ribbons, labels, data-processing forms, terminal stands, data workstations, cables and a variety of products and services. It features compatibility charts to match data-access and -processing systems with appropriate products. **American National Supply Corp**, 1243 W 134th St, Gardena, CA 90247.

Circle No 201

Applications data for microcomputer line

This collection of microcomputer literature includes the "PIC Series Microcomputer Data Manual," which describes the family's architecture, instruction set, electrical specs and support hardware and software. Another manual details commonly used software routines, while a third highlights the PIC Field Demo System, a pc module used to demonstrate and test an application program before it's committed to masked ROM. Other brochures outline features of an in-circuit-emulation system and a cross assembler. Microelectronics Div General Instrument Corp, 600 W John St, Hicksville, NY 11802. Circle No 202

Study advanced TRS-80 interfacing techniques

TRS-80 Interfacing-Book 2 introduces advanced interfacing techniques that permit an operator to accomplish realworld tasks with the TRS-80 computer. For example, the 256-pg book details how to drive high-current and high-voltage loads, generate voltage and current signals, measure unknown voltages and currents and use remote-control circuits. It explains how to use the latter circuits to allow the computer to control universal asynchronous receiver/transmitter chips, A/D and D/A converters and other devices located some distance from the unit. Included are complete software examples. \$9.95 (softbound). Howard W Sams and Co Inc, 4300 W 62 St. Indianapolis, IN 46268. INQUIRE DIRECT



A look at computer storage peripherals

A monthly review of industry and market developments in storage peripherals, "Random Access Int'l" looks at data streaming in its first issue. The newsletter covers rigid- and flexible-disk drives, tape drives and associated magnetic media, component requirements and new storage technologies. \$240 annually; \$264 outside US. **RAI Publishing Inc,** 4943 Bosworth Ct, Newark, CA 94560.

INQUIRE DIRECT



Options in choosing circular connectors

A 36-pg catalog features a line of standard circular connectors. The selection auide furnishes data on environmental capabilities, wire gauges, plug and receptacle requirements, shelltype needs (solid or split), socket locations and finish options. A chart summarizes the range of available circular-connector styles-wall, cable and box receptacles, plus straight, quickdisconnect and angle plugsand cross-references them by insert number. Amphenol North America, 2122 York Rd, Oak Brook, IL 60521. Circle No 203

How to utilize disk- and tape-storage subsystems

Outlining hardware, software and system considerations for connecting disk- and tapestorage subsystems to DEC computers, the "Peripheral Controller Handbook" includes illustrations and comparison tables. Section I discusses disk controllers and provides data on disk drives and subsystems, hardware design, and microcode implementations, as well as software considerations. Section II describes tape controllers and features device-selection considerations. Emulex Corp, 2001 E Deere Ave, Santa Ana, CA Circle No 204 92705.

Characteristics of manual switches

A 148-pg catalog describes a line of pushbutton, toggle, rotary-selector and interlock switches. Catalog 30's 4-pg selection guide provides panelarea, display, illumination, behind-panel-depth, mounting, termination, sealing, electrical and circuitry data. Mounting drawings, cutaways and expanded views accompany all product descriptions. Dimensions are provided in English and metric equivalents. Micro Switch, 11 W Spring St, Freeport, IL 61032. Circle No 205



Capabilities of A/Dconversion systems

Performance tables in a 28-pg booklet detail overall accuracy and speed of a family of A/D-conversion systems. The brochure also describes the operation of Model GMC Logic Control Systems, which permit both front-panel and computer selection of input channel address and sequence, and includes operational examples of how to program and interconnect those systems. Lastly, it features a computer-interfacing subsystem for use with the Hewlett Packard 93596L interface system and many DEC and Data General Computers. Preston Scientific Inc, 805 E Cerritos Ave, Anaheim, CA 92805. Circle No 206



For more information, Circle No 107

Utilizing dataacquisition systems


A 12-pg brochure details electrical and mechanical specs for 16- and 8-channel, singleended, 12-bit-resolution, 72-pin miniature data-acquisition systems, Models MDAS-16 and -8D. Block diagrams and app notes explain the capabilities that suit the modules for use in low-level-signal applications involving bridge amplifiers, transducers, strain gauges and thermocouple interfaces. **Datel-Intersil Inc,** 11 Cabot Blvd, Mansfield, MA 02048.

Circle No 207

Overview of optoelectronic devices

Highlighting a line of LED lamps, displays and optoisolators, a 20-pg catalog suggests applications for the products covered and provides data on color options, including green, yellow, orange, red and high-efficiency red. It lists specs on MAN Series LED displays, showing actual digit size for each product and describing 13 display-package styles. It also pictures package sizes for the LED-lamp series and includes specs for luminous intensity at forward current. maximum power and typical viewing angle. For the optoisolator line, the catalog details device size, output configurations, emitter voltage and the detector's minimum output voltage (BV_{CEO}), presenting three package styles. Optoelectronics Div General Instrument Corp, 3400 Hillview Ave. Palo Alto, CA 94304.

Circle No 208

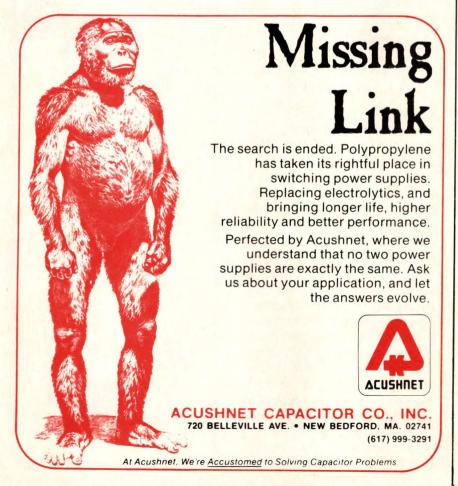

<text>

Choosing uninterruptible power systems

A 12-pg foldout brochure features a 173-point checklist for cost-effective uninterruptiblepower-system evaluation and selection. It enumerates considerations for performing a cost-justification analysis, determining necessary equipment and system features, evaluating prospective suppliers, properly installing a system and ensuring reliable performance. Lortec Power Systems Inc, 5214 Mills Industrial Parkway, North Ridgeville, OH 44035. Circle No 209

Programs and publications on computer graphics

A 32-pg catalog describes computer-mapmaking and supplementary programs, cartographic data bases, and related publications. It outlines nine programs related to computergraphics and geographicinformation systems, including KWIC, a bibliographic processing system; GIMMS, a useroriented thematic mapping system; and MDS(X), a collection of multidimensional scaling algorithms linked under one command language. Laboratory for Computer Graphics and Spatial Analysis, Graduate School of Design, Harvard Univ, 520 Gund Hall, Cambridge, MA 02138. Circle No 210



... in the Big Town

New York... the nation's number one market for electronics... and almost everything else... hosts *Electro/81* on April 7, 8 and 9. It will be the East's biggest high-technology exhibition and convention, featuring:

- 800-plus exhibit booths displaying state-of-the-art products, systems, and techniques.
- 150 Professional Program presentations on leading-edge electronics.


Make your plans now to attend this memorable event at the New York Coliseum (exhibition) and Sheraton Centre Hotel (Professional Program). To take advantage of a pre-registration discount of \$10 (half the door price of \$20), complete and mail the coupon below with your check before March 20. It will also save you time and avoid a long wait in line.

Clip and mail with your check for \$10 to: Electro 999 N. Sepulveda Blvd. El Segundo, CA 90245



April 7 – 9, 1981 New York Coliseum and Sheraton Centre Hotel

A	101	A	Electrical/Electronic Engineering
• (Fk	ectro/81 00000 PRE-REGISTRATION \$10	В	Mechanical/Product Engineering
		C	Test Engineering
	Show & Convention	D	Production/Mfg g Engineering
New York April 7-9	Coliseum 0	E	Engineering Services
Abu i - a		F	Quality Engineering/Control
		G	Purchasing
	Please PRINT as you want shown on badge	H	Sales/Marketing
Name	FIRST OR INITIALS LAST	T	Management
		J	Student/Educator
		ĸ	Other
Position • Telephone	AREA CODE NUMBER (OPTIONAL)	L	Active Components
	AREA CODE NUMBER (OPTIONAL)	M	Passive Components
Company/Organization	NATE OF A DE OF	N	Electro-Mechanical Components
		0	Tools and Production Equipment
Address: Bus. or Home	ž	P	Computers and Peripherals
	OH:	0	Instrumentation/Test Equipment
	Z	R	Control Systems
City, State, Zip Code	STATE ZIP CODE	S	Mechanical/Electronic Packagin
	P. C.	T	Data Communications
Important Note:	To receive your badge in advance, complete this card and mail to arrive no later than March 20.	U	Power Sources
	Or, bring completed card to typist in Registration area during Electro.	V	Other

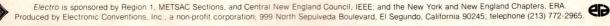



for space reservation contact Kathy Huestis (617) 536-7780

Ask about our combination rates!

ENGINEERS/ MANAGERS

As one of the nation's most respected recruitment firms for high technology industries, we can offer you a wide variety of opportunities, all fees, interviews, and relocation paid by our many national client companies. Some of our most pressing client company needs follow.

Software Engineers, all levels to \$47,000 Hardware Engineers, all levels to \$45,000

Quality Engineers, Electronics to \$37,000 Manufacturing Engineers to \$35,000

Our clients include many of

the "big name" and smaller, fast growing companies in commercial, scientific, the and defense industries, with a specialization in the mini and micro computer fields.

Dick Ray Career Consultants 540 Meadow St. Ext. Agawam, MA 01001 413-789-0907



A Professional Recruiting Agency 620 S.W. 5th-Suite 825 Portland, Oregon 97204

CRITICAL NEED OPENINGS: Engineering Managers (2) to \$40K+ - ECL SCHOTTKY_TTL

Principal Development Engineers (4) to \$42K — Acoustic Data Management

Systems Engineers (4) to \$38K — Marine Related Cabling Systems to \$32K

Shipboard/Off Shore FORWARD YOUR RESUME FOR CONFIDENTIAL CONSIDERATION. OR PHONE:

KEITH NYMAN (503) 222-6461

Our Search fees are Exclusively Employee Paid



Corporate Recruiting Nationwide Electronic SpecialistsDead Ended?Low Salary?No Challenge? Let us work for you Send us your resume or... Call me & let's talk LET US WORK FOR YOU All positions Fee Paid

26949 Chagrin Boulevard • Beachwood, Chio 44122 · 216 / 464-5100

DESIGN ENGINEERS PROJECT ENGINEERS ANALYTICAL ENGINEERS.

As one of the country's leading high technology recruiting firms, we are in an ideal position to represent you in your pursuit of a more challenging career. Although all our fees are paid by our client companies, we dedicate ourselves to finding the unique situation best suited to your capabilities, ambition, and location preferences. While we have specialists in the computer, instrumentation, electro-optics, communication, radar and BCW industries, we cover ALL areas of expertise. Send your resume for a professional, confidential representation throughout the country. All candidates must have current permanent residency or

BAXTER REYNOLDS 179 Allyn St. Hartford, Connecticut 06103 (203) 241-0200

ELECTRONIC ENGINEERS

We have over 50 years experience in placing professionals in all engineering disciplines with a special emphasis on electronic professionals. Your career move should be an A-1 priority. Working with professionals can insure that. Your skills are our trade at Nationwide.

> NATIONWIDE BUSINESS SERVICE 145 State St., Suite 310 Springfield, MA 01103 "in Our 43rd Year"

SOUTHEAST Our 12 Offices in NC, SC, GA and FL specialize in Control Systems, Instrumentation, Electronic Design, and Engineering positions from 18 to 40K. confidential. Fee-Paid 6 Aggressive. service. Send resume to Walt Loescher, BEALL PERSONNEL, P.O. Box 4006ED, Anderson, SC 29622

WIRING DEVICE, SWITCHING OR CONTROLLER			
27 openings Connector Engr to \$33K Switch Engineer to \$30K Wiring Engineer to \$28K 1 year exp. and up to \$26K			
Call Chuck Hensel COLLECT (312) 887-1220 F C INC. P.O. Box 1281 Oakbrook, IL 60521			

SENIOR APPLICATION ENGINEER

Service APPLICATION Engineering Design and implementation of microprocessor base control systems. Requires an MS in Elec-trical Engineering and 24 months experience in designing of peri-mutuel wagering systems. Should have knowledge of Zilog 8000, Intel 8085, and knowledge of establishing com-munications protocol. Salary 18 - 24K, 40 hour week. Send resume to: week. Send resume to: Microtote, Inc. 640 West Rich St. Columbus, Ohio 43215

Systems Engineers Sr. Eng - Micro Processors Based Systems 41K Sr. Eng - A&D, TTL, CMOS, OP, AMPS Sr. Eng - Digital Logic, Displays, Data Tranx to....38K Many positions in Micro Processors based systems Send resume or call Noel P. Rice COLLECT (312) 887-1220 FC INC. P.O. Box 1281 Oakbrook, IL 60521

Who will be first to see into the depths of space?

It could be you and Hughes Electro-Optical and Data Systems.

We built the first long wavelength infrared sensor ever launched into space, and a cryogenic rocket-borne infrared telescope that's sighted hundreds of new celestial objects. Looking earthward, also, our scanners map the globe every eighteen days. In fact, we're making a wide range of electro-optics, fiber-optics, thermal imaging and infrared systems that are like second sight on earth for mankind's benefit and the defense of the nation.

Today, Hughes is one of the nation's largest employers in virtually every engineering, scientific, computer and technical discipline with 1,500 projects and a \$5 billion backlog. Yet, we're decentralized to give you the kind of environments that stimulate innovation and individual recognition.

And our new facility in El Segundo will be a 140-acre city of research and development, manufacturing and testing excellence to help thrust your vision into the future.

Who will be first with the optical and data systems of the future? It could be you and Hughes.

At Hughes Electro-Optical and Data Systems, we'll introduce you to people, ideas and jobs that could change your world. And maybe ours.

It could be you and Hughes Electro-Optical and Data Systems. Call or send resume to: Dept. NDE-2A Hughes Aircraft Company Electro-Optical & Data Systems Group, P.O. Box 913, El Segundo, CA 90245 (213) 616-3374

Current openings:

Test Equipment Design **Designers/Drafters Quality Assurance** Production Industrial Facility CAD/CAM/CAT **Production Control Program Controls** Materials & Processes Systems/Procedures Planners **Electromechanical Packaging Components & Materials** Analog/Digital Design **Computer Science**



HUGHES AIRCRAFT COMPANY

& DATA SYSTEMS

Proof of U.S. Citizenship Required Equal Opportunity Employer



If you worked for GTE in Phoenix, you could have...

sailed in a weekend regatta or enjoyed the quiet scenic beauty of one of the major lakes within an 80 mile radius from downtown Phoenix. These lakes cover 31,130 acres and Arizona ranks #1 nationally per capita in boat ownership. All this ... and GTE too!

If you're a software specialist interested in upgrading your career and your lifestyle, **GTE Automatic Electric Labs** has a position for you. We offer the newest telecommunications technology plus the chance of becoming a contributing member of our team, where professional advancement is limited only by your own initiative.

Positions are available in the following areas if you have a degree and experience in Computer Science, Electrical Engineering or Computer Engineering.

GTE Automatic Electric Laboratories

Research and Development Operating System Software On-Line Recovery and Diagnostic Software Development Support Software Call Processing & Administrative Software Test Utility Software System Test & Control Data Base Development

GTE provides competive salaries, a complete benefits package including relocation assistance and a chance to change the quality of your lifestyle!

Please send your resume or letter of interest to: GTE Automatic Electric Laboratories, Manager of Manpower, Dept. EDN0204, 11226 N. 23rd Avenue, Phoenix, AZ 85029.

An Equal Opportunity Employer M/F/H

GA

LIKE TO REACH OVER 113,000 ENGINEERS.....? THEN PLACE YOUR RECRUITMENT MESSAGE HERE IN......

EDN CAREER OPPORTUNITIES CONTACT: Kathy Huestis 617-536-7780



ENGINEERS Join the Spirit of Emerson. We're part of the Spirit of St. Louis.

If you are interested in career accomplishment in a working atmosphere of constant challenge, you'll like our spirit.

There are more than 3,000 Emerson people now living in St. Louis and take their word for it... St. Louis is a great place to live and raise a family.

Just consider a city with all the advantages of a large metropolis and yet only a short drive from Ozark country with its many rivers, lakes and recreational areas.

Then too, St. Louis is a great sports town. It's strictly big league baseball, football and hockey. And the weather makes it easy to participate in sports such as golf, boating, fishing, bicycling, skating, riding, tennis and much more. Our four-season climate is stimulating without the hardships of extreme heat or cold.

Yes, a great place to live but what about the cost of living? Well, we're below the national average in cost of food, utilities and transportation.

Interested? We're interested in electronics and mechanical engineers at all levels in these areas:

ATE

Coherent/Non-Coherent Design & Development

Software/Hardware Design
 & Development

Product Development

Packaging

• Airborne/GSE Electronics

• Electro/Mechanical Control

RADAR

- Systems Analysts
 - Maintenance Engineers

Plus many other excellent positions available. Why not call or send your resume and see what happens. We think you'll want to Join the Spirit of Emerson.

> Toll Free 1-800-325-0783 Mail Station: 4303 Dept. EDN-02

Electronics + Space Division

EMERSON ELECTRIC CO. 8100 W. Florissant, St. Louis, Mo. 63136 We are an equal opportunity employer in every respect.



AVCO SYSTEMS AVCO PEOPLE A PRODUCTIVE RELATIONSHIP

The rapidly growing AVCO ELECTRONICS DIVISION is a successful division of the billion dollar AVCO CORPORATION. AVCO's people have worked on a variety of projects, including the design and installation of the world's largest and fastest real-time computer data acquisition network systems and the largest hierarchal industrial test system. AVCO ELECTRONICS DIVISION is seeking engineers for various assignments. The varying nature of projects that we design, develop, and manufacture requires that we find that effective combination of technical know-how and "hands-on" experience that will get the job done. AVCO wants to give you stimulating work while producing quality systems.

SYSTEMS HARDWARE ENGINEERS

State-of-the-art techniques give us an edge in the highly competitive field of Computerized Control and Data Acquisition. AVCO has immediate openings for systems engineers with three years experience in digital logic design and mini-computer interface.

A BSEE is required as well as experience in writing proposals to technical specifications and estimating engineering cost.

SYSTEMS SOFTWARE ENGINEERS

State-of-the-art techniques are required by our customers who need custom systems for their application. We need people with two or more years of experience in scientific applications.

Requires a degree in electronics, mechanical engineering, physics, or math and a background in FORTRAN and assembly languages. Programmer/Analysts need experience in real-time process control systems. Distributed processing experience on DEC and MOD-COMP equipment is desirable.

COME TO THE CITY BETWEEN THE MOUNTAINS AND THE RIVER AND LIVE IN AN UNBEATABLE SUNBELT COMMUNITY WITH MULTI-RECREATIONAL AND CULTURAL DIVERSIONS.

FOR CONSIDERATION, CONTACT THE PERSONNEL MANAGER:

ZAVCO ELECTRONICS DIVISION

4807 Bradford Drive Huntsville, AI 35805

Telephone: (205)837-6500 or (800) 633-7202

Equal Employment Opportunity and Affirmative Action Employer

Advertisers Index

Aavid Engineering	
Abbott Transistor	
ACDC Electronics	
Acopian Corp	
Acushnet Capacitor Co Inc	
Advanced Magnetics	
Advanced Micro Devices 110	
Airpax Electronics/Cambridge Div.	
AMPIncorporated	
Amphenol North America	
Amphenol North America, Div Bunker Ramo Corp	42-43
Analog Devices	25 167
Arnold Magnetics	
Autotest	
BMC-Nashua Div	
Boschert Power Supply	
Bowmar ALI	
Burndy Corp	
Cambridge Thermionic Corp	
Ceag Electric Corp	
Condenser Products Corp	
CondorInc	
Converter Concepts	
Dale Electronics Inc	C2
Data Display Products	. 185, 187, 189
Data Precision Corp	
Digital Equipment Corp	
Eaton Corp. Cutler-Hammer	
EDN Caravan	
Electronic Convention	
Electronic Measurements Inc	
Elpac Power Systems	
Endicott Research Group	
Erie Technology Products Inc	
Fairchild Semiconductor Operations Div	
Ferroxcube	
Grand Transformers Inc	
Harris Semiconductor	
Heinemann Electric Co	
Heyman Mfg	
Hewlett-Packard Co	
Hi-G Inc	
Illinois Lock Co	
IMC Magnetics Corp	146
Industrial & Scientific	
Conference	
Intersil Inc	
ITT Cannon Electric	
KEC Electronics Inc	
KepcoInc	
Ledex Inc	
Litronix	

Mallory Capacitor Corp	
Mepco/Electra	
Mini-Circuits Laboratory	3 4 160 170
Motorola Inc	10-11
NEC Microcomputers Inc	
NJE	
Nortel	
OK Machine & Tool	
Paratronics	
PermagCorp	
Phoenix Data Inc	
Power Concepts	
PowerOneInc	
Powercube Corp	
Power/Mate Corp	61
Power Products	
Powertec Inc	
Practical Automation Inc	
Projects Unlimited	
RCA Solid State Div	
RFL Industries Inc	
RSM Sensitron Semiconductor	
Semiconductor Circuits Inc	
Shugart Associates	
Siemens Corp, OEM Div	
Sierracin-Alpha Inc	
	147-154, 172, 190
Signal Transformer Co Inc	64
Silicon General	
Solitron Devices Inc	
Sorenson Co	
Spectrol Electronics Corp	
Sprague Electric Co	
Stacoswitch	
Stevens Tubing	
Superior Electric Co	
Technipower Div	
Tempil	
Texas Instruments Inc	
Trans-Tek Inc	
TRW/Capacitors	
TRW/LSI Products	
Union Carbide Corp	
Xycom Inc	

This index is provided as an additional service. The publisher does not assume any liability for errors or omissions.

Looking Ahead: Trends and Forecasts


\$1.05B resistor market predicted for 1981

Increasing costs, undercapacity, changing technology, overseas competition and recession all contributed to last year's lackluster 7% resistanceproduct market growth and \$956 million in US sales. But the market should do better this year: It's expected to exhibit a 9% growth rate and reach the \$1.05 billion mark. And with a predicted 9.8% compound annual growth rate (CAGR) between 1979 and 1984, total US sales should swell to \$1.4 billion, according to Gnostic Concepts Inc. Menlo Park. CA.

Spearheading market growth, automotive-industry demand is doubling the overall resistormarket growth rate. Sales to car manufacturers—primarily for engine-performance systems should increase from approximately \$40 million in 1979 to approximately \$90 million in 1984.

Resistor networks' performance and package compatibility with ICs will enable them to exhibit an 18% CAGR and capture 18% of the OEM market by 1984. Thick-film technology will dominate, but thin-film devices are also expected to rack up vigorous sales increases.

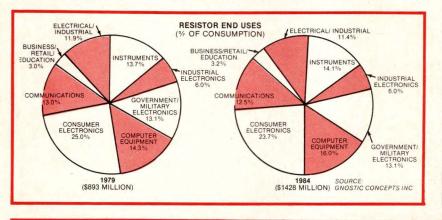
But although advanced IC technology should boost network sales, it will impede trimmers' market share. Because LSI devices and smart linear ICs permit less precise current control and have higher inherent stability, these devices' increased use should soften trimmer demand.



Chip densities to rise at slower rate

Although the electronics industry has become accustomed since the early '60s to a 16-fold increase IC density every 5 yrs, designers should not expect that rate to continue, warns Integrated Circuit Engineering Corp, Scottsdale, AZ.

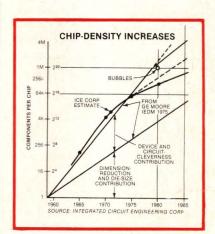Thus, although chip featureand die-size reductions have kept pace with the 16-fold/5-yr rate, the "circuit-cleverness"



5.2M desktop computers worldwide by 1984

No longer low-end products geared primarily to the homecomputer market, increasingly powerful desktop computers now offer up to 192M bytes of on-line storage, multiuser capabilities and multiple peripherals. Such qualities will help fuel an impressive 972% increase in worldwide installed base, rising from 535,000 units in 1979 to more than 5.2 million machines by the end of 1984. US installed base over the period will jump from 371,000 to approximately 3.1 million units, forecasts International Data Corp (IDC), Waltham, MA.

US sales of business/professional systems will show a 52% compound annual growth rate (CAGR) from 1979 to 1984 with approximately 1.7 million installed units by 1984.

Despite healthy growth rates, though, the future isn't all rosy for the desktop-computer industry. Improperly running software (a complaint of many users), an expected absence of dramatic price reductions in the foreseeable future and an industry shakeout by 1983 could create problems for desktopcomputer manufacturers.

contribution to rising chip densities has been leveling off as designers find it increasingly difficult to effectively utilize smaller chip dimensions.

The result? The experience curve will flatten, resulting in less dramatic price reductions.

Material for this page developed from *Electronic Business* magazine and other sources by Jesse Victor, Assistant/New Products Editor, and Joan Morrow, Assistant Editor.



Whatever your ferrite requirements for power conversion applications Ferroxcube has the size, shape and material to fill your needs.

The power material 3C8 is produced in our full range of standard configuration: Pot Cores, Toroids, E or E-LAM Style E Cores, as well as EC Cores complete with bobbins and mounting hardware. All can be gapped for output choke applications. We've even established standard "power gaps" for Pot Cores and EC Cores.

We've got it all and it's called The Power Line. If you'd like more information about the most complete ferrite product line in the industry, Speak To The Specialists. If we can't help you, chances are nobody can.

FERROXCUBE Speak To The Specialists

Division of Amperex Electronic Corporation Saugerties, New York 12477 TWX 510-247-5410 (914) 246-2811

Our special designs... for your special designs.

Special Precision Potentiometers

Our customers have discovered that Spectrol's special designs often help make their special designs superior. If you have applications for unique potentiometers, here's why you should consult Spectrol: 25 years experience making both standard and special potentiometers...a strong applications engineering department...expertise in all technologies, wirewound, cermet, and conductive plastic...worldwide design and manufacturing facilities, backed up by UTC, one of the world's largest international companies. Let us quote your special designs – non-linear, sine-cosine, sectors, and linear position models. Let us help you meet "impossible" environmental operating conditions. Start with your local Spectrol representative, or call our applications engineering manager today.



SPECTROL ELECTRONICS GROUP

UNITED STATES Spectrol Electronics Corporation P.O. Box 1220, City of Industry, Calif. 91749, U.S.A. • (213) 964-6565 • TWX (910) 584-1314 UNITED KINGDOM Spectrol Reliance Ltd. Drakes Way, Swindon, Wiltshire, England • Swindon 21351 • TELEX: 44692 ITALY SP Elettronica SpA Via Carlo Pisacane 7, 20016 Pero (Milan) Italy • 35 30 241 • TELEX: 330091 GERMANY Spectrol Electronics GmbH Oberauerstrasse 15, 8000 Munich 70 West Germany • (089) 7145096 • TELEX: 52/3014 PUERTO RICO Spectrol Caribe Corporation Las Marias Industrial Park, Anasco, Puerto Rico • (809) 826-3012 • TELEX SCC PR 3452012 For more information, Circle No 110