

# ELECTRONIC DESIGN

FEBRUARY 6, 1992

FOR ENGINEERS AND ENGINEERING MANAGERS--WORLDWIDE





## MEMORY-CONTROLLER MODULE ORGANIZES DATA FOR FASTER DRAM ACCESSSES

PENTON PUBLICATION  
U.S. \$10.00

**40**  
YEARS  
OF EDITORIAL  
EXCELLENCE

- **SPECIAL REPORT:**  
CAE SYSTEM SIMULATION  
HOLDS PROMISE
- **A PREVIEW OF**  
BUSCON '92 WEST
- **POWER-FACTOR**  
CORRECTION FOR  
SWITCHING SUPPLIES

QUICKLOOK

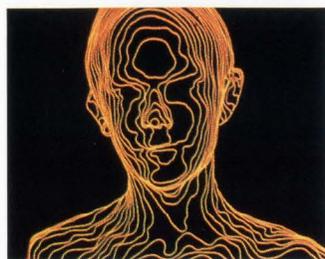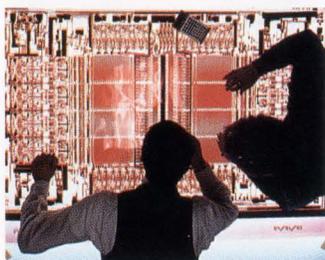

# WHO NEEDS THE SIGNAL PROCESSING WORKSYSTEM?

Anyone involved in DSP and communications design can benefit from the Signal Processing WorkSystem.<sup>®</sup> Because SPW<sup>™</sup> is the only complete, integrated CAE software tool for signal processing design, simulation, analysis and implementation.

Satellite communications. Modems. Mobile radios. Cellular phones. Radar. Sonar. Speech encoding. Voice processing. Image processing. Digital audio. Multimedia. Automotive electronics. Robotics. Neural nets and pattern recognition. Data compression. HDTV. Biomedical instrumentation. All these and much more can be designed using SPW on industry-standard platforms from Sun, DEC and HP/Apollo.

That's why over 200 of the world's leading telecommunications, aerospace and electronics companies around the world now use SPW.

With SPW you first create a high-level, hierarchical design using its extensive libraries of DSP and communications function blocks, as well as your own custom blocks. SPW then automatically converts your design into an error-free simulation program that can accept real-world signals and parameters for accurate design analysis.


SPW also provides several optional paths to implementation, including bit-accurate fixed-point simulation, VHDL generation, logic synthesis and other ASIC/PCB support. A code generation system produces generic-C for fast prototyping on any DSP platform, links SPW to DSP chips from AT&T, Motorola and TI, and supports boards from leading vendors.

To preview the Signal Processing WorkSystem, call (415) 574-5800 for a free video demonstration tape. In fifteen minutes, you'll see how SPW can save hundreds of hours and thousands of dollars in DSP design.

**COMDISCO<sup>®</sup>**  
**SYSTEMS, INC**

919 East Hillsdale Blvd., Foster City, CA 94404 (415) 574-5800

# Control Tower

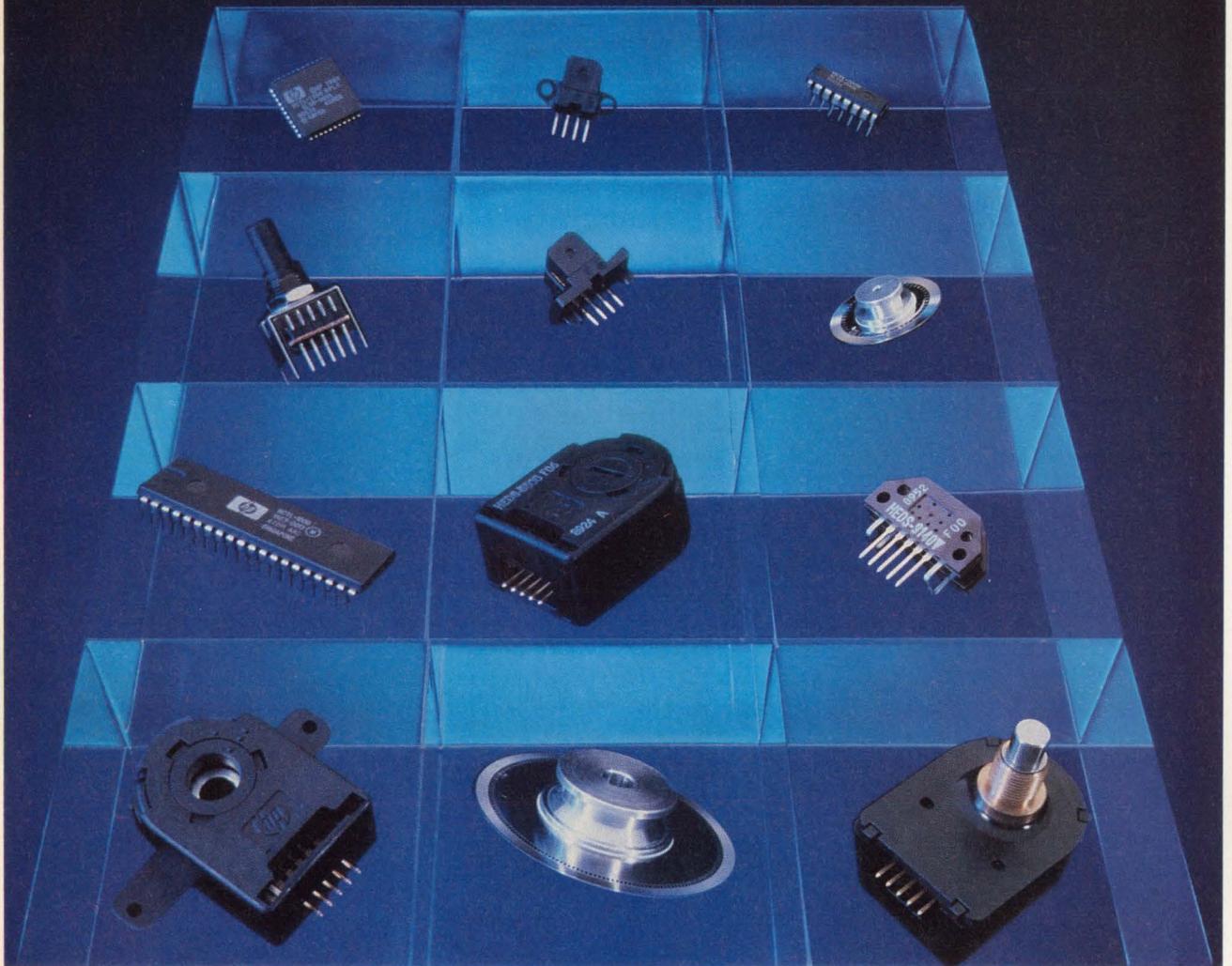

When it comes to motion control products, Hewlett-Packard towers over the rest with a more diversified and innovative line of solutions. Giving you one source to meet all your design needs.

Just look at our award-winning HEDS 9000 series of encoder modules. Using HP's unique optical technology, these modules are the ideal building blocks for creating precision high-speed linear or rotary applications.

Your choices include everything from a 3-channel module for industrial applications to the small footprint of our 9700 collection for business equipment.

## **Control panel: the HRPG series.**

For front panel applications, turn to our RPG series of potentiometers. Offering you full configuration flexibility, improved rotational feel, and small footprint, HP delivers the perfect line of data entry devices for your test, medical, analytical, and computer equipment.

## **Controlled performance: the HCTL series.**

Our new line of high-speed HCTL ICs give you high performance servo control in low-power CMOS. The result: superior performance and more microprocessing

power left over for your laboratory, medical, and industrial automation designs.

And because these motion control solutions come from HP, you're assured of our on-going commitment to excellence in service, support, and reliability.

So why take a chance, when you can take control. With motion control products from HP. Call for our free brochure: 1-800-752-0900, ext. 1497.

There is a better way.



**HEWLETT  
PACKARD**

In Europe, fax inquires to  
(49) 7031-14-1750

# The 29K Family.



*Low-cost 32-bit  
RISC processor.*



*Original 32-bit  
RISC processor.*



*32-bit RISC processor  
with on-chip floating point.*



*32-bit RISC processor  
with 8K cache and  
Scalable Clocking technology.*



*32-bit RISC processor  
with 4K cache and  
programmable bus sizing.*

It's all in the family—the 29K™ Family, that is. All the performance you need in a 32-bit embedded RISC processor. And all the support you need from our Fusion29K™ Partners, to bring your products to market faster than ever.

The 29K Family is the 32-bit embedded RISC architecture that keeps your performance high and your system costs low. And all 29K Family members are binary compatible, so your software runs on each device, without modification.

New family members push the performance envelope further: Our Am29030™ and Am29035™ processors offer advanced features like large on-chip caches, Scalable Clocking™ technology and programmable bus sizing—which ease design and lower system costs. With additional family members on the way.

The 29K Family also has the best embedded RISC support available—the Fusion29K Partners. The Fusion29K Partners include over

# The 29K Family.



80 leading independent hardware and software vendors and consultants prepared to shorten your design cycle.

Together, they offer hundreds of development tools to get you to market quickly: Everything from compilers, debuggers, emulators, and logic analyzers, to complete application solutions.

So call AMD at **1-800-292-9263 Ext. 3** for information on the 29K Family, or a Fusion29K

product catalog or newsletter. You'll find all the support you need in one big happy family.



## Advanced Micro Devices

901 Thompson Place, P.O. Box 3453, Sunnyvale, CA 94088 © 1991 Advanced Micro Devices, Inc.  
29K and Scalable Clocking are trademarks and Fusion29K is a servicemark of Advanced Micro Devices. All other brand or product names are trademarks or registered trademarks of their respective holders.

# ELECTRONIC DESIGN



**TECHNOLOGY  
ANALYSIS**

**35 BUSCON '92 WEST: MEZZANINE BUSES REGAIN POPULARITY**

Less-strict specifications permit mezzanine modules to add functionality without the traditional trade-offs.

**COVER  
FEATURE**

**47 ACCELERATE DRAM ACCESSES WITH CONTROLLER MODULE**

A memory controller trims bus-transfer delays and boosts cache efficiency by manipulating wide memory words.

**ELECTRONIC  
DESIGN REPORT**

**53 SYSTEM SIMULATION STILL HOLDS PROMISE**

Most designers profit from some element of system simulation, but few practice it in pure form.

**DESIGN  
APPLICATIONS**

**67 SOLVE SWITCHER PROBLEMS WITH POWER-FACTOR CORRECTION**

Correcting power factor at the input to switchers can be far more effective than fighting to boost their efficiency.

**PRODUCT  
INNOVATIONS**

**95 SOPHISTICATED INSTRUMENTS TAKE ON EMI TESTING**

A sextet of electromagnetic-interference testers sports a price/performance ratio and modularity to suit any budget.

**98 PORTABLE ANALYZER AUTOMATES SCSI TESTING**

With 16-bit-wide capability and 20-ns time stamping, this analyzer handles the fastest and widest SCSI buses.

**100 BIDIRECTIONAL SINGLE-BANK FIFOS TRIM SYSTEM COSTS**

Chip size, and thus cost, is reduced by using an asynchronous sharing scheme that allows one internal memory bank to serve both directions.

**14 EDITORIAL**

**18 TECHNOLOGY BRIEFING**

Will VHDL be a missed opportunity?

**23 TECHNOLOGY NEWSLETTER**

- Enhanced ISDN moves to Pacific Bell switches
- Proposal puts tiny PCs in embedded applications
- Fast-accessing drive possesses 1.24 Gbytes
- Programmable filter needs no multipliers
- Simulation model backs 68302 processor
- PC motherboard logic IC trims power drain
- Fast RISC processor fits car controls
- MPU-ASIC combo eases laser-printer design

**29 TECHNOLOGY ADVANCES**

- Soldering-technology gains mean better cable assemblies
- Asymptotic waveform analysis accurately predicts FPGA timing
- Windows programming standards hasten software development

**81 IDEAS FOR DESIGN**

- Cable tester is expandable
- Multiplex temperature data
- Monitor across isolation barriers

**87 QUICK LOOK**

- Without a leader, there can be no skunk works
- Multimedia DSP chip market heats up
- Employment guide for engineers
- Measuring time to market and break-even time

**91 PEASE PORRIDGE**

What's all this dead car stuff, anyhow?

**NEW PRODUCTS**

- 103 Digital ICs**  
VGA chip enhances colors, speeds graphics with local bus interface
- 104 Communications**  
10Base-T Ethernet LAN chip integrates key control features
- 105 Packaging & Production**
- 106 Instruments**
- 107 Components**
- 109 Computer Boards**

**112 INDEX OF ADVERTISERS**

**113 READER SERVICE CARD**

**COMING NEXT ISSUE**

- ISSCC Special Report: The latest advances in digital, linear, communications, and special-purpose ICs
- Designing with negative resistors
- Generating 100-MHz signals with direct digital synthesis
- New CAE tools ease multichip module design
- First details on a new high-speed cache DRAM
- PC Design Special Section
  - Combining an i860 RISC processor with an i486
  - A preview of the imminent XGA graphics standards
  - The latest PC-design products
- PLUS:  
Ideas for Design  
Pease Porridge  
Technology Advances  
QuickLook

ELECTRONIC DESIGN (USPS 172-080; ISSN 0013-4872) is published semi monthly by Penton Publishing Inc., 1100 Superior Ave., Cleveland, OH 44114-2543. Paid rates for a one year subscription are as follows: \$95 U.S., \$175 Canada, \$255 International. Second-class postage paid at Cleveland, OH, and additional mailing offices. Editorial and advertising addresses: ELECTRONIC DESIGN, 611 Route #46 West, Hasbrouck Heights, NJ 07604. Telephone (201) 393-6060. Facsimile (201) 393-0204.

Printed in U.S.A. Title registered in U.S. Patent Office. Copyright © 1992 by Penton Publishing Inc. All rights reserved. The contents of this publication may not be reproduced in whole or in part without the consent of the copyright owner.

Permission is granted to users registered with the Copyright Clearance Center Inc. (CCC) to photocopy any article, with the exception of those for which separate copyright ownership is indicated on the first page of the article, provided that a base fee of \$1 per copy of the article plus \$.50 per page is paid directly to the CCC, 27 Congress St., Salem, MA 01970 (Code No. 0013-4872/92 \$1.00 + .50). (Can. GST # R126431964) Copying done for other than personal or internal reference use without the express permission of Penton Publishing, Inc. is prohibited. Requests for special permission or bulk orders should be addressed to the editor.

For subscriber change of address and subscription inquiries, call (216) 696-7000.

POSTMASTER: Please send change of address to ELECTRONIC DESIGN, Penton Publishing Inc., 1100 Superior Ave., Cleveland, OH 44114-2543.



Jesse H. Neal Editorial Achievement Awards:  
1967 First Place Award  
1968 First Place Award  
1972 Certificate of Merit  
1975 Two Certificates of Merit  
1976 Certificate of Merit  
1978 Certificate of Merit  
1980 Certificate of Merit  
1986 First Place Award  
1989 Certificate of Merit



# OUR LOW-COST 68HC05 CSICs CAN TAKE YOUR DESIGNS TO NEW HEIGHTS.

It's more than low-cost that helps our 8-bit microcontrollers get your design off the ground.

It's Customer-Specified Integrated Circuits designed to meet real world needs.

Whether you're moving up from 4-bit, or replacing discrete components, Motorola's newest 68HC05 CSICs make it easier and more affordable than ever.

As part of our growing family, the K-Series, J-Series, and P-Series of 68HC05 microcontrollers offer a high level of subsystem integration in a variety of pin counts. Options include a full range of memory combinations, communication interfaces, A/D converters, and many of the subsystems that have made Motorola the world's leading 8-bit supplier.

Virtually every 68HC05 CSIC is supported by One-Time Programmable EPROM-versions for prototyping and limited-production when code changes for model variations are required. Plus, every 68HC05 is backed by extensive development tool support.



Whether your application requires a simple alert tone, personality EPROM for a remote control, or processing power for precision motor control, our 68HC05 CSICs have the features and prices to fit your needs.

Take your next design to new levels of performance. Complete the coupon below for your free copy of our 68HC05 K-Series Source Level Simulator. Develop, debug, and simulate hardware execution with this extremely versatile and easy-to-use PC-based software program.

## FREE Source Level Simulator!

Help your design rise above the rest! For a free copy of the 68HC05 K-Series Source Level Simulator and more information on our low-cost 68HC05 MCUs, return this coupon to:

Motorola, Inc. P.O. Box 1466, Austin, Texas 78767

Name \_\_\_\_\_  
Title \_\_\_\_\_  
Company \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_  
State \_\_\_\_\_ Zip \_\_\_\_\_  
Phone \_\_\_\_\_ Fax \_\_\_\_\_

Free Source Level Simulator offer ends May 29, 1992.

ED 2/6/92

## THE PATHWAY TO PERFORMANCE.



# MOTOROLA

# TURBO POWER CONVERTIBLES™

Tired of wasting board space on an expensive, space guzzling DC/DC Converter? Check-out the new HPR7XX Power Convertible. It is unbelievably small and sleek with 5 Watts of isolated output power. This is a turbo charged SIP - only 2.22" long and .35" wide.

You get 16 Watts per cubic inches of unregulated power under the hood.

The HPR7XX is no big ticket item either. It is priced less than DC/DC Converters twice it's size and with less output power capacity - only \$20 in O.E.M. quantities. This high-performance model drives as great as it looks with an efficiency rating of 80%. Take it for a spin, you will have no trouble finding a parking spot on your board.

For the dealer near you:  
Call 1-800-548-6132  
Fax 1-602-741-3895  
Write P.O. Box 11400 Tucson, AZ 85734




Your Partner in Quality

Power Convertibles is a trademark of Power Convertibles Corporation, an affiliate of Burr-Brown Corporation.

CIRCLE 165 FOR U.S. RESPONSE  
CIRCLE 166 FOR RESPONSE OUTSIDE THE U.S.
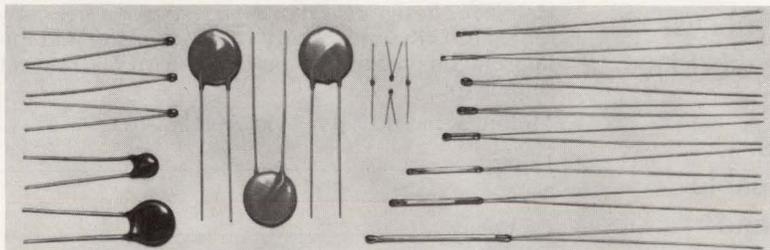
## High Volume, Low Cost Passive Components: Thermistors and Varistors from Victory Engineering



VECO's reputation for producing 'Hi-Rel' components for aerospace applications is matched by its ability to manufacture high volume, low cost passive components for commercial and industrial applications.

VECO Thermistors and Varistors are manufactured to exacting industrial and governmental requirements. Extensive quality control and inspection assure their quality and reliability in highway flashers, radar speed detectors, soldering irons, telecommunications, small appliances, copiers, oven temperature controls, temperature compensation, fluid or airflow measurement, auto engine performance monitoring and hundreds of other products where price and performance are paramount considerations.

For a complete listing of VECO Thermistors and Varistors, request VECO's Condensed Catalog MGP681.

**VECO VICTORY ENGINEERING CORP.**  
VICTORY ROAD, P.O. BOX 559 • SPRINGFIELD, NEW JERSEY 07081  
Phone: 201/379-5900 Fax: 201/379-5982

CIRCLE 171 FOR U.S. RESPONSE  
CIRCLE 172 FOR RESPONSE OUTSIDE THE U.S.

## ELECTRONIC DESIGN

**Editor-in-Chief:** Stephen E. Scrupski

**Executive Editor:** Roger Allan

**Managing Editor:** Bob Milne

**Senior Editors:** Frank Goodenough,  
Milt Leonard, John Novellino

**Technology Editors:**

*Analog & Power:* Frank Goodenough

*Communications & Industrial:*

Milt Leonard (San Jose)

*Components & Packaging:* David Maliniak

*Computer-Aided Engineering:*

Lisa Maliniak

*Computer Systems:* Richard Nass

*Semiconductors:* Dave Bursky (San Jose)

*Software:* Sherrie Van Tyle

*Test & Measurement:* John Novellino

**Field Bureaus:**

*West Coast Executive Editor:*

Dave Bursky (San Jose)

*Communications & Industrial:*

Milt Leonard (San Jose)

*Dallas:* Jon Campbell

*Frankfurt:* John Gosch

*London:* Peter Fletcher

**Chief Copy Editor:** Roger Engelke, Jr.

**Contributing Editors:**

Ron Kmetovicz, Robert A. Pease

**Editorial Production Manager:**

Lisa Iarkowski

**Production Coordinator:** Pat A. Boselli

**Associate Art Director:** Tony Vitolo

**Staff Artist/Designer:** Tom Pennella

**Editorial Support Supervisor:** Mary James

**Editorial Assistant:** Ann Kunzweiler

**Editorial Secretary:** Bradie Guerrero

**Editorial Offices:** (201) 393-6262

**Advertising Production:**

(201) 393-6093 or FAX (201) 393-0410

**Production Manager:** Michael McCabe

*Production Assistants:*

Donna Marie Bright, Lucrezia Hlavaty,

Eileen Slavinsky

**Circulation Manager:** Robert Clark

**Promotion Manager:** Clifford Meth


**Reprints:** Helen Ryan 1-800-835-7746

**Group Art Director:** Peter K. Jeziorski

**Published by Penton Publishing**  
**Vice President-Editorial:** Perry Pascarella

**Publisher:** Paul C. Mazzacano

# Afford. Ability.

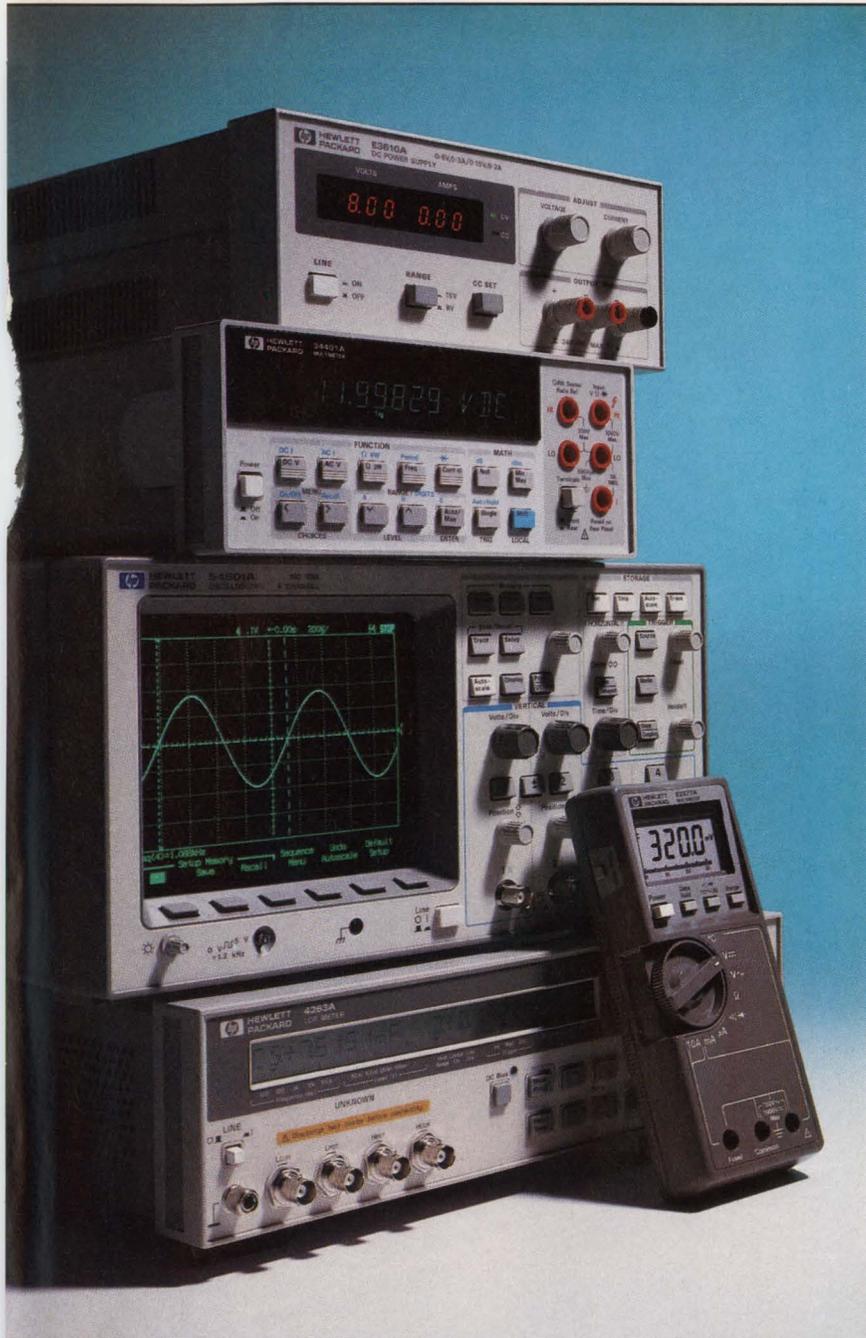

© 1991 Hewlett-Packard Co. TMIN112/ED

**With HP basic instruments, performance costs less than you expect.**

Now you don't have to accept trade-offs in a basic test instrument. Because HP offers the performance you want at prices you can afford.

Need a dual-range output power supply? The HP E3610 Series makes choosing a 30-watt dc power supply easy—especially when you consider the low noise and **\$300\*** price.

What about a digital multimeter for bench or system use? The rugged 6 1/2 digit HP 34401A does both with uncompromised performance for **\$995\***.

You won't find a better 100 MHz digitizing scope than the HP 54600 Series. It combines analog look and feel with digital troubleshooting power for only **\$2,395** (2-channel) or **\$2,895** (4-channel)\*.

At **\$3,800\***, the HP 4263A LCR Meter lowers the cost of high-precision 100 Hz to 100 kHz benchtop and system component measurements.

And the 8-function HP E2377A is just one of the HP E2300 Series 3 1/2 digit handhelds priced from **\$99** to **\$189\***.

**☎ For more information or same-day shipment from HP DIRECT, call 1-800-452-4844\*\*. Ask for Ext. T514 and we'll send you a data sheet that shows how affordable performance can be.**

\* U.S. list price

\*\* In Canada call 1-800-387-3867, Dept. 433


There is a better way.

 **HEWLETT  
PACKARD**

CIRCLE 104 FOR U.S. RESPONSE

CIRCLE 105 FOR RESPONSE OUTSIDE THE U.S.

# “Compre

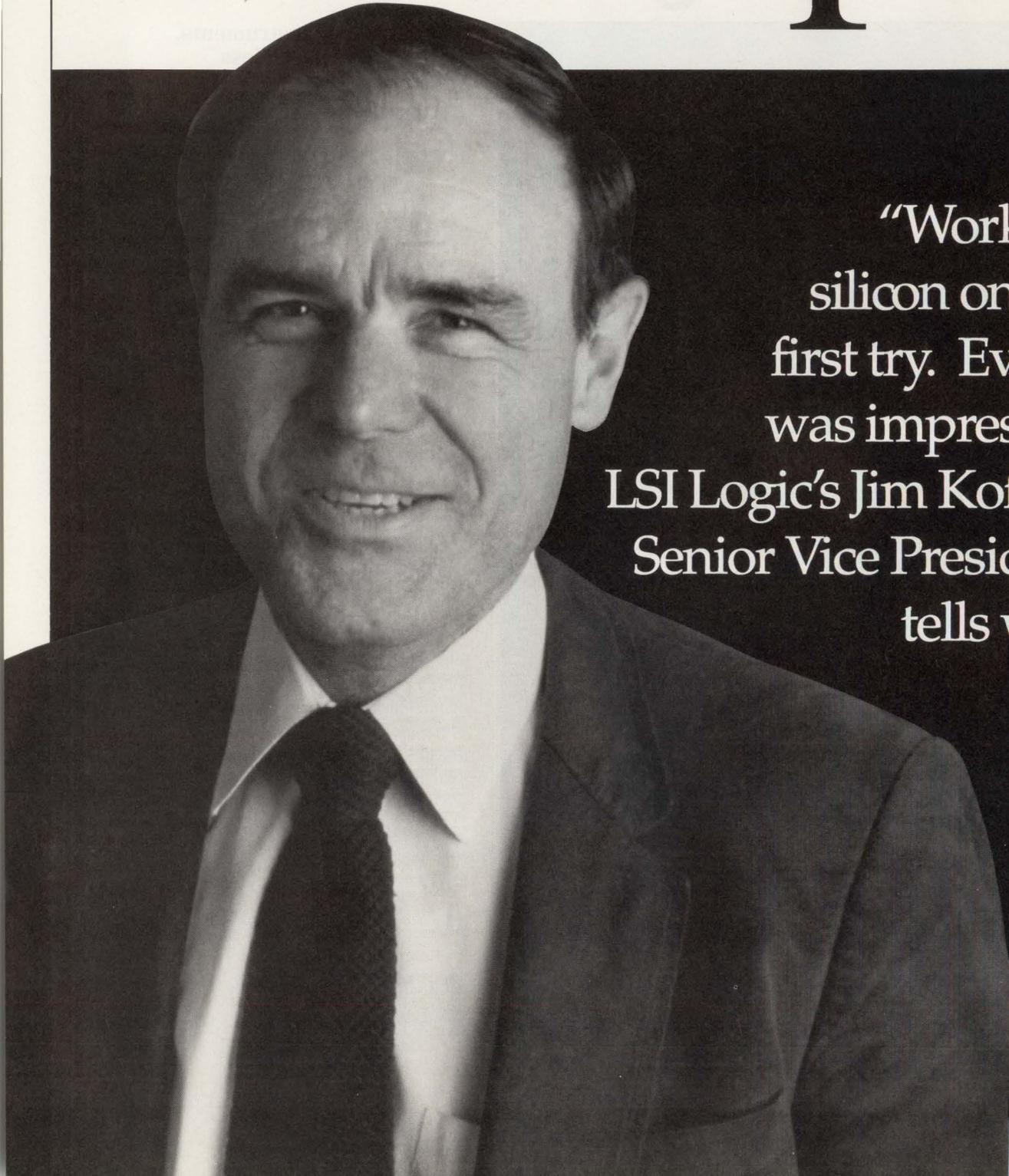A black and white portrait of a middle-aged man with short, dark hair, wearing a dark suit jacket, a white dress shirt, and a dark tie. He is smiling slightly and looking towards the camera. The background is dark and out of focus.

“Working  
silicon on the  
first try. Even I  
was impressed.”

LSI Logic's Jim Koford,  
Senior Vice President,  
tells why.

# hensive”

It's easy to see what initially attracted LSI to Viewlogic. Not only does Viewlogic's Workview provide comprehensive and open electronic systems design solutions for VHDL synthesis, mixed analog/digital simulation, FPGA, ASIC, IC and PCB design, it also runs on the broadest array of computer platforms.

As Jim Koford tells it, "Our relationship started by using Workview with our MDE<sup>®</sup> design tools for designing mixed A/D IC's and complex cells for ASIC applications. We soon discovered that Workview interfaces well with our MDE design tools. And our standard products groups have used their system level tools extensively.

"Simply put, Viewlogic has improved our time to market by complementing our own MDE design tools. We feel good about that and our relationship continues to grow."

See for yourself what tough critics like Jim Koford are discovering about Viewlogic. Call us at 800-422-4660, Extension 500 and ask for our Solutions Brochure. We'll show you what comprehensive really means.

  
**VIEWlogic**<sup>®</sup>  
*Do it right up front*

MDE<sup>®</sup> is a registered trademark of LSI Logic Corporation.

CIRCLE 140 FOR U.S. RESPONSE  
CIRCLE 141 FOR RESPONSE OUTSIDE THE U.S.

A person is shown in a meditative pose, sitting cross-legged on a patterned rug. Their right hand is held palm-up, and a small black square with the text "i387" in white is placed on the palm. The background is a dark, moody landscape with a blue sky and a dark horizon.

i387™

# Only one math coprocessor with the




When you enhance your Intel CPU with an Intel Math CoProcessor, you're destined for good karma.

It's simple. They were both invented by Intel, the microprocessor leader. And they were specifically designed to work together, ensuring 100% compatibility.

No wonder Intel's been the de facto standard in math coprocessors for the last ten years.

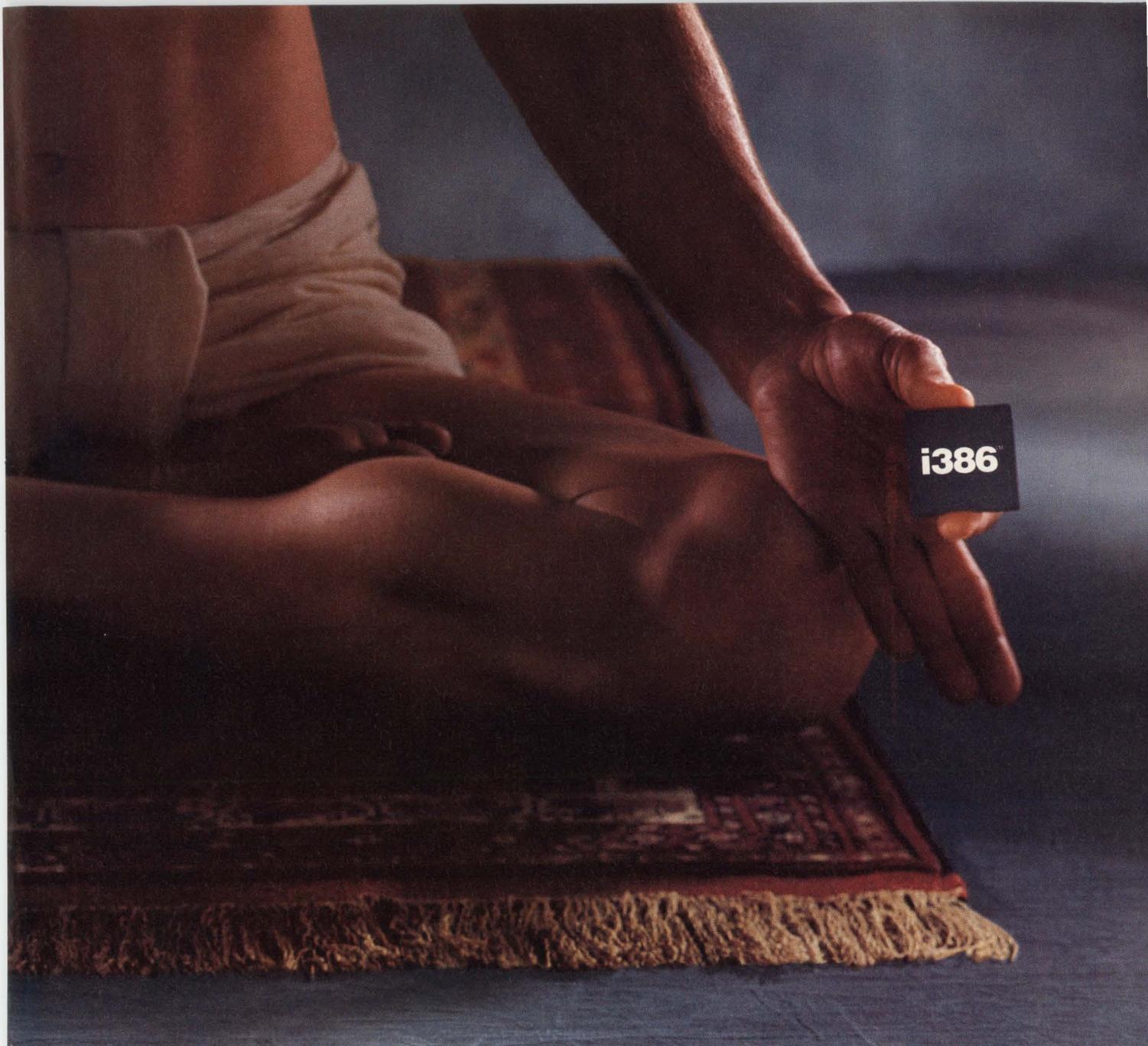Intel Math CoProcessors are also compatible with more than 2,100 applications. They come with a lifetime warranty. And they now account for nine out of ten math coprocessors currently in use. All of which should effectively put your mind at peace



# your computer has achieved oneness with an Intel CPU.

when you buy one.

It's all part of Intel's commitment to providing powerful solutions today, with industry-leading microprocessors, plus the enhancements for even greater performance. Today and down the road.

To receive a detailed information packet about the full line of Intel Math CoProcessors, call

(800) 538-3373. It has everything you need to find complete enlightenment.


**intel**®

The Computer Inside.™

CIRCLE 1
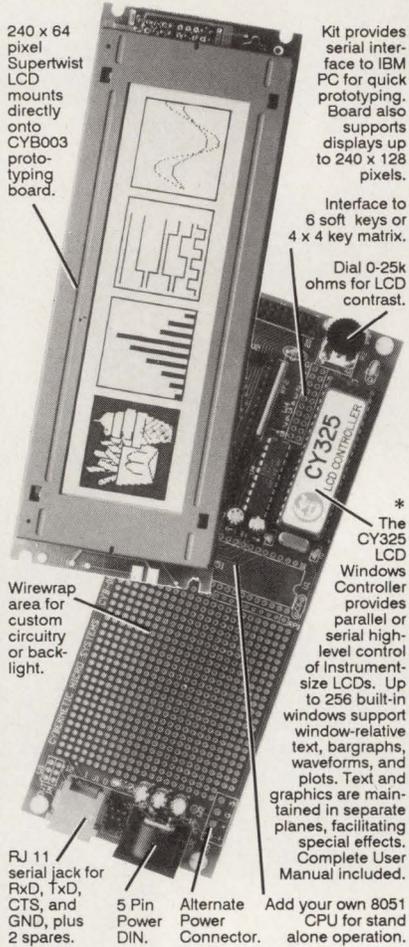
## LCD Proto Kit

Everything you need to start your LCD application ... create complex screens in just a few hours!



Kit provides serial interface to IBM PC for quick prototyping. Board also supports displays up to 240 x 128 pixels.

Interface to 6 soft keys or 4 x 4 key matrix.

Dial 0-25k ohms for LCD contrast.

\* The CY325 LCD Windows Controller provides parallel or serial high-level control of Instrument-size LCDs. Up to 256 built-in windows support window-relative text, bargraphs, waveforms, and plots. Text and graphics are maintained in separate planes, facilitating special effects. Complete User Manual included.

Wirewrap area for custom circuitry or backlight.

RJ 11 serial jack for Rx, Tx, CTS, and GND, plus 2 spares.

5 Pin Power Connector.

Alternate Power Connector.

Add your own 8051 CPU for stand alone operation.

### Kit also includes:

Power supply provides +5v and Gnd for board, -12v for LCD, and +12v spare.

Sample routines in 8051 Assembler and QuickBasic.

LCD Paint™ for creating your own graphics images.

4-wire RJ11 style cable with DB25F connector for your IBM PC.

Demo routines preprogrammed into 8751 for immediate gratification.

**\$495 - Kit**  
Popular LCD Starter Kit.



(\$595 pre-assembled & tested)

\*The CY325 CMOS 40-pin DIP and 44-pin PLCC LCD Controller IC are available from stock @ \$75/singles, \$20/1000s.

## CyberneticMicroSystems

Box 3000 • San Gregorio CA 94074  
Tel: 415-726-3000 • Fax: 415-726-3003

## EDITORIAL

# No Monopoly On Ingenuity

I can recall, back in the late 1960s, interviewing a Japanese engineer working at Bell Labs here in New Jersey about a gallium-arsenide Gunn-effect-based device. It generated signals whose wave shape was determined by the physical shape of the device itself — make the device as a triangle, and you got triangular waveforms. When I asked how he created the precise shapes of the tiny devices (less than 40 mils on a side), he answered “Good old Japanese ingenuity.” (Actually, he created the devices with painstaking shaping on a grinding wheel.) That being the 1960s, and being steeped in tales of Yankee ingenuity, I got a chuckle out of his turn of phrase, and essentially wrote it off as just that — a clever turn of phrase. Boy, did I have a lot to learn.


Looking back on this incident, I regret not picking up on those early signs of what has become a major force in the electronics industry: Japanese ingenuity. But it was more than simple (or not-so-simple) ingenuity that accounted for the rise of Japanese products. It also was a focus on quality in mass production. Japan stepped into the U.S. semiconductor market spotlight back in the late 1970s, when a Hewlett-Packard engineer issued a report stating that Japanese-made dynamic-memory chips were of higher quality than comparable U.S.-made devices. The rest of the U.S. computer makers eventually agreed with that assessment, and now the commercial DRAM market is being driven by Japan's semiconductor industry.

A similar trend occurred in automobiles — first, a recognition of quality by customers, and then a major sales impact in the U.S. Though Electronic Design doesn't focus on the automotive industry, I can't help commenting on the recent presidential trade mission to Japan. There's an American tradition of calling 'em like you see 'em; so, from what I see, the leaders of the big three U.S. car manufacturers have no one to blame but themselves for their present predicament. They lost a large portion of the U.S. market because they didn't respond to customer preferences for reliable, economical cars. As for exports to Japan, how could they expect to sell large numbers of traditional American left-side steering wheel cars — cars designed to drive on the right side of the road — in a country that drives on the left side of the road? Unless we're missing something, it doesn't seem to take much ingenuity to figure that one out.

What all of this shows is that neither the U.S., Japan, nor Europe can monopolize ingenuity. But it does take good, forward-looking management, beginning right at the top, to harness that ingenuity and to set up the manufacturing organization to produce quality products.

*Stephen E. Scrupski*

Editor-in-Chief

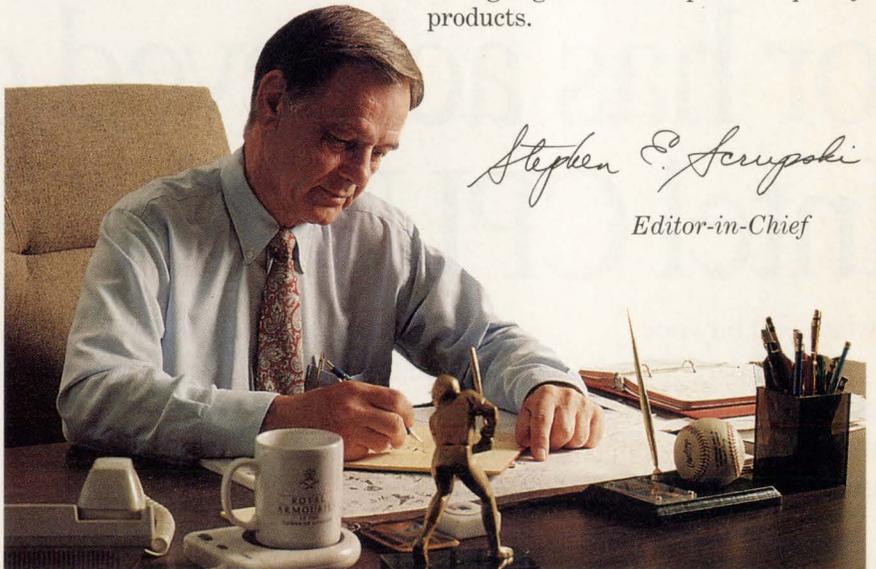

# rugged plug-in amplifiers



0.5 to 2000 MHz from \$13<sup>95</sup> (10 to 24 qty)

Tough enough to meet full MIL-specs, capable of operating over a wide -55° to +100°C temperature range, in a rugged package... that's Mini-Circuits' new MAN-amplifier series.

The MAN-amplifier's tiny package (only 0.4 by 0.8 by 0.25 in.) requires about the same pc board area as a TO-8 and can take tougher punishment with leads that won't break off. Models are unconditionally stable and available covering frequency ranges 0.5 to 2000 MHz, NF as low as 2.8dB, gain to 28dB, isolation greater than 40dB, and power output as high as +15dBm. Prices start at only \$13.95 including screening, thermal shock -55°C to +100°C, fine and gross leak, and burn-in for 96 hours at 100°C under normal operating voltage and current.

Internally the MAN amplifiers consist of two stages, including coupling capacitors. A designer's delight, with all components self-contained. Just connect to a dc supply voltage and you are ready to go.

### The new MAN-amplifiers series...

- wide bandwidth • low noise • high gain
- high output power • high isolation

MODEL	FREQ. RANGE (MHz)	GAIN dB		MAX PWR†	NF (dB)	ISOL. (dB)	DC PWR	PRICE
	$f_L$ to $f_U$	min	flat††	dBm	(typ)	(typ)	V/ma	\$ ea. (10-24)
MAN-1	0.5-500	28	1.0	+8	4.5	40	12/60	13.95
MAN-2	0.5-1000	18	1.5	+7	6.0	34	12/85	15.95
MAN-1LN	0.5-500	28	1.0	+8	2.8	39	12/60	15.95
◊MAN-1HLN	10-500	10	0.8	+15	3.7	14	12/70	15.95
MAN-1AD	5-500	16	.05	+6	7.2	41	12/85	24.95
MAN-2AD	2-1000	9	0.4	-2	6.5	28	15/22	22.50
MAN-11AD	2-2000	8	0.5	-3.5	6.5	22	15/22	29.95

††Midband 10 $f_L$  to  $f_U/2$ ,  $\pm 0.5$ dB † 1dB Gain Compression ◊ Case Height 0.3 in. Max input power (no damage) +15dBm; VSWR in/out 1.8:1 max.

Free... 48-pg "RF/MW Amplifier Handbook" with specs, curves, handy selector chart, glossary of modern amplifier terms, and a practical Question and Answer section.

finding new ways ...  
setting higher standards

## Mini-Circuits


A Division of Scientific Components Corporation  
P.O. Box 350166, Brooklyn, New York 11235-0003 (718) 934-4500  
Fax (718) 332-4661 Domestic and International Telexes: 6852844 or 620156

CIRCLE 118 FOR U.S. RESPONSE

CIRCLE 119 FOR RESPONSE OUTSIDE THE U.S.

IN THE ERA OF MegaChip™ TECHNOLOGIES
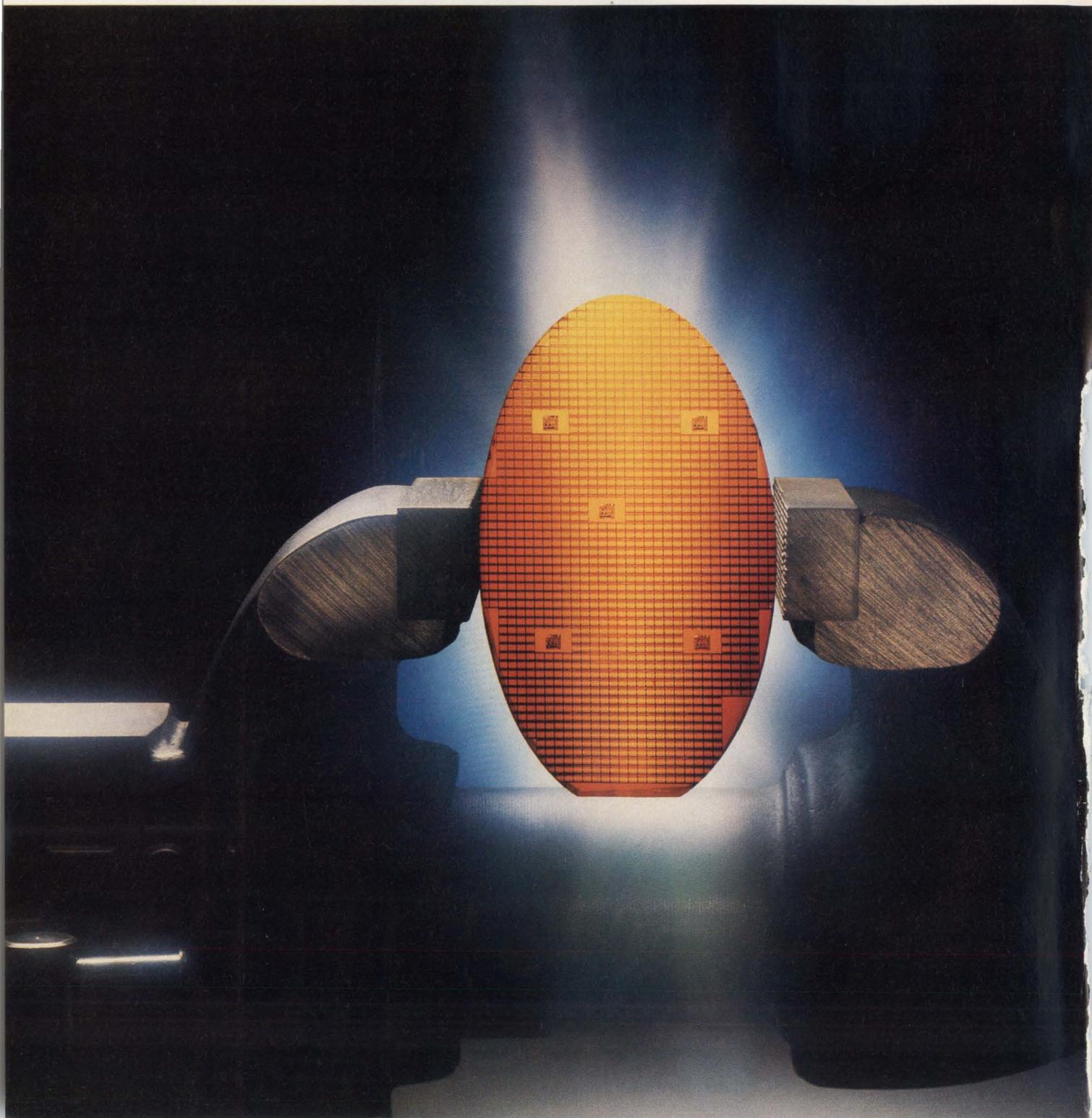
# We've squeezed more ABT Widebus as fast



# speed from our logic. as 4.1 ns!

**W**ith our new Advanced BiCMOS interface logic (ABT) family, you get the speed, drive and low power you need to optimize the performance of processors operating at 33 MHz and above.

Fabricated in our 0.8-micron BiCMOS process, this new family delivers maximum speeds down to 4.1 ns over recommended operating conditions. Typical performance of the devices is in the 2.5- to 3.0-ns range.

Other critical performance parameters are as impressive. Drive capability is 32 to 64 mA. Static power consumption is typically 2 mA ( $I_{CCH}$ ,  $I_{CCZ}$ ) and 30 mA ( $I_{CCL}$ ). Ground bounce is less than 800 mV typ.

## All this in Widebus

Our ABT family, a second-generation advance of our leadership BiCMOS (BCT) family, includes versions of our 16-, 18- and 20-bit-width Widebus™ functions.

Among the many ABT Widebus functions released is the 'ABT16244, a 16-bit buffer and line driver. It exhibits much greater stability of propagation delay (see chart), which results in a lower derating factor across the number of outputs switched.

Also in volume production are the Widebus 'ABT16245 16-bit bidirectional bus transceiver and the 'ABT16543 and 'ABT16952 16-bit bidirectional registered bus transceivers.


As in our successful Advanced CMOS Logic (ACL) Widebus family, these devices come in our leadership surface-mount shrink small-outline package (SSOP) that gives you twice the number of I/Os as a standard small-outline package in the same space.


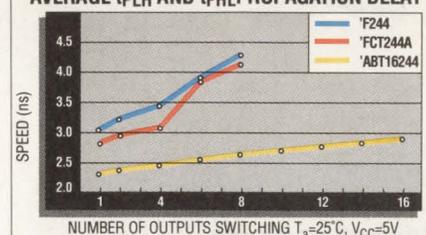
## Unique additions included

There are also new devices in our ABT Widebus family featuring greater density and functionality. Our 'ABT16500A is a good example. An 18-bit registered transceiver, it combines D-type latches and D-type flip-flops to allow data flow in transparent, latched and clocked modes.

AVERAGE  $t_{PLH}$  AND  $t_{PHL}$  PROPAGATION DELAY



**TI's speed advantage:** In a one-to-one comparison, a TI 'ABT16244 16-bit Advanced BiCMOS driver proves to be much faster and more stable than Advanced Bipolar and standard CMOS octal drivers.

To complement our full line of Widebus products, our ABT family will include at least 39 octal buffers/drivers, flip-flops, transceivers and registered transceivers.

**Squeeze more out of your system with a free sample 'ABT16500A: Call 1-800-336-5236, ext. 3009**

To learn firsthand how our new ABT family can boost the performance of your bus-interface designs, get a free 'ABT16500A transceiver and data sheet. Just complete and mail the return card or call the number above.




 **TEXAS  
INSTRUMENTS**


**UNIVERSAL INPUT  
3"x5" SWITCHERS**



SU30P

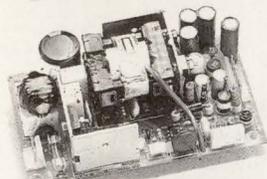

SU40P

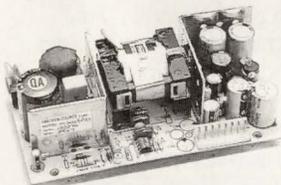

SU65P

- 85-264 VAC universal input
- 30W/40W/65W output power
- Single to quad outputs
- compact footprints
- 2.76"x5.12"x1.5" (30w series)
- 3"x5"x1.5" (40W series)
- 3.5"x6"x1.7" (65W series)



1. Fully agency approved
2. Available from stock
3. Low cost

Call today for quantity pricing and complete details on standard or custom-made products.



6818-G Patterson Pass Road,  
Livermore, CA 94550  
**TEL: (415) 373-1008**  
**Fax: (415) 373-1168**  
Tlx: 559291 FORTRON UD

CIRCLE 157 FOR U.S. RESPONSE  
CIRCLE 158 FOR RESPONSE OUTSIDE THE U.S.

**WILL VHDL BE A MISSED OPPORTUNITY?**

**A**ny future prosperity in the electronic-design-automation (EDA) industry hinges on developing standards. Users need tools and data that are interchangeable. Proprietary tools don't offer any practical way to integrate systems from different suppliers, and designers can't exchange data between them in a meaningful manner. What results is redundant work, uncomparable data, uncertainties, and other headaches. VHDL, an IEEE standard since 1987, has the capability to secure the software and data interchangeability that users seek. Yet the EDA industry has hesitated in embracing VHDL, which adversely affects both vendors and users.



LISA MALINIAK  
COMPUTER-AIDED ENGINEERING

Industry studies and surveys continue to reveal that users want standards. For instance, an EDA survey commissioned by ELECTRONIC DESIGN each year showed that in 1990 and 1991, compatibility was the first concern of 90% of those designers questioned. In addition, almost 80% listed adherence to industry standards as their major interest when selecting design software.

When VHDL was made a standard, EDA companies responded with public support. But they pointed at the language's shortcomings and made comparisons to their own hardware description languages (HDLs). Most vendors took a wait-and-see attitude, and expended little effort to make practical and useful VHDL products.


This lack of serious effort to develop tools, create innovative ways to blend VHDL with known design approaches, write utilities to convert proprietary HDL code into VHDL, and spread education has had negative repercussions on the language and the industry. Jan Geusens, vice president of Ascent Technology Inc., a San Jose, Calif.-based company involved with many popular HDLs, maintains that "the industry has done a great disservice to itself and its customers." He explains that many of today's problems with the language exist because vendors didn't quickly and totally adopt VHDL.

VHDL could have been the justification and investment motivation for a new wave of innovative EDA systems. "That opportunity has been missed, or at least the window of opportunity is closing unless the industry does something now, and fast," states Geusens. "VHDL is exposed to the danger of becoming another interesting experiment."

One complication arising from the industry's hesitation is that the international competitors of the U.S. electronics industry have caught up with their rivals in VHDL support. European manufacturers, in particular, are strongly driven by standards in their product planning. The U.S. lost at least two years of their head start due to the lack of products and support. In addition, the international contribution to the standard can result in marginally compatible derivatives or "flavors" of VHDL, which in turn defeats the goal of a standard. Geusens points out that VHDL could turn into another case of the U.S. having a good concept, but other countries reaping the benefits.

To speed VHDL's acceptance, U.S. companies must develop products that are attractive because of their performance, and not just because they're based on VHDL. And vendors must offer migration paths for customers from whatever proprietary languages they're using. Isolated point tools are inadequate because engineers don't want to trash their existing designs.

In addition, VHDL will never become the industry standard if companies continue to offer VHDL-based products while promoting their own proprietary software. Although the last few years have seen EDA vendors and users push for the standard, the industry must do more to quickly and fully adopt VHDL because the lack of a standard inhibits industry growth. "Whether it's the best language or not," remarks Geusens, "VHDL is established and has the capability to unite EDA vendors and users alike."

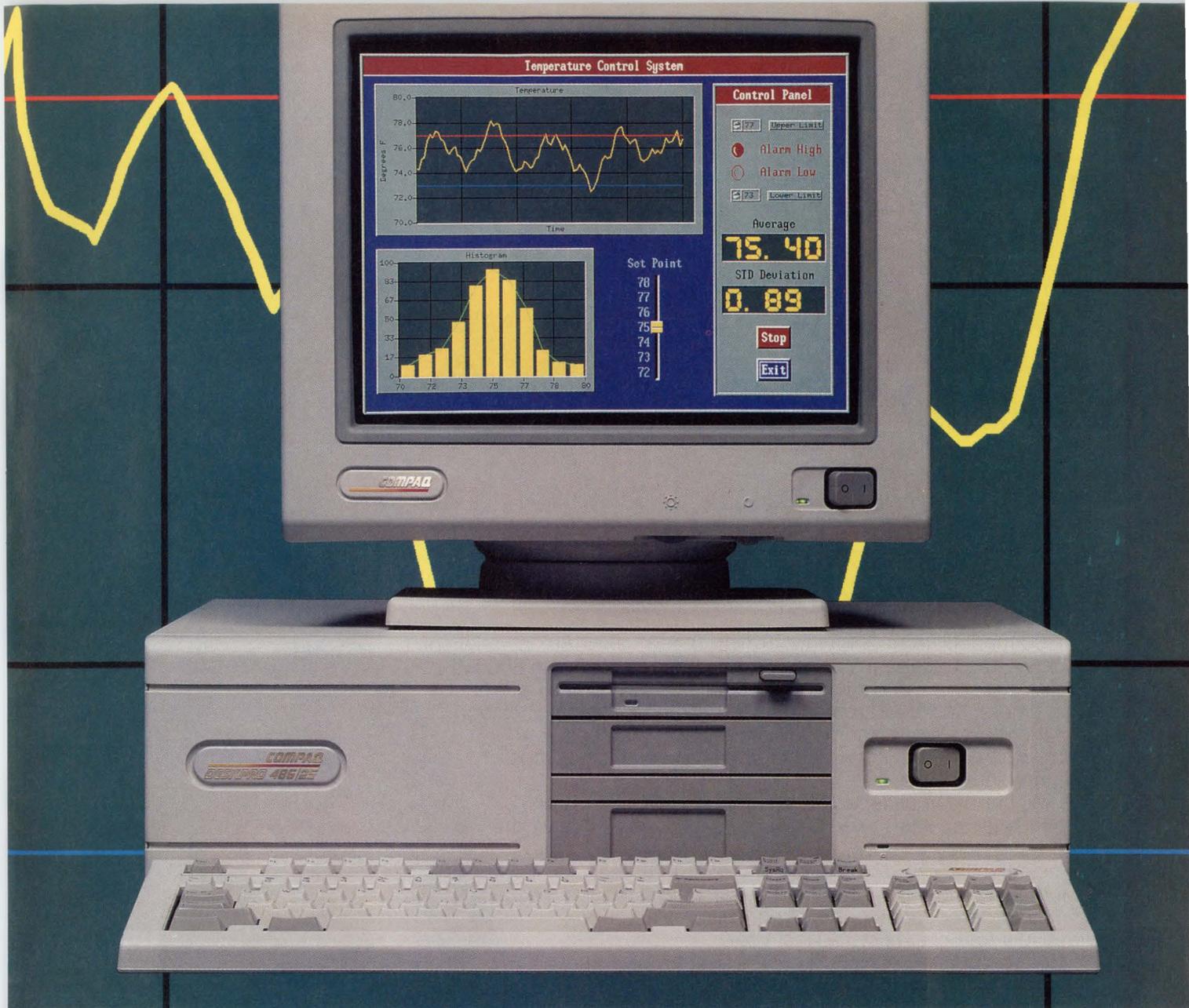

# Take a Look at LabWindows® 2.0

LabWindows 2.0 brings a new look to data acquisition and instrument control. The new look is graphical—a graphical user interface for your acquisition and control system.

## Create a Graphical User Interface

With LabWindows 2.0, you can easily create custom graphics panels to interface with your DOS-based system. Using the graphical editor and standard development tools, you can develop a system that combines data acquisition, data analysis, and data presentation.

## Program with C or BASIC

When you develop a system with LabWindows 2.0, you have the benefit of using standard programming languages with development tools designed specifically for data acquisition and instrument control.

## Use any Acquisition Hardware

LabWindows 2.0 has libraries of functions to control data acquisition hardware ranging from plug-in boards to industry-standard GPIB, VXI, and

RS-232 instruments. You can develop a system with LabWindows to meet all of your measurement and control needs.

Take a look at the new LabWindows 2.0. You'll like what you see.



6504 Bridge Point Parkway  
Austin, TX 78730-5039

(512) 794-0100


(800) 433-3488 (U.S. and Canada)

International Branch Offices: Australia (03) 879 9422, Denmark (45) 76 73 22, France (1) 48 65 33 70, Germany (089) 714 5093, Italy (02) 4830 1892, Japan (03) 3788 1921, Netherlands (01720) 45761, Norway (03) 846 866, Spain (908) 604 304, Switzerland (056) 45 58 80, U.K. (0635) 523 545. Product names listed are trademarks of their respective manufacturers. Company names listed are trademarks or trade names of their respective companies. © Copyright 1991 National Instruments Corporation. All rights reserved.

CIRCLE 122 FOR U.S. RESPONSE

CIRCLE 123 FOR RESPONSE OUTSIDE THE U.S.



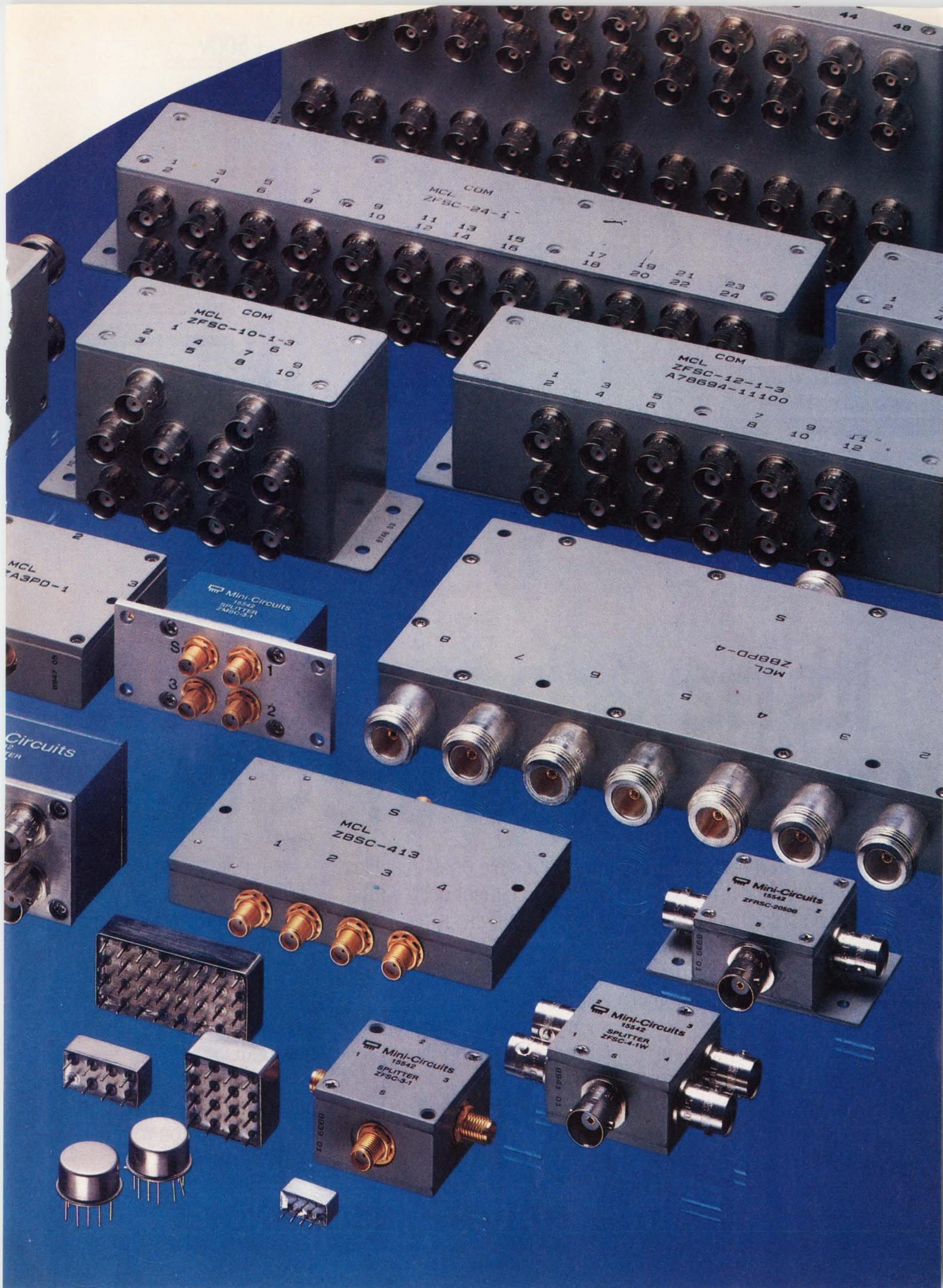

MCL COM  
ZFSC-24-1  
1 2 3 4 5 6 7 8 9 10 11 12 13 14 15 16 17 18 19 20 21 22 23 24

MCL COM  
ZFSC-10-1-3  
1 2 3 4 5 6 7 8 9 10

MCL COM  
ZFSC-12-1-3  
A78694-11100  
1 2 3 4 5 6 7 8 9 10 11 12

MCL  
TA3PD-1  
1 2 3

Mini-Circuits  
15542  
SPLITTER  
ZFSC-3-1  
1 2 3

MCL  
ZB8PD-4  
1 2 3 4 5 6 7 8 9

MCL  
ZBSC-413  
1 2 3 4

Mini-Circuits  
15542  
ZFSC-2050B  
1 2 3 4 5


Mini-Circuits  
15542  
SPLITTER  
ZFSC-3-1  
1 2 3

Mini-Circuits  
15542  
SPLITTER  
ZFSC-4-1W  
1 2 3 4 5

Mini-Circuits  
15542  
SPLITTER  
ZFSC-3-1  
1 2 3 4 5

Mini-Circuits  
15542  
SPLITTER  
ZFSC-3-1  
1 2 3

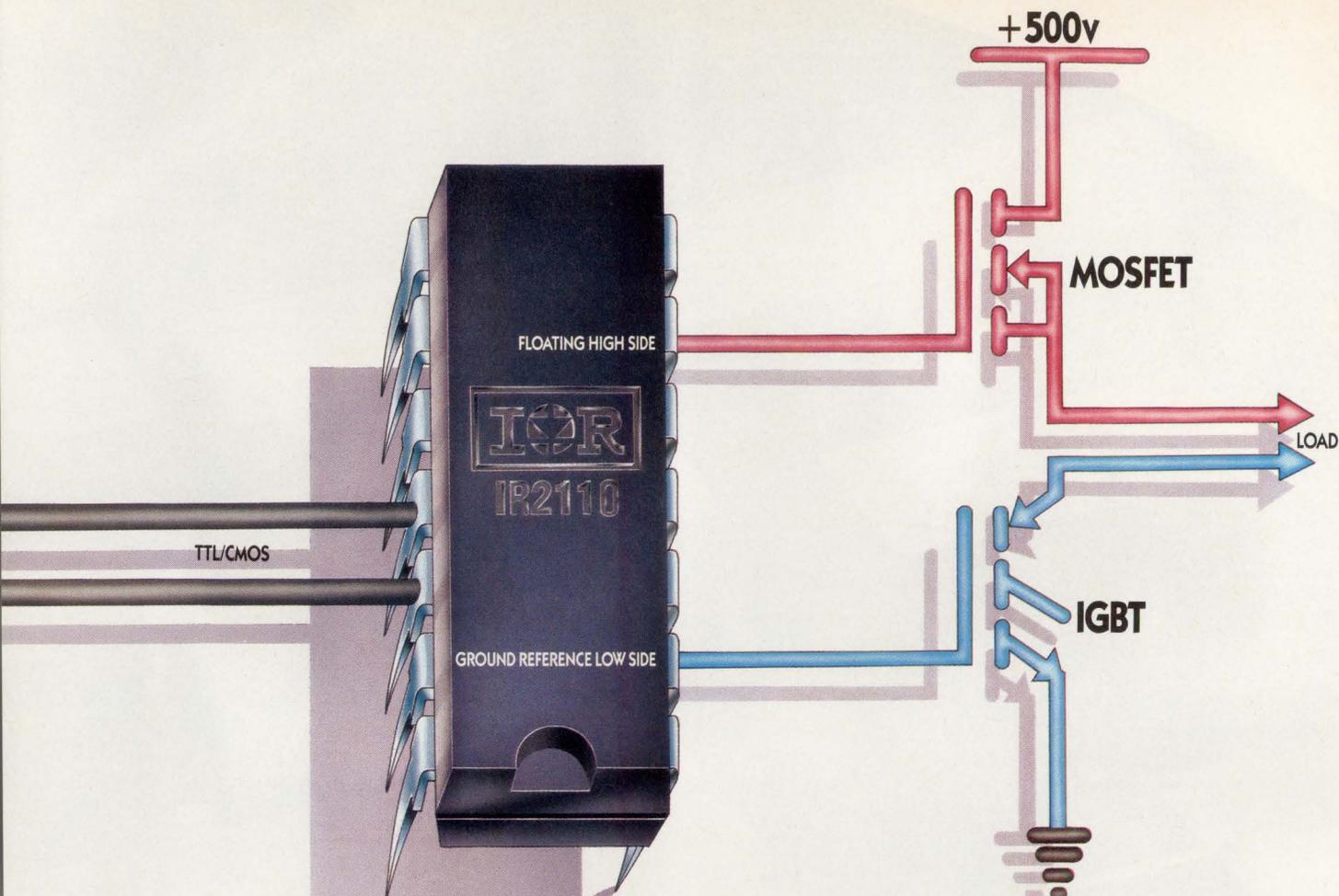Mini-Circuits  
15542  
SPLITTER  
ZFSC-3-1  
1 2 3



# It's never been easier to get a gate off the ground.

Now you can replace a fistful of components, and drive power FETs and IGBTs with one cost-effective part: The IR2110 monolithic dual channel 2A gate driver with floating high side and ground reference low side.

Count your design time in hours instead of days. And cut assembly time to a fraction.

The IR2110 runs as fast as it designs. With operation above

1 MHz. On-chip bootstrap. Plus matched channel delay within 10 ns. That's right. 10 ns.

It takes good care of your circuit too, with gate under-voltage protection.

And latched shutdown makes current mode control both simple and easy.

## IR2110



Is it rugged? 50 V/ns dv/dt at -55 to 150°C in plastic. Versatile? Operates off 12 to 500 V rails with 5 to 20 V input, in any circuit topology. Reliable? The IR2110 meets the same high standards as IR's incomparable HEXFET® power MOSFETs.

Call (800) 245-5549 for more information. We'll get it off the ground and on your desk in no time.

**IR** International Rectifier

WORLD HEADQUARTERS: 233 KANSAS ST., EL SEGUNDO, CA 90245, U.S.A. (213) 772-2000. TWX 910 348-6291, TELEX 472-0403. EUROPEAN HEADQUARTERS: HURST GREEN, OXTED. SURREY RH8 9BB, ENGLAND TELEPHONE (0883) 713215, TELEX 95219

CIRCLE 149 FOR U.S. RESPONSE

CIRCLE 150 FOR RESPONSE OUTSIDE THE U.S.

## ENHANCED ISDN MOVES TO PACIFIC BELL SWITCHES

An agreement between Pacific Bell, a subsidiary of San Francisco-based Pacific Telesis Group, and Northern Telecom Inc., headquartered in Nashville, Tenn., marks a major step toward converting Pacific Bell's telephone network to new national standards for the integrated services digital network (ISDN). Beginning in early 1993, Pacific Bell will incorporate the new standard in its DMS-100 central-office switches, which are produced by Northern Telecom. This move will eliminate the problems associated with existing ISDN standards that allow broad interpretations to lead to noncommunicating proprietary systems and equipment. The new standards will mean universal compatibility between both existing and new products and services. Over the next six years, Pacific Bell will order 112 ISDN modules containing Northern Telecom's National ISDN One-compliant hardware and software. When completed, the enhanced technology will be available to some 2.5 million customers. *ML*

## PROPOSAL PUTS TINY PCs IN EMBEDDED APPLICATIONS

A proposed extension to the IEEE-P996 AT-bus specification defines the PC/104 form factor for a family of compact modules. The family offers PC compatibility in places where PC cards simply didn't fit, such as embedded environments. The 3.6-by-3.8 boards, which provide a unique self-stacking "stack-through" header, contain two bus connectors, a 64-pin P1 type and a 40-pin P2 type. With the proposal, designers can build lower-cost and reduced-power systems by eliminating backplanes and card cages. A typical power consumption of about 1 or 2 W will result from the 6-mA bus-drive requirement. The PC/104 specification is based on Ampro Computers' MiniModule form factor, originally designed as a daughterboard expansion module for the company's Little Board family of single-board computers. The twelve-member PC/104 Consortium includes Ampro Computers, Automation Instruments, BG Technologies, Diamond Systems, DMS Systems, Enclosure Technologies, IOtech, Quantum Software Systems, Real Time Devices, Reflection Technology, Voice Connexion, and Xecom. For more information, call Rick Lehrbaum, Consortium Chairman, at (408) 245-9348. *RN*

## FAST-ACCESSING DRIVE HOLDS 1.24 GBYTES

Through a combination of a low-mass actuator, a high rotational speed (6300 rpm), and a novel digital-hybrid servo mechanism, a 3.5-in. full-height disk drive achieves the industry's shortest average access time of just 8.5 ms. The digital-hybrid servo lets designers increase the number of tracks per inch, enabling the drive to pack the highest level of formatted storage for a 3.5-in. unit—1.24 Gbytes. With the disk's high rotational speed, data can transfer between the disk and the read/write heads at 44 Mbits/s. Moreover, the high speed keeps the rotational latency to just 4.76 ms, also one of the shortest times in the industry. Designers at Maxtor Corp., San Jose, Calif., have also applied a higher level of silicon integration to the drive's internal controller than seen in previous Maxtor storage products. An internal 256-kbyte cache provides a buffer between the read channel and the 10-Mbyte/s SCSI-2 byte-wide system interface. The cache can be split into multiple segments and can implement a read-ahead algorithm to maximize performance, especially when the SCSI tag-queuing commands are employed. Furthermore, through the drive's internal firmware, the cache can be tuned to optimize its use in various applications. Samples of the drive sell for \$1795 and are available immediately. *DB*

## PROGRAMMABLE FILTER NEEDS NO MULTIPLIERS

An innovative approach to digital filtering lets a single-chip filter provide full programmability of its pulse response without the need for a chain of on-chip expensive, high-speed multipliers. Developed by SGS-Thomson Microelectronics in Milan and Paris, the MH27HC68 operates at up to 40 MHz, suiting it for HDTV, video conferencing, and other applications requiring real-time video signal filtering. The chip addresses video-filtering applications that require only static programming of the filter response. Because filter coefficients are never reprogrammed during operation, the product of the filter coefficient and a given input signal magnitude will always have the same value. By storing this value as a precomputed entry in a lookup table, the M27HC68 eliminates the continuous recalculating of the input-sample and filter-coefficient products. The filter function is implemented as a transposed configuration, with the input sample being applied to 16 EPROM 256-word lookup tables simultaneously. The table outputs, which are the precomputed products of the input sample and the filter coefficients, are transferred in parallel to the arithmetic unit that contains a chain of 32 22-bit adders and 62 22-bit-wide registers. The M27HC68 is built with a 1.2- $\mu$ m CMOS process. Custom versions may be developed or integrated into ASICs to meet particular requirements. *JG*

## **SIMULATION MODEL BACKS 68302 PROCESSOR**

The 68302 multiprotocol communications processor from Motorola Inc., Austin, Texas, is now supported by the 302 SmartModel behavioral-level simulation package developed by Motorola and Logic Automation Inc., Beaverton, Ore. The simulation model enables hardware designers to develop, debug, and optimize the hardware operation of 302-based board- and system-level designs for a shorter time-to-market. Advanced modeling features include timing checks that look for undefined interrupts, uninitialized registers, illegal conditions, and timing violations. VHDL interoperability allows designers to mix models from multiple sources. The 302 SmartModel is available for a one-time \$4000 licensing fee paid to Motorola. Also required is a SmartModel Library license purchased separately from Logic Automation. For more information, contact Trey Oprendek at Motorola at (512) 891-3434, or Diane Landers at Logic Automation at (503) 690-6900. *ML*

## **PC MOTHERBOARD LOGIC IC TRIMS POWER DRAIN**

Although single-chip PC motherboard logic implementations for 80386SX systems have already been done, most are targeted at desktop systems. And they don't include any power-saving features. A forthcoming logic chip, which operates from as low as 2.7 V and offers four slow-clock options as well as a sleep mode, can considerably reduce average system power consumption. This is especially so when coupled with the AM386SXLV version of the 80386 from Advanced Micro Devices Inc., Austin, Texas. The HT22LV motherboard logic chip from Headland Technology Inc., Fremont, Calif., operates at system clock frequencies of up to 20 MHz and permits systems to select a clock division ratio of 2, 4, 8, or 16 to conserve power during operation (many applications, such as word processing or modem control, don't require that the processor run at maximum speed). The sleep mode allows the system to mostly power-down during long periods when the keys aren't depressed, a feature that resembles a bookmark. With the chip's "bookmark" operation, users can stop what they're doing and then re-open the system to where they left off. Housed in a 208-lead package, the logic chip supports 8- or 16-bit system BIOS and 4 Mbytes of DRAM. It sells for \$30 each in lots of 1000. Contact Ken Plewa, (510) 623-7857. *DB*

## **FAST RISC PROCESSOR FITS CAR CONTROLS**

With the development of a car signal processor (CSP), a universal signal processor can now execute and monitor a wide range of real-time in-car control applications. Examples of such tasks include anti-blocking, active shock absorption, wheel-slip control, and fuel injection. The heart of the CSP, developed by the ITT Semiconductors Group in Freiburg, Germany, is an 80-MIPS microcontroller using a RISC architecture and operating with an effective computing power of 32 MIPS. It's surrounded by a standard periphery optimized to meet automotive requirements. The CSP handles twenty-four 10-bit analog inputs and has eight 16-bit outputs that can be flexibly adapted to the desired control task via software. The 1.2- $\mu$ m CMOS IC is supplied in a 68-pin PLCC package and is available as engineering samples. *JG*

## **MPU-ASIC COMBO EASES LASER-PRINTER DESIGN**

Through an agreement with Advanced Micro Devices, Sunnyvale, Calif., Destiny Technology Corp. can port their line of printer-controller ASICs to AMD's Am29200 microcontroller. Destiny, located in Milpitas, Calif., announced its edge-enhancement technology (EET) and raster-image-device-accelerator (RIDA) controller ASICs last year. "This is a further customization of an embedded MPU for the laser-printer market. And it's an additional integration step beyond what Intel has done with their 82961KA," claims David Larrimore, vice president of marketing for Destiny. Instead of using a processor chip, an interface part, and a printer controller, the AMD-Destiny solution requires just the Am29200 and the Destiny ASIC. Designers will get similar results from using a two-chip solution, the i960 plus the 82961KA, or a one-chip solution, AMD's Am29200.

This solution follows a trend toward distributed processing, which is to incorporate as much of the common core functionality as possible on to the system board or the MPU. More detailed functions, which requires a specialized piece of hardware or firmware like EET or RIDA, can then fit onto the system board more easily. As distributed processing becomes more of a factor in printer controllers, the software that drives the hardware and even the hardware itself becomes more tightly integrated. The combination of reduced board space and the price-performance level of the Am29200 suit it for next-generation laser printers. *RN*

# THREE of a KIND

A Winning Hand of Power Amplifiers

## PA04

### Sonar

The combination of voltage rating of up to 200V, current up to 20A, and a power bandwidth of 90KHz makes PA04 ideal for sonar transducer drive. Resonant output circuits improve efficiency and power output. 100+ pricing is \$168.00.

## PA03

### Motor

Super power describes the PA03. With 500W of internal power dissipation, a 150V supply and  $\pm 30A$  of output current, the PA03 is a complete high power motor drive solution. 100+ pricing is \$320.00.

## PA05

### Deflection

High speed makes the PA05 operational amplifier the choice for deflection applications. Combining a 100V/ $\mu s$  slew rate with a 100V supply,  $\pm 30A$  output current, thermal protection, and a 360kHz power bandwidth, makes the PA05 a cost effective solution. 100+ pricing is \$189.00.

## Special Pricing on Evaluation Units!

Sample any one of these powerful parts at the 100-piece price\*. Plus save 50% on an EK04 evaluation kit with the purchase of a PA05 or PA04—just \$49.50 (kit includes heatsink, PC board, mating socket and hardware kit). See ordering information below. But hurry, this offer expires March 27, 1992\*.

\* Offer good for a one-time order of up to three sample units and evaluation kits.

For Immediate  
Product Information,  
or to Place an Order  
Call 1-800-448-1025  
or FAX (602) 888-3329



APEX MICROT TECHNOLOGY CORPORATION  
5980 N. SHANNON ROAD, TUCSON, ARIZONA 85741

For Applications  
or Product Selection  
Assistance Call Toll  
Free 1-800-421-1865


AUSTRALIA, NEW ZEALAND (08) 277-3288 BELGIUM/LUXEMBOURG (03) 458 3033 CANADA (416) 821-7800 DAEHAN MINKUK (02) 745-2761 DANMARK 42 24 48 33  
DEUTSCHLAND (6152) 61081 ESPAÑA (1) 409 47 25 FRANCE (1) 69 07 08 24 HONG KONG 8339013 INDIA (212) 339836 ISRAEL (3) 9345171 ITALIA (2) 99041977  
NEDERLAND (10) 451 9533 NIPPON (3) 3244-3787 NORGE (2) 50 06 50 ÖSTERREICH (222) 505 15 220 PEOPLES REPUBLIC OF CHINA (86) 500 7738  
REPUBLIC OF SOUTH AFRICA (021) 24-4071 SCHWEIZ (56) 26 54 86 SINGAPORE 284-8537 SUOMI (0) 8041-041 SVERIGE (8) 795 9650  
TAIWAN—REPUBLIC OF CHINA (02) 721-9533 TURKIYE (1) 337 22 45 UNITED KINGDOM (844) 278781

CIRCLE 86 FOR U.S. RESPONSE

CIRCLE 87 FOR RESPONSE OUTSIDE THE U.S.

# RF TRANSFORMERS

Over 50 off-the-shelf models...

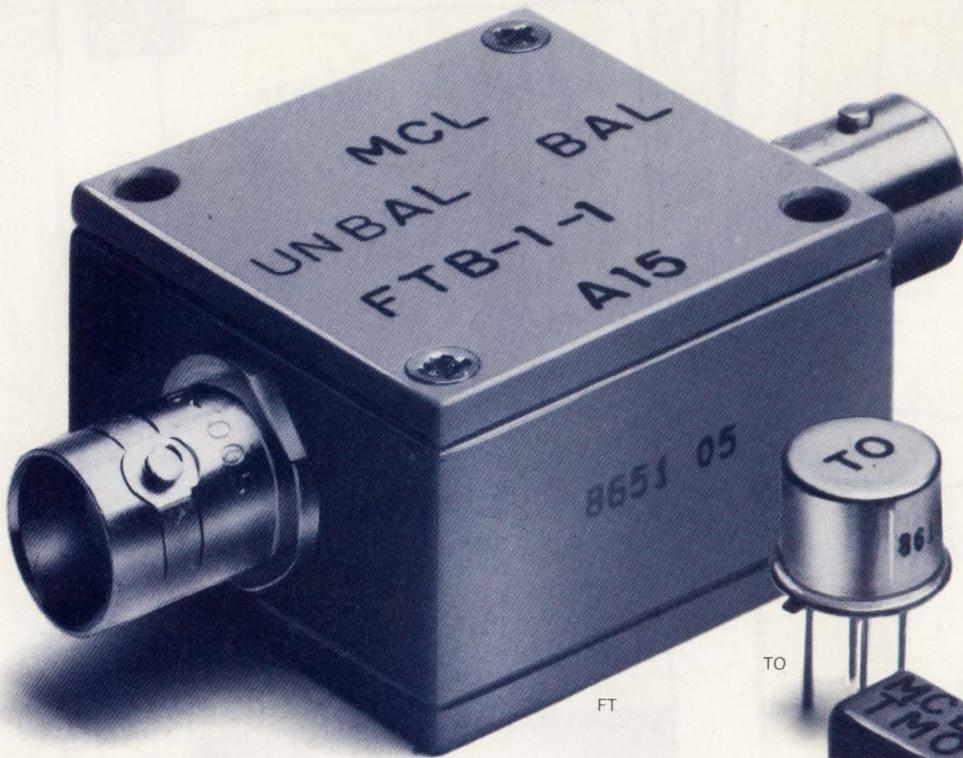


Having difficulty locating RF or pulse transformers with low droop, fast risetime or a particular impedance ratio over a specific frequency range? ... Mini-Circuits offers a solution.

Choose impedance ratios from 1:1 to 36:1, connector or pin versions (plastic or metal case built to meet MIL-T-21038 and MIL-T-55831 requirements\*). Ultra-wideband response achieves low droop and fast risetime for pulse applications. Ratings up to 1000M ohms insulation resistance and up to 1000V dielectric voltage. For wide dynamic range applications involving up to 100 mA DC primary current, use the T-H series. Coaxial connector models are offered with 50 and 75 ohm impedance; BNC standard; request other types. Available for immediate delivery with one-year guarantee.

Call or write for 68-page catalog or see our catalog in EEM, or Microwaves Product Data Directory.

\*units are not QPL listed

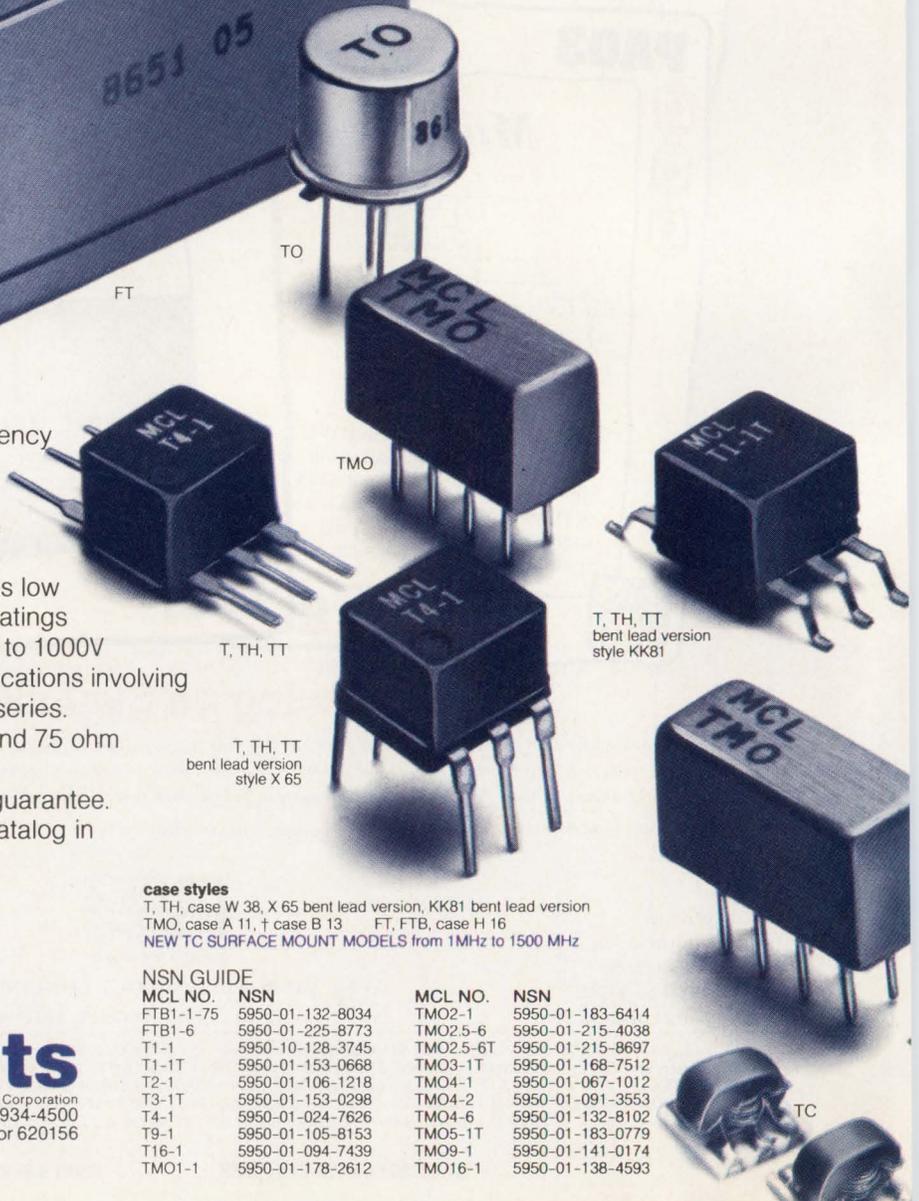

#### case styles

T, TH, case W 38, X 65 bent lead version, KK81 bent lead version  
TMO, case A 11, † case B 13 FT, FTB, case H 16  
NEW TC SURFACE MOUNT MODELS from 1MHz to 1500 MHz

#### NSN GUIDE

MCL NO.	NSN	MCL NO.	NSN
FTB1-1-75	5950-01-132-8034	TMO2-1	5950-01-183-6414
FTB1-6	5950-01-225-8773	TMO2.5-6	5950-01-215-4038
T1-1	5950-10-128-3745	TMO2.5-6T	5950-01-215-8697
T1-1T	5950-01-153-0668	TMO3-1T	5950-01-168-7512
T2-1	5950-01-106-1218	TMO4-1	5950-01-067-1012
T3-1T	5950-01-153-0298	TMO4-2	5950-01-091-3553
T4-1	5950-01-024-7626	TMO4-6	5950-01-132-8102
T9-1	5950-01-105-8153	TMO5-1T	5950-01-183-0779
T16-1	5950-01-094-7439	TMO9-1	5950-01-141-0174
TMO1-1	5950-01-178-2612	TMO16-1	5950-01-138-4593

finding new ways ...  
setting higher standards

## Mini-Circuits







A Division of Scientific Components Corporation

P.O. Box 350166, Brooklyn, New York 11235-0003 (718) 934-4500

Fax (718) 332-4661 Domestic and International Telexes: 6852844 or 620156

# FORMERS

3KHz-800MHz from \$3<sup>25</sup>

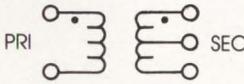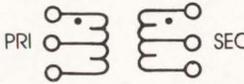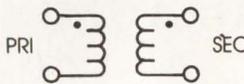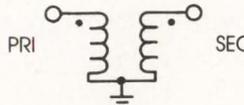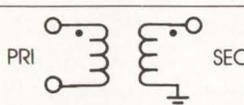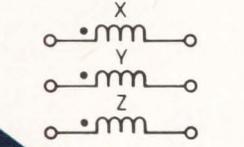case style number see opposite page	MODEL NO.	$\Omega$ RATIO	FREQUENCY MHz	INSERTION LOSS			PRICE \$ Qty. (1-9)			
				3dB MHz	2dB MHz	1dB MHz				
A* 	T	T1-1T	1	.05-200	.05-200	.08-150	2-80	4.45		
		T1-6T	1	.003-300	.003-300	.01-150	.02-50	6.95		
		T2-1T	2	.07-200	.07-200	1-100	5-50	4.95		
		T2.5-6T	2.5	.01-100	.01-100	.02-50	.50-20	4.95		
		T3-1T	3	.05-250	.05-200	1-200	5-70	4.95		
		T4-1	4	2-350	2-350	.35-300	2-100	3.25		
		T4-6T	4	.02-250	.02-250	.05-150	0.1-100	4.45		
		T5-1T	5	3-300	3-300	6-200	5-100	4.95		
		T8-1T	8	.03-140	.03-140	10-90	1-60	7.95		
		T13-1T	13	3-120	3-120	7-80	5-20	4.95		
		T16-6T	16	.03-75	.03-75	.06-30	1-20	5.65		
		TH	T4-1H	4	10-350	10-350	15-300	25-200	5.95	
			TMO1-1T	1	.05-200	.05-200	.08-150	2-80	7.95	
			TMO2-1T	2	.07-200	.07-200	1-100	5-50	8.45	
			†TMO2.5-6T	2.5	.01-100	.01-100	.02-50	.05-20	8.45	
			†TMO3-1T	3	.05-250	.05-250	1-200	5-70	7.95	
TMO4-1	4		2-350	2-350	.35-300	2-100	6.25			
TMO	TMO5-1T	5	3-300	3-300	6-200	5-100	8.45			
	TMO13-1T	13	3-120	3-120	7-80	5-20	8.45			
	B* 	TT	TT1-6	1	.004-500	.004-500	.02-200	1-50	6.95	
TT1.5-1			1.5	.075-500	.075-500	2-100	1-50	5.95		
TT2.5-6			2.5	.01-50	.01-50	.025-25	.05-10	6.45		
TT4-1			3	.05-200	2-50	2-50	1-30	5.95		
TT4-1A			4	0.1-300	0.1-300	0.2-250	0.3-180	6.95		
TT25-1			25	.02-30	.02-30	.05-20	1-10	9.95		
TTMO			TTMO25-1	25	.02-30	.02-30	.05-20	1-10	11.95	
			TTMO1-1	1	.005-100	.005-100	.01-75	.05-40	11.45	
			TTMO4-1A	4	0.1-300	0.1-300	0.2-250	0.3-180	13.95	
C 			T	T1-1	1	.15-400	.15-400	.35-200	2-50	3.25
	T1.18-3	1.18		0.01-250	0.01-250	0.02-200	0.03-50	5.65		
	T1-6	1		.01-150	.01-150	.02-100	.05-50	5.65		
	T1.5-1	1.5		1-300	1-300	2-150	5-80	4.45		
	T1.5-6	1.5		.02-100	.02-100	.05-50	0.1-25	5.65		
	T2.5-6	2.5		.01-100	.01-100	.02-50	.05-20	4.45		
	T4-6	4		.02-200	.02-200	.05-150	1-100	4.45		
	T9-1	9		.15-200	.15-200	3-150	2-40	3.95		
	T16-1	16		3-120	3-120	7-80	5-20	4.45		
	T36-1	36		.03-20	.03-20	.05-10	1-5	6.95		
	TO	TO-75		1	10-500	—	10-500	40-250	6.95	
		T1-1H		1	8-300	8-300	10-200	25-100	5.95	
	TH	T9-1H		9	2-90	2-90	3-75	6-50	6.45	
		T16-H		16	7-85	7-85	10-65	15-40	6.45	
	TMO	TMO1-02		1	1-800	1-800	2-500	—	9.45	
		TMO1-1		1	.15-400	.15-400	.35-200	2-50	6.25	
		TMO1.5-1		1.5	1-300	1-300	2-150	5-8	8.45	
		†TMO2.5-6		2.5	.01-100	.01-100	.02-50	.05-20	7.95	
		†TMO4-6		4	.02-200	.02-200	.05-150	1-100	7.95	
		TMO6-1		6	3-200	3-200	5-150	5-50	7.95	
TMO9-1		9	.15-200	.15-200	3-150	2-40	7.95			
TMO16-1		16	3-120	3-120	7-80	5-20	7.95			
D 		T	T2-1	2	.050-600	.050-600	1-400	5-200	3.95	
			T3-1	3	5-800	5-800	2-400	—	4.45	
	T4-2		4	2-600	2-600	5-500	2-250	3.95		
	T8-1		8	.15-250	.15-250	25-200	2-100	3.95		
	TMO	T14-1	14	2-150	2-150	5-100	2-50	4.95		
		TMO2-1	2	.050-600	.050-600	1-400	5-200	7.95		
		TMO3-1	3	5-800	5-800	2-400	—	8.45		
		TMO4-2	4	2-600	2-600	5-500	2-250	7.95		
		TMO8-1	8	.15-250	.15-250	25-200	2-100	7.95		
		TMO14-1	14	2-150	2-150	5-100	2-50	8.45		
		FT	FT1.22-1	1.22	.005-100	.005-100	.01-50	.05-25	35.95	
			FT1.5-1	1.5	1-400	1-400	5-200	1-100	35.95	
		E 	FTB	FTB-1	1	2-500	2-500	5-300	1-100	36.95
				FTB1-6	1	.01-125	.01-125	.05-50	1-25	36.95
■FTB1-75	1			5-500	5-500	5-300	10-100	36.95		
F 	T	T-622	1	0.1-200	0.1-200	0.5-100	5-80	3.25		
		T626	1	0.01-10	0.01-10	0.2-5	.04-2	3.95		

■ Denotes 75 ohm models


\* FOR A AND B CONFIGURATIONS

Maximum Amplitude Unbalance  
0.1 dB over 1 dB frequency range  
0.5 dB over entire frequency range


Maximum Phase Unbalance  
1.0° over 1 dB frequency range  
5.0° over entire frequency range

CIRCLE 116 FOR U.S. RESPONSE

CIRCLE 117 FOR RESPONSE OUTSIDE THE U.S.

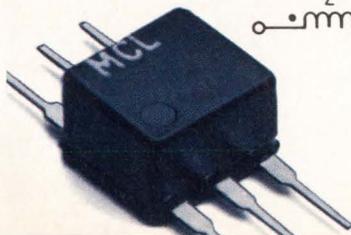

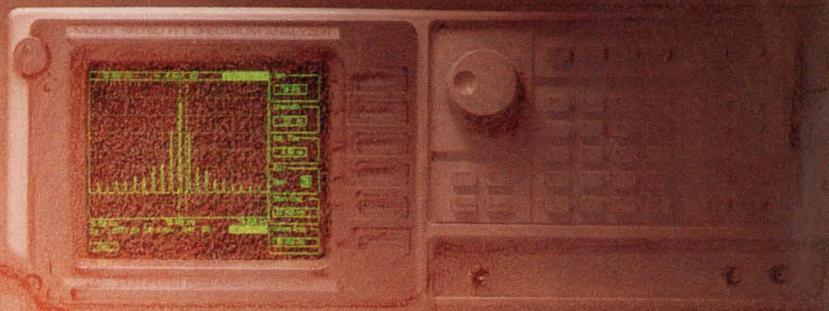In 1807, Joseph Fourier had a great idea.  
In 1991, SRS makes it affordable.



## Presenting the SR760 FFT Spectrum Analyzer. 16-bit 100kHz performance for only \$4350.

Have you been waiting for someone to make a truly affordable FFT spectrum analyzer? One with 90 dB dynamic range, 100 kHz frequency span, and a blazing 50 kHz real time bandwidth?

The wait is over.

SRS delivers the SR760. The perfect spectrum analyzer for a wide range of applications, including acoustics, vibration, noise analysis, electronic design and testing. Applications that previously meant buying a \$15,000 instrument.

The SR760. Power, performance and price. Everything you've been waiting for.

---

### SR760

---

- DC to 100 kHz frequency span
  - 90 dB dynamic range
  - 16 bit A/D conversion
  - Single channel with true differential input
  - 50 kHz real-time bandwidth
  - Internal or External Trigger
  - Limit testing and data tables
  - Menu based user interface
  - 3.5 inch DOS compatible disk drive
  - Direct hardcopy to printers and plotters
  - GPIB, RS232, and Printer interfaces
- 




**STANFORD RESEARCH SYSTEMS**

1290 D Reamwood Avenue, Sunnyvale, CA 94089 TEL (408)744-9040 FAX 4087449049 TLX 706891 SRS UD

CIRCLE 184 FOR U.S. RESPONSE

CIRCLE 185 FOR RESPONSE OUTSIDE THE U.S.

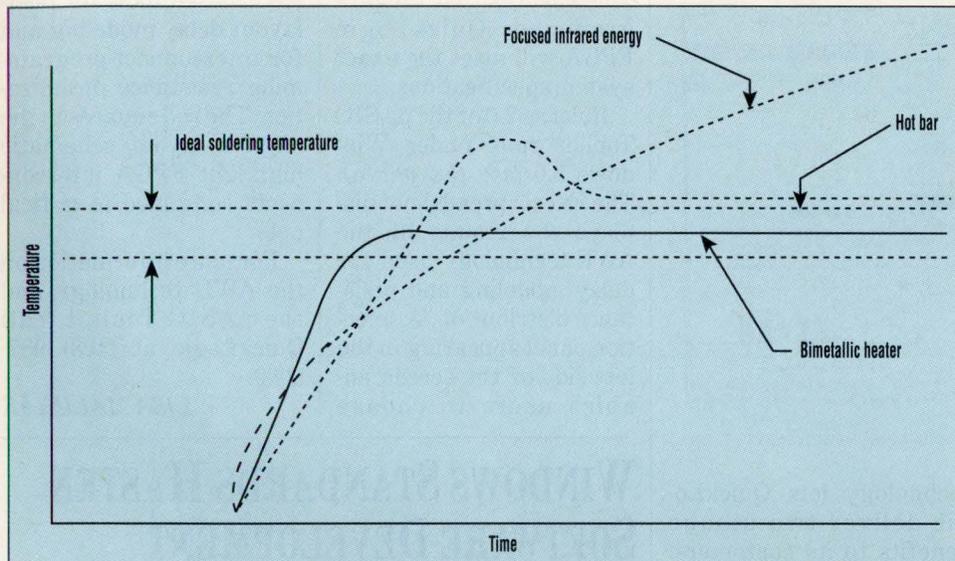

## SOLDERING-TECHNOLOGY GAINS IMPROVE CABLE ASSEMBLIES

The integrity of high-speed signals traveling from board to board depends on many variables, a significant one being the quality of solder joints in the cable assemblies linking those boards. A new soldering process for automatic cable-assembly terminations is expected to significantly advance solder-joint quality toward six-sigma levels.

Scientists at AMP Inc., Harrisburg, Pa., have devised a soldering technology that relies on a combination of electrical and metallurgical phenomena to maintain temperatures across the heater strip within a narrow range, independent of thermal load and application time. Because the strip can't overheat or underheat, the result is uniformly high-quality solder joints.

In conventional hot-bar soldering of cable assemblies, a heater bar typically comes in contact with a linear array of stripped wires.

Direct current heats the bar enough to melt the solder and form joints. The heater then shuts off to let the solder set before the assembly moves to the next manufacturing stage.

The temperature-time curve for each joint depends on such variables as the physical contact of the hot bar with the wire, the heating current, and ambient conditions. Overheating can damage connector parts while underheating causes poor solder joints.

The process takes advantage of a magnetic material's change in permeability as temperature increases. The heater strip consists of a bimetallic strip of a magnetic material over a nonmagnetic material. The magnetic material has a Curie temperature somewhat higher than the solder's melting point. Power comes from an RF constant-current source, which allows the skin effect to be exploited in order to control the heat-

er strip's temperature.

Direct currents flow throughout the entire cross section of a conductor, but high-frequency currents flow only in a narrow band near the conductor's surface. As frequency increases, the current becomes confined to an increasingly narrow band. The depth of the band is referred to as the "skin depth." For a magnetic material, the skin depth depends directly on the electrical resistivity and inversely on the frequency of the current source and the magnetic permeability.

With power on, the skin

effect confines current to the magnetic layer of the bimetallic heater strip. The layer's resistance is high and skin depth is small, so it heats up rapidly. As the magnetic layer approaches its Curie temperature, the skin depth increases enough for current to flow into the highly conductive nonmagnetic layer. Therefore, the Joule heat generated decreases and all points along the strip reach an equilibrium temperature—the Curie temperature of the magnetic layer. The current shifts from layer to layer as thermal loads change, maintaining this temperature independently at every point along the heater's length.


The maximum temperature of the strip, then, is fixed by the Curie temperature of the magnetic layer. That value is determined by the composition of the magnetic material. The result is a temperature-time curve that compares favorably with that of hot-bar and focused-infrared soldering (see the figure). AMP plans to expand the use of the technique to other connector lines to take advantage of its improved consistency.

DAVID MALINIAK
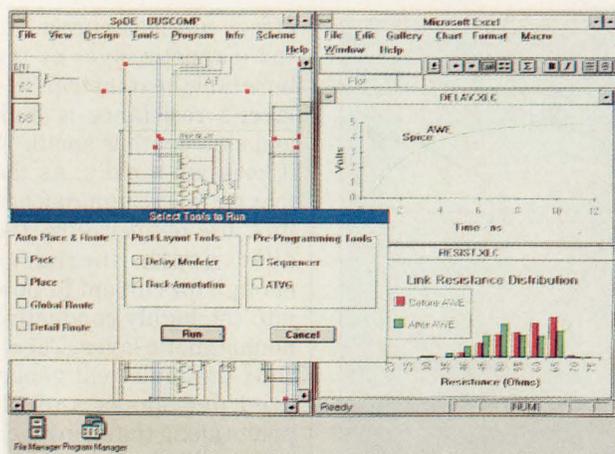
## WAVEFORM ANALYSIS YIELDS ACCURATE FPGA TIMING

Accurate characterization of interconnect resistance and capacitance effects become critical as field-programmable-gate-array (FPGA) speeds approach 100 MHz. At that speed, the analog details of the digital-signal waveforms become an issue, and sig-

nal characterization must be done in terms of waveform calculations as opposed to the more traditional delay calculations. That's because delay RC tree models can describe FPGA circuit interconnects to only a first-order approximation. However, a new technique called As-



ymptotic Waveform Evaluation (AWE) describes FPGA circuit interconnects to an nth-order approximation. As a result, simulations of the same run time as previous techniques produce far more accurate results.

The AWE technique was developed by Professors Lawrence T. Pillage of the University of Texas at Austin and Ronald R. Rohrer of Carnegie-Mellon University, Pittsburgh, Pa. It uses moment-matching approximations to efficiently evaluate the delays caused by distributed resistance and capacitance. For large interconnects, the AWE technique yields results that are as accurate as Spice simulations, while reducing simulation computing time by orders of magnitude. AWE employs frequency-domain techniques to successively converge on the actual waveform, similar to the Spice time-domain analysis that serially evaluates the waveform in small increments of time.

QuickLogic Corp., Santa Clara, Calif., is the first company to apply AWE analysis in a commercial product—the pASIC Toolkit Release 2.0. The AWE

technology lets QuickLogic deliver two unique benefits to its customers. First, AWE can increase overall FPGA speed by optimizing the programming sequence of the interconnects. To accomplish this, AWE first identifies the most heavily loaded nets in an FPGA design. Then the device interconnects that make up these nets are identified and targeted for programming in a specific sequence that provides the lowest possible resistance values. Thus, the highest possible operating frequency is obtained. Maximum performance is available when these links are programmed in the range of 30 to 50  $\Omega$ . Most users will see a 20-25% FPGA speed increase with AWE technology.

A second customer benefit from AWE technology is the precision of the timing simulations. The AWE technique is used in the pASIC Toolkit to provide the most accurate timing models possible for the back-annotation of delay information into the timing simulator. The accurate timing models allow users to establish the precise system-level performance available from the FPGA.

This ensures that the programmed QuickLogic FPGA will meet the exact system specifications.

Release 2.0 of the pASIC Toolkit runs under Windows 3.0 (see the photo). The Excel spreadsheet displays the results of the AWE technology used for delay modeling and resistance distribution. A selection panel appearing in the left side of the screen enables users to choose

AWE-based tools for post-layout delay modeling and for interconnect-programming resistance optimization. The red squares in the physical-layout schematic highlight FPGA interconnects contained in critical nets.

For more information on the AWE technology and the pASIC Toolkit, call QuickLogic at (408) 987-2000.

LISA MALINIAK

## WINDOWS STANDARDS HASTEN SOFTWARE DEVELOPMENT

The role of software in image processing and data acquisition continues to grow as developers migrate toward Microsoft Windows 3.0 for their development environment. Now software development and operation using Windows has taken another step forward with the creation of DT-Open Layers, an open software architecture devised by Data Translation, Marlboro, Mass., that simplifies software development. Open Layers, which is offered free of charge to the public, consists of integrated, modular programming interface specifications. The company also offers a series of applications that conform to Open Layers called Global Lab. The applications include data acquisition, image processing, function libraries, and device interfaces.

The architecture removes the software's hardware dependence. By supporting one Open Layers-compliant board, it allows other boards to be added in the future, almost transparently. This is achieved by taking advantage of

Windows' dynamic link libraries.

Open Layers speeds software development: The company defined all of the interfaces between application function libraries and their respective device interfaces. By coding any one of those layers, a new application could easily be integrated with existing code and conform to the standard. In addition, such tools as interpreted-C scripting at the application layer are provided so that designers can prototype their applications before using the libraries.

Within the applications programming interface (API), which is the interface between the applications and the function libraries, the function calls are defined. Function calls assist in board configuration, such as setting up the acquisition speed or number of channels for a data-acquisition board. For an image-processing board, things to configure include the type of input signal and display type.

Open Layers defines function calls for such operations as acquiring, dis-

“Speed fascinates me. The Air Force has a jet that hit 2,193 mph. Instant face lift. A Lamborghini Diablo can push the needle over 200 mph. There’s a guy who once served a tennis ball 138 mph. And the fastest mile ever run? 3:46.32. Now that’s fast. Especially when you consider it takes a snail five days to cover the same ground. And speaking of speed, there’s Altera’s MAX 7000 family of programmable logic. With pin-to-logic delays of 12ns and system clock frequencies over 80 MHz. Plus fast, low skew routing with a predictable delay of 3ns or less. Whoosh! It just doesn’t get any faster than Altera’s MAX 7000. We’re talking warp speed.”



They're big. They're fast. They're everything you've asked for. Want to know more? Speed dial 1-800-800-7256.

**MAX7000**


CIRCLE 147 FOR U.S. RESPONSE

CIRCLE 148 FOR RESPONSE OUTSIDE THE U.S.
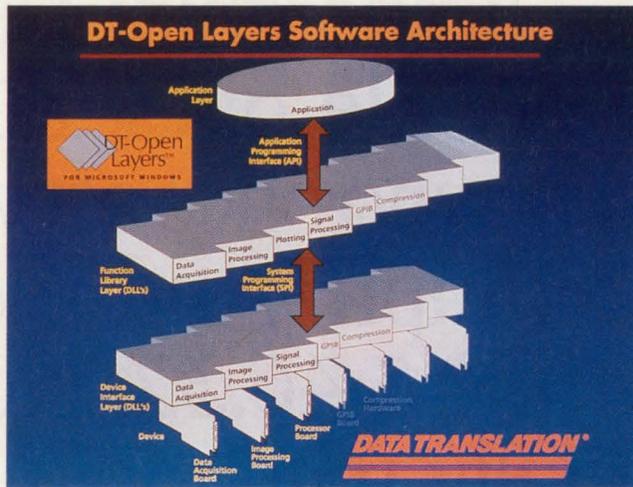
## TECHNOLOGY ADVANCES

playing, or storing data, and for protocols of buffer management and data locations. For example, if data is acquired using a data-acquisition board and a fast Fourier transform (FFT) is to be performed with a processor board, the processor board can find the data by invoking the buffer-management function once the data-acquisition board acquires and stores the data. Similarly, with an image-processing board, the data is acquired and stored in memory using the Open Layers protocols. A compression board then can access the data.

The System Programming Interface (SPI) defines the device interfaces as well as the interface between function libraries,



which are hardware independent. It contains the protocols for allocating devices in terms of whether the device is being used by a particular library or application. For example, if an FFT board is being im-


plemented, it allocates the processor board to the appropriate library to perform the FFT. After completion, the processor board is released for use by another application.

The SPI also allocates

the memory assignments for all devices. Then the board configuration and other functions are performed by the device control (this is automated by Open Layers).

Open Layers consists of three levels—the application layer, the function-library layer, and the device-interface layer. Data-acquisition and image-processing libraries are supplied at the function-library layer. Plotting and signal-processing libraries will be offered in the future. In addition, GPIB and compression libraries are available from third parties. Data Translation will provide the device interfaces for the company's boards as well as the function libraries. Third parties
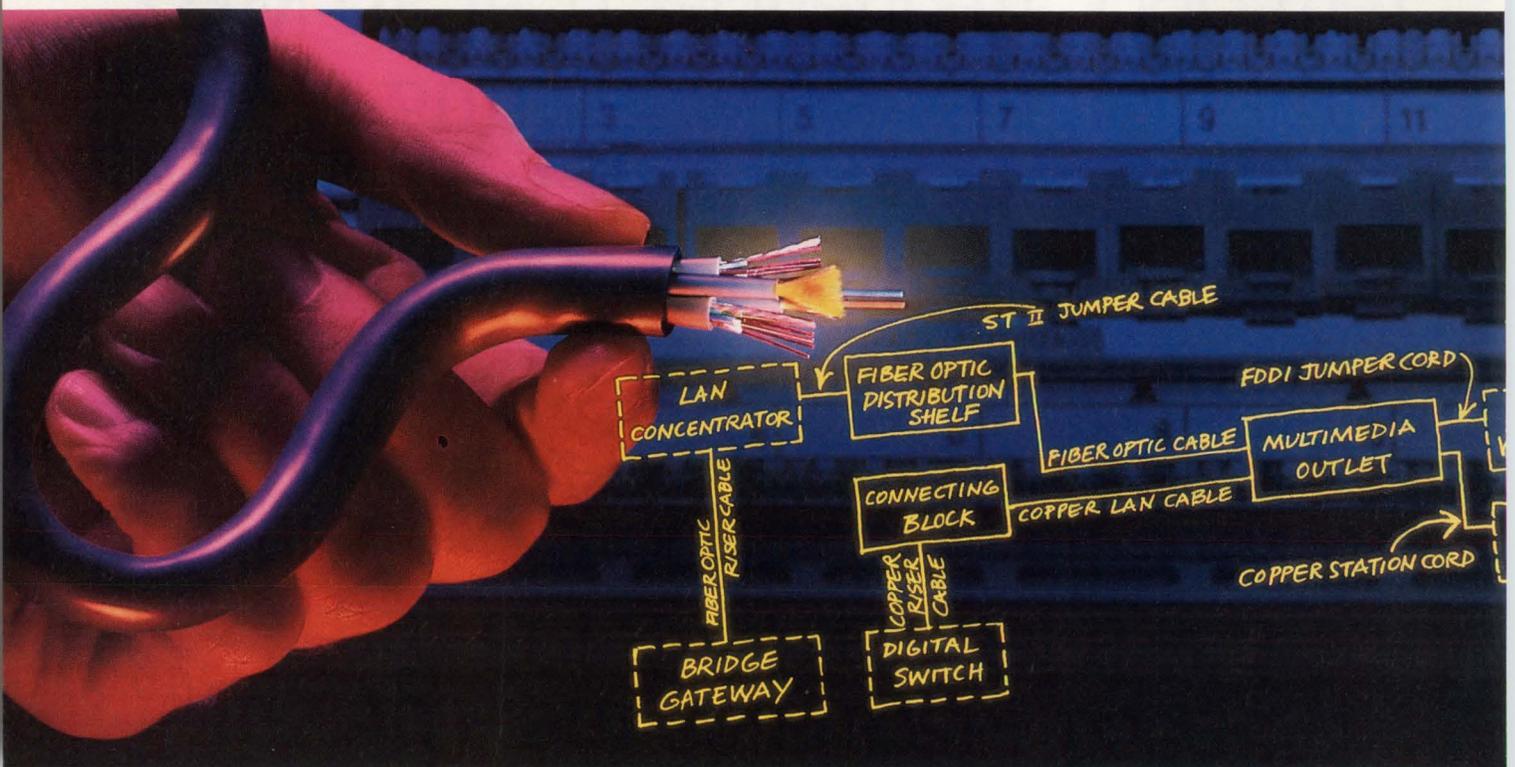
## Every connecting product for every kind



## TECHNOLOGY ADVANCES

could design signal-processing-device interfaces that would operate directly with Data Translation's signal-processing function library.

Windows introduces a method of modularization, one that's standardized when Open Layers is used. Windows essentially acts as a traffic cop, controlling all communications between the application, the function library, and the drivers. The operating system allows for and encourages the invocation of dynamic linking, which makes it easy to add new applications, function libraries, and drivers almost at will. And existing software needn't be recompiled and relinked to be joined with new software:

Windows provides the linking mechanism between each of those. For example, new hardware could be added to a system by simply loading the new driver interface.

Seeing Windows' modularization methods, Data Translation realized that the dynamic-linking capability would be a key element if Windows is to be used effectively. The standard was thus adopted so that designers don't have to be concerned with those interfaces. And because future software and hardware will fit into the same structure with very little, if any, change, simple software upgrades can be made.

The company is targeting three classes of cus-

tomers—end users, developers, and OEMs. Each class of users interacts with the various layers and interfaces of Open Layers in a different way. End users wanted applications optimized for themselves, which allowed future hardware additions without requiring changes to their application. It's not important how it gets implemented, just as long as they can add hardware later.

Developers want to be able to customize their applications with the knowledge that those applications will work with the function libraries, SPI, and drivers supplied by the hardware manufacturers. Using Open Layers, they set a software standard to ensure that their applica-

tions can simply plug into the function libraries and hardware support, and that they have full compatibility.

OEMs have needs at all three levels. At the application level, they want to do quick prototyping. Scripting capabilities were included to permit relatively fast prototype development of application software, so that a "test run" could be performed before production starts. The API's specifications allow the OEMs to do a test run, and encourages them to interface with the function libraries.

For more information on DT-Open Layers, call Data Translation at (508) 481-3700.

RICHARD NASS

# of connection.

© 1991 AT&T

## That's AT&T "Customerizing."

**AT&T is your one-stop quality source for everything from cable to splicing and test equipment.**

Whether it's data cable, composite cable, optical cable or fiber, AT&T has it all.

Along with 110 Connecting Blocks, ST<sup>®</sup> Connectors, FDDI Jumpers, and any number of other connecting products.

Everything you need in copper and fiber optics for the transmission of voice, data, image, and remote sensing.

Everything you need for all your applications, such as LAN and harsh environment, off-the-shelf or custom designed.

Technical support? We'll work side-by-side

with you to design special situation connections. And we'll provide system as well as component solutions.

You also have AT&T's assurance of product quality and reliability. Backed by the design and technology expertise of AT&T Bell Laboratories. And by a century of AT&T cable and apparatus manufacturing experience.

Giving you everything you need. Exactly the way you need it. That's what we mean by "Customerizing."




For more information, just give AT&T a call at 1 800 344-0223, ext. 1053. Outside the U.S. call: 602 233-5855.



CIRCLE 90 FOR U.S. RESPONSE

CIRCLE 91 FOR RESPONSE OUTSIDE THE U.S.

GRAPHICS  
WORKSTATION  
ISDN  
STATION

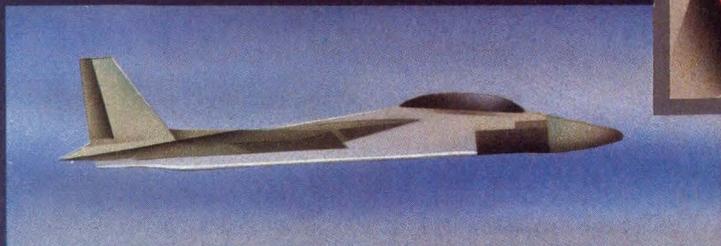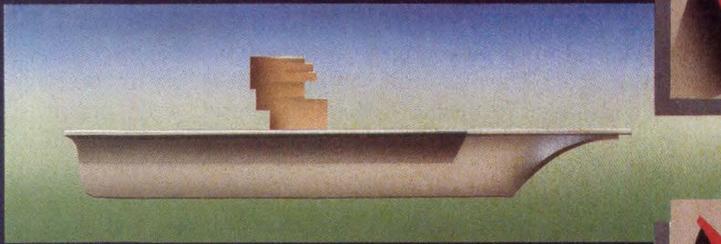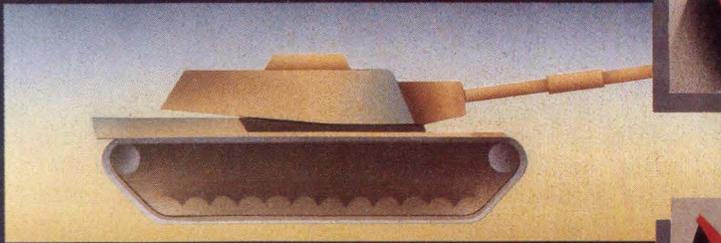


# Mil-Spec NDI Computer Sub-Systems to Meet the Standards of the U.S. Army, Navy, Air Force, Marines ...and the U.S. Taxpayer.

The urgent need for reliability in Mil-Spec equipment and systems requires no further justification. If you're designing or integrating computer systems for any of the Armed Forces, reliability is paramount. And it must be achieved at reasonable cost levels.

At Radstone Technology, we have a proven strategy that enables you to control costs without compromising reliability, quality or performance. Our Mil-Spec computer boards and sub-systems meet the most stringent U.S. and international military requirements *and* the increasing mandate for NDI (Non-Developmental Item) products. Radstone NDI Mil-Spec VME provides proven economies in terms of hardware, software development and compatibility, plus reduced time to market and performance-proven reliability. That's why, now more than ever, the DoD, military and prime contractors are counting on Radstone for Mil-Spec NDI VME.

Radstone Mil-Spec VME. It's the right way to cut costs without cutting corners. Let us show you how *your* programs can take advantage of our technology, using an accepted standard and a winning strategy. We'll help you meet the requirements of the military *and* the taxpayer.

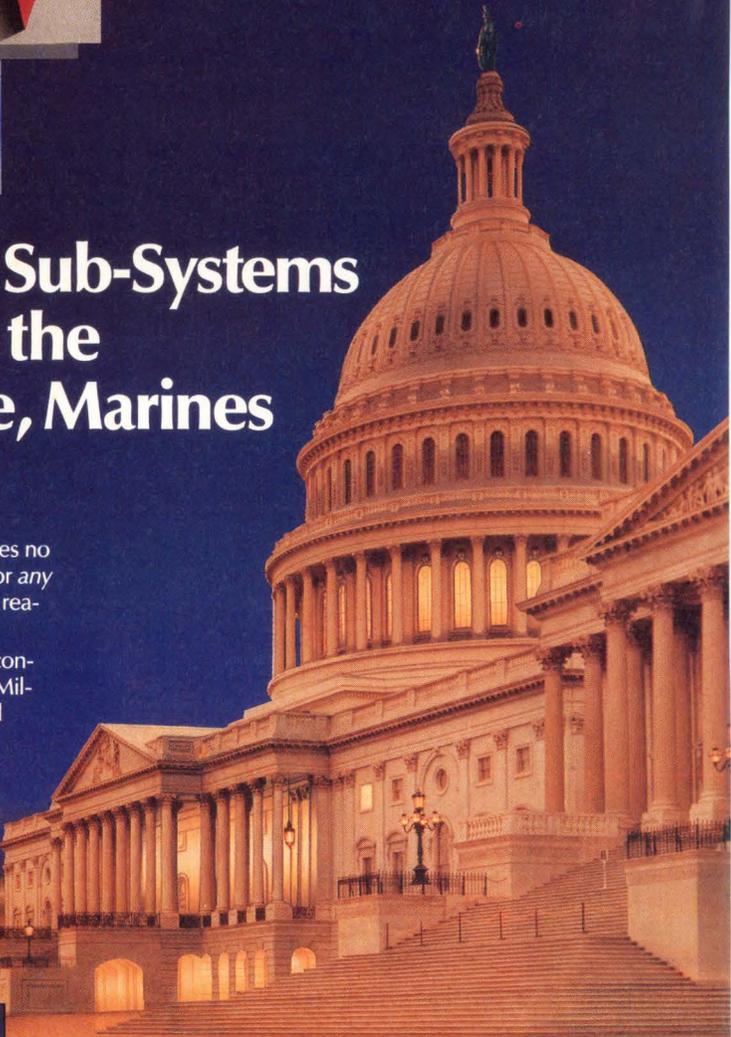**Radstone Technology Corporation**  
20 Craig Rd., Montvale, NJ 07645-1737  
**Call Toll-Free: (800) 368-2738**  
Eastern Region: (201) 391-2700  
Central Region: (708) 304-0202  
Western Region: (408) 727-4795



See Us At Buscon/92-West  
Booth #426



**RADSTONE**  
TECHNOLOGY

CIRCLE 167 FOR U.S. RESPONSE

CIRCLE 168 FOR RESPONSE OUTSIDE THE U.S.

# BUSCON '92 WEST: MEZZANINE BUSES RIDE A NEW WAVE OF POPULARITY

LESS-STRICT SPECIFICATIONS PERMIT MEZZANINE MODULES TO ADD FUNCTIONALITY WITHOUT THE TRADITIONAL TRADE-OFFS.

# W

hen the doors swing open at the Long Beach Convention Center in California for this year's Buscon '92 West show, being held Feb. 4-6, attendees will encounter a technical program and exhibits with a wide range of computer-technology subjects. One particular topic that's sure to pique interest is the use of mezzanine buses, an approach that adds flexibility and allows customization of computer boards.

Computer-board makers always seek out ways to differentiate their boards from the competition. One approach is to incorporate a mezzanine bus that can accommodate different daughterboard modules for almost any application. The performance trade-offs are minimal and there's a significant cost savings over designing full-size boards.

Users continually demand more performance, functionality, and customization on their boards, thus putting manufacturers at a disadvantage. A board customized for one user may not suit another, or it may have more functionality than is required, raising the cost. Mezzanine boards can solve this problem: By adding a mezzanine board to a general-purpose CPU board or a single-board computer, users can get the customization they desire, without the overkill.


Mezzanine boards perform many functions. They offer a finer grade of modularity when building a system in terms of memory, I/O, etc. They can also be a mechanism to implement custom interfaces rapidly and inexpensively. The modules have adapted long-standing architectures, such as VME, STD, and Multibus I and II, to new applications. They offer an easy integration path for multiprocessing on a standard bus without paying the

RICHARD NASS

typical performance and cost penalties associated with the standard buses.


Boards for almost all standard buses are now being built with some type of expansion capability. Some of the functions supplied by mezzanine boards include serial and parallel I/O, memory expansion, SCSI ports, networking, video controllers, and communications. In addition, customized modules can be built for unique functions.

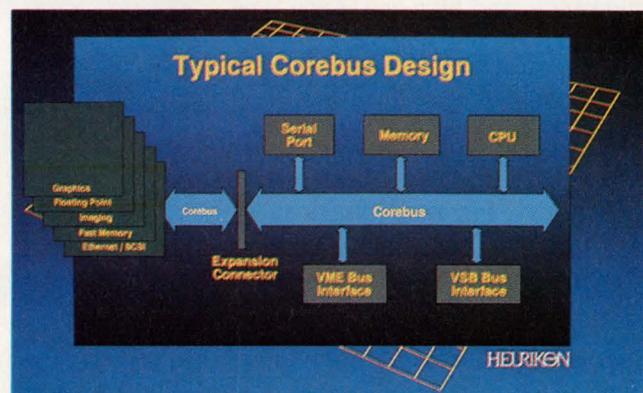The CPU board is typically used as the baseboard, and the mezzanine boards help to evolve the platform. Board makers discovered that CPU technology is progressing at a much faster pace than I/O technology. Therefore, users can keep their I/O functionality and just upgrade the CPU. From the users' point of view, they can buy base platforms and then add whatever modularity is



**1. COREBUS IS A HIGH-END synchronous mezzanine bus** from Heurikon that features a 50-MHz clock speed and a maximum bandwidth of 200 Mbytes/s. The bus can handle graphics, networking, and floating-point operations. It also supports four interrupt lines, each with a separate Acknowledge signal.

## BUSCON PREVIEW

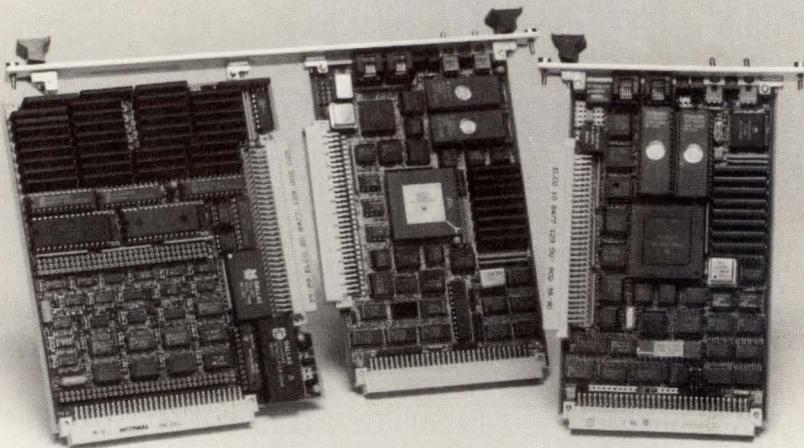

**2. WITH THE 3U CARDS' MXBUS CONNECTOR** mounted on the side, two cards can be joined together to fit into a 6U slot. The proprietary structure from Mizar contains a family of modules ranging from simple I/O ports to complex parallel-processor expansion modules.

needed to support those baseboards, whether it's I/O, memory, disk storage, or communications.

Another advantage to using mezzanine boards is that an extra slot isn't taken up because they become part of the baseboard. And the end-users win because they can buy a low-cost mezzanine board for a fraction of what a full-sized board containing the same functionality would sell for.


### LOW, MID, AND HIGH

Mezzanine buses can be loosely divided into three categories: low-end, mid-range, and high-end. Each type has its pluses and minuses, with the application dictating the appropriate one to implement. Some buses could be placed into more than one category. Low-end boards add some simple I/O functionality. They're basically inexpensive, but their functionality is somewhat limited. Examples of this type of implementation include SBX from Intel Corp., Hillsboro, Ore., and Industry Pack from Green Spring Computers, Menlo Park, Calif.

Industry Pack boards use a 2-in.<sup>2</sup> module with a low-cost interconnect scheme. The bus doesn't operate at a high speed and a minimum number of data and address lines are used. In addition, some interrupts are han-
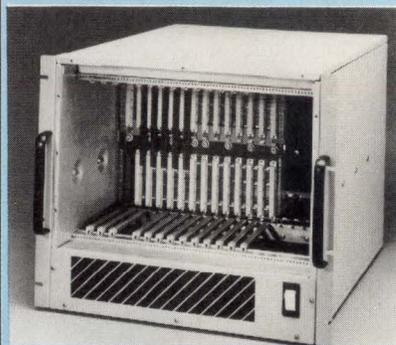
## BACKPLANE HOLDS BOTH AT, VME CARDS

**S**tandard PC/AT boards can be mixed with high-performance VME boards in the N6280 AT/VME backplane. The industrial-grade enclosure mounts in a 19-in. rack and has positive locking for both types of cards. A 750-W power supply and two high-volume exhaust fans give the N6280 the power and cooling needed



to support a twenty-board system in a factory environment. Prices start at \$4000, with OEM discounts available.

**Nissho Electronics Corp., Inwood Park, Suite 200, 17320 Red Hill Ave., Irvine, CA 92714; (714) 261-8811. **CIRCLE 571****  
■ Booth 626

dled. Silicon requirements for the interface can be managed by a few gates or a PAL.

The mid-range mezzanine bus enables the use of some memory or other higher-functionality I/O, such as SCSI, Ethernet, or alternative communication ports. These modules require more data, address, and control lines because a semi-intelligent microcontroller is synchronized to the local bus. This type of circuitry can generate some interrupts and allow some direct-memory access. Examples of mid-range mezzanine buses include SBus from Sun Microsystems, Mountain View, Calif. and DBUS-68 from Matrix Corp., Raleigh, N.C.

A full-function or high-end mezzanine bus can contain some intelligent devices and a sophisticated interface. Two examples of the high-end mezzanine bus are Corebus from Heurikon Corp., Madison, Wis., and FLXibus from Force Computers, Campbell, Calif., both of which are multiprocessing buses. SBus almost fits into this category because it's modules can contain reasonably-intelligent devices, but the bus can't be controlled from the mezzanine.

Corebus appears on both RISC and CISC CPU baseboards from Heurikon. To interface both high-speed modules (such as zero-wait-state memories) and slower peripheral modules (such as disk controllers), Corebus contains synchronous and peripheral buses. The synchronous bus features a 50-MHz clock speed and a maximum bandwidth of 200 Mbytes/s (Fig. 1). Using the bus' two-wire handshake, masters can control all key timing parameters. There's also support for four interrupt lines, each containing a separate Acknowledge line.

FLXibus uses 32-bit data and address lines decoupled from the processor-to-memory bus. It offers VMEbus master and slave capabilities and is fully compatible with the 68020 asynchronous interface. The FLXi daughterboards designed by Force are called Eagle modules. They come equipped with an ASIC to handle the FLXi interface and some other logic to make the modules in-



If your VAX or VMEbus needs  
16.7 Million Colors, call (510) 531-6500.

**Peritek**

Peritek Corporation

5550 Redwood Road, Oakland, California 94619

West Coast (510) 531-6500 fax (510) 530-8563


Mid West (303) 791-9161 fax (303) 791-9160

CIRCLE 163 FOR U.S. RESPONSE

CIRCLE 164 FOR RESPONSE OUTSIDE THE U.S.
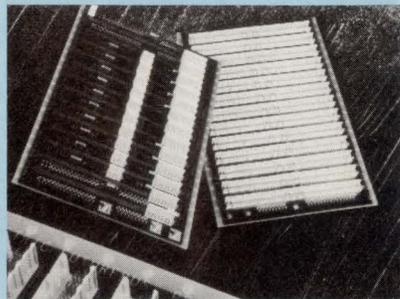
## FUTUREBUS+ BACKPLANE SUITS HIGH-SPEED APPLICATIONS

**A** 13-slot, 16-layer backplane from BICC-VERO complies with Profile F of the Futurebus+, IEEE P896.2 specification. The spec supports a 128-bit data bus with central arbitration. Skew is minimized by the surface-mounted 33-Ω resistors and high-speed capacitors that are arranged to exactly match the length of each signal trace. The capacitors supply local high-speed charge storage to each line. Further protection from ground-bounce effects is made possible by combining multiple power and ground planes with a ground-tracking pattern. Conforming mechanically to IEEE 1301.1, the backplane is 300-mm high and supports hard-metric Futurebus+ 265-by-288-mm daughterboards. Power for the 5-, 3.3-, 2.1-, and



0-V rails is supplied to the backplane through the company's LOMET connector, which offers a low-impedance interconnect to the multiple power and ground planes. The backplane costs about \$2000.

**BICC-VERO Electronics Inc., 1000 Sherman Ave., Hamden, CT 06514; (203) 288-8001. CIRCLE 572**  
**■ Booth 618**

terchangeable. Force currently offers modules for a host of applications, including the recently announced Eagle-10 and -11 boards with Ethernet and SCSI interfaces.


### STRICTLY FORMAL

The specifications for a system bus, such as Multibus or VME, are very formal, in terms of timing and conformance to the standard. "Any-

time you introduce formality into electronic interfaces, you introduce a certain level of performance degradation because there are a lot of timing issues that everyone has to conform to," says Ray Alderman, technical director of the VFEA International Trade Association (VITA), Scottsdale, Ariz. In a local or mezzanine interface, the guidelines aren't that formal. This aspect becomes sig-
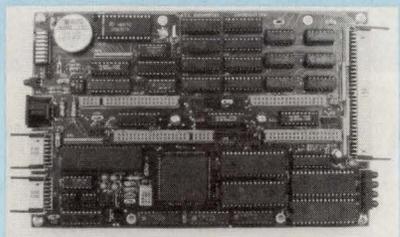
## EXPANDABLE SBC RUNS WITHOUT A BUS

**D**esigned for embedded applications, the SBX-C186EB 16-bit single-board computer (SBC) lets engineers design custom products without expensive and complicated bus systems. Although the SBC contains no bus, it can be expanded through four on-board iSBX connectors. The board is built with an 80C186 16-bit processor and an 80C187 coprocessor, both running at 16 MHz. On-board functions include a real-time clock, an interrupt controller, five 16-bit counter-timers, and 32 parallel I/O lines. Prices start at \$425.



Connector kits, mounting hardware, and power supplies are available.

**R.L.C. Enterprises, 4800 Templeton Rd., Atascadero, CA 93422; (805) 466-9717. CIRCLE 573**  
**■ Booth 802**

nificant when a board maker is building a board for a specific customer. Custom-application boards are easier to build, allowing them to reach the market faster.

Mezzanine buses simplify some of the tasks that would otherwise be difficult to implement on a system bus. One example involves using multiple processors. On the system bus, it's difficult to work out the interprocessor communications, such as how data will be shared, how tasks will be assigned, and how the processors will be synchronized, among other considerations. Adding a second processor doesn't necessarily supply twice the processing power. If the first processor can produce at 90% of its potential (bus-overhead issues sap some of the power), the second adds about 70 to 80% because it must arbitrate for the bus and exchange data. Plus there's twice as much overhead. The power supplied by each additional processor diminishes as more are added. This varies from bus to bus because different buses contain different levels of overhead.

Mezzanines alleviate this problem because there are very few standard-related restrictions on the bus. Consequently, mezzanine buses like Corebus, FLXibus, and, to some degree, SBus are turning up with multiprocessing configurations. These buses permit multiprocessor integration, saving time and reducing complexity when compared to doing the same implementation over the system bus. "Mezzanines are an enabling technology for multiprocessing and solve the bottleneck problems associated with the system bus," adds Alderman.

Quite often, a mezzanine architecture is configured around a processor. If an Intel processor is used, timing and gating obstacles must be overcome. For most cases, some type of state machine would be required. If it's a Sparc processor, then SBus becomes a wise mezzanine choice because most of the timing work is already done. In addition, many companies have laid most of the groundwork needed to implement Motorola 68000-based processors.

## BUSCON PREVIEW


Radstone Technologies, Montvale, N.J., based its two mezzanine architectures, PEX (Processor Extension) and APEX (Advanced PEX), on the 68000 interface. The signal conventions used on a PEX board offer easy integration into the 68000-family environment because the interface's predefined signals are optimized for this architecture. Little or no conditioning of the interface signals is needed. The PEX interface implements the data and address paths in a non-multiplexed fashion, reducing the complexity of the on-board module and increasing the bus' throughput. Because the processor handles the module's control and data movement, the PEX interface is implemented as a slave interface. This lessens the bus' complexity because no arbitration circuitry is needed on the module or the baseboard.

APEX implements full 32-bit data and addresses to efficiently move data over the mezzanine bus. It supports such processor features as dynamic bus sizing and caching to increase flexibility and performance. Another feature of APEX is that it can inform the processor as to whether the data residing on the bus should be cached. Because APEX implements a full master-slave interface, the module can gain access to resources, such as memory, on the baseboard.

Another reason for opting to implement one architecture over another can be pinpointed to the number of
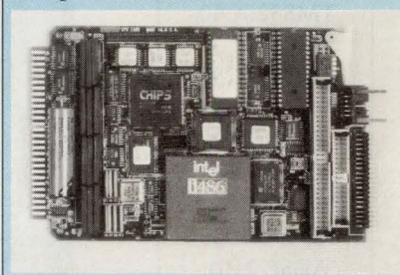
## STDBUS ADVANCES To 486 LEVEL

**D**esigned for industrial computing applications, the 7874 STDBus single-board computer (SBC) is based on Intel's i486 microprocessor running at 25 or 33 MHz. Full 32-bit data transfers can be made to the on-board RAM (4 to 16 Mbytes). The SBC operates with any STD I/O card that conforms to the STD-80 series specification for adding application-specific I/O functions. Microsoft's DOS 5.0 is included in the on-board ROM. Up to seven 80X86 CPU boards can be installed in the same backplane with the 7874. The board



comes with standard PC/AT peripheral devices, including a keyboard interface, two RS-232 serial ports, a parallel port, interrupt and DMA controllers, a counter-timer, and a battery-backed real-time clock. An optional VGA video board can be added. With 4 Mbytes of RAM, the 25-MHz board goes for \$2995.

*Pro-Log Corp., 2555 Garden Rd.,  
Monterey, CA 93940; (408) 372-  
4593. **CIRCLE 575**  
■ Booth 104*

## VME BOARD INTERFACES TWO MIL-STD-1553B BUSES

**T**wo MIL-STD-1553B buses can be interfaced using the MBI-2, an advanced full-military-specification intelligent VME-based board from Radstone Technology. Key features of the MBI-2 include one or two dual-redundant MIL-STD-1553B buses, a master-slave VMEbus interface with high-speed DMA controllers, and a 68020 processor subsystem to handle all of the 1553B protocols. A second offering from Rad-

stone, the single-slot FDDI-1 commercial FDDI controller, comes with separate data paths for control and processing elements. The board can hold up to 8 Mbytes of DRAM with 128 kbytes of FDDI buffer static RAM. Built with AMD's Supernet-2 chip set, the FDDI-1 offers concurrent 100-Mbit/s data transfers.

*Radstone Technology Corp., 20  
Craig Rd., Montvale, NJ 07645;  
(201) 391-2700. **CIRCLE 574**  
■ Booth 426*

mezzanine modules that are already available. For example, Sun Microsystems claims that at least 70 companies currently build SBus modules. Hence, almost any function a user could need is available. The baseboard manufacturer needn't worry about building a new module for each customer.

At last count, 22 mezzanine buses were being implemented on the VMEbus. Twelve of those have been placed in the public domain (meaning anyone can use them without incurring any costs). Making them public, though, causes them to be somewhat rigid: The governing companies can't just change the specifications on a whim. VITA became the holder for every mezzanine specification that's in the open domain, but doesn't rule on or change them (VITA publishes a document containing the specifications for each mezzanine bus, which is available for \$49). VITA looked into the possibility of standardizing one mezzanine bus for the VMEbus. But the idea was rejected after determining that different architectures are needed for the countless applications.

The twelve open architectures are: LEB (a mid-range bus) from Eltec, Germany; FLXibus (high-end); SAMbus (mid-range) from General Micro Systems, Montclair, Calif.; Industry Pack (low-end); Corebus (high-end); IV-XXXX (mid-range) from Ironics, Ithaca, N.Y.; DBUS-68 (mid-range); Omni (mid-range) from Omnibyte, West Chicago, Ill.; E-PAK and I/O PAK (mid-range) from Performance Technologies, East Rochester, N.Y.; EXMbus (mid-range) from RadiSys, Beaverton, Ore.; PEX (low-end) and APEX (mid-range); and SBus (high-end).

## THREE-IN-ONE


The Modular Interface eXtension (MIX), from Intel, offers something that VME-based mezzanine buses don't—the ability to stack up to three daughterboard modules on one baseboard. The 386 and 486 MIX baseboards include everything needed to connect the boards to the Multibus II bus, including the controller logic. The maximum transfer rate across

# Tap a reliable source of DSP

Times being what they are, now more than ever you need a faithful partner who can help you rise to the top.

A partner like Spectrum Signal Processing. One who saves you time, money and headaches by offering the broadest range of off-the-shelf DSP board-level solutions available. Solutions that fit your needs and put DSP to work. Each one fully tested. Fully warranted. And easy to implement.

Buses	I/O Options	All major DSPs
PC/AT	32 channel analog	TMS320C40
VME	16 channel analog	TMS320C30
SBUS	1 MHz transient capture	TMS320C50
Media-Link™	SCSI direct to disk	TMS320C25
	AES/EBU digital audio	DSP96002
	Multiprocessing communications	DSP56156
	Frame grab/display	DSP56001
		ADSP-21020
		ADSP-2101
		ADSP-2100
		DSP32C

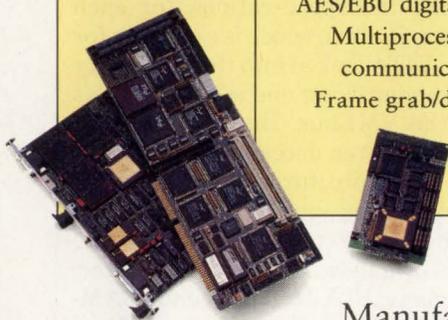

All backed by our Manufacturing Resource Planning System. That means the best service for you. From production scheduling to order processing. Plus, we provide complete support including extensive documentation, development software, applications notes and engineering assistance.

So go to the source that's gushing with DSP solutions by calling today for your free catalog or a distributor near you: 1-800-323-1842 (Western U.S.), 508-366-7355 (Eastern U.S.) or 604-438-7266 (Canada).



*Putting DSP to work*



Old Faithful, Yellowstone National Park

# solutions from Spectrum.



© 1991. Spectrum and Media-Link are trademarks of Spectrum Signal Processing, Inc. All other trademarks are trademarks of their respective holders.

CIRCLE 169 FOR U.S. RESPONSE

CIRCLE 170 FOR RESPONSE OUTSIDE THE U.S.

## BUSCON PREVIEW


the MIX bus is about 22 Mbytes/s, compared to about 2 Mbytes/s across Intel's SBX bus. In addition to the modules offered by Intel, users can customize their baseboards by designing company-specific modules using Intel's module-development kits.

The recently introduced 486 MIX baseboard has expanded-memory addressability—up to 68 Mbytes using two memory modules. Intel will continue to proliferate the daughter modules. "When people seem to be running out of gas with the 486 board, we'll throw something faster at them from a processor point of view. People have yet to exhaust MIX's bandwidth, so that's not a problem yet," says Dick Binns, hardware marketing manager at Intel. The idea behind MIX was to disassociate CPU technology from I/O technology so they could evolve at their own paces.

The initial modules offered by Intel were about half the size of a Multibus II card. Later, users were permitted to implement full-size daughterboards by stacking them under the baseboard. The original half-size cards are stacked on top of the baseboard.

Multibus II contains built-in testing circuitry that was extended into the MIX architecture. Each module contains an EPROM containing the system tests. Consequently, those boards are tested in the same manner as the baseboard. Multibus II also contains the logic needed to identify what types of boards are connected to the bus. That interconnect access was also included in the MIX modules so that the modules will identify and include themselves in the baseboard's interconnect information. An agent on the bus can then determine if a MIX baseboard is present, where it resides, if MIX modules are attached to the baseboard, and what type of modules they are.

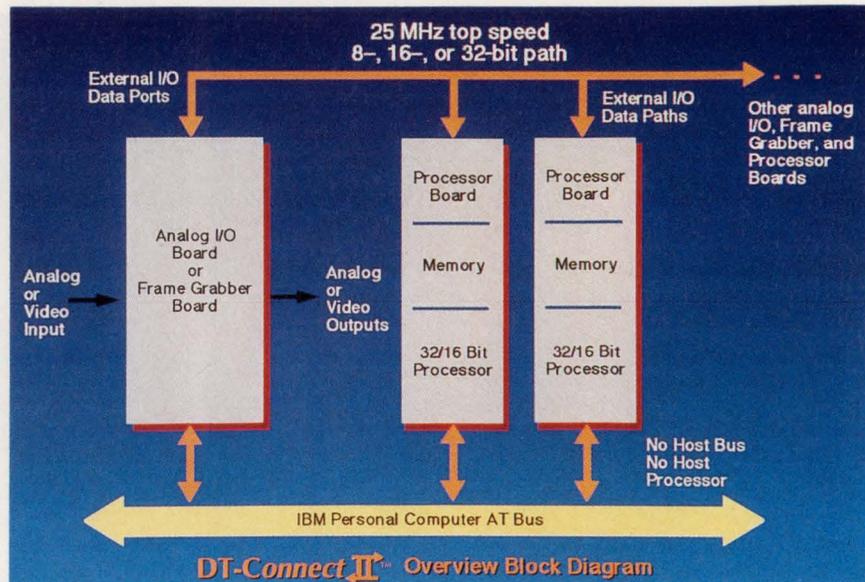The Futurebus+ specification incorporates a mezzanine architecture. Users will be able to stack multiple modules on its Futurebus+ Small Computer Expandability Module (FSCEM) bus. These credit-card-



**3. DESIGNED FOR THE PC/AT'S ISA architecture, DT-Connect II from Data Translation transfers data at speeds up to 100 Mbytes/s. This specification is logically and electrically compatible with its predecessor, DT-Connect, thus making it backward-compatible. Because the standard's 32-bit modes are symmetrical, any board can transfer data to and from any other board within the connection.**

size modules will boast a maximum operating speed of 250 MHz.

MIX and Onboard Modular Expansion (OME) from Siemens, Munich, Germany, also designed for the Multibus II environment, differ from SBX in the amount of available processing power. SBX is usually an extension of a base CPU board that's just looking for one extra feature. The MIX and OME boards are being relied on for independent functions, such as digital-signal processing or some high-performance I/O or communication application.

OME is similar in ability to MIX, but has a bandwidth of 40 Mbytes/s, compared to MIX's 22 Mbytes/s. It's not processor-specific and has been implemented on i860- and i960-based boards. In 1991, the number of MIX- and OME-based mezzanine boards grew by about 20%, from about 40 to around 50. SBX modules, now numbering around 200, increased by about 5 to 10%.

SBX has appeared on other buses besides Multibus. In fact, it's quite common on the STD bus. Computer Dynamics, Greer, S.C., offers SBX

## SPARC COMPATIBLES ADD INTERNAL MBUS

**T**wo Sparc-based VME boards, the SparcCards 2LC and 2SE, are compatible with the Sun Microsystems SparcStation 2, but contain an internal high-speed Mbus architecture. The two cards are fully VMEbus compliant, including address mapping for multiprocessing. The boards' integer performance is 30 MIPS at 40 MHz. The 2LC contains a 32-kbyte cache memory and 8 or 32

Mbytes of main memory, while the 2SE can hold 32 or 64 kbytes of cache and 8, 32, or 64 Mbytes of main memory. In addition, the 2SE has a built-in SCSI II controller and contains two SBus expansion slots. The 2LC sells for \$5995, while the 2SE is priced at \$7995.

*Themis Computers, 6644 Owens Dr., Pleasanton, CA 94566; (415) 734-0870. **CIRCLE 576***  
**Booth 723**

For years, people have been trying to run  
100 meters in under 9 seconds, clear 8 feet in the high jump,  
and hit 5.5 ns in a 22V10 PLD.



We're still having some trouble with the first two.



OK, the Olympics may not be in our future.

But the 5.5 ns barrier is history.

The 125 MHz\* TriQuint GA22V10-5 isn't just a pipe dream. It's proven. TTL-compatible. Price-competitive. And shipping right now.

We make it available in both surface-mount and DIP packages.

The GA22V10-5 is only one of a slew of record-setting performances in speed, quality, technology and service that you can count on from TriQuint — now comprising the combined forces of Gazelle Microcircuits,

GigaBit Logic, and TriQuint Semiconductor.

If you want a 25% performance advantage for your logic devices, and you're working on a fast track, call or write TriQuint for complete details on the GA22V10-5 today! **Call (408) 982-0900.**

CIRCLE 134 FOR U.S. RESPONSE


CIRCLE 135 FOR RESPONSE OUTSIDE THE U.S.

\*125 MHz external, 200 MHz internal  
Copyright©1991, TriQuint Semiconductor, Inc. All rights reserved. CN-001

**TriQuint**   
SEMICONDUCTOR
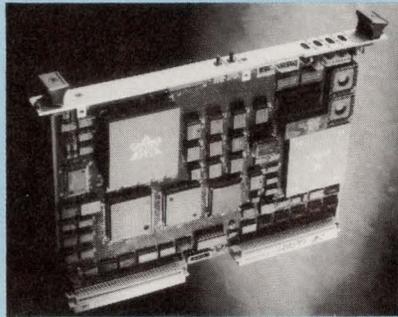
## RISC-BASED SBC SUITS COMPUTE-INTENSIVE TASKS

**M**otorola's latest single-board computer is based on the company's 88110 symmetric superscalar RISC microprocessor, which operates three to five times faster than its 88100 processor. The single-slot 6U board's architecture enables the 88110 to operate at peak performance during all operations. The board can be used for SCSI II peripheral I/O, multiple users, and networking. The 3D-graphics execution units and enhanced floating-point capability of the 88110 suit the board for compute-intensive applications. Flexibility is maximized using an expansion mezzanine port and a standard VMEbus subsystem bus



(VSB). Limited quantities should be available by the middle of the year.

**Motorola Computer Group, 2900 South Diablo Way, Tempe, AZ 85282; (800) 234-4VME. CIRCLE 577**  
**■ Booth 502**

modules for video control, parallel I/O, and memory, as well as other applications. The company's recently released CDX-COM is a communications module that offers PC/XT/AT-compatible serial and parallel ports. Standard features include two serial communications ports; RS-232, RS-422, or RS-485 communications; an asynchronous baud rate to

115 kbaud; and a bidirectional parallel printer port.

A variation of the mezzanine bus is the MXbus from Mizar Inc., Carrollton, Texas. The proprietary MXbus is based on the company's family of 680X0 VME CPU modules that contain VMEbus master and slave interfaces, EPROM, DRAM, full four-level system controllers, serial I/O, and

interrupt features. These boards were designed with a standard 16-bit expansion interface, but can be used with 32-bit CPU modules. Any 16-bit MXbus expansion card can be connected to a higher-speed 32-bit CPU module without requiring an expensive redesign.

## SIDE BY SIDE


The expansion interface can be placed on the edge of a 3U VMEbus card. By plugging in a 3U "side card," both boards can fit into a standard 6U chassis (*Fig. 2*). Current MXbus modules range from simple I/O ports to complex parallel-processor expansion modules.

Motorola's VME Subsystem Bus (VSB) is a secondary bus that offloads the VMEbus. The VSB lets a multiprocessor system functionally divide into local subsystems, with each processing one part of an application. By removing traffic from the VMEbus, overall system performance is improved. The Extensible VSB (EVSB) is a superset of VSB, with allowances for propagation delays. It allows a ribbon cable of up to one meter between the host, and as many as six EVSB modules. The downside to EVSB is that it takes up slots in the VME backplane or some other I/O area.

On the Industry Standard Architecture (ISA) bus, DT-Connect II from Data Translation, Marlboro, Mass., transfers data at speeds up to 100 Mbytes/s. The 32-bit interconnect scheme eliminates the host computer from the data-acquisition or image-processing loop (*Fig. 3*). This lets time-critical data bypass the bottleneck in the host bus (*ELECTRONIC DESIGN, Dec. 19, 1991, p. 24*). Data acquired from an I/O board can be transferred at a rate of 25 MHz to other boards for immediate processing and analysis through DT-Connect II. Up to five I/O, processor, or memory boards can be tied together. □
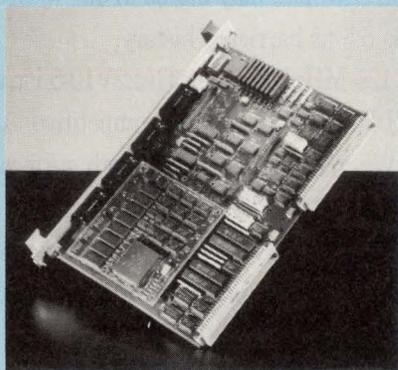
## CHOOSE AT&T OR TI PROCESSORS WITH DSP BOARD

**U**sers can elect to use either one or two of AT&T's DSP32C or Texas Instruments' TMS320C31 processors in Burr-Brown's ZPB3400 floating-point DSP board. The processors are mounted separately on plug-in daughterboards. With the attached daughtercard, the ZPB3400 can supply 25, 33, 50, or 66 MFLOPS of performance, in addition to handling real-time data-input sample rates up to 10 MHz. Each processor has its own serial bus to allow for parallel processing of multiple data channels or serial processing of one data channel. The board can hold either 1 or 4 Mbytes of triple-ported DRAM. Data to and from the processors can be sent through the VMEbus, the input FIFO




buffers, or the high-speed serial port. Prices start at \$4495.

**Burr-Brown Corp., P.O. Box 11400, Tucson, AZ 85734; (602) 746-1111. CIRCLE 578**  
**■ Booth 912**


HOW VALUABLE?	CIRCLE
HIGHLY	524
MODERATELY	525
SLIGHTLY	526

# Low-power DRAMs

## The Low-down on Memory Power

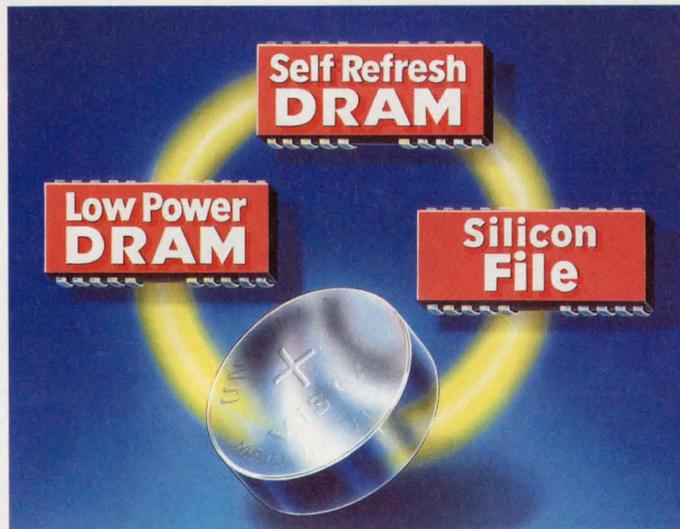

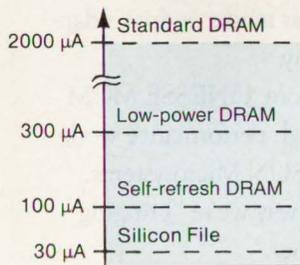Memory devices are as varied as the applications they are designed for, but in this age of miniaturization and mobility they have one thing in common: power consumption must be rockbottom. Capacity, speed, price or package choice may be your highest priority,



but you'll be glad to know that DRAM memories from NEC operate on an absolute minimum power supply. Based on a 0.7 µm, stacked capacitor process, NEC's 4 Megabit DRAMs offer high access speeds and convenient configurations for a wide range of desktop and portable applications. Competitively priced standard DRAMs have

the high capacity required by stationary systems, while

low-power DRAMs with a 300 µA data retention current are ideal for laptops and other equipment frequently on the move. NEC's Silicon File, only needs a 30 µA refresh current, and is designed to do duty as a solid-state disk in mainframes, workstations and PCs. Data retention by way of a 3 V battery gives this memory static RAM quality. Another device with extremely low power consumption is the self-refresh DRAM with a byte and word structure and optional parity. Intended for new low-power designs, such as notebook and palm PCs, it requires a mere 100 µA standby current. Compatible as to function, speed and pin assignment, all these DRAMs can also be configured as SIMM modules or memory cards.

For fast answers, call us at:

USA Tel: 1-800-632-3531. Fax: 1-800-729-9288. Germany Tel: 0211-650302. Fax: 0211-6503490.  
 The Netherlands Tel: 040-445-845. Fax: 040-444-580. Sweden Tel: 08-753-6020. Fax: 08-755-3506.  
 France Tel: 1-3067-5800. Fax: 1-3946-3663. Spain Tel: 1-504-2787. Fax: 1-504-2860. Italy Tel: 02-6709108.  
 Fax: 02-66981329. UK Tel: 0908-691133. Fax: 0908-670290. Ireland Tel: 01-6794200. Fax: 01-6794081.  
 Hong Kong Tel: 755-9008. Fax: 796-2404. Taiwan Tel: 02-719-2377. Fax: 02-719-5951. Korea Tel: 02-551-0450.  
 Fax: 02-551-0451. Singapore Tel: 253-8311. Fax: 250-3583. Australia Tel: 03-8878012. Fax: 03-8878014.  
 Japan Tel: 03-3454-1111. Fax: 03-3798-6059.


# NEC

Our new MCM designs have already taken off.



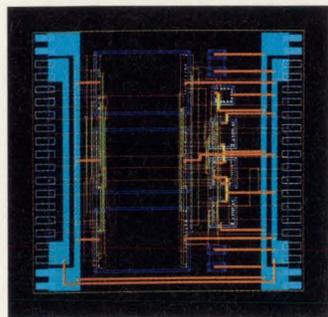**Now you can blaze new trails in multichip module design. Introducing new FINESSE™ MCM/CAD software.**

In initial applications, from aerospace to high-speed computing, FINESSE MCM's process-driven



An HDI process using FINESSE.

design features and powerful database delivered the proven accuracy and flexibility needed for evolving MCM design.

Here are just a few of the features that make FINESSE your best choice for MCM, thin-film, chip-on-board, HDI, and surface mount technology.

- **Extensive design rule files** let you design to your process parameters.
- **Powerful, 32-bit database** is scalable or variable, with sub-micron feature resolution.
- **Complex via structures** let you specify staircase, stacked or staggered via patterns.

• **CAM outputs** are specially designed to produce glass masks or drive adaptive lithography.

What's more, FINESSE MCM operates on high-performance workstations from SUN Microsystems. Just one more way we're "bringing the best together."

For complete information about new FINESSE MCM, write or call today: 1-800-4-HARRIS, Ext. 4470. In Canada, call 1-800-344-2444. And see how fast we can get your MCM design off the ground.



Finesse is a trademark of Harris Corporation. Sun is a trademark of Sun Microsystems, Inc.  
© 1991, Scientific Calculations, a division of Harris Corporation, 7796 Victor-Mendoza Road, P.O. Box H, Fishers, NY 14453.

**CIRCLE 180 FOR U.S. RESPONSE**  
**CIRCLE 181 FOR RESPONSE OUTSIDE THE U.S.**

MEMORY CONTROLLER TRIMS BUS-TRANSFER DELAYS AND BOOSTS CACHE EFFICIENCY BY MANIPULATING WIDE MEMORY WORDS.

# ACCELERATE DRAM ACCESSES WITH CONTROLLER MODULE


DAVE BURSKY

**A**s the latest high-performance 32- and 64-bit microprocessor systems boost their clock rates to 30 MHz and beyond, on-chip first-level caches become a necessity to ensure that the processor receives a constant flow of data and instructions. The cache also acts as a buffer between the slower second-level cache or slow DRAM main memory and the host processor. Although the cache solves bus bottlenecks to the host processor, it creates another bottleneck between the cache and the main memory.

One way to reduce that bottleneck is by using a second-level cache. But that just pushes the bottleneck out one level. Other alternatives include the widening of the memory bus that connects the DRAM to the processor's first-level cache, or employing faster main memory. Currently, most system manufacturers opt for the wider buses to move more data every cycle.

At the DRAM-to-cache-controller interface, the bus is typically 128-bits wide, while 64-bit-wide buses are used between the cache controller and the cache. At the same time, larger second-level caches are being designed in—128 kbytes to 1 Mbyte is not uncommon. However, to tie the cache into the wide buses, designers must typically develop custom cache and memory controllers.

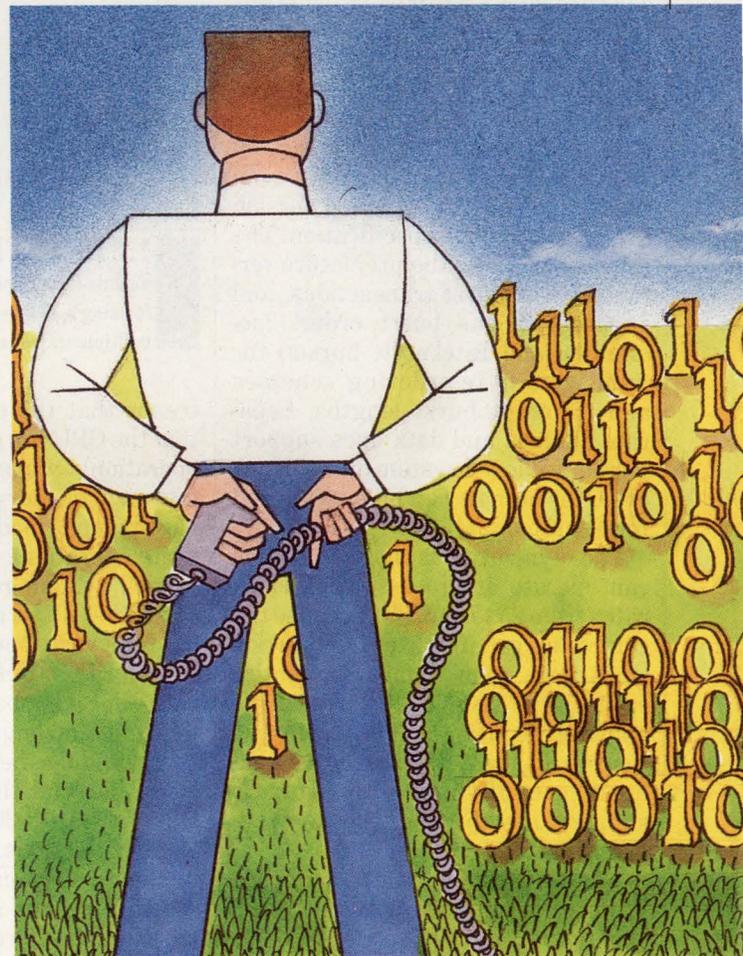Because time-to-market and cost for high-performance systems have become key considerations, engineers at Cypress Semiconductor predesigned the memory controller, which comes in a multipackage module that handles several functions. These include word slicing and reassembly, DRAM system refresh with scrubbing, error detection and



correction, and uniprocessor or multiprocessor system bus interfacing. There will be two versions of the 400-pin 7.8-in.<sup>2</sup> controller—one for 32- or 64-bit processor buses (the CYM7232) and one for 64-bit CPU buses (the CYM7264). The 7232 performs error detection and correction on 32-bit words; the 7264 does 64-bit error correction and detection.

By using the wide main-memory words, the controller can match the peak burst-transfer


# DRAM ACCELERATOR MODULE

rate of the data from the DRAM array to that of the second-level cache. That's because it will supply words to the CPU at the maximum rate the CPU's internal cache can absorb the data. Furthermore, it allows relatively inexpensive DRAMs to be used—memory subsystems with 80-ns access times can be employed rather than expensive 50-ns DRAMs. Module applications range from high-performance workstations and multiprocessor compute servers, to massively parallel computing and video-graphics accelerators.

On the host-processor side, the 7232 provides a 32- or 64-bit-wide bus (plus parity bits for each byte and four parity bits for the address). On the DRAM side, there are seven check bits per 32-bit word. For the 7264, there are eight check bits on the DRAM bus interface. Both modules implement an extended version of the Sparc Mbus specification. The extensions allow the premature termination of burst transactions, and support various burst orders (sequential and Intel-style bursts) for numerous byte-ordering schemes and different burst lengths. Separate address and data lines support non-multiplexed system buses. However, the signals can be multiplexed for Mbus compatibility.

The synchronous host interface can operate at processor-bus clock rates from 25 to 50 MHz. Because the controller can fetch a 128-bit-wide word from main memory, an entire cache line of four 64-bit words can be transferred in 240 ns (two wide-word reads from the DRAM array). An address space of 4 Mbytes to 1 Gbyte is supported by the module's 36-bit address bus.

First-in/first-out buffers on the host-processor side of the data-path chip are eight 32-bit words deep. For a 64-bit-wide CPU bus, the FIFO buffers would be configured as 16-levels-deep by 64-bits wide. The outputs from the FIFO buffers are then reassembled, when necessary, into the 128-bit-wide words that are actually written to the DRAMs. Each time the processor writes to the external memory array, the FIFO buffers capture the data and tell the pro-

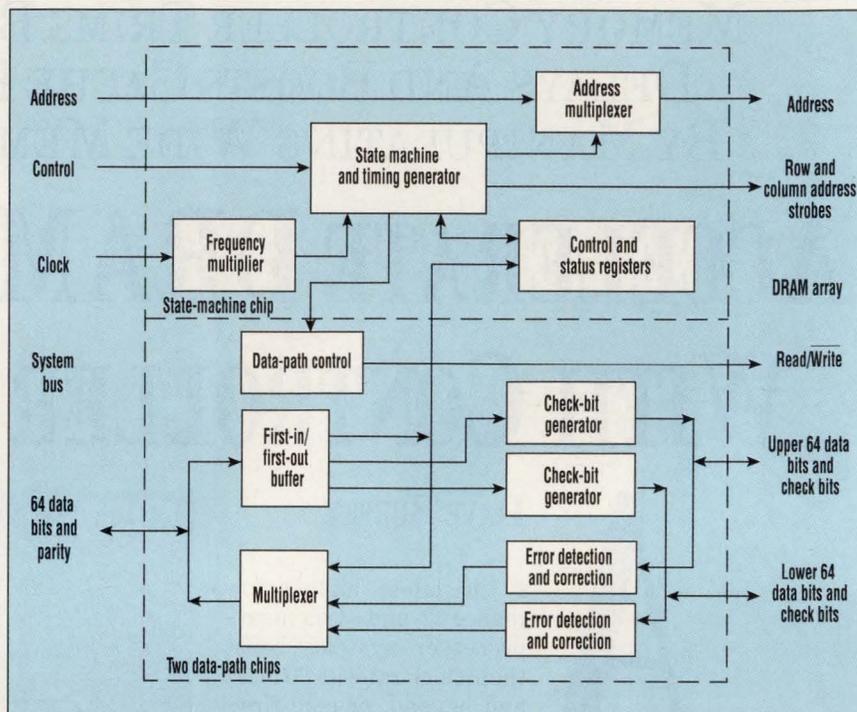

**1. THREE CHIPS** form the CYM7232 or 7264 DRAM accelerator and controller module from Cypress Semiconductor. Two of the three custom chips are identical, with each forming a 32-bit slice (7232 only; 64-bit paths in the 7264) of the data path. The third chip, a multiple-state-machine IC, controls the module's interfaces and word-transfer timing.

cessor that the data is written (so that the CPU can go off to do another operation), while the actual write into main memory is done in a sort of background mode (typical posted-write operation). That improves the overall system responsiveness, because the CPU is rarely left idle waiting for a write operation to finish.

The FIFO buffers also support cache-line copyback and fill operations, minimizing a system's bus activity because the data can be sent as a line burst at the maximum FIFO transfer rate—20 ns/word for the 50-MHz versions. Reads and writes to the memory can be inhibited for multiprocessor support. Furthermore, inhibited reads can be turned into reflective reads, and inhibited writes may be turned into reads-for-ownership—operations ideal for multiprocessor support.

Reflective reads begin when a secondary cache in a multiprocessor system goes to main memory for a line fill. If the valid data is in another secondary cache rather than in the DRAM (stale data is in DRAM), the

read from the DRAM must be inhibited by the secondary cache that owns the data. That secondary cache then supplies the data to the requesting secondary cache and writes the valid data into the DRAM.


Reads for ownership keep the system from stalling if requested data is not in a cache. The read-for-ownership operation does that by turning a write from a processor into a read by the cache to fill a cache line. When a CPU tries to write a byte into a line that turns out isn't in the cache (and doesn't know if the line is cacheable to start with), the cache must first read the line from DRAM and then write the data into the line.

Thus, the write operation for the byte is started, but at the same time the cache checks for the line. If the line isn't found, the byte-write operation is inhibited while the cache checks to see if the line is cacheable. If it is, the cache brings the line in and the byte is written into the line. If the line is not cacheable, the byte-write operation started at the beginning of the cycle continues and the

BUSCON  
'91 East  
Product of the Year.

Some people  
think we're power crazy,  
obsessed with quality  
and downright  
cheap.

And it's all true.

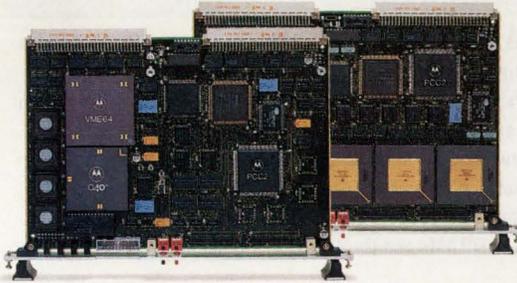

Okay, we admit it. We're hopeless perfectionists. Driven to produce the best boards at the best price.

Take our new MVME187 and MVME167 single board computers, for instance. Best in performance at 38 MIPS\* (RISC) and 26 MIPS\* (CISC), respectively. Best in value at \$105 (RISC) and \$154 (CISC) per MIPS.

Which comes out to just \$3,995 per board. And which compares rather nicely with the \$8,000 to \$12,000 you could pay for the competition's boards. Based on the 88100 and 68040, Motorola's highest performance

32-bit microprocessors, the MVME187 and MVME167 employ VME D64 architecture. Boosting the VMEbus bandwidth to a full 40MB/s. And both boards come with four 32-bit timers, as well as SCSI and Ethernet connections.

Naturally, since they're made by Motorola, you can expect the best in quality. The Malcolm Baldrige Award is a powerful testament to that fact.



So call 1-800-234-4VME for a free color brochure. And see why so many people are obsessed with Motorola products.



**MOTOROLA**  
Computer Group

For a free color brochure, call 1-800-234-4VME.

Motorola and the  are registered trademarks of Motorola, Inc. © 1992 Motorola, Inc. All rights reserved. \*MIPS rating based on Dhrystone 1.1 test results where 1757 Dhrystones/s is 1 MIPS (VAX™ 11/780). MIPS performance is based on the Diab 2.36E compiler.

CIRCLE 161 FOR U.S. RESPONSE

CIRCLE 162 FOR RESPONSE OUTSIDE THE U.S.

# DRAM ACCELERATOR MODULE

byte is written directly to the main memory as a write-through cycle.

Single-byte and partial-word transfers are also permitted with the read-modify-write (RMW) DRAM cycle. The old word is accessed and combined with the new data under control of the address and size inputs. A new set of error-detection and check bits is generated, and the modified word is written back into memory. In the 7232, a RMW cycle takes place for all writes less than 32 bits. In the forthcoming 7264, a RMW cycle occurs for all writes less than 64 bits.

The 7232 multichip module subsystems consist of three 184-lead CMOS chips (Fig. 1). Two of the chips are identical, and each forms a 32-bit-wide slice of the 64-bit host-processor data path. In the forthcoming 7264, there will also be two identical data-path chips that are interleaved to handle alternate words. These chips perform only 64-bit error detection and correction. Together, the two data-path chips form the 128-bit-to-64-bit, or 128-bit-to-32-bit (7232 only) data funnel for reads from the main DRAM to the system bus. In the other direction, the chips accept 32- or 64-bit words and concatenate them, check bus parity, and then feed a 128-bit-wide word to the DRAM array. A simple error-logging facility is available; errors will be logged by recording their syndrome values in a FIFO buffer and their burst address (or scrubbed address) location in a register. Interrupts will be generated to the CPU whenever an error occurs.

To perform those operations, the data-path chips include check-bit generators, error-detection-and-correction logic, the scrubbing data path for the DRAM background refresh, and a pipelined and buffered data multiplexer-demultiplexer (Fig. 1). The third chip in the trio contains multiple state machines that control all of the operations—including

DRAM refresh—and ensure a close coupling to the various microprocessor buses. Processor buses, such as the Sparc, the Motorola 88110 and 68040, the MIPS R4000, and the Intel i860 and i486, are all supported, along with their respective secondary cache memories.

To ensure proper system timing, the state machines on the control chip operate at high speed. Four of the state machines run at 100 MHz; eight others run at 50 MHz. Many programmable options exist on the controller chip to set up the DRAM refresh timing, the bus interface, the

simple case results in a range of bus utilization from about 45% with a 0.90 cache hit rate to about 8% if the cache hit rate goes to 0.98.

More efficient bus utilization (lower utilization percentages) improves the ability of the bus to handle more processors before saturating—such as is needed in compute servers and symmetrical multiprocessor systems. However, in multiprocessor systems, the memory bus tends to be the weakest link. By reducing bus utilization, additional CPUs can be added without negatively impacting the performance of CPUs already in the system.


As faster 50-ns DRAMs are employed, the bus utilization improves by decreasing to a range of 31% with a cache hit rate of 0.9 down to about 6%, if the hit rate goes up to 0.98. By adding the accelerator to the DRAM subsystem, 80-ns DRAMs plus the CYM7232 would yield the same results as a system based on very expensive 50-ns DRAMs. Still higher-performance systems can be implemented by adding the accelerator to DRAM arrays that employ the 50-ns chips. Such a combination starts with less than a 25% bus utilization that has only a 0.9 cache hit rate and only about a 5% bus-

usage level as the cache hit rate increases to 0.98. □
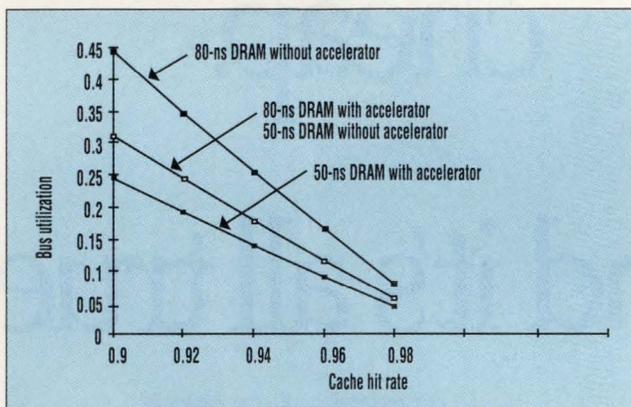
## PRICE AND AVAILABILITY

The CYM7232 and CYM7264 DRAM accelerator and control modules come as 400-lead pin-grid-array building blocks. They will be available in speed grades from 25 to 50 MHz. Prices peak at \$327 apiece in lots of 100 for the 50-MHz versions. Samples will be available in the early second quarter. The 7264 is expected by midyear.

Cypress Semiconductor Corp., 3901 N. First St., San Jose, CA 95134; John Murphy, (408) 432-7100. CIRCLE 511



**2. IN A TYPICAL**, simple RISC-based system that only uses an on-chip cache and external DRAM, bus utilization changes considerably as the cache hit rate increases. Four cases are shown in the graph: using 80- and 50-ns DRAMs with and without the accelerator module. Matching performance can be achieved using the accelerator with 80-ns DRAMs or 50-ns DRAMs without the accelerator. The smallest bus utilization percentage is achieved using 50-ns DRAMs and the accelerator module.

bus timing, and other aspects of the system. The clock's rising edge is used by the synchronous host side of the interface. Every system transaction is split into an address or control phase and one or more data phases.

When building high-performance systems, one goal is to minimize system bus utilization. That can be done by speeding up the transfer of data from the memory array to the processor or vice versa. Some system examples might better illustrate the performance impact of different-speed DRAMs and systems with and without the module. The simplest case could be a 50-MHz CPU with secondary cache and off-chip DRAM that accesses in 80 ns (Fig. 2). That

## HOW VALUABLE?

HIGHLY	527
MODERATELY	528
SLIGHTLY	529

## CIRCLE

# Our DSP development tool kit hammers the competition on performance.




## And at \$499, it nails them on price.

Granted, that's a pretty tough statement. But it wouldn't be made if it couldn't be backed up.

Our EZ-KIT is a complete package, with everything you need to define, code, debug, evaluate and demonstrate your DSP design, yet it costs about half of what the nearest competitor demands for equivalent tools.

To help get your design to market even faster, we've made the EZ-KIT the easiest kit to use. Its comprehensive Applications Textbook contains a full library of source code, while the algebraic assembly language lets you code your DSP algorithms just the way you would write them. Plus the kit includes a simulator for debugging, and an EZ-LAB™ Evaluation Board that lets you test your code in real time at 12.5 MIPS.

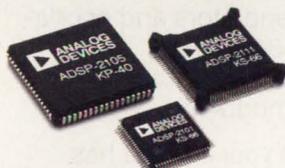

The code compatibility of the ADSP-2100 fixed-point DSP processors lets you easily migrate within the family, even as your designs get more complex.

Now, if all that's not enough to hammer the competition, we also hit them on compatibility. The ADSP-2100 family is a complete line of code-compatible fixed-point DSP processors, so programs you develop with the EZ-KIT can be easily ported and used on your next design.

The low cost and high performance of our EZ-KIT opens the possibility of using DSP to a whole new range of applications – even yours. For more information, or to charge a kit by phone, call us at (617) 461-3771.



The EZ-KIT includes our EZ-LAB™ Evaluation Board with preprogrammed demos, and microphone and speaker jacks; software which includes an assembler; a simulator for the ADSP-2101 and ADSP-2105; a comprehensive DSP Lab Book; an Applications handbook with sample source code; and a discount coupon for our 3-day System Programming and Development workshop.



Analog Devices, One Technology Way, P.O. Box 9106, Norwood, MA 02062-9106. Distribution, offices and applications support available worldwide.


Authorized North American Distributors: Alliance Electronics 505-292-3360 • Allied Electronics 817-595-3500 • Anthem Electronics 408-453-1200 • Bell Industries 213-826-8778 • Future Electronics 514-694-7710 • Hall-Mark Electronics 214-343-5000 • Newark Electronics 312-784-5100 • Pioneer Standard 216-587-3600 • Pioneer Technologies Group 1-800-227-1693

CIRCLE 84 FOR U.S. RESPONSE

CIRCLE 85 FOR RESPONSE OUTSIDE THE U.S.

# SIEMENS

## Accurate timing at all frequencies

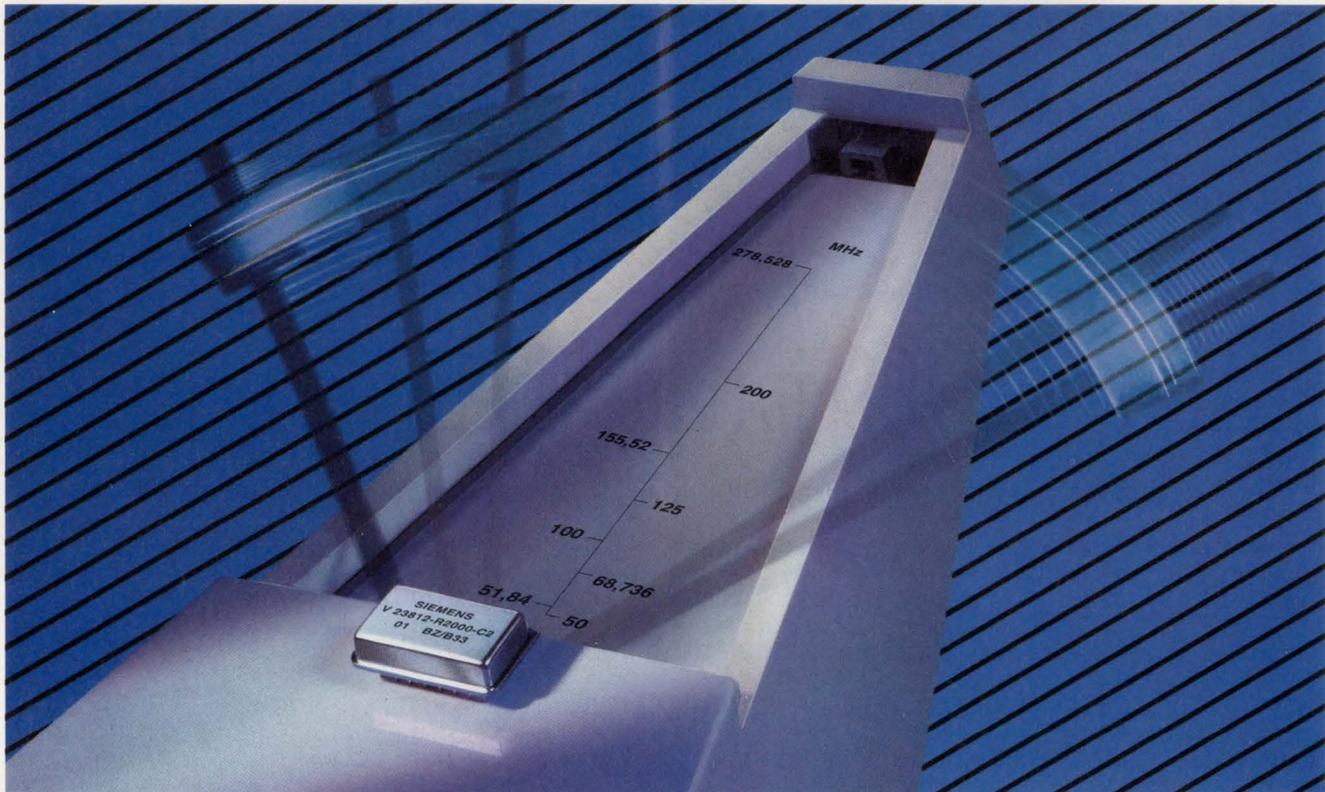

A23001-G40-Z012-X-7600

The clock regenerators from Siemens are the ideal components for the development of innovative network solutions on an optical basis.

They feature high quality, reliability and exceptional performance, they cover all standard frequencies, and are suitable for all optical data and communications networks currently being introduced worldwide, such as FDDI, SONET and VBN.

Individual technical highlights:

- Smallest dimensions worldwide
- Very low power consumption
- Very high integration density
- Very low jitter

- 1 LSI semi-custom IC and a surface-wave filter for all timing recovery functions
- High frequency stability

The Siemens clock regenerators are particularly versatile in the implementation of new, customer-specific requirements. Individual solutions between 50 and 300 MHz can be achieved rapidly and flexibly.

Siemens offers a complete range of fiber optic components:

- FDDI transceiver, 125 Mbaud
- Transmitters and receivers up to 280 Mbaud
- Video modules for 850 nm and 1300 nm


- Clock regenerators and oscillators up to 300 MHz
- Optical relays
- Interface modules.

Write to us if your interest has been awakened, we will be pleased to provide detailed information:

Siemens AG  
Infoservice EC/Z552  
Postfach 23 48, W-8510 Fürth 2



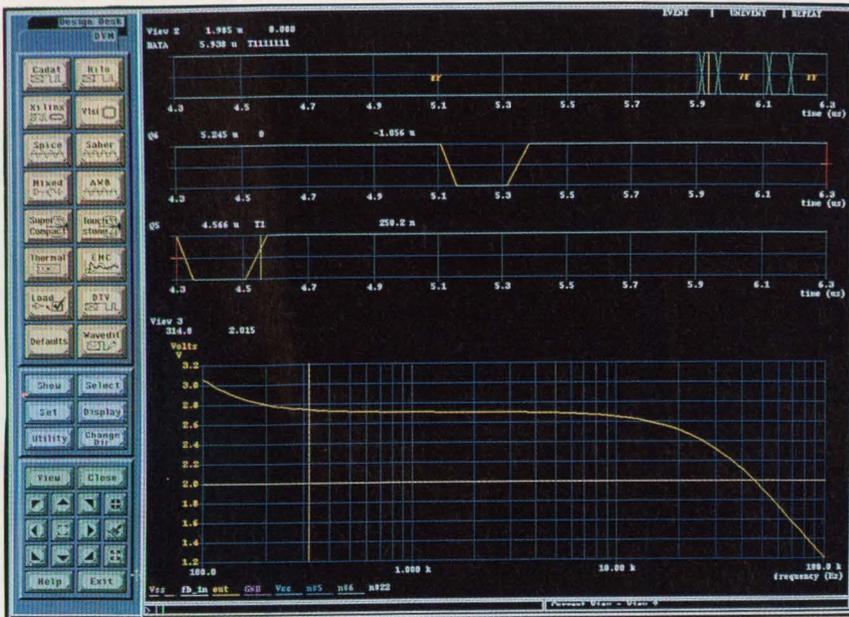Fiber optic  
components  
from Siemens.  
Quality for sure.



Courtesy of Computervision

LISA MALINIAK

**MOST DESIGNERS PROFIT FROM SOME ELEMENT OF SYSTEM SIMULATION, BUT FEW PRACTICE IT IN PURE FORM.**

# SYSTEM SIMULATION STILL HOLDS PROMISE

**I**t's the dream of both EDA vendors and users to one day eliminate prototypes and completely automate system design. As the EDA industry slowly inches toward that goal, system-level simulation is increasingly thrust into the spotlight. System-level simulation can range from modeling an entire multiboard system at the behavioral level to simulating every element in that system before any prototype is ever built. And though many design teams are practicing some degree of system simulation within that range, no design teams are creating products without building prototypes.

System-level simulation—simulating an entire system at a high lev-

el to verify that the architecture is correct—is typically done when a brand new system is being designed and lots of thought must be given to architectural issues. Very high-level simulation is possible with products like SES/workbench from Scientific and Engineering Software Inc., Austin, Texas. With SES/workbench, engineers can model hardware- and software-based systems at a high level, and simulate the complete system including the application software. Users can address design trade-off issues early on, before any architectural commitments are made. "The cost of making a bad decision is very steep," comments Doug Neuse, vice president of simulation software products for the company. "Our product helps answer strategic questions about what a product is going to be, not just its implementation."

The practice of simulating a system at the low level to ensure it meets the specifications is driven by ASIC design and the need to get the ASICs working on a board. Most designs tend to be incremental, explains Steve Caplow, director of market development for Cadence Design Systems Inc., Lowell, Mass., so large amounts of simulation aren't usually necessary.

Although most of today's engineers would like to simulate anything and everything in a system,

## SYSTEM-LEVEL SIMULATION

most simulate only where they think a problem will occur (Fig. 1). Systems consist of hardware, software, and firmware that may contain analog and digital components, ASICs, standard devices, programmable devices, memory devices, and peripherals. In addition, systems may have high-speed backplanes and complicated interfaces to the outside world that could in themselves be other systems. Engineers also need to simulate components like transducers, actuators, and sensors with their circuits, all in one environment (see "Expanding simulation to meet total system needs," p. 56).

In many situations, a thorough system simulation entails modeling non-electrical effects. For instance, a communications engineer may want to model his entire system, including such mechanical components as antennas and fiber-optic cables. One useful simulator in that type of application is the Saber simulator from Analogy Inc., Beaverton, Ore. The Saber simulator can model components in many different disciplines, not just electrical, and have them simulated in one environment.


The benefits of system simulation are numerous. For instance, by using simulation, managers can compare the performance and functionality of systems designed by different design teams and vendors. Simulation also reveals chip behavior that surfaces only when the chip is installed in its working environment. In addition, simulation can attempt to model the behavior of a stand-alone chip by itself and on a board, the behavior of that board in a backplane, and that backplane's behavior in a system of boards and backplanes. One of the biggest benefits, says David Smith, vice president of engineering at Analogy, is that simulation not only helps engineers build a more correct design, but also helps them to better understand the design's boundaries and limits. In other words, simulation will indicate both when a product will and will not work.

With today's complex designs, verifying a design with simulation before costly prototyping is nearly

essential. Generally speaking, a 25k- to 30k-gate array can cost between \$25,000 and \$30,000, depending on the geometry and technology. A circuit board that contains several of these custom chips can become pricey. At that point, it's critical that the chips be verified within the target system before the designer commits to any silicon.

Also, most system designs are partitioned into several blocks and assigned to different design teams. Continually checking the interfaces between and within these blocks is critical. Very often, design teams create blocks that function perfectly as standalones, but malfunction when plugged together.

A different way to assess what simulation can do for engineers, points out Kuhoo Goyal, digital marketing manager for Dazix, Sunnyvale, Calif., is to look at what prototyping won't let engineers do today. For instance, there's no room for any form of "what-if" analysis with a prototype. Consequently, manufacturing variations can't be accounted for. Critical margins, such as voltage, power, timing, and thermal tolerances, can't be varied with prototypes. Although it's a good practice to get a prototype working in the lab, the engineers verifying a design with that prototype can't determine how close it came to failing. Nuances like that can't be uncovered with prototyping because the engineer is analyzing an already

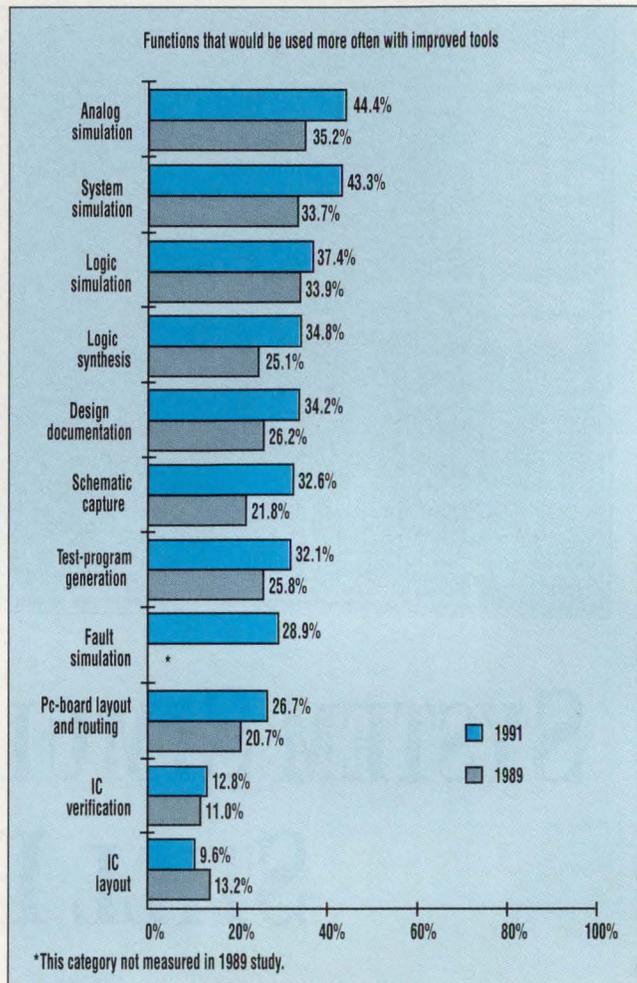

**1. RESULTS FROM** a 1991 design-automation survey commissioned by *Electronic Design* show that users continually want to simulate more, but feel that they need better tools to do it. Almost half of those questioned wanted to perform system-level simulation, up from 33.7% in 1989.

"manufactured" device or devices. In other words, there's no way to cover any type of manufacturing variation unless it's related to the particular device that's being used for the prototype.

David Hardman, product planning manager for Logic Automation Inc., Beaverton, Ore., also feels that prototypes fail in many areas where simulation succeeds. For example, engineers can't get to the internal workings of buried chips with prototypes. There's less observability, which means it's difficult to perform different types of analysis.

Although the benefits of simulation can be immeasurable, problems

ANALOG

Digital

ANALOG

Digital

Analogy

DIGITAL

Analogy

digital

ANALOG

.digital.

ANALOG

DIGITAL

# DON'T BUY IT.



There is a far side to the world of oscilloscopes, a place filled with all sorts of bizarre characters. Like those who swear you need digital, for the sole reason that digital is all they wish to sell. Then there's the gang

that wants to push nothing but analog. Luckily, there's also a place called Tektronix. Where they manufacture a complete line of analog and digital scopes. Making them uniquely qualified to provide you with a more honest assessment of your needs. With anyone else, you could be hearing only half the story. For complete information



on the full line of Tektronix analog and digital oscilloscopes, get in touch with a Tek representative today. **TALK TO TEK/1-800-426-2200**

**Tektronix**

Test and Measurement

03W-188147 Copyright © 1991, Tektronix, Inc.

CIRCLE 136 FOR U.S. RESPONSE

CIRCLE 137 FOR RESPONSE OUTSIDE THE U.S.

## SYSTEM-LEVEL SIMULATION

can abound for engineers trying to implement system-level simulation (see "Simulation solves only part of the design-verification problem," p. 58). The electronics industry faces a very big hurdle to full system simulation—the lack of simulation models for every device in the system. Ping Chao, co-founder of PiE Design Systems Inc., Sunnyvale, Calif., explains that there's a spectrum of options open to engineers, each with a different level of speed and flexibility. Such options include hardware modelers like those from Logic Modeling Systems Inc., Milpitas, Calif., and software models from third-party sources like Logic Automation Inc. The company carries over 13,000 software models, including their new Simubus model that simulates a VME bus, enabling engineers to verify if a board or boards meet VME specification.

Even though EDA vendors have provided users with many options, often they fall short. Kevin O'Leary, electronic CAE product manager for

Computervision, Bedford, Mass., contends that the customers he has talked to can't get more than 75% of all the models they need. He adds that many times they can do other things to get around that, such as in-house modeling service.

However, engineers end up paying for these model options in terms of money, accuracy, and time. For instance, Kuhoo Goyal of Dazix points out that although hardware modelers have come a long way in performance, they're usually still the slowest segment of a system-level simulation. Also, because third-party modeling services provide behavioral models, fault simulations are limited to the I/O ports of devices, leaving the internal states unknown. According to Goyal, the model solution boils down to engineers "making up in time what they lose in accuracy."

For true system-level simulation to become a common-practice reality, silicon vendors must shoulder more responsibility in supplying models of their standard parts. Ter-

ry Strickland, test and simulation product marketing manager for Compass Design Automation, San Jose, Calif., explains that there are varying levels of model support among silicon vendors at the moment. ASIC vendors, he goes on to say, must begin offering hardware-description-language (HDL) models because that's the direction in which most engineers are headed.

Logic Automation's David Hardman points out that getting the models is only the beginning. Timing problems can arise when mixing models from different sources, creating yet another kink for engineers to iron out. And as systems run at higher clock rates and timing margins narrow, this kink grows more ominous. Open Verilog International chairman Bruce Bourbon adds that because more of the simulation is being done at higher levels of abstraction, the interoperability of models described in different HDLs is also important.

With simulators like AdvanSIM

## EXPANDING SIMULATION TO MEET TOTAL SYSTEM NEEDS

**W**hen electronic engineers conceive of system-level simulation, they most likely think of chips and pc boards. The fact is, however, that other portions of a system, like mechanical parts, can affect the way the electronics function. That's why Computervision, Bedford, Mass., is leveraging their strength in mechanical design tools to help electronic engineers address non-electronic problems.

The company's definition of system simulation extends well beyond the board level. It includes the backplane, enclosure, cabling, and so on. Kevin O'Leary, electrical CAE and framework product manager for the company, explains that Computervision is looking to standards and third parties to help with the lower-end ASIC simulation while they focus on the higher-end system problems. In addition, the company has a framework they believe can

tie everything together in one user-friendly environment. Frameworks are useful because they make data accessible to all of the tools and they supervise design flow.

Computervision is helping engineers tackle such problems as the dynamics of the heat generated from multiple boards in a box. Their tools look at the problem mechanically, finding electronic problems that ignite from the physical side. For example, in the automotive industry, there's often interaction between the engine electronics. Components like spark plugs, however, aren't conducive to having pc boards anywhere nearby because of several factors, including noise and stress. Therefore, the Computervision system defines restrictions (where the board can and can't go) from the mechanical end.

Engineers must start looking toward larger-scale system simulation because even if their boards

work when tested, they may not work when they're installed in, for example, an automobile. A sophisticated car or truck may have up to 25 pc boards in it, all wired together with lots of interaction going on through the wires. The system engineer must verify that the wires are connected correctly, or none of the boards may function properly.

Computervision approaches this problem with a combination of its own wire-harness tool, the Analogy Saber simulator for analog portions and Racal-Redac's Cadat simulator for the digital portions, all tied together under a framework. The wire harness is the collection of wires that connects all of the boards and switches to the control system. Because an automobile prototype may take several months to build, and even then a wiring problem is hard to locate, this type of system-level simulation is critical for time-to-market success.


## SYSTEM-LEVEL SIMULATION

from Dazix, users can write their own simulation models in languages like C and VHDL, providing yet another angle for the user in terms of model resources. A key question is one of accommodation: Does the simulator to be used for system simulation accommodate any type of model, defined at any level of abstraction, without performance or accuracy degradation?

Whether an engineer writes his or her own models or buys them, explains Analog's David Smith, the models need to be "appropriate to the questions that need to be answered." For example, a behavioral model won't help the engineer who's looking to verify detailed timing. To be useful, models must use the right level of abstraction. Engineers who write their own models can guarantee that the models are appropriate. If an engineer needs a microprocessor model, for example, he or she can build that model to suit his or her particular application and cut out unnecessary features. If the processor has four operating modes and only one is used in the application, there's no need to model all four. This type of tailored model saves the engineer much time.

Simulation performance can also become a big headache for engineers doing system simulation (Fig. 2) Performance is affected by both a host computer's processing speed and the available memory. Another factor, according to Jim Kenney, simulation product marketing manager for Mentor Graphics Corp., Wilsonville, Ore., is the amount of time a simulator takes to load in a design. This is especially true when an engineer is saving design changes often and must reload the data each time.

Actually, the simulator's speed in relation to the time spent by the engineer can be a relatively small portion of the overall simulation-verification cycle. For example, time spent on creating good test vectors that exercise the circuit require lots of time from the user. Also, the iterative cycle of changing, recompiling, and resimulating the circuit makes up a major component of the simulation cycle.

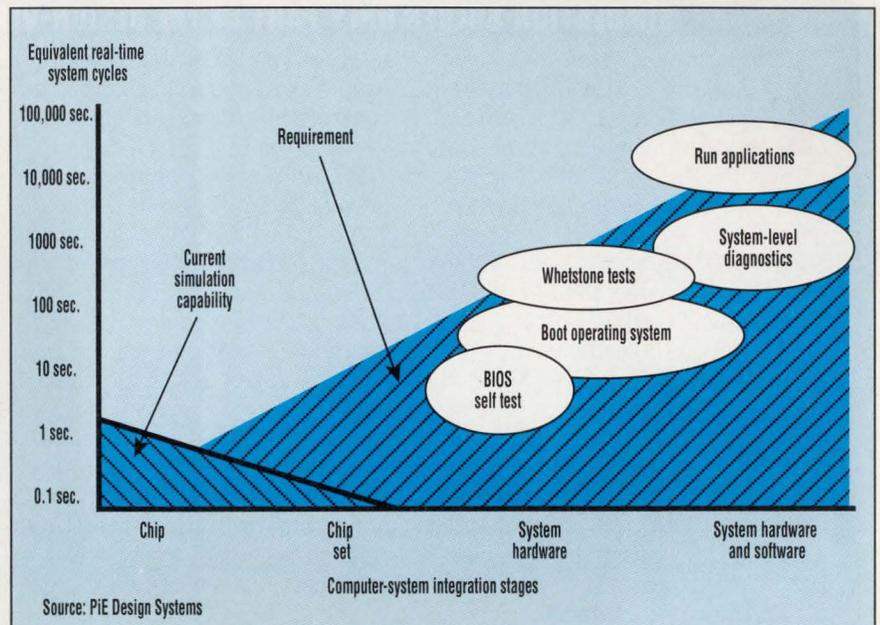

**2. THIS GRAPH ILLUSTRATES** why today's software-simulation approaches fall short when trying to verify a computer system. The simulator must perform almost 100 seconds of equivalent real-time system cycles just to boot the operating system.

Eliminating the system-simulation speed problem calls for software that allows for quick-turnaround "what-if" analysis. Basically, this implies the need for simulators that provide incremental compilation, and are tightly integrated with the design-entry and analysis environment so that quick viewing, analysis, and tweaking of circuit and signal values are possible. Another way engineers can keep down long simulation times is to model everything at a high level except for the areas they're most worried about. Those problem areas should be modeled in detail. In addition, compiled-logic technology like that used in Mentor Graphics' QuickParts product can help create models that use less memory and execute faster. Efficient use of simulation cycles that run only the most important cycles can also save time. And finally, the proven method of hardware acceleration is becoming a more frequently used simulation option despite its high price tag.

System simulation is often carried out at multiple levels. The level at which an engineer chooses to simulate basically depends on what he or she is looking for in the design. To-

day's engineer can perform either some or all of the system simulation at a high level of abstraction using a language like VHDL.

Historically, engineers have needed to perform "proof of concept" before they've actually been able to do it, notes Kuhoo Goyal of Dazix. Proving a concept involves levels of abstraction that go beyond the behavioral levels. Therefore, the engineer can verify a concept before any kind of system definition is even accomplished. Dazix, for instance, is one company that offers tools in this architectural realm. ForeSight, a rapid prototyping tool, verifies the system specification before any steps are taken to implement the specifications. Engineers can perform design exploration and design alternatives. And, traversing down the design hierarchy is automated with ForeSight by converting the design specifications into VHDL source code.

The behavioral level is often used to validate system specifications in the form of system blocks. Then, as these blocks are implemented, the engineer can verify a gate-level block's interaction with the other behavioral blocks. Actually, the implementation that the engineer decides

## SYSTEM-LEVEL SIMULATION

## SIMULATION SOLVES ONLY PART OF THE DESIGN-VERIFICATION PROBLEM

Engineers often lose sight of the real requirements for solving a problem when the problem becomes known by its solution. One example of this is using software simulation to solve system design-verification problems. When simulation reaches the limits of its capabilities, there's still a great deal of system-verification work to be done before delivering final products to customers. Therefore, system designers must not depend solely on the capabilities of system simulation to verify designs. If that's the case, they'll pay a stiff penalty in time-to-market, which translates to lost profits and lower customer satisfaction.

Design verification begins during design creation, and continues until the final product is shipped to customers. In the late stages of the development cycle, design verification becomes the primary objective and the primary obstacle to time-to-market goals. Although simulation is a valuable tool during design creation, it has serious limitations when used for verification. It doesn't have enough speed and capacity to handle applications that have software-intensive hardware or need long periods of real-time operation during verification.


The system verification problem can be characterized by a 3D model (see the figure). The speed-and-completeness axis represents the speed of operation and the portion of the system that can be modeled by the verification solution. Speed and completeness are key factors in determining how much real-time operation can be simulated in a reasonable period of time. The form-factor axis represents how well the solution fits the form of the final product's size, cost, power, and so on. The

interactivity axis illustrates how easy it is to observe, change, and control the model during design verification.

All simulation is mapped to the lower-left-front corner of the design, and will slowly climb up the y axis toward higher speed and more system representation. Also, little movement will occur along the x axis toward the final product form. It's important to note that the y-axis scale isn't linear. If it were linear, the simulation solution would be just a specification on the model. Today's popular simulation tools can achieve speeds of a few cycles/s, yet most electronic systems oper-

right-front corner. There, designers would have the speed, completeness, and form factor of the final product. They would also have the interactivity they need for an effective design-verification environment.

ASIC emulation can move the engineer closer to this nirvana by providing a solution that's further up the y axis than simulation. The spectrum of possibilities opened up by this technology can be referred to as computer-aided prototyping. Computer-aided prototyping combines design translation and optimization software with reprogrammable hardware to create hardware prototypes of ASIC designs. Engineers still have some level of interactivity, but speed of operation is within one or two orders-of-magnitude of real time. Entire systems can be modeled by emulating the ASICs and implementing the rest of the system with off-the-shelf components. In addition, computer-aided prototyping enables early system integration where

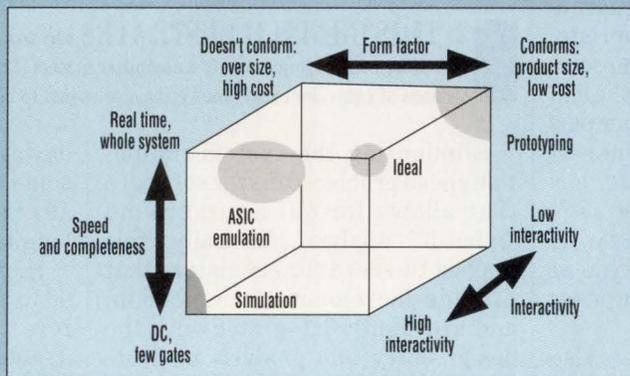

ate in the MHz range. This represents a spread of more than six orders-of-magnitude.

Prototyping with ASIC prototype chips occupies the top-right-rear corner where maximum conformity, speed, and completeness are achieved, but where interactivity is at its most restrictive level. Debugging in silicon isn't tenable because engineers can't observe internal operations or make design changes. In spite of this, most design teams don't debug today's systems until well after the first prototype is built and the complete system is integrated with all of its hardware and software. A possible drawback, though, is extended product-delivery schedules.

The nirvana of design-verification solutions occupies the top-

the boards of the final product may be used as a test bed, and diagnostics, operating system, and applications can be fully verified on the system hardware before ASICs are fabricated in silicon.

System simulation combined with computer-aided prototyping gives designers a good way to verify their products before any silicon is created. Simulation is good for the early stages of design creation when changes are major and frequent. Later on in the design cycle, however, computer-aided prototyping can help integrate the system in hardware while still maintaining interactivity.

*Contributed by Stephen Walters, director of marketing for Quickturn Systems Inc., Mountain View, Calif.*

## SYSTEM-LEVEL SIMULATION

on can depend greatly on the behavior of the high-level description. In the final stage of verification, all of the blocks can be simulated together at the lowest level that time permits. David Smith of Analogy points out that "a lot of design is done at the high level, but design verification must be done at the low level."

Designing and simulating at higher levels is becoming more common as standards like VHDL are adopted and as synthesis tools gain the trust of engineers. Even without synthesis, system-level behavioral modeling and simulation are useful for numerous reasons. For example, if done properly, the test vectors verifying the device's behavior at the high level can and should be used in the gate-level verification as stimulus and as expected outputs.

Behavioral simulation, however, shields timing details from the engineer. Although behavioral simulation can have a concept of time, in theory it's mainly used to verify a system's behavior. For instance, behavioral simulation may answer the question of whether the bits toggle

to the right values, instead of whether the bits toggle to the right values at the right time.

Compass Design's Terry Strickland agrees with that, adding that "the behavioral level will never eliminate the need for gate-level simulation." That's because the detailed timing information contained in lower-level ASIC models is critical for the standard timing analysis, which is key to system-level success. The required level of detail can come from a model of an ASIC that's had floor planning or has been placed and routed. Accurate timing analysis is needed because today's boards work at such high clock speeds.

Logic simulation can pass over problems just like behavioral simulations. Because logic simulation doesn't delve down into the transistor level, engineers can't see problems in the design caused by, say, ringing and noise.

Timing simulation, in terms of worst-case timing or static timing, is typically used when some implementation detail is defined. It's basically a post-synthesis process, used once

the technologies and geometries of the parts are defined. However, timing simulation can also be performed at the data-path levels, prior to synthesis, when timing is implied along with the design's behavior. Timing simulation is always warranted for those engineers designing at the structural level. Manufacturing variations, including timing, power, and voltages, can be thoroughly explored by engineers with in-depth timing simulations.

The number of system-simulation passes that must be done throughout the design cycle depends on both the design and the designer. Factors that influence the amount of simulation passes include: what the engineer is trying to validate; the amount of attention being paid to manufacturing variations as they pertain to timing, temperatures, voltages, and so on; how much trust the engineer has in the results of a simulation run; and the amount of fault coverage that's satisfactory. The decision is really a trade-off, because engineers want to get the product to market quickly. But they also know that the

## PROGRAMMABLE INTERCONNECT ADVANCES SYSTEM VERIFICATION

**V**erifying today's complex systems can be a significant limitation in engineering productivity and time-to-market. Current techniques, such as simulation, have varying degrees of functionality, form factor, and flexibility in interaction. The challenge for the 1990s is to develop new verification approaches that maximize all of these attributes.

Software simulation—the use of software models and test vectors to verify design behavior under conditions specified by the engineer—is undeniably the most flexible electronic-design-automation tool available to system designers for validating concepts. Despite this flexibility, though, simulation doesn't meet all the needs of today's engineers because it's far removed from the physical design.

A good step toward the ulti-

mate solution is a flexible, hardware-based tool. The tool should have unlimited observability and changeability during the development phase of a project, and is a form, fit, and function physical duplicate of the final product. This latter requirement enables the tool to perform at, or near, actual performance; to be shipped to customers for evaluation; and even to be used as a final product in low-volume applications.

Aptix Corp., San Jose, Calif., is following that path with a new programmable-hardware technology. The company recently announced details of its proprietary interconnect architecture and field-programmable interconnect components (FPICs). The Aptix programmable-interconnect technology enables user-configurable component-to-component interconnection. It can interconnect several thousand universal con-

nections per system.

Two field-programmable interconnect components initially use programming elements based on SRAMs and nonvolatile, one-time-programmable memory technologies. Both programming elements are packaged in a proprietary 1024-pin land-grid-array multilayer ceramic package.

The reprogrammable SRAM-based FPIC is aimed at systems requiring dynamic in-system programming. It has over one million transistors, and is processed in 0.8- $\mu$ m CMOS technology. Programming is done using conventional memory-addressing techniques. The low-impedance, one-time-programmable interconnect version is optimized for higher speed as well as low cost. Programming and configuration software from the company universally interconnects any combination of pins.

## SYSTEM-LEVEL SIMULATION

more simulation iterations completed indicates the more fault-free the design will probably be.

Deciding on the correct number of system simulation passes actually ends up being a schedule-driven process, meaning that most engineers simulate as much as their development schedules will allow. A good rule of thumb is to perform some sort of simulation at every level of abstraction. After that, engineers should go through as many iterations as possible. In other words, every time a richer implementation detail is reached, the engineer should verify that the functionality matches the previous level of abstraction.

Verifying a diverse system usually involves various simulators, which poses a problem to both engineers and EDA vendors. EDA vendors have a tough job in hand: Making disparate simulators perform a perfect "handshake" isn't a simple task. For example, simulators have different logic-value systems. A simulator manager must map, on the fly, logic values from one simulator to another. There's also the question of how an analog simulator will represent a digital don't-care state. Moreover, each simulator that's used may have a different time wheel, and these must be synchronized.

Other issues that cause problems are how the user partitions a system over several simulators, how activities get scheduled between these simulators, and how the user debugs in a multi-simulation environment. "The compile environment is where the real problems are," notes Bill Fazakerly, chief technical officer of Ikos Systems Inc., Sunnyvale, Calif., "because simulator databases are not compatible." Vendors are trying to ease the problem with simulation backplanes, like those from Tera-dyne Inc., Santa Clara, Calif., and Mentor Graphics. The general industry consensus, though, is that much work still must be done in this field.

Some engineers who employ more than one simulator for a system actually use the simulators separately on different parts of the design. Then they try to get interaction between the simulators with the stimulus and

results, instead of having them interact during the actual simulation run. Simulator interaction is definitely a problem. It's the opinion of David Hardman of Logic Automation that as system simulation becomes more of a common practice, engineers will migrate to simulators that handle a wider range of models, reducing the need for simulators to interact.

In fact, one key to success is to have very few simulators fully performing the system-level simulations. Digital simulators should be multilevel simulators that can simulate anything from the switch level to high behavioral levels. Analog

## A GOOD RULE OF THUMB IS TO PERFORM SOME SORT OF SIMULATION AT EVERY LEVEL OF ABSTRACTION.

simulators should be able to handle anything from the transistor levels to analog behavioral languages. Some simulators can take both analog and digital inputs. For example, Dazix has a single-engine, mixed-mode simulator that works with analog components and digital behavioral models.

The Contec Microelectronics simulator can handle both analog and digital portions of a design by modeling both portions with analog behavioral models. The analog behavioral representations of the digital components give more detailed time-domain waveforms than does logic simulation. In addition, the models are more than an order-of-magnitude faster than circuit simulation with comparable accuracy.

System-level simulation can have a significant effect on the final


stages of a traditional design cycle (the prototype-debug stages) because it moves some of the knowledge usually learned at the breadboarding stage up into the design stage (see "Programmable interconnect advances system verification," p. 59). This results in a better prototype than if it had been built without any simulation. And, employing design-for-test (DFT) methodologies, fault simulations, and automatic-test-pattern-generation (ATPG) tools can help ensure smoother production runs. Another benefit is that simulation supplies engineers with test vectors for prototype stimulus, which eliminates a lengthy process in that verification stage. Without the simulation vectors, engineers are often stymied as to how to stimulate their prototype boards.

Despite the benefits, true system-level simulation is rarely performed today. System design in the computer and telecommunications industry rely heavily on simulation because time-to-market is such a critical factor for their success. Other industries, however, require much less simulation to be competitive.

Although the system-simulation process is riddled with problems, Terry Strickland of Compass Design Automation notes that "the people who need to do it have built their own systems with much pain and suffering." There's lots of work involved with integrating software tools. Strickland explains that Compass Design's ASIC Navigator product simplifies this task somewhat by automatically generating the ASIC information needed by a system-level tool. In general, however, there's simply no elegant way of tying everything together.

Old practices of trusting a prototype in a lab versus trusting an automation tool still prevail. There's also a lack of in-depth expertise in using existing automation tools for tasks as big as system-level simulation. Norm Kelly, vice president of engineering for Logic Modeling Systems Inc., Milpitas, Calif., does indeed feel that culture and knowledge are two barriers blocking the road to system-

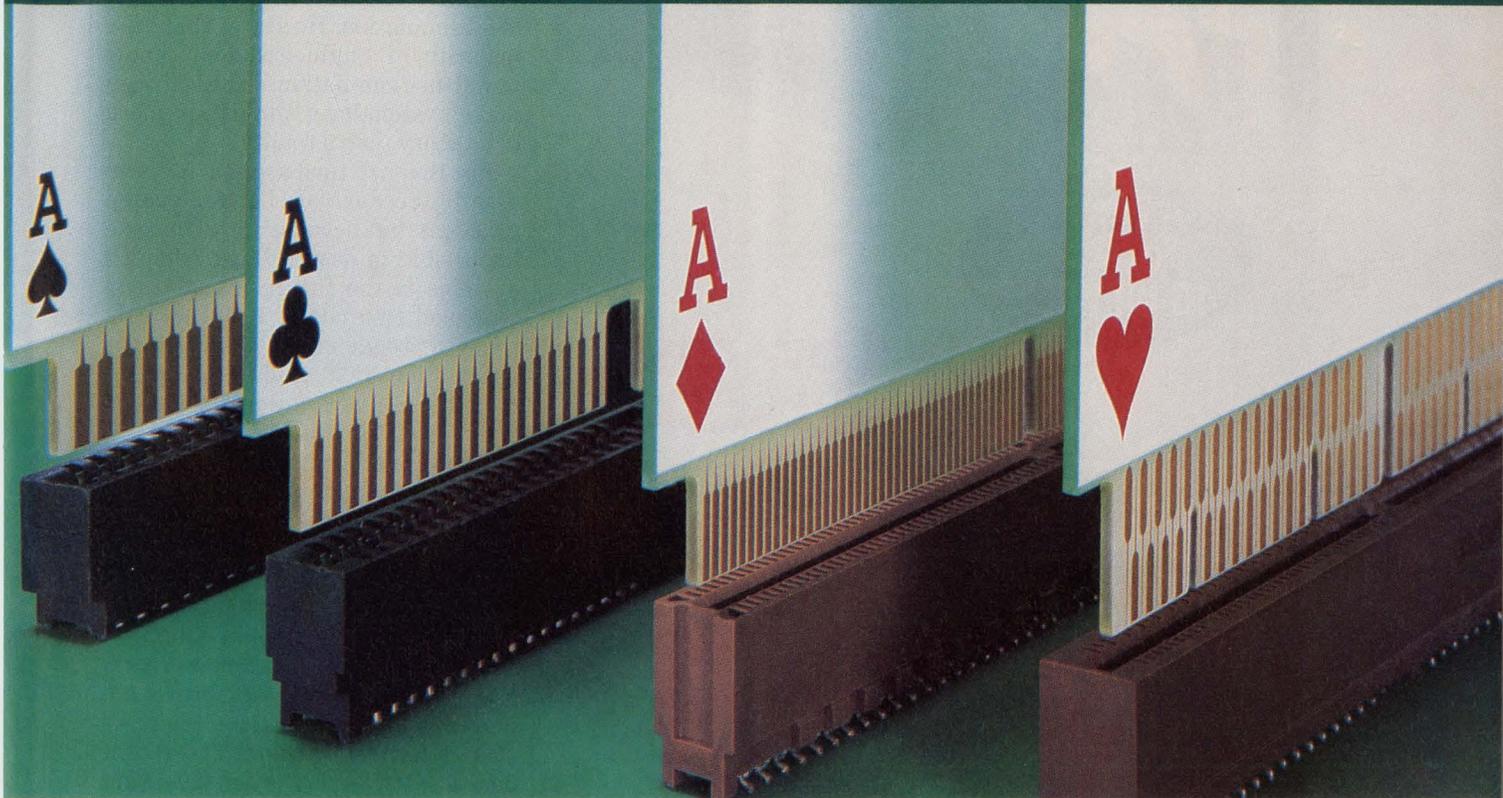*The winning edge for any  
game in town.*



## ***THIS IS AMP TODAY.***

Whether you're looking for .050" center MCA styles, dual-function ISA/EISA types, or .100" or .125" center versions, you can be sure you get the edge connector you need, when you need it.

AMP Standard Edge Connectors come in all the right styles and sizes, with all the engineering advantages you'd expect from the people who established edge connectors as an industry standard. And the immediate availability and in-depth application support you need, from the largest supplier in the world.

Whatever you're looking for in edge connectors, compare selection, value, and delivery with the industry standard—the AMP Standard Edge lines—and come up a winner. For information on AMP Standard Edge II (.100" and .125"), Standard Edge .050, or Standard Edge EISA connectors, call our Product Information Center at 1-800-522-6752 (fax 717-986-7575). In Canada call 416-475-6222. AMP Incorporated, Harrisburg, PA 17105-3608.

AMP is a trademark of AMP Incorporated

# **AMP**


CIRCLE 144 FOR U.S. RESPONSE

CIRCLE 145 FOR RESPONSE OUTSIDE THE U.S.

# FAST TEST

New  
For 1992  
16-bit WIDE

## Low-cost, PC-Based SCSI-2 Testers

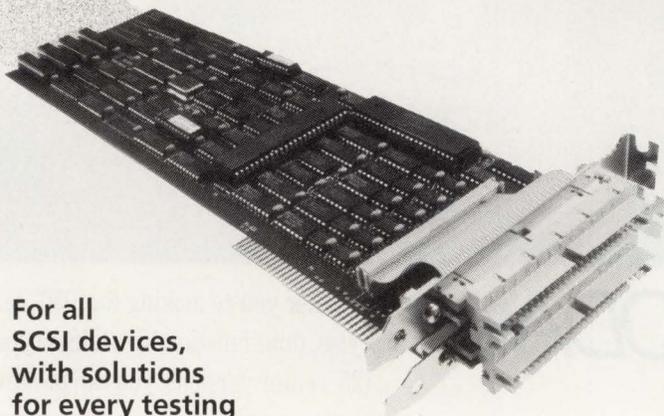

For all  
SCSI devices,  
with solutions  
for every testing  
situation — design  
through manufacturing to field service.

I-TECH'S new **SCSI-2 Fast Testers**, the first of their kind in the marketplace, transfer data at 10 MBytes/second. In addition, they feature:

- **SCSI-2 Command Queuing**
- **SCSI-2 Message System Support**
- **High-level Multi-threading Support**
- **Initiator and Target Emulation**

We offer complete development systems, low-cost manufacturing platforms and portable turn-key systems, all available with integrated bus analysis.

Ask us about **SCSI-2 Solutions**. We'll be happy to give you the details. For Information or prompt quotation call, write or FAX us.

**I-TECH**  
C O R P.

6975 Washington Ave. So. • Suite 220 • Edina, MN 55439  
612/941-5905 • FAX 612/941-2386

CIRCLE 159 FOR U.S. RESPONSE

CIRCLE 160 FOR RESPONSE OUTSIDE THE U.S.

level simulation. He states that "the majority of engineers don't know how to use simulation." These things make system-level simulation more of a theory than a reality.

But this will turn around, not necessarily because of changed design practices, but because it will become impossible to design these complex systems in the future without system-level simulation. As users continue to broaden their knowledge of automation tools, and as mandates from the military require designs be done using languages like VHDL, system-level simulations will become more common.

In the future, design teams will include the simulation of software in their system-level simulation. Few, if any, engineers can achieve that today. For example, a limited number of processor design teams perform low-level software (assembly or microcode) simulation in the realm of system-level simulation. Those that do use software in system-level simulation have performed such tasks as booting Unix.

Design teams at Intergraph Corp., Huntsville, Ala., have simulated the Clipper, a CPU for the company's workstations, running limited amounts of software. Hardware acceleration is being used to execute Unix instructions, and in turn to boot Unix. However, most design teams today have separate hardware and software development groups that perform actual hardware and software integration at the breadboard levels, after every piece is developed.

Simulating hardware running software is a high growth area for automation. EDA and CASE vendors need to provide more solid and integrated automated solutions. The abilities within VHDL, for example, that allow for text I/O, will let designers read ROM instructions from a file, emulating the behavior of the CPU processing actual microcode during "real" operations. □

HOW VALUABLE?	CIRCLE
HIGHLY	530
MODERATELY	531
SLIGHTLY	532

# Tap AMP.

For connectors and help...from custom products to system design. This is AMP today!




## Product Information by FAX-24 Hours a Day

Need product specs? Drawings? Instruction sheets? Get all these and more, any time. Call our Product Information Center (1-800-522-6752) and choose the AMP FAX option at the voice prompt. All you need is a part or document number - the system will guide you from there, and fax the information you need in minutes!



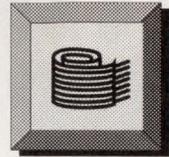
## EADS Connector Library

Meet our exciting models! We have connector drawings and engineering data (AMPTIFF files), plus 2D footprint/panel templates and 3D CAD models (AMPIGES files) on ISO 9660-compatible CD-ROMs. Our Electronic Application Design System is a real time-saver. Call 1-800-522-6752. If you use SPICE, call for licensing details: Dick Granitz, 717-986-7119.


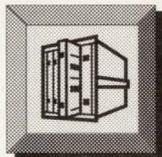
## Precision Cable Assemblies

Controlled-impedance cable and cable assemblies are required for today's high-speed hardware. We know how to engineer solutions to high-performance applications, and put that knowledge to work for you. Check our hybrid cables for applications like Smart House, and our flat copper power bus assemblies, too! Jack O'Brien, 717-780-7349.




## Backplanes and System Packaging

AMP Packaging Systems offers state-of-the-art capabilities, with expertise in advanced, high-speed systems design. We build custom and semi-custom backplanes, card cages, and enclosure systems - with complete design, characterization, and fabrication as needed, to your specifications. Call 512-244-5100 for details!



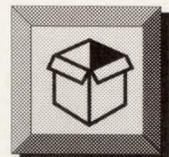
## Application Tooling...and Our Support Hotline

The key to productivity? Connector and tooling designed together, to integrate into production. The key to *continued* productivity? Total support: installation and setup, training, and service. Your key to both? For AMP customers, the AMP Field Engineering Service Hotline, 1-800-722-1111. Help at your fingertips!


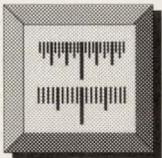
## EXCELL-PAK Program

We're shipping in new package sizes and new styles - smaller lots, more unit packaging, anti-static materials, and ergonomic design. We've also eliminated the use of CFCs and loose fill, and we're putting standard recycling codes - and bar code logos - on all packaging. Ask for our brochure!



## Inch or Metric?

Many of our most popular product families are available in both inch and hard metric sizes. If you're at all concerned with global marketing these days (and who isn't?), be sure to ask your AMP Sales Engineer for details. Or give us a call at 1-800-522-6752!



## Design Analysis

High-speed logic requires a new approach to interconnect design, and AMP Interconnect Systems delivers it. We provide a total systems solution, including analysis of your design, complete interconnect simulation and board assembly, card cage design and fabrication, power distribution/thermal analysis, and system fabrication. Fast time-to-market for fast silicon! Ben Bennett, 717-986-7824.



## A.C.E.S.

Looking for value-added interconnect systems? AMP Cooperative Electronics Subcontractors (A.C.E.S.) are fully qualified to meet your needs. Trained partners offer high-tech assemblies, backplane systems, and more. They're part of a premiere network of local, regional, and national AMP distributors. For the distributor near you, call 1-800-522-6752.

AMP is a trademark of AMP Incorporated.  
EXCELL-PAK is a service mark of AMP Incorporated.

**THIS IS AMP TODAY.**


**AMP**

CIRCLE 82 FOR U.S. RESPONSE

CIRCLE 83 FOR RESPONSE OUTSIDE THE U.S.


# Now, one family drives all FETs.
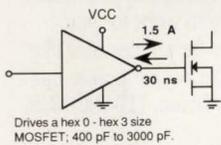
## High Speed, High Current Low Side MOSFET Drivers




### MIC426/7/8 (Original)

- 30 nS into 1000 pF
- 4.5 V to 18 V supply
- 1.5 A peak output
- 6  $\Omega$  output impedance
- Available in surface mount packages

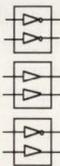


MIC426  
MIC427  
MIC428

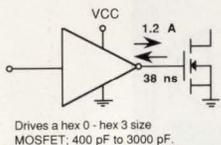


### MIC1426/7/8 (Low Cost)

- Low cost predriver
- 38 nS into 1000 pF
- 4.75 V to 16 V supply
- 1.2 A peak output
- 8  $\Omega$  output impedance
- Available in surface mount packages

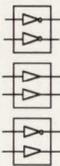


MIC1426  
MIC1427  
MIC1428

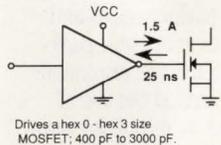


### MIC4426/7/8 (Protected)

- Latch-up protected
- 25 nS into 1000 pF
- 4.5 V to 18 V supply
- 1.5 A peak output
- 7  $\Omega$  output impedance
- Withstands 5 V negative swing
- Available in surface mount and high temperature packages

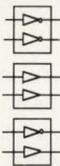


MIC4426  
MIC4427  
MIC4428

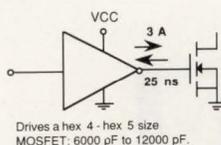


### MIC4423/4/5 (High Current)

- Latch-up protected
- 25 nS into 1800 pF
- 4.5 V to 18 V supply
- 3 A peak output
- 3.5  $\Omega$  output impedance
- Withstands 5 V negative swing
- Available in surface mount packages

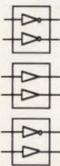


MIC4423  
MIC4424  
MIC4425

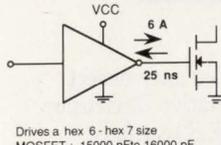


### MIC4420/4429 (Singles)

- Latch-up protected
- 25 nS into 10,000 pF
- 4.5 V to 18 V supply
- 6 A peak output
- 2.5  $\Omega$  output impedance
- Withstands 5 V negative swing
- Available in surface mount packages

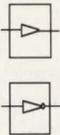


MIC4420  
MIC4429

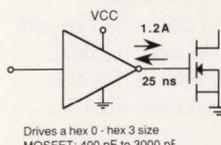

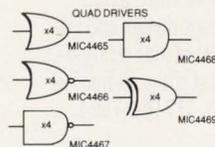
### MIC4465/6/7/8/9 (Quad)


- Latch-up protected
- 25 nS into 470 pF
- 4.5 V to 18 V supply
- 1.2 A peak output
- Available in surface mount packages
- Five logic choices




## High Side, Protected MOSFET Drivers

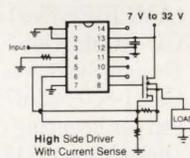


High Side Driver With Current Sense

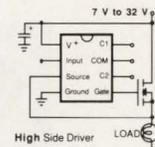

High Side Driver

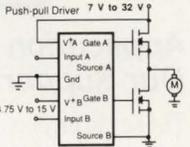


Push-pull Driver 7 V to 32 V

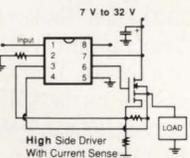

High Side Driver With Current Sense
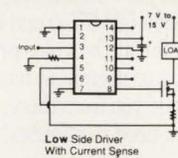
### MIC5010


- Full Featured predriver
- Optional speed up caps
- 7 V to 32 V supply
- Internal charge pump
- 60  $\mu$ S into 1 nF
- Over current sensing
- Fault flag output
- Surface mount packages
- Dynamic sensing threshold



Low Side Driver With Current Sense
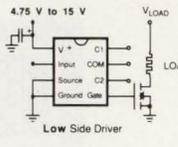
### MIC5011


- Minimum parts count
- Optional speed up caps
- 4.75 V to 32 V supply
- Internal charge pump
- 60  $\mu$ S into 1 nF
- Surface mount packages



Low Side Driver
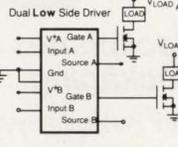
### MIC5012

- Dual predriver
- Provides high and low side
- 4.75 V to 32 V supply
- Internal charge pump
- 60  $\mu$ S into 1 nF
- Surface mount packages



Low Side Driver With Current Sense

### MIC5013

- Over current sensing
- 7 V to 32 V supply
- Fault flag output
- Internal charge pump
- 60  $\mu$ S into 1 nF
- Surface mount packages
- Dynamic sensing threshold

Choose from the widest selection of MOSFET predrivers in the industry. Whether your specification requires ultrafast low side driving, overcurrent protected high side driving, or overcurrent protected low side driving of 1 Amp to 100 Amp MOSFETs, we can supply the right product from our family of CMOS drivers to reliably meet your needs. For details contact: Micrel Semiconductor, 560 Oakmead Parkway, Sunnyvale, CA 94086. Or call (408) 245-2500.

**MICREL**  
SEMICONDUCTOR

*The Intelligent Power Company<sup>tm</sup>*

To place **orders** or receive a copy of **Micrel's 1991 Data Book** please contact the sales locations listed below. For application information please call Micrel Inc. at **408-245-2500**.

**AUTHORIZED REPRESENTATIVES WORLDWIDE**

**UNITED STATES**

**ALABAMA**

Electronic Marketing Assoc.  
Tel: 205-880-8050

**ARIZONA**

Sun State Technical Sales  
Tel: 602-220-0595

**ARKANSAS**

Barry Sales  
Tel: 214-234-0255

**CALIFORNIA (Northern)**

W-J Electronic Sales  
Tel: 408-982-9222

**CALIFORNIA (Southern)**

D2 Sales Incorporated  
Tel: 619-481-9310

**CALIFORNIA (Southern)**

RTS Associates  
Tel: 714-730-9561

**CALIFORNIA (Southern)**

The LCS Company  
Tel: 619-868-5844

**COLORADO**

Component Sales Inc.  
Tel: 303-779-8060

**CONNECTICUT**

Dynamic Sales  
Tel: 203-693-6567

**DELAWARE**

Omega Electronic Sales  
Tel: 215-244-4000

**GEORGIA**

Electronic Marketing Assoc.  
Tel: 404-448-1215

**IDAHO**

SPS Electronics Inc.  
Tel: 503-697-7768

**ILLINOIS**

ESA Technical Marketing  
Tel: 708-544-0120

**INDIANA**

Applied Data Management  
Tel: 317-257-8949

**IOWA**

J R Sales Engineering  
Tel: 319-393-2232

**KANSAS**

Midwest Technical Sales  
Tel: 913-888-5100

**LOUISIANA**

Barry Sales  
Tel: 214-234-0255

**MASSACHUSETTS**

Dynamic Sales  
Tel: 617-272-5676

**MARYLAND**

Boyle Associates  
Tel: 703-620-9558

**MICHIGAN**

Applied Data Management  
Tel: 313-741-8558

**MICHIGAN**

Applied Data Management  
Tel: 313-485-2974

**MINNESOTA**

George Russell Associates  
Tel: 612-854-1166

**MISSISSIPPI**

Electronic Marketing Assoc.  
Tel: 205-880-8050

**MISSOURI**

Midwest Technical Sales  
Tel: 314-298-8787

**NEW HAMPSHIRE**

Dynamic Sales  
Tel: 617-272-5676

**NEW JERSEY**

Comp Tech Sales  
Tel: 201-288-7400

**NEW MEXICO**

Nelco Electronix  
Tel: 505-293-1399

**NEW YORK CITY**

Comp Tech Sales  
Tel: 201-288-7400

**NEW YORK (Upstate)**

Smith Technical Sales  
Tel: 716-924-8612

**NEBRASKA**

J R Sales Engineering  
Tel: 319-393-2232

**NORTH CAROLINA**

Electronic Marketing Assoc.  
Tel: 919-847-8800

**OHIO**

Crest Components  
Tel: 216-543-9808

**OKLAHOMA**

Barry Sales  
Tel: 214-234-0255

**OREGON**

SPS Electronics Inc.  
Tel: 503-697-7768

**PENNSYLVANIA**

Omega Electronic Sales  
Tel: 215-244-4000

**SOUTH CAROLINA**

Electronic Marketing Assoc.  
Tel: 803-233-4637

**TENNESSEE**

Electronic Marketing Assoc.  
Tel: 404-448-1215

**TEXAS**

Barry Sales  
Tel: 214-234-0255

**UTAH**

Component Sales, Inc.  
Tel: 801-561-5688

**VERMONT**

Dynamic Sales  
Tel: 802-476-4223

**VIRGINIA**

Boyle Associates  
Tel: 703-620-9558

**WASHINGTON**

SPS Electronics Inc.  
Tel: 206-794-0154

**WASHINGTON D.C.**

Boyle Associates  
Tel: 703-620-9558

**WISCONSIN**

ESA Technical Marketing  
Tel: 708-544-0120

**WYOMING**

Component Sales, Inc.  
Tel: 303-779-8060

**EUROPE**

**FRANCE**

Rep France  
Tel: 011-331-420-42925

**GERMANY**

Adicom GmbH  
Tel: 011-49-089-723-7078

**ISRAEL**

I.E.S. Electronic Agencies  
Tel: 011-972-3-752-6333

**ITALY**

Acis s.r.l.  
Tel: 011-39-2439-0832

**UNITED KINGDOM**

Mogul Electronics  
Tel: 011-44-732-741841

**ASIA**

**JAPAN**

Kawasho Corporation  
Tel: 011-813-35-78-5190

**KOREA**

Acetronix  
Tel: 011-822-796-4561

**SINGAPORE**

QuadRep Electronics (T) Ltd.  
Tel: 011-886-2-5522372

**TAIWAN**

QuadRep Electronics (T) Ltd.  
Tel: 011-886-2-5522372

**AUTHORIZED DISTRIBUTORS WORLDWIDE**

**Calder Electric**

Grand Rapids, MI  
Tel: 616-698-7400

**Competitive Components**

Fullerton, CA  
Tel: 714-871-8700

**Connec Tek, Inc.**

Carrollton, TX  
Tel: 214-245-1266

**Connec Tek, Inc.**

Houston, TX  
Tel: 713-956-9091

**Connec Tek, Inc.**

Austin, TX  
Tel: 512-837-9892

**Ditz Schweitzer**

Denmark  
Tel: 011-45-42-459244

**Electronitel**

Switzerland  
Tel: 011-41-37-410060

**Elcontrol S.p.A.**

Italy  
Tel: 011-39-51-86-10-79

**High Technology Semi**

Tustin, CA  
Tel: 714-259-7733

**ISC France**

France  
Tel: 011-331-45-064275

**Integrated Electronics**

Finland  
Tel: 011-358-351-3133

**Jan Devices Incorporated**

Reseda, CA  
Tel: 818-708-1100

**Kawasho Corporation**

Japan  
Tel: 011-813-35-78-5190

**Lagerkrantz Keltech**

Sweden  
Tel: 011-46-08-754-7400

**Microlink S.A.**

Belgium  
Tel: 011-32-2-5218650

**Nu Horizons**

Amityville, NY  
Tel: 516-226-6000

**Nu Horizons**

Pine Brook, NJ  
Tel: 201-882-8300

**Nu Horizons**

Wakefield, MA  
Tel: 617-246-4442

**Nu Horizons**

Rochester, NY  
Tel: 716-248-5980

**Nu Horizons**

Columbia, MD  
Tel: 301-995-6330

**Nu Horizons**

Marlton, NJ  
Tel: 609-596-1833

**Nu Horizons**

Ft. Lauderdale, FL  
Tel: 305-735-2555

**Nu Horizons**

Huntsville, AL  
Tel: 205-722-9330

**Nu Horizons**

Norcross, GA  
Tel: 404-416-8666

**Opto Plus + Incorporated**

Mission Viejo, CA  
Tel: 714-380-8654

**R&D Electronics**

Australia  
Tel: 011-61-03-808-8911

**R-Theta**

Canada  
Tel: 416-890-0221

**Solid State Supplies**

United Kingdom  
Tel: 011-44-892-35366

**Taylor Electric**

Mequon, WI  
Tel: 414-241-4321

**Unitronics S.A.**

Spain  
Tel: 011-34-1-542-5204

# 100kHz DATA ACQUISITION DESIGNED FOR THE OEM

**"Our DT2812 data acquisition board for the PC is the most cost effective board of its kind on the market."**

—Fred Molinari, President

## Complete feature set

- 12-bit A/D, D/A
- 16 single ended or 8 differential analog inputs
- Two analog outputs
- 16 digital I/O lines
- Counter/Timers

## High performance

- DMA data transfer to 100kHz
- Interrupt driven acquisition frees PC bus
- User selectable gain
- Analog input range up to  $\pm 10V$
- Pacer clock automates multiple A/D and D/A conversions

## High reliability

- Shielded interconnect
- Excellent DC stability
- $>70dB$  common mode rejection

## FREE software

- Device driver and subroutine library

## Discounted OEM pricing available



- Call today to become qualified

## Fast 5 day delivery

Call for FREE Catalog

**(508) 481-3700**

In Canada, call (800) 268-0427

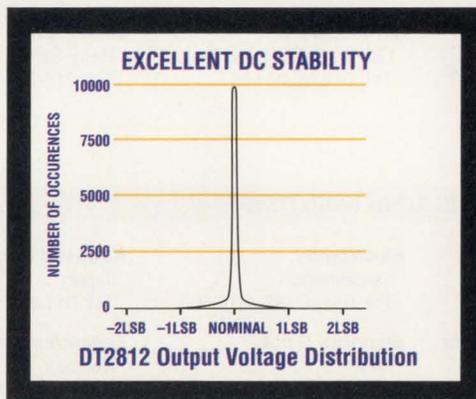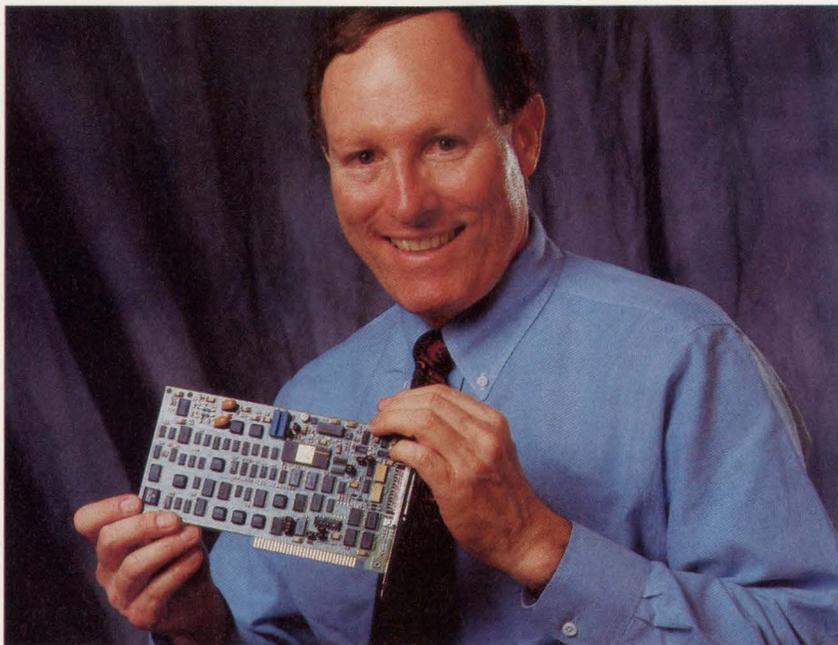

**THE LEADER IN DATA ACQUISITION AND IMAGE PROCESSING**

# DATA TRANSLATION®

**World Headquarters:** Data Translation, Inc., 100 Locke Drive, Marlboro, MA 01752-1192 USA, (508) 481-3700, Fax (508) 481-8620, Tlx 951646

**United Kingdom Headquarters:** Data Translation Ltd., The Mulberry Business Park, Wokingham, Berkshire RG11 2QJ, U.K., (734) 793838, Fax (734) 776670, Tlx 94011914

**Germany Headquarters:** Data Translation GmbH, Im Weilerlen 10, 7120 Bietigheim-Bissingen, Germany 7142-54025, Fax 7142-64042

**International Sales Offices:** Australia (2) 699-8300; Belgium (2) 466-8199; Brazil (11) 240-0598; Canada (416) 625-1907; China (1) 513-7766 x 1222; Denmark 42 274511; Finland (0) 3511800; France (1) 69077802; Greece (1) 361-4300; Hong Kong (5) 448963; India (22) 23-1040; Israel 52-545685; Italy (2) 82470.1; Japan (3) 502-5550, (3) 5379-1971; Korea (2) 718-9521; Malaysia 3-2486788; Netherlands (70) 399-6360; New Zealand (9) 415-8362; Norway (2) 53 12 50; Poland (22) 580701; Portugal (1) 7934834; Singapore 338-1300; South Africa (12) 803-7680/93; Spain (1) 555-8112; Sweden (8) 761 78 20; Switzerland (1) 723-1410; Taiwan (2) 3039836

Data Translation is a registered trademark of Data Translation, Inc. All other trademarks and registered trademarks are the property of their respective holders.

CIRCLE 98 FOR U.S. RESPONSE

CIRCLE 99 FOR RESPONSE OUTSIDE THE U.S.

CORRECTING POWER FACTOR AT THE INPUT TO SWITCHERS CAN BE FAR MORE EFFECTIVE THAN FIGHTING TO BOOST THEIR EFFICIENCY.

# SOLVE SWITCHER PROBLEMS WITH POWER-FACTOR CORRECTION

**PATRICK L. HUNTER**  
Unipower Corp.,  
2981 Gateway Dr.,  
Pompano Beach, FL 33069;  
(305) 974-2442.

**W**hen specifying power supplies, system engineers always focus on the supplies' output end: voltages, currents, regulation, filtering, and output protection. Little concern is given to the input end, except perhaps to meet electromagnetic-interference (EMI) standards. With higher-power, off-line switching power supplies in wide use, new questions have arisen concerning the input end and its effect on the ac-power line and other electronic systems in the local environment. This article explores the subject of power factor at the input to switching power supplies, the problems it causes, and solutions to those problems.

Power factor is a well-known term in standard ac-circuit theory. It refers to the effect of a reactive load on an ac-power system. In a linear ac circuit with a purely resistive load, the ac current is in phase with the ac voltage, and the average power consumed by the load is the product of the rms (root mean square) voltage and rms current. For a linear load combining resistance and reactance, the current lags the voltage for an inductive reactance and leads the voltage for a capacitive reactance. The product of rms voltage and rms current gives a quantity called "apparent power":

$$\text{Apparent power} = P_A = E_{\text{rms}} \times I_{\text{rms}} \quad (1)$$

This quantity, however, isn't the average or "real" power, consumed by the resistive part of the load.

Real power is calculated as the average of the instantaneous product of voltage and current taken point by point over a full period of the source waveform:


$$\text{Real power} = P_R = \frac{1}{T} \int_0^T (e \times i) dt \quad (2)$$

and for a linear circuit:

$$P_R = E_{\text{rms}} \times I_{\text{rms}} \times \cos \theta = P_A \times \cos \theta \quad (3)$$

where  $\theta$  is the phase angle between the sinusoidal voltage and current waveforms.

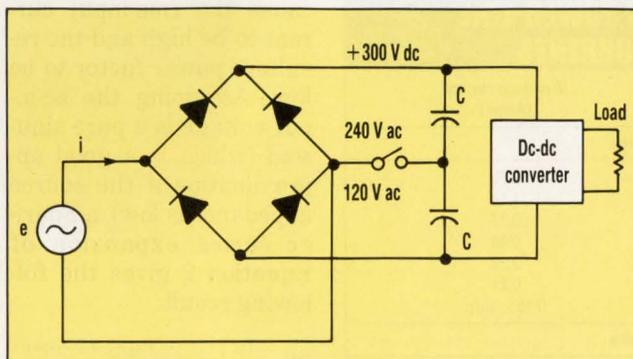Power factor is a measure of how close apparent power is to real power, defined by the ratio:



**1. AN OFF-LINE SWITCHING** power supply's input circuit has a full-bridge rectifier and storage capacitor. The circuit is a voltage doubler for 120-V ac input.

# POWER FACTOR AND SWITCHING POWER SUPPLIES

**TABLE 1: EXAMPLES OF MAXIMUM POWER AVAILABLE FROM STANDARD AC OUTLETS**

	15-A circuit			20-A circuit		
	1	2	3	1	2	3
VA available (UL)	1440	1440	1440	1920	1920	1920
Efficiency of supply	75%	90%	75%	75%	90%	75%
Efficiency of PFC	-	-	97%	-	-	97%
Total efficiency	75%	90%	73%	75%	90%	73%
Power factor	0.65	0.65	0.95	0.65	0.65	0.95
Maximum load power	702 W	842 W	995 W	936 W	1123 W	1327 W

$$\text{Power factor} = \text{PF} = \frac{P_R}{P_A} = \frac{\text{Real power}}{\text{Apparent power}} \quad (4)$$

$$= \frac{P_R}{E_{\text{RMS}} \times I_{\text{RMS}}}$$

$$= \cos \theta \quad (\text{for a linear load})$$

If the load in an ac circuit is purely resistive, then apparent power and real power are identical, and power factor is its maximum value of 1.


A common problem that plagues ac-power systems is caused by a factory operating electric motors. The inductive component of the motors causes the ac current to lag the voltage, resulting in a low power factor. Assuming the load elements are linear, power factor can be corrected to near unity by connecting a bank of capacitors across the ac-power line at the factory.

Switching power supplies present a problem to ac-power systems that's quite different from motor loads. Here, the term "switching power supply" means an off-line switcher with an input rectifier and filter capacitor connected directly to the ac-power line, without an intervening transformer.

The input circuit of a switching power supply with the commonly used full-wave bridge rectifier and voltage-doubler circuit is shown (Fig. 1). This circuit produces an average dc-output voltage of about 300 V with a 120-Hz ripple-voltage component.

The switch, or jumper wire, lets the power supply operate from either 120- or 240-V ac nominal line voltage, with the circuit acting as a voltage doubler when operating from a 120-V ac input.

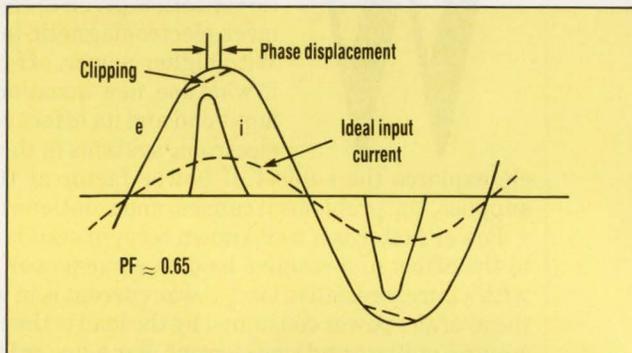A switching power supply presents a nonlinear load to the ac-power line—one in which the input current isn't a sinusoid but rather a series of pulses (Fig. 2). The current pulse lasts for a small portion of each half-period of the voltage, is non-



**2. THE INPUT CURRENT** of a switching power supply is a non-symmetrical pulse that occurs near the peak of the ac voltage. This pulse can cause clipping of the voltage waveform.

**TABLE 2: IEC CLASS-A LIMITS ON 220/240-V AC POWER-LINE HARMONIC CURRENTS**

Harmonic order (n)	Maximum current (Amps)
Odd harmonics	
3	2.30
5	1.14
7	0.77
9	0.40
11	0.33
13	0.21
15 ≤ n ≤ 39	0.15 × 15/n
Even harmonics	
2	1.08
4	0.43
6	0.30
8 ≤ n ≤ 40	0.23 × 8/n

symmetrical in shape, and may either slightly lead or lag the ac-input voltage depending on the impedance of the ac source. Also, the input-voltage waveform may be significantly clipped near the peaks, depending on the amount of ac-source impedance that is present.

The current pulse occurs because the filter capacitors remain charged to nearly the peak value of the ac-input voltage. During most of each half-period of input voltage, the rectifier diodes remain back-biased and no current flows. However, because the capacitors partly discharge during each half period, the input voltage exceeds the capacitor voltage for a short time near the peak of the voltage waveform.

As the input voltage goes higher than the capacitor voltage, current begins to flow into the capacitor. After the capacitor is charged to near the peak value of the voltage and the voltage begins to decrease, the current falls back to zero.

Once the input-current waveform is examined, it's easy to understand the power-factor problem. The current pulse has a high peak value and is extremely distorted with respect to a sinusoidal waveform. It has high levels of harmonic currents, and a fundamental component that leads or lags the input voltage depending on source impedance.

These characteristics cause the rms-input current to be high and the resultant power factor to be low. Assuming the ac-input voltage is a pure sinusoid (which is a good approximation if the source impedance is low), a Fourier series expansion of Equation 2 gives the following result:

$$\text{PF} = \frac{I_F}{I_{\text{RMS}}} \cos \theta = \frac{E_{\text{RMS}} \times I_F \cos \theta}{E_{\text{RMS}} \times I_{\text{RMS}}}$$

$$= \frac{P_R}{P_A} \quad (5)$$

# Limited Only By Your Imagination



Remember how quickly you could turn a concept into reality with a set of quality building blocks? How you always seemed to have just the right parts and how well they fit together? How easily you could modify your creation to explore creative alternatives?

Our VI-200 and VI-J00 families of high density converters, along with a host of compatible modular peripheral products, are designed to "plug and play" perfectly... offering you the flexibility, ease-of-use, quality and repeatability needed to implement virtually any power system solution. And with hundreds of standard models to choose from...input ratings from 10 to 400 Volts, outputs from 2 to 95 Volts and power expansion from Watts to kiloWatts... you won't be stuck at the last minute with "missing" parts.

You're not playing with toys anymore...which may be the most important reason for specifying Vicor's component-level "building blocks" for your next power system.




*Component Solutions For Your Power System*



23 Frontage Road Andover, MA 01810  
TEL: (508) 470-2900 FAX: (508) 475-6715

CIRCLE 138 FOR U.S. RESPONSE  
CIRCLE 139 FOR RESPONSE OUTSIDE THE U.S.

# How Teradyne helps Northern Telecom

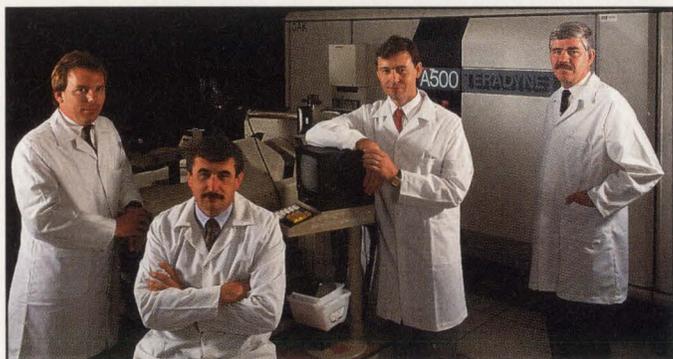

John Haydon, Ken Bradley, Gary Hobin, Terry Caves of Northern Telecom Electronics, Ottawa.

*"To us, time is a strategic tool, a way of getting the edge it takes to gain a leadership role in world markets. With Teradyne testers, test development and manufacturing setup times are shorter, and actual test performance is far superior."*

KEN BRADLEY, General Manager

Northern Telecom believes a quality message begins with a commitment: to deliver the highest performance products at the lowest cost – quickly and on time.

That's why Northern Telecom Electronics chose the Teradyne A500 Family of systems to test its most advanced mixed-signal chips. Pushing the performance envelope can be risky, but Teradyne is helping Northern Telecom avoid the pitfalls.

*"Our Norstar key system is extremely silicon intensive. The A500 provided virtually unlimited test capability and reduced test time."*



## send the world a quality message.

*I believe without it, the entire project would not be nearly as successful as it is."*

GARY HOBIN, Manager,  
Test & Product Engineering

Because the A500 Family's IMAGE™ programming environment permits full tester simulation at off-line workstations, test program development parallels design. That cuts product development times dramatically. And because test data is fed back quickly and early in the process, Northern Telecom engineers can eliminate bottlenecks, enhance manufacturability, and accelerate time-to-market.

*"Teradyne helps us meet our high-volume production goals — on time. And they perform beyond our expectations in terms of operating costs; tester maintenance cost is 80% lower than budget — and tester uptime measures in the 98%-plus range."*

JOHN HAYDON, Business Unit Manager,  
Test Operations

Teradyne's A500 Family testers run reliably, producing the accurate, repeatable results that let Northern Telecom engineers ramp up fast to high-yield, high-volume production. So when a customer needs devices, Northern Telecom Electronics is ready to deliver quantity as well as quality.

*"Teradyne's service continues after the sale. It's as if they take our priorities as their own. That's helped us achieve the quality it takes to succeed in such highly competitive markets as the U.S., U.K., Germany, and Japan."*

TERRY CAVES, Director of Operations

Teradyne's A500 Family of Test Systems. Helping companies like Northern Telecom send their customers the right message. To see how we can help you, call Beth Sulak at (617) 422-2746.

Or write today to:  
Teradyne, Inc.,  
321 Harrison Ave.,  
Boston, MA 02118.

**TERADYNE**

CIRCLE 196 FOR U.S. RESPONSE

CIRCLE 197 FOR RESPONSE OUTSIDE THE U.S.

# POWER FACTOR AND SWITCHING POWER SUPPLIES

where  $I_F$  is the rms value of the fundamental frequency component of the input current,  $I_{rms}$  is the rms value of the total input current, and  $\theta$  is the phase angle of displacement between the fundamental frequency component and the source voltage.  $I_{rms}$  is the square root of the sum of the squares of the fundamental plus all harmonic components of the input-current waveform.

Equation 5 states the power factor in terms of a distortion factor,  $I_F/I_{rms}$ , and a phase-angle factor,  $\cos \theta$ . The phase angle is generally small, so the dominant factor in switching power supplies is waveform distortion. If the source voltage is a near-perfect sinusoid, then the following statement is true:


*Only the fundamental component of input current contributes to the real (average) input power; the other harmonic components merely increase the magnitude of rms-input current and lower the power factor.*

## TYPICAL INPUT CURRENTS

To appreciate actual values of current for a typical switching power supply, consider a supply that operates from a 120-V ac source and delivers 1000 W to its load. The efficiency of such a supply is typically 75% and the measured power factor about 0.65. The rms-input current is about 17 A and the peak input current about 46 A.

Compare these current levels to those of an idealized power supply that doesn't distort the input current but has a purely resistive input with the same 75% efficiency. In this case, the power factor is 1.0, the sinusoidal input current is 11.1 A, and the peak input current is only 15.7 A. In the real-world example, rms-input current is 53% higher and peak-input current is 193% higher than the ideal.

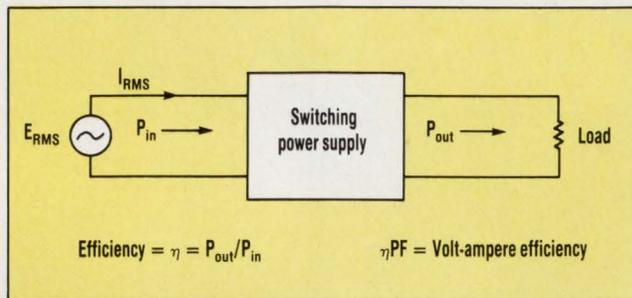It should be noted here that in making power-factor measurements, the current must be measured with a true-rms ammeter and



**3. VOLT-AMPERE** efficiency,  $\eta$ PF, is the figure of merit that determines the input current for a switching power supply.

the input power with an average-reading wattmeter.

An important figure of merit for switching power supplies is "volt-ampere (VA) efficiency." To understand this term, it helps to look at a power-supply diagram (Fig. 3). From the figure:

$$PF = \frac{P_R}{P_A} = \frac{P_{IN}}{E_{RMS} \times I_{RMS}} = \frac{P_{OUT}/\eta}{E_{RMS} \times I_{RMS}} \quad (6)$$

where  $\eta$  is the efficiency of the power supply. Rearranging terms gives:

$$I_{RMS} = \frac{P_{OUT}}{(\eta PF) E_{RMS}} \quad (7)$$

The product of efficiency and power factor ( $\eta$ PF), called VA efficiency, is the figure of merit that determines input current. Maximizing a power supply's  $\eta$ PF minimizes input current.

In the previously discussed example of a 1000-W power supply, the efficiency is 75% and power factor is 0.65. Therefore:

$$VA \text{ efficiency} = PF = 0.75 \times 0.65 = 0.4875 \quad (8)$$


and

$$I_{RMS} = \frac{1000}{0.4875 \times 120} = 17.1 \text{ A} \quad (9)$$

which is the value that is given in the example.
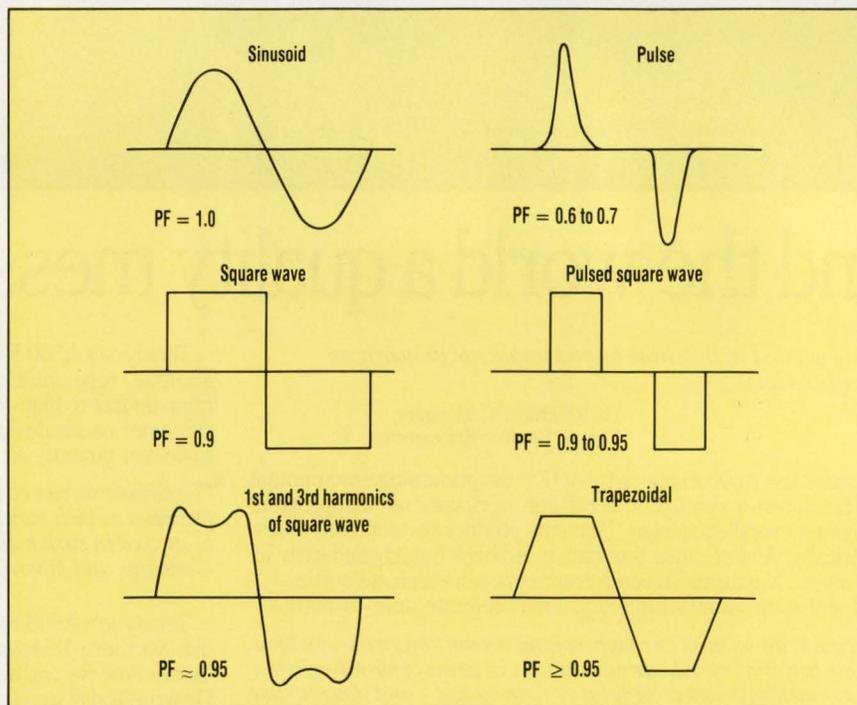
## WHY PFC IS NEEDED

Safety-regulatory agencies, such as Underwriters Laboratories (UL), have safety limits on current levels for standard ac-service outlets. For standard 120-V ac, 15- and 20-A outlets, the rated load must be main-



**4. MANY INPUT-CURRENT** waveshapes yield a relatively high power factor, but the shape must be close to a sinusoid to also attain low harmonic currents.

# POWER FACTOR AND SWITCHING POWER SUPPLIES

tained at 80% or less of the source rated current. This means maximum currents of 12 and 16 A, respectively, and maximum apparent power ( $E_{rms} \times I_{rms}$ ) of 1440 and 1920 VA, respectively.

In the example of the 1000-W power supply in Equation 9, the input current was 17.1 A, giving an apparent power of 2052 VA. This exceeds the UL standard for both 15- and 20-A service outlets.

Equation 7 can be used to solve the maximum power output of a switching power supply operating within UL limits from standard 15- or 20-A circuits. Assuming 75% efficiency and 0.65 power factor, the power available is 702 and 936 W, respectively.

To increase the output power from standard ac outlets, it's necessary to correct the power factor in a switching power supply. This substantially reduces peak and rms-input current, which makes it possible to achieve a much higher output power. Power-factor correction (PFC) is a much more effective approach than trying to boost efficiency. Component limitations make efficiencies of more than 75% impractical. On the other hand, boosting power factor to 0.95 and higher is a fairly simple task, resulting in 995 and 1327 W of output power, respectively, from 15- and 20-A outlets.

The various efficiencies and power factors of switching power supplies produce diverse results in terms of the amount of power that can be drawn from standard outlets (Table 1). When a PFC circuit is added, its efficiency must also be considered as part of the total power-supply efficiency.

The low power factor caused by high rms-input currents in switching power supplies gives rise to a number of serious problems in

### TABLE 3: PASSIVE POWER-FACTOR CORRECTION

Advantages	Disadvantages
<ul style="list-style-type: none"> <li>• Simple and rugged</li> <li>• High MTBF</li> <li>• Low EMI</li> </ul>	<ul style="list-style-type: none"> <li>• Large size and weight</li> <li>• High PF difficult</li> <li>• Frequency-dependent</li> <li>• Load-dependent</li> <li>• Narrow line-voltage range</li> <li>• Dual-voltage ranges are difficult to implement</li> <li>• May have large, circulating currents</li> </ul>

### TABLE 4: ACTIVE HIGH-FREQUENCY POWER-FACTOR CORRECTION

Advantages	Disadvantages
<ul style="list-style-type: none"> <li>• High PF (0.97 to 0.99)</li> <li>• Very low harmonic distortion</li> <li>• Wide line-voltage range (90 to 264 V ac)</li> <li>• Wide frequency range</li> <li>• Regulated high-voltage bus</li> <li>• Small magnetics</li> <li>• Holdup time constant with input-voltage change</li> </ul>	<ul style="list-style-type: none"> <li>• Complex circuitry</li> <li>• Double power conversion</li> <li>• Reduced MTBF</li> <li>• Higher cost</li> <li>• Highest EMI</li> <li>• May require synchronization of converters</li> <li>• Lower efficiency</li> </ul>

electronic equipment. For one, equipment fuses and circuit breakers must be increased in size. Costly EMI filters must have higher current ratings. The distorted input-current waveform, which may cause interference with other equipment, may have to be further filtered to reduce harmonic frequencies. If the equipment is operated from an uninterruptible power supply (UPS) or standby generator, the size and cost of these items will increase. And finally, the input currents can cause problems in three-phase power systems.

limit on the third harmonic of 1.08 A. These limits seriously curtail the amount of power that a switching power supply can deliver without PFC.

## THREE-PHASE PROBLEMS

Switching power supplies with uncorrected power factor can cause difficult problems in three-phase power systems. For example, in a four-wire wye-connected system, loads throughout a building are connected from each phase to the neutral line. Under ideal conditions with each phase's load current sinusoidal, in phase, and equal, the currents in the neutral line cancel to give zero current. Even with a different load on each phase there is partial cancellation of the neutral line currents.

If, however, switching power supplies are on each phase, the distorted non-sinusoidal input currents don't cancel each other, but rather combine into a larger current. The third-harmonic currents generated in each phase load combine directly

### TABLE 5: ACTIVE LOW-FREQUENCY POWER-FACTOR CORRECTION

Advantages	Disadvantages
<ul style="list-style-type: none"> <li>• High efficiency</li> <li>• Simple circuitry</li> <li>• High MTBF</li> <li>• High PF (0.96-0.98)</li> <li>• Low EMI</li> <li>• Low harmonic distortion</li> <li>• Wide frequency range</li> <li>• Lowest cost</li> <li>• Moderate input-voltage range (90 to 132 V ac or 180 to 264 V ac)</li> </ul>	<ul style="list-style-type: none"> <li>• Holdup time changes with line voltage</li> <li>• Dc bus not regulated</li> <li>• Larger and heavier than HF method</li> </ul>

# POWER FACTOR AND SWITCHING POWER SUPPLIES

in-phase in the neutral wire. Uncorrected switching power supplies, therefore, have very high third-harmonic currents.

The result can be large currents in the neutral line that far exceed currents in the phase lines and therefore surpass the current rating in the neutral wire.


Because the neutral line has no circuit protection, there may be overheating that can cause damage to the wire.

In such cases, circuit breakers or other protection devices on the phase lines fail to protect the wiring, sometimes setting off fires. PFC is a solution to this nasty problem in three-phase systems.
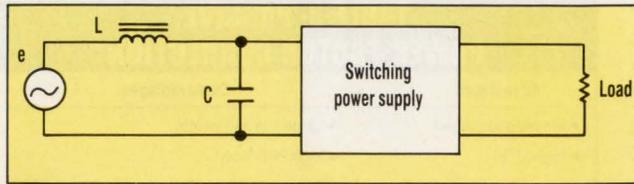
## PFC METHODS

PFC in a switching power supply is accomplished by reshaping the distorted input-current waveform to approximate a sinusoidal current that's in-phase with the input voltage. The important question remains, though, of how good the reshaping must be to achieve a power factor of, say, 0.95 or higher.

Some indication of what must be done is shown in several potential current-waveform shapes with corresponding typical power factors (Fig. 4). High power factors can be achieved by current waveforms that aren't very sinusoidal in shape. But



**5. A PASSIVE** power-factor-correction circuit can be a simple LC filter when the correction must be performed external to the power supply.

undesirable harmonic currents is another factor to consider, and some of these waveforms are high in harmonic content.

There are several effective techniques for achieving a good input-current waveform with low distortion. Because the supply's output is smooth dc, the PFC circuit must store a minimum amount of energy to correct for instantaneous differences between input and output power functions.

The minimum amount of stored energy will depend upon the input-current waveform, the line frequency, and the load power, and will be independent of the intermediate switching frequencies that control the current waveform and process the power throughout.

PFC can be designed as a separate box between the ac-power source and the power supply or as an integral part of the input rectification and filtering process. The energy storage needed for PFC already exists in the high-voltage capacitor of

the switching power supply. By coordinating the input-current waveshaping with rectification and energy storage, the highest performance is achieved at the lowest cost.

Three of the most-used techniques for PFC are passive correction, active high-frequency correction, and active low-frequency correction.

These techniques are discussed in detail later on. Only single-phase-input power supplies are considered in this article.

As power levels move up to the multi-kilowatt range, three-phase systems become important, and PFC unique to these systems must be used. Those techniques, though, aren't discussed in this article.

## PASSIVE PFC


Passive PFC techniques shape the input-current wave by using a passive input filter consisting of inductors and capacitors. This method is effective as a front-end box, where the system already has an uncorrected power supply, and the engineer must implement PFC without changing the power supply (Fig. 5).

Because it operates at line frequencies of 50 or 60 Hz, the passive filter requires relatively large inductors and capacitors to reduce the low-frequency harmonic currents. To produce power factors of 0.90 or greater, sophisticated filters are needed to properly smooth and attenuate harmonics.

Generally, such filters use resonant-pass or -trap circuits sensitive to both frequency and load. It's difficult to achieve power factors of 0.95 or higher with passive filters. Another problem is very large currents that may circulate in the filter.

Nevertheless, the passive filter can be an effective PFC solution in cases where line frequency, line voltage, and load are relatively constant. The advantages and disadvantages are summarized (Table 3).

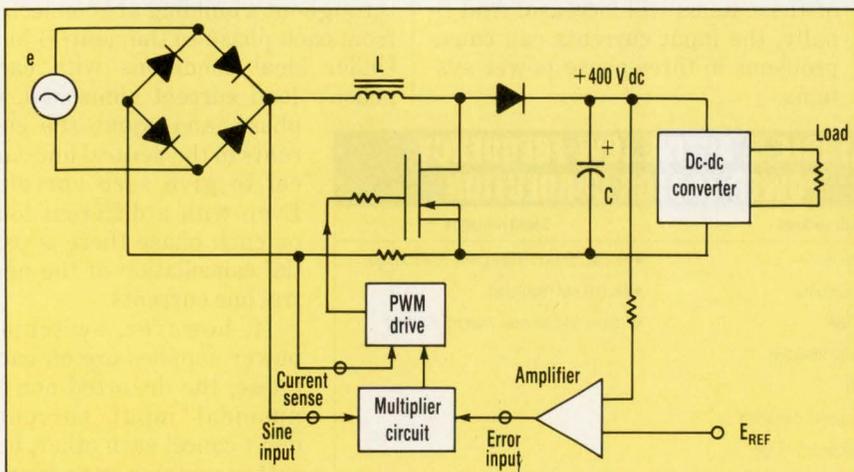As discussed, active PFC is a better solution when compared with the passive method. The circuit is an integral part of the power-supply's



**6. THE ACTIVE HIGH-FREQUENCY** power-factor-correction circuit forces the input current to be sinusoidal. It also regulates the voltage going to the dc-dc-converter part of the power supply. Power factors from 0.97 to 0.99 are achieved.


## Under the DIP caps - Micro/Q 1000 & 2000

### Standard Capacitors:

- Improve board performance without redesign.
- Solve noise problems by retrofitting existing boards.

### Custom Capacitors:


- Special pinouts to address wide variety of specialty DIPs such as analog devices, op-amps, center pinout advanced CMOS devices.
- Applications: decoupling, EMI/RFI filtering, compensation.

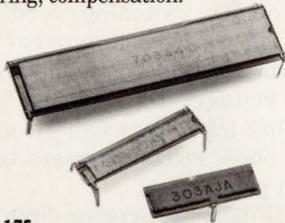

Circle 175

## Under the PGA caps - Micro/Q 3000

- Reduce PGA and PLCC noise.
- Several part sizes address a variety of package sizes.
- Designed for all 16/32-bit MPUs, DSPs, GSPs, FPPs, gate arrays, standard cells, and fully custom ASICs.

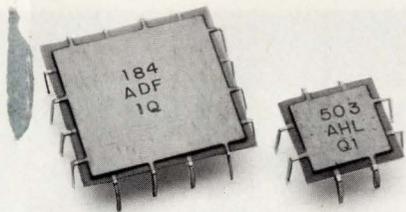

Circle 176

## Two layer PCBs power distribution and decoupling caps - Mini/Bus and Q/PAC

### Mini/Bus Bars

- Distributes power to ICs
- Eliminates up to half the decoupling caps
- Fits between or beneath the ICs

### Q/PAC Components

- Deliver efficient power distribution
- Provide built-in capacitance
- Eliminate decoupling capacitance
- 2-layer economy, 4-layer low noise levels

### High Current/High Capacitance Components

- High current power distribution up to 64 amps
- Provide voltage equalization
- High cap values available
- Board rigidizer
- Heat sinking function


Circle 178



Circle 173 for Immediate Need (U.S. Response)

Circle 174 for Immediate Need (Response Outside U.S.)
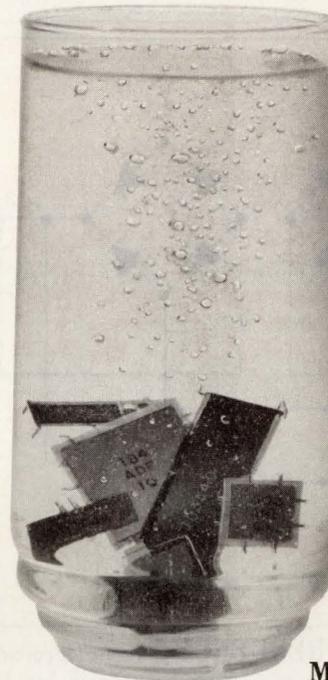
# For fast relief from noise and space problems turn to Micro/Q® Capacitors.



Micro/Q® capacitors, Q/PAC® components and Mini/Bus® bars take the headache out of a host of design problems quickly and easily.

**Micro/Q** decoupling capacitors reduce EMI/RFI and noise voltage spikes in ICs by as much as a factor of ten. They can mount under the IC or share mounting holes to improve noise suppression where it's most effective - at the source.

**Q/PAC** components give two-layer boards multilayer electrical performance, elimi-

nate discrete decoupling capacitors, and boost the reliability of the PCB assembly.

**Mini/Bus** bars provide high current distribution and high capacitance, eliminate up to half the decoupling capacitors, and fit between or beneath ICs to reduce required board layers.

Find out more about how we can solve your noise, EMI/RFI or space problem today. Call a Product Specialist at (602) 967-0624 (Fax 602-967-9385) and ask for more information.

*Technology for tomorrow built on TQC today.*

## Circuit Components

2400 S. Roosevelt Street, Tempe, AZ 85282

A Division of

 **ROGERS**


DISTRIBUTION: Europe, Japan, Taiwan, Singapore, Hong Kong, Korea, Brazil, Australia, India

Micro/Q, Q/PAC and Mini/Bus are registered trademarks of Rogers Corporation. Another Mektron® Interconnection product.

Circle 177


## Under the PLCC - SMT caps Micro/Q 3500

- Surface mount capacitors.
- Fit under 44, 52, 68, 84/larger pin count PLCCs.
- Low inductance, 0.5 - 0.6 nanoHenries.
- Pads absorb coefficient of thermal expansion mismatch between board and device during soldering.
- Supplied in tape and reel or in bulk.
- Available with Z5V or X7R dielectrics.

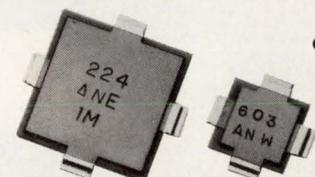

Circle 179
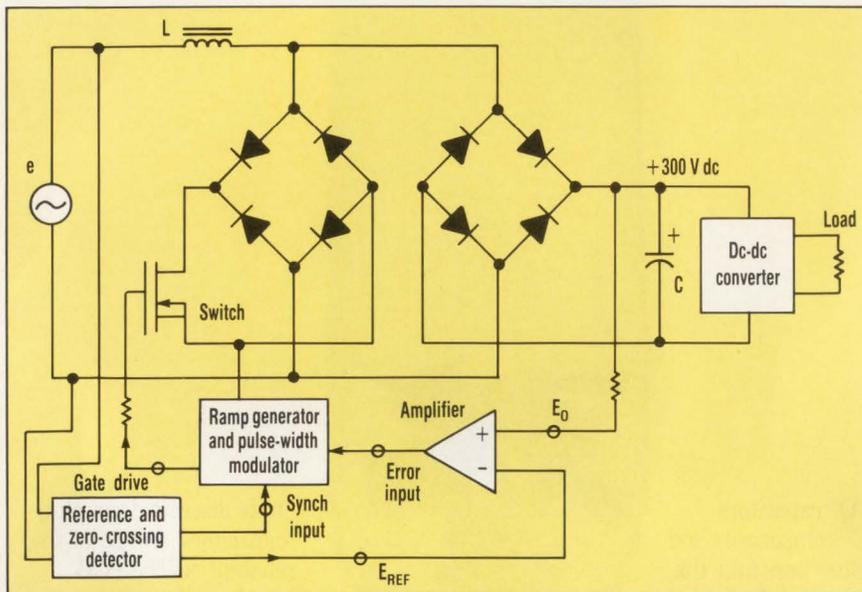
## POWER FACTOR AND SWITCHING POWER SUPPLIES



**7. THE ACTIVE LOW-FREQUENCY** power-factor-correction circuit uses a switched inductor to produce a pseudo-sinusoidal input current with low harmonic currents. A pulse-width modulator controls the operation of the MOSFET switch. Power factors between 0.96 and 0.98 are realized.

front-end, performs much better, and is significantly smaller and lighter. Active high-frequency (HF) correction circuits typically operate at switching frequencies of 20 kHz to 100 kHz, far higher than the line frequency, to permit a large reduction in the size and cost of filter elements. HF-circuit functions include switch control of input-current flow, filtering of the HF switching, feedback sensing of the source current for waveform control, and feedback control of voltage. Buck, boost, and buck-boost topologies can be used, but the boost circuit appears to be the most popular.

The HF-boost-converter circuit is shown in simplified form (Fig. 6). The rectified sinusoidal input voltage goes to a multiplier circuit, providing a current reference to the multiplier and a feed-forward signal proportional to the rms value of the line voltage. The boost converter's

## A relay line designed to be




## POWER FACTOR AND SWITCHING POWER SUPPLIES

filtered dc-output voltage is compared to a reference voltage  $E_{REF}$  and amplified.

The error signal is applied to the input of the multiplier. The multiplier's output follows the shape of the input voltage, with an average value inversely proportional to the rms value of the ac-input voltage. This signal is compared to the current-sense signal in the pulse-width-modulator drive circuit to shape the current waveform from the source and maintain a constant output of about 400 V dc.

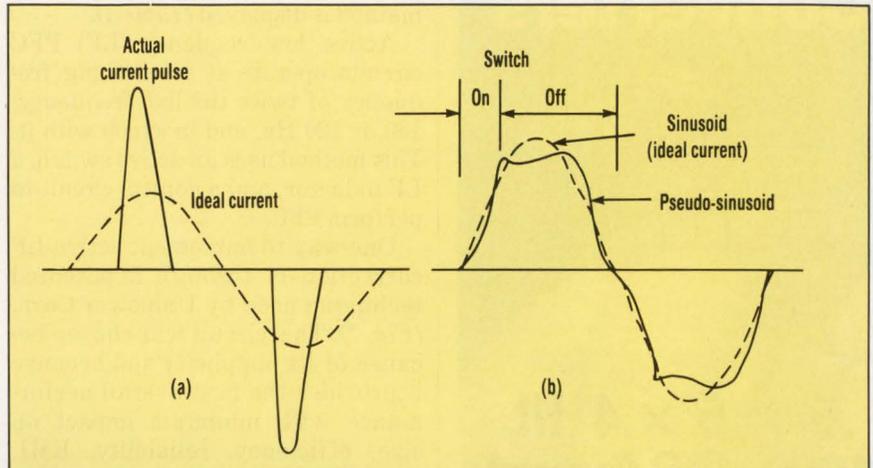This PFC circuit can be implemented using available ICs. The power supply, however, must process the total power twice—first through the HF-boost converter and then through the HF dc-dc converter. This serial power processing adds to complexity, reduces efficiency and mean time between failure (MTBF), and increases both size and cost. But the



**8. BOTH THE UNCORRECTED** input current to a switching power supply (a) and the pseudo-sinusoidal input current produced by active LF power-factor correction (b) are illustrated.

technique achieves a power factor of 0.97 to 0.99 with very low harmonic distortion, produces a regulated 400-V dc bus, and provides operation

over a wide input-voltage range of 90 to 264 V ac.

A summary of the advantages and disadvantages of the active-HF

# solid state of the art.

## That's AT&T "Customerizing."

AT&T now offers one of the industry's most complete portfolios of high-voltage, <1 amp solid-state relays (SSRs).

### State of the art in variety

Our new LH1500 line includes normally open (1 Form A). Normally closed (1 Form B). And combinations (1 Form A/B, C; 2 Form A; Dual Form A; Dual Form B). All offer logic-level Input Control, and come in 6 or 8 pin DIPs, through-hole or surface-mountable. That's what we mean by "Customerizing."

### State of the art in performance


Our LH1500 SSRs offer 3750V Input/Output isolation. Built-in current limiting. And on-resistances as low as 3 ohms (lower in DC

mode operation!). And our low (3 to 7 mW) input drive gives you the flexibility to meet your design needs.
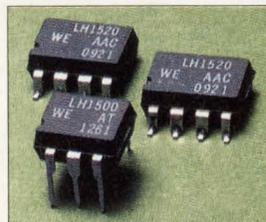
### State of the art in reliability

Current limiting protects against unwanted transients. Built-in break-before-make reduces component count. Advanced silicon technology adds ruggedness by reducing number of internal wire bonds. All designed by AT&T Bell Laboratories to meet U.L., C.S.A. and B.A.B.T. standards.

To sample an AT&T SSR or to place an order, call your AT&T local distributor. For more information, just call AT&T at 1 800 372-2447, ext. 628. In Canada: 1 800 553-2448, ext. 628.



CIRCLE 151 FOR U.S. RESPONSE  
CIRCLE 152 FOR RESPONSE OUTSIDE THE U.S.



**AT&T**  
Microelectronics

# High Voltage DC-DC Converters



ACTUAL  
SIZE

**.5" x .5" x .4" Ht.  
1000 VDC Output**

- **New Series AV—  
56 Standard Models**
- **100 VDC to 1000 VDC  
Output**
- **Ultra-miniature Size  
Weight: 4 Grams  
0.1 Cubic Inch Volume**
- **Standard Input Voltages  
5, 12, 24 and 28 Volts DC**
- **Operating Temperature  
Standard: -25°C to +70°C  
Optional: -55°C to +85°C**
- **MIL-STD-883  
Screening Available**
- **Isolated: Input to Output  
up to 1500 VDC**

PICO also manufactures over 800 regulated and isolated DC-DC Converters and AC-DC Power Supplies and over 2500 standard ultra-miniature Transformers and Inductors.

Delivery—  
stock to  
one week

SEE EEM,  
THOMAS REGISTER  
OR SEND DIRECT FOR  
FREE PICO CATALOG

**PICO  
Electronics, Inc.**

453 N. MacQuesten Pkwy. Mt. Vernon, N.Y. 10552

Call Toll Free **800-431-1064**

IN NEW YORK CALL **914-699-5514**

CIRCLE 130 FOR U.S. RESPONSE

CIRCLE 131 FOR RESPONSE OUTSIDE THE U.S.

## DESIGN APPLICATIONS

# POWER FACTOR AND SWITCHING POWER SUPPLIES

method is displayed (Table 4).

Active low-frequency (LF) PFC circuits operate at a switching frequency of twice the line frequency, 100 or 120 Hz, and in synch with it. This method uses an active switch, a LF inductor, and a control circuit to perform PFC.

One way to implement active-LF correction is through a patented technique used by Unipower Corp. (Fig. 7). This circuit was chosen because of its simplicity and because it provides the best overall performance with minimum impact on size, efficiency, reliability, EMI, and cost.

The MOSFET-switch circuit is driven into conduction at the zero crossing of the ac-source voltage, and current builds up in the inductor, L, from the ac source. At a controlled time after the zero crossing (typically 1 to 2 ms), the switch is turned off and the source current through L transfers to the output rectifier and filter circuit. The MOSFET switch is driven by a pulse-width-modulation (PWM) circuit that compares an error-feedback signal to a ramp signal that is synchronized by a zero-crossing signal.

The reference for the error amplifier is proportional to the rms value of the ac-line voltage, and the output voltage (about 300 V dc) is load-regulated by adjusting the conduction time of the MOSFET switch. The input-current waveform is enhanced by maintaining an optimum relationship between the magnitude of the ac-input voltage and the dc-output voltage.

The result is a pseudo-sinusoidal current waveform which gives a high power factor of 0.96 to 0.98 with low harmonic currents (Fig. 8).

Power factor at rated load is relatively constant over line voltage ranges of 90 to 132 V ac or 180 to 264 V ac. These input ranges can be made switch-selectable, or autoranging techniques can be used to provide automatic switching.

This method is highly efficient, with lower total losses than the HF method. Its low component count also results in high MTBF. A summa-

ry of the advantages and disadvantages of the active LF method is given (Table 5).

## OTHER CONSIDERATIONS

While PFC certainly solves a difficult problem at the input end of a switching power supply, the systems engineer must also consider a few other items: PFC moderately increases the size and weight of the power supply, increases its cost by some 10 to 20%, and results in a slightly lower total efficiency because of losses in the PFC circuit. There's also a slightly lower MTBF caused by additional circuit complexity and components.

Moreover, in the case of three-phase power systems, a simple implementation of active PFC that maintains the current balance between phases is difficult to achieve. These obstacles are minor ones, however, when considering that in most applications, PFC solves a major problem associated with the ac-power source.

PFC will be used in switching power supplies more frequently in the future as equipment users and manufacturers better understand its benefits. Most interest today appears in the 1000-to-2000-W power range, because that's where benefits in using standard ac-power outlets are greatest. With the IEC 555-2 standard on the verge of being implemented in Europe for 220- and 240-V ac circuits, PFC takes on increasing importance. Undoubtedly, U.S. and Canadian regulations on harmonic line currents will be put in place. There will also be future interest in PFC at lower power levels as the negative effects of multiple smaller power supplies on ac-power lines is felt. □

*Patrick L. Hunter, a founder of Unipower, is vice president and technical director. He holds BS and MS degrees in electrical engineering from Ohio State University, Columbus.*

### HOW VALUABLE?

HIGHLY  
MODERATELY  
SLIGHTLY

### CIRCLE

533  
534  
535

# Introducing the New Generation 574 A/D




## A New Classic

We designed our new 12-bit CMOS A/D converter with you in mind...by adding several innovative features to the standard ADC574 pinout. ADS574 and ADS774 drop into most applications without any system modifications, use minimal power, and operate from a single +5V supply. Complete with on-chip sample/hold, clock, reference,  $\mu$ P interface, three-state outputs, and internal scaling resistors, ADS574 and ADS774 set a new standard for your design.

## A New Standard in Savings

Replace your old standard with our new classic and save...design time, power, board space and money. Designed to operate from a single power supply while still supporting all of the


ADC574 input ranges, ADS574 and ADS774 use only one-fourth the power of that old standard. On-chip sampling combined with our new skinny-DIP package (0.3" wide) or SOIC gives you a lot more board space. And, our pricing sets a new standard—starting at \$14.15\*

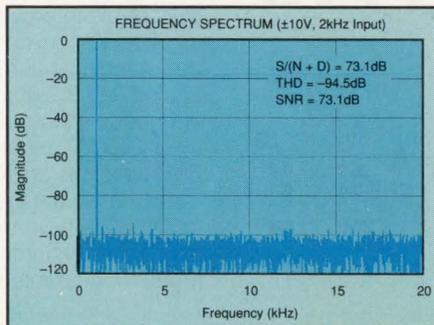

ADS574
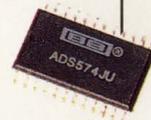
## Innovative Features

- Throughput time (acquire & convert)  
25 $\mu$ s max.....ADS574  
8.5 $\mu$ s max.....ADS774
- Power consumption  
100mW max....ADS574  
120mW max....ADS774
- Single +5V supply
- Guaranteed AC, DC performance
- Industry standard input ranges
- Industry standard digital interface
- Compact 0.3" or 0.6" wide 28-pin plastic or ceramic DIP, 28-pin SOIC, die
- From \$14.15\*




## Try it

We're so convinced that our new parts are the next industry standard—we'll give you the first one free! Just call **1-800-548-6132** for samples and detailed data sheets or contact your local Burr-Brown sales office for assistance.

**Burr-Brown Corp.**  
P.O. Box 11400  
Tucson, AZ 85734

\* U.S. OEM prices, in 100s.

**BURR-BROWN®**  
**BB**

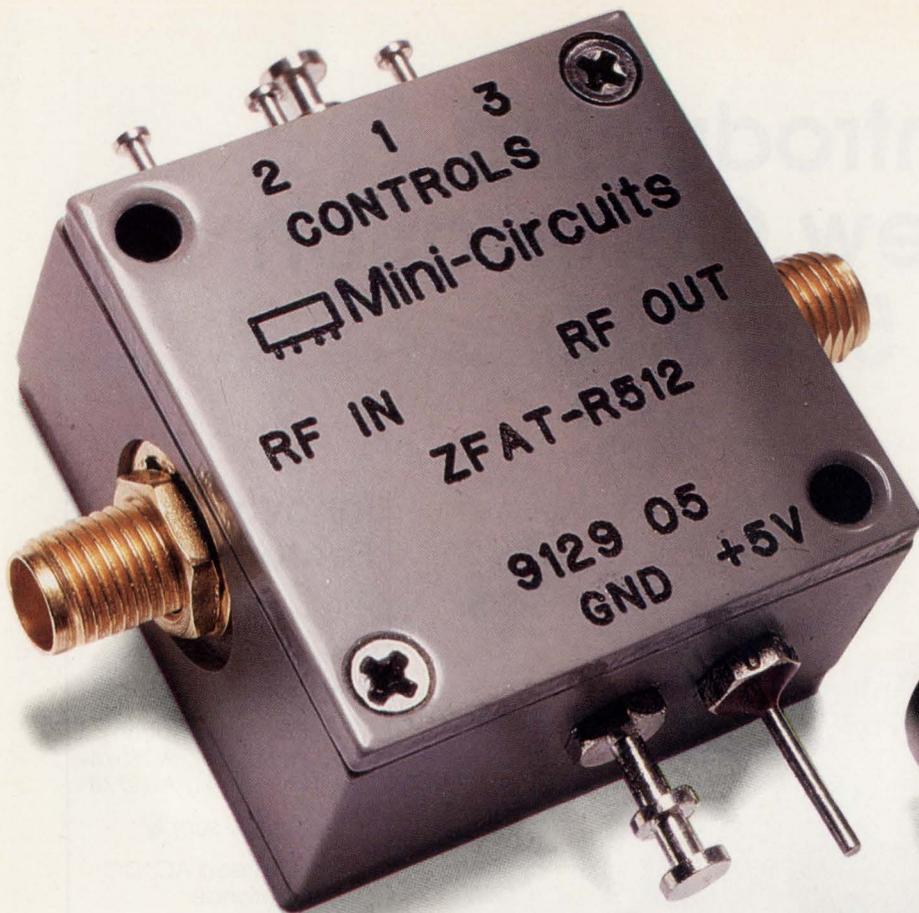

# PRECISION TTL- CONTROLLED ATTENUATORS

up to 35dB  
10 to 1000MHz  
FROM **\$59.95**

TOAT-R512 ZFAT-R512 Accuracy (dB) (+/-dB)	TOAT-124 ZFAT-124 Accuracy (dB) (+/-dB)	TOAT-3610 ZFAT-3610 Accuracy (dB) (+/-dB)	TOAT-51020 ZFAT-51020 Accuracy (dB) (+/-dB)
<b>0.5</b>	<b>0.12</b>	<b>1.0</b>	<b>0.2</b>
<b>1.0</b>	<b>0.2</b>	<b>2.0</b>	<b>0.2</b>
1.5	0.32	3.0	0.4
<b>2.0</b>	<b>0.2</b>	<b>4.0</b>	<b>0.3</b>
2.5	0.32	5.0	0.5
3.0	0.4	6.0	0.5
3.5	0.52	7.0	0.7
		<b>3.0</b>	<b>0.3</b>
		<b>6.0</b>	<b>0.3</b>
		9.0	0.6
		13.0	0.6
		16.0	0.6
		19.0	0.9
		<b>5.0</b>	<b>0.3</b>
		<b>10.0</b>	<b>0.3</b>
		15.0	0.6
		20.0	0.4
		25.0	0.7
		30.0	0.7
		35.0	1.0

Price \$ (1-9 qty) TOAT \$59.95/ZFAT \$89.95  
bold faced values are individual elements in the units

Finally...precision attenuation accurate over 10 to 1000MHz and -55°C to +100°C. Standard and custom models are available in the TOAT(pin)- and ZFAT(SMA)-series, each with 3 discrete attenuators switchable to provide 7 discrete and accurate attenuation levels.

The 50-ohm components perform with 6μsec switching speed and can handle power levels typically to +10dBm. Rugged hermetically-sealed TO-8 units and SMA connector versions can withstand the strenuous shock, vibration, and temperature stresses of MIL requirements. TOAT pin models are priced at only \$59.95 (1-9 qty); ZFAT SMA versions are \$89.95 (1-9 qty).

Take advantage of this striking price/performance breakthrough to stimulate new applications as you implement present designs and plan future systems. All units are available for immediate delivery, with a one-yr. guarantee, and three-sigma unit-to-unit repeatability.

finding new ways ...  
setting higher standards

 **Mini-Circuits**

WE ACCEPT AMERICAN EXPRESS AND VISA

P.O. Box 350166, Brooklyn, New York 11235-0003 (718) 934-4500 Fax (718) 332-4661 Telexes: 6852844 or 620156

CIRCLE 188 FOR U.S. RESPONSE

CIRCLE 189 FOR RESPONSE OUTSIDE THE U.S.

F 140 REV. A

**CIRCLE**  
**521**  
**CABLE TESTER**  
**IS EXPANDABLE**

NOOR SINGH KHALSA  
 EG&G Inc., P.O. Box 809,  
 Los Alamos, NM 87544; (505) 667-0213.


Cables can have almost any number of conductors. It is handy, therefore, to have a cable tester that can be readily expanded as necessary. Because of the 32-bit shift register at its heart, the basic tester can handle up to 32 conductors (see the figure). However, the Data-out line of the UCN 5833A shift register allows additional UCN 5833As to be cascaded, so the tester can be expanded in 32-conductor increments.

The tester operates by propagating a single pulse through the shift register, turning on the LEDs in a LED array one at a time. One end of the cable under test is connected to the shift register outputs and their associated LEDs. The other end of the cable is connected to a second LED array. The LEDs at the shift register end of the cable light up to indicate which conductor is being energized. The LEDs at the other end turn on when there is continuity.

The pulse can be propagated through the shift register manually or automatically. In the manual mode, a 555 timer IC is set up as a monostable multivibrator, which clocks the shift register once for every push of the Single-step button.

When the Mode switch is set to Auto, the 555 operates as an astable multivibrator. It clocks pulses through the register at a rate deter-

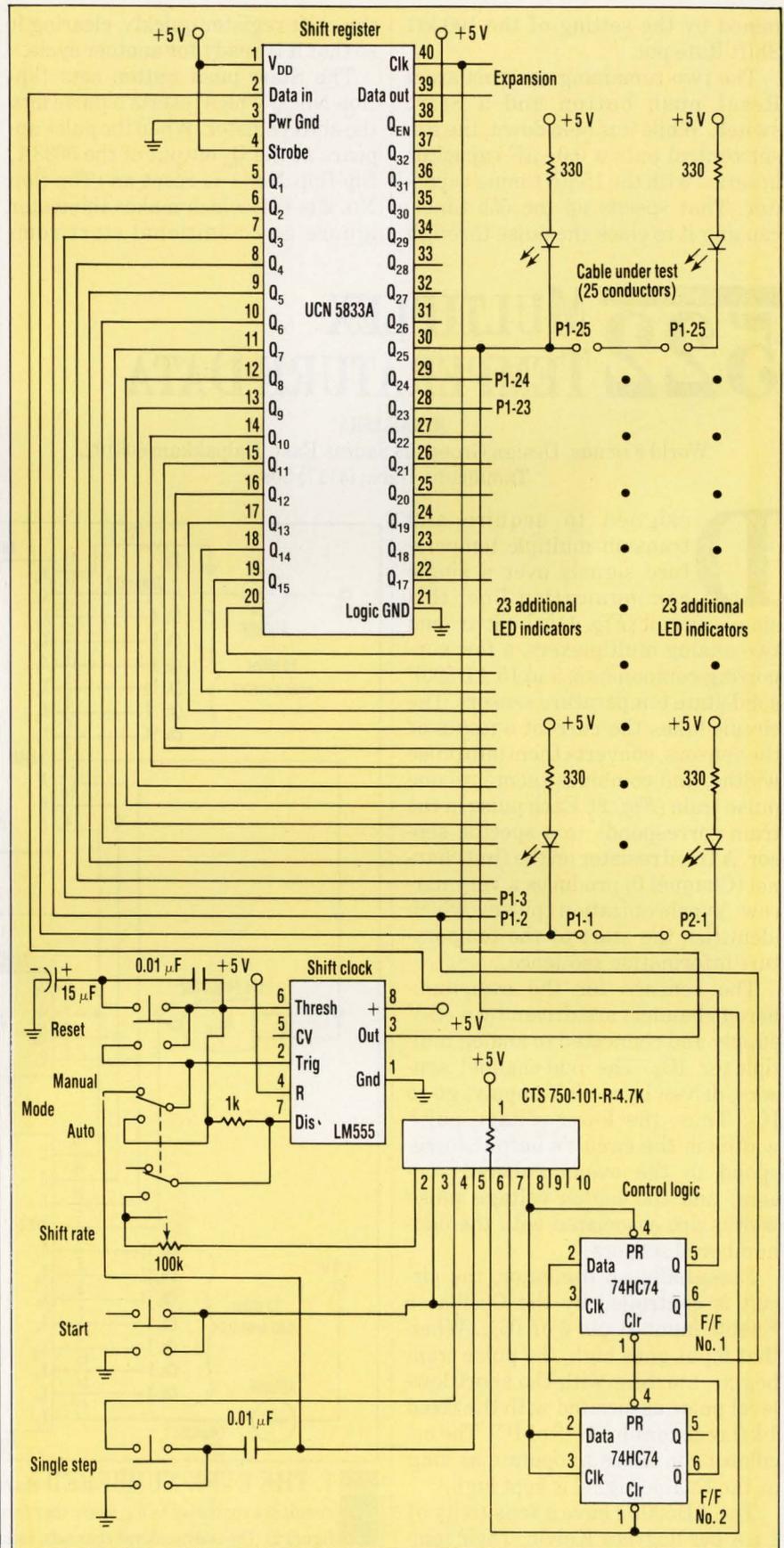**THE SHIFT REGISTER** at the heart of this cable tester has open-collector outputs that can drive LEDs. The 32-bit unit also has a Data-out line through which additional registers can be cascaded, so the tester can be expanded to handle very large cables.



mined by the setting of the 100-k $\Omega$  Shift Rate pot.

The two remaining controls are a Reset push button and a Start switch. While it is held down, the Reset control puts a 0.01- $\mu$ F capacitor in series with the 15- $\mu$ F timing capacitor. That speeds up the 555 timer, causing it to clock the pulse through

the shift register quickly, clearing it so that it is ready for another cycle.

The Start push button sets flip-flop No. 1, which inserts a pulse into the shift register. When the pulse appears at the Q<sub>2</sub> output of the 5833A, flip-flop No. 1 is reset and flip-flop No. 2 is set, which makes the tester ignore any additional start com-

mands until the test cycle is over—when the first pulse has propagated to the last shift register output.

Although the LEDs in the figure are shown as individual units, the tester built by the author actually used 10-element LED bar graphs (Hewlett-Packard HDSP4820s) for convenience.  $\square$

## CIRCLE 522 MULTIPLEX TEMPERATURE DATA

M. RAILESHA

World Friends, Design Group, 53 Sadras East, Kalpakkam 603102,  
Tamilnadu, India; (4117)-508.


**D**esigned to acquire and transmit multiple temperature signals over a single communication line, this simple circuit (Fig. 1) is built around two analog multiplexers, a few supporting components, and 15 AD590F solid-state temperature sensors. The circuit takes the current outputs of the sensors, converts them into pulse widths, and combines them into one pulse train (Fig. 2). Each pulse in the train corresponds to a specific sensor. A fixed resistor on the first channel (Channel 0) produces a very narrow synchronization pulse, which identifies the start of the temperature information sequence.

The sensors for the even-numbered channels are driven by a -5-V supply and connected to analog multiplexer IC<sub>2</sub>. The odd-channel sensors, driven by a +9-V supply, go to IC<sub>3</sub>. Thus, the lower-voltage pulse widths in the circuit's output correspond to the even-numbered sensors, and the higher-voltage pulse widths are associated with the odd-numbered sensors.


Essentially an oscillator, the circuit is controlled by the Oscillator Enable input at pin 2 of IC<sub>1A</sub>. When that input goes high, the pulse train begins, starting with the short low-level pulse associated with the fixed 1-k $\Omega$  resistor on pin 13 of IC<sub>2</sub>. The oscillator continues to operate as long as the Enable signal is kept high.

The AD590Fs have a sensitivity of 1  $\mu$ A per degrees Kelvin. Their tem-

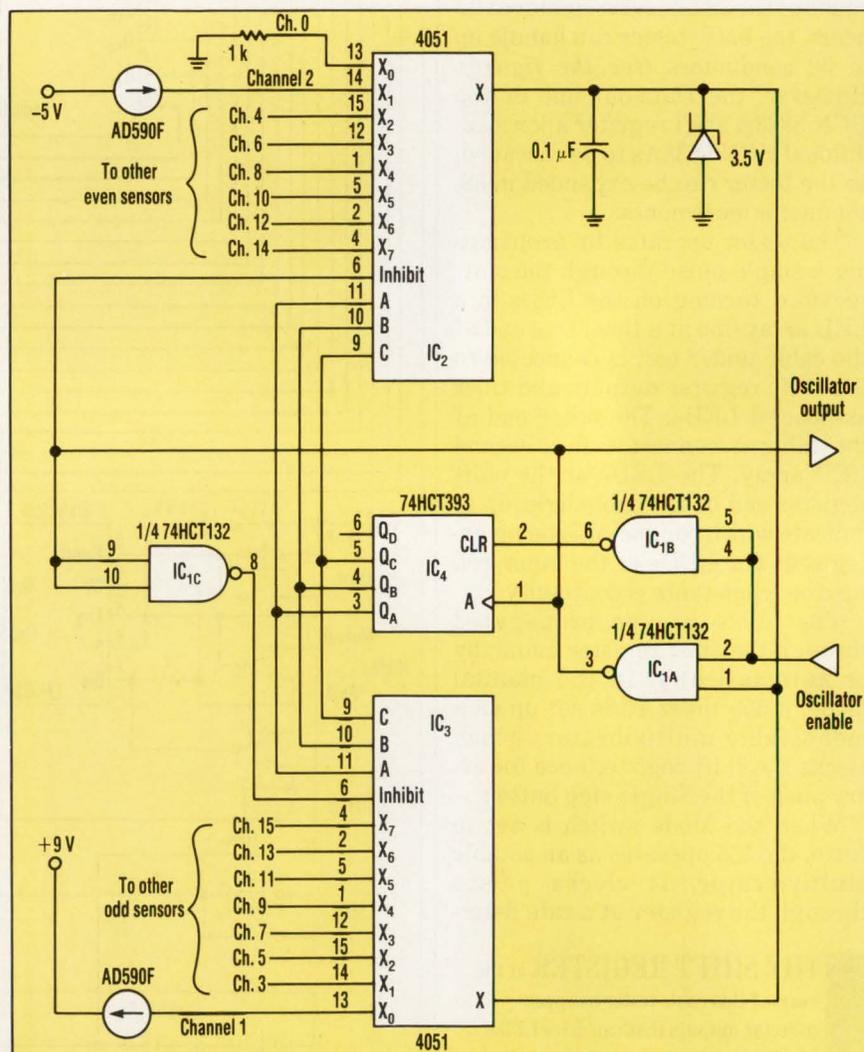
perature-dependent current outputs are converted into voltage signals by the charge-collecting 0.1- $\mu$ F capacitor at the (joined) outputs of the multiplexers. Over the course of each oscillator period, one of the odd-numbered sensing elements dumps charge onto the capacitor, and one of



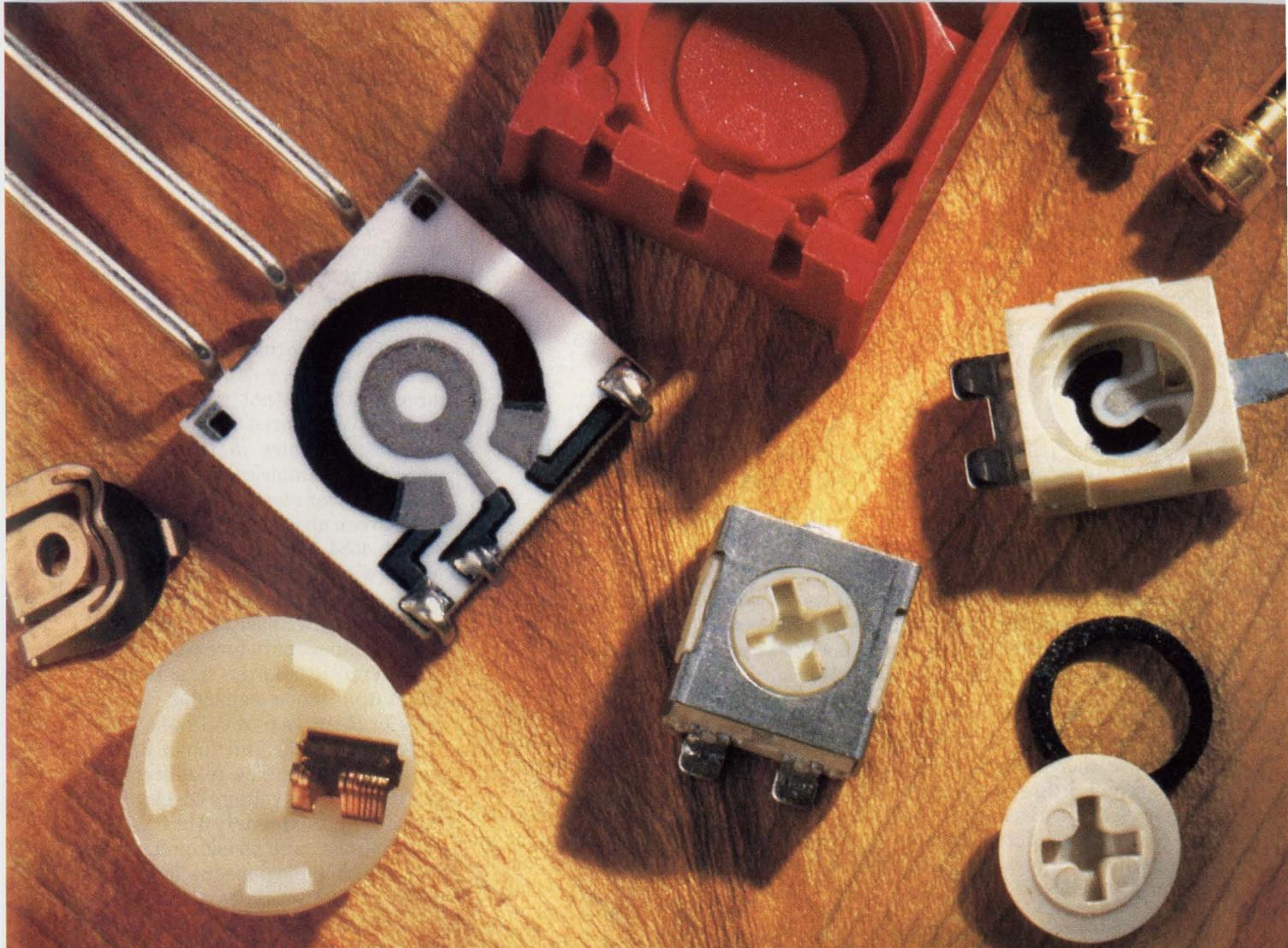**1. THE EVEN-NUMBERED** channels in this multiplexed temperature-sensing circuit are connected to IC<sub>2</sub>, where they form the lower half of the output pulse train (see figure 2). The odd-numbered channels, connected to IC<sub>3</sub>, make up the other half.



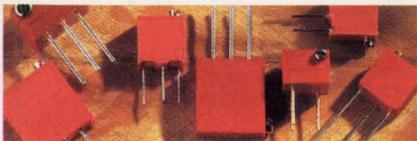Wipers, collectors and screws  
can't help you trim  
circuit adjustment costs.




**MILITARY TRIMMERS** from the Techno Division include broad MIL qualification to RT24, 26, 27; RTR24; RJ24, 26 and RJR24, 26. Techno RJ24 and RJR24 trimmers offer you 25 turns for precision adjusting, while the RJ26 and RJR26 offer 22 turns. They have zero backlash and offer a monolithic clutch.

In addition, Techno offers  $\frac{1}{4}$ " and  $\frac{3}{8}$ " multiturn trimmers with a TCR of  $\pm 50$  PPM/ $^{\circ}$ C for precision applications. All Established Reliability trimmers meet the requirements of MIL-STD-202, Method 208.

Contact: **Techno Division**, Dale Electronics, Inc., 7803 Lermona Avenue, Van Nuys, California 91405-1139 Phone (818) 781-1642.

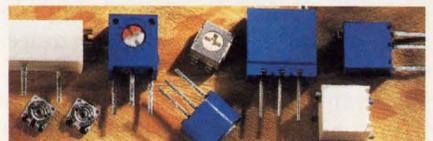
## Dale® Can.

Add trimmers to the list of ways Dale® can help keep your project under budget and on-time. We offer immediate interchangeability with models you're using now. Cermet, wirewound. Military, industrial, commercial. Square, round, rectangular. Surface mount and through-hole. Discover how Dale trimmers can end your search for multiple suppliers. More than ever we're your 1-stop source for resistive components — always ready to match your delivery schedule from factory or distributor stock. Call today.




**COMMERCIAL TRIMMERS** include Surface mount: Thick film chips (.2W) plus .197" (.2W) and 1/4" (.25W) square cermet styles. Through-hole cermet styles include: .276" (.5W) round, 1/4" (.25W), 9/32" (.5W), and 3/8" (.5W) square cermet. Rectangular: 3/4" (.75W) wirewound.

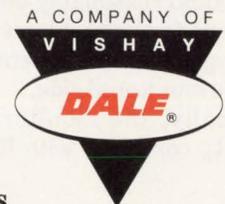For more information contact: **Dale Electronics, Inc.**, 1155 West 23rd Street, Tempe, Arizona 85282-1883. Phone (602) 967-7874.



CIRCLE 96 FOR U.S. RESPONSE

CIRCLE 97 FOR RESPONSE OUTSIDE THE U.S.

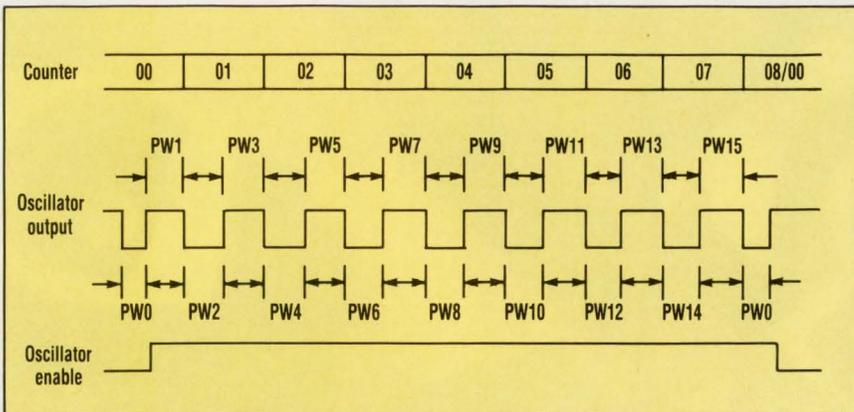

**2. THE OUTPUT PULSE TRAIN** consists of 16 consecutive pulse widths, 15 being proportional to the temperature of an individual sensor. The exception is the first pulse, designated PW0, which is distinguished by its narrowness. It serves as the synchronizing pulse to indicate the start of the train.

the even-numbered elements removes charge from it. The width of each pulse, therefore, is proportional to the temperature of its associated sensor element. Because the oscillator frequency is determined by the input threshold voltages of the

74HCT132 quad NAND gate (IC<sub>1</sub>), it's essential that the power supply voltage for those components be well regulated.

The Zener diode provides overvoltage protection by clamping input pin 1 on IC<sub>1A</sub> to 3.5 V. □

an ac voltage divider isolated by the transformer. It loads down the signal at the junction of R<sub>2</sub> and the transformer despite the lack of a common ground. The lower the value of R<sub>4</sub>, the lower that voltage. Therefore, the output voltage, V<sub>O</sub>, varies directly, though not quite linearly, with the monitored resistance (the component values in the diagram were chosen empirically to provide a roughly linear response for values of R<sub>4</sub> between about 400 Ω and 2 kΩ.)

The 4584 CMOS inverter, IC<sub>1A</sub>, works with R<sub>1</sub> and C<sub>1</sub> to provide the ac drive signal, which is then buffered by IC<sub>1B</sub>. Capacitor C<sub>2</sub> removes the dc component before passing the drive on to R<sub>2</sub> and the transformer. The output diode, capacitor C<sub>3</sub>, and resistor R<sub>3</sub> serve to rectify and filter the voltage at the junction of R<sub>2</sub> and the transformer. The resulting output, V<sub>O</sub>, is a dc voltage level in the range of approximately 0 to 1 V.

Variations on the basic circuit provide an economical means for transmitting different types of non-precision signals across isolation barriers. The tiny pulse transformer used in the circuit is sufficient to transfer a few dozen milliwatts of power across the barrier—enough to drive such components as a small light-emitting-diode display, an audible indicator, or a meter. □

## CIRCLE 523 MONITOR ACROSS ISOLATION BARRIERS


JAMES HENDEN

Continuum, Inc., 3150 Central Expy., Santa Clara, CA 95051; tel.: (408) 727-3240; fax: (408) 727-3550.

**T**his simple yet effective circuit is designed to monitor switch closures or changes in a variable resistance across a galvanic isolation barrier (see the figure). It exhibits a high degree of noise immunity and requires very little power.

Even more significantly, at least for some applications, it has no components on the monitored side of the isolation barrier except, of course, for the switch or pot. Therefore, if the signal under observation comes from a difficult environment—a high temperature, for example—the circuit could reasonably be expected to present fewer problems than one requiring active components or power on the monitored side.

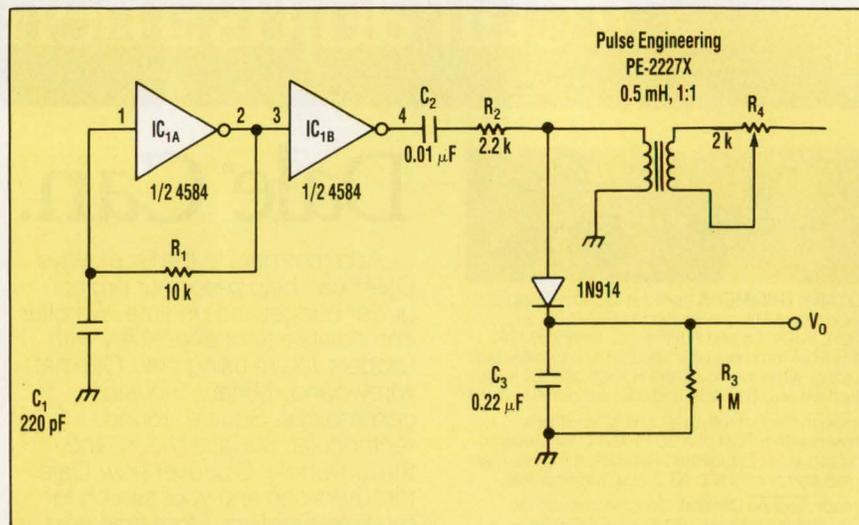Basically, the monitored resistance, R<sub>4</sub>, combines with R<sub>2</sub> to form



**NO ACTIVE COMPONENTS** are required on the far side of the isolation barrier with this monitor circuit. The monitored resistance, R<sub>4</sub>, loads down the voltage at the output end of R<sub>2</sub> despite the interposed transformer.

# OUR SALES ARE UP!

There Must Be Reasons.

## REASON NO. 1:

The *largest* line of enclosures in the industry . . . meeting *any* need.

## REASON NO. 2:

Local inventory and support means *fast* service and delivery from our nationwide network of the *finest* distributors.



## REASON NO. 3:

Our Distributor Network is second to none.

## REASON NO. 4:

Bud VALUE eliminates waste. Don't downgrade your product with cheap substitutes.

## REASON NO. 5:

When you go with the *best*, you are the *best*.

These are only a few of the *hundreds* of reasons to buy Bud. Call, FAX or write today for a complete catalog and the names of your local Bud Distributors.

**Bud East, Inc.**  
4605 East 355th Street  
P.O. Box 431  
Willoughby, Ohio 44094  
(216) 946-3200  
FAX: 216-951-4015


**BUD**  
Bud Industries, Inc.

**Bud West, Inc.**  
7733 West Olive Avenue  
P.O. Box 1029  
Peoria, Arizona 85345-0350  
(602) 979-0300  
FAX: 602-878-5371

CIRCLE 92 FOR U.S. RESPONSE

CIRCLE 93 FOR RESPONSE OUTSIDE THE U.S.
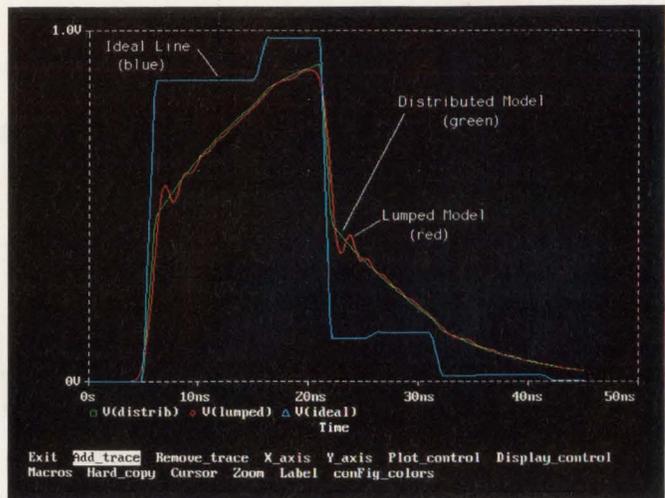
# Our Lossy Transmission Lines Have the Edge!



Comparison of the ideal and lossy transmission line models

## Faster Simulation and Greater Accuracy

That's our lossy transmission line edge. We've extended PSpice's intrinsic T device to model lossy transmission lines using the distributed approach rather than the traditional lumped approach. What you get is a smoother approximation of the line's behavior in significantly less time. Here's why.

## The Distributed Model Advantage

Our lossy line behavior is computed using impulse responses instead of the commonly used ladder structures associated with lumped models. Using this technique, lossy lines can be easily specified in terms of their electrical length and the resistance, inductance, capacitance, and conductance distributed along the entire length of the line.

## Elimination of Spurious Oscillations

Modeling lossy lines as continuous lines eliminates the frequency artifacts observed in lines modeled as a finite set of lumped segments. With the lumped model, oscillations are produced at points where abrupt changes occur in the signal

traveling along the line segments. Using the distributed model, these oscillations vanish.

## Optimized Simulation Performance

For any given circuit, simulation time using the distributed model can be several times faster than the simulation time using the lumped model. With the lumped model approach, the number of segments required for accurate results can become large. Hence, the simulation time can become very long. The continuous lines produced by the distributed model avoid the performance overhead created by multiple line segments.

## Get the PSpice Lossy Line Edge

That way, you can efficiently model the loss and dispersion in your non-ideal lossy transmission lines. Discover for yourself why PSpice continues to hold the industry edge in mixed analog and digital circuit simulation. For more information on PSpice and the **Design Center**, call MicroSim Corporation toll free at (800) 245-3022 or FAX at (714) 455-0554.



**MicroSim Corporation**

*The Standard for Circuit Design*

20 Fairbanks • Irvine, CA 92718

**THE MAKERS OF PSpice**

PSpice is a registered trademark of MicroSim Corporation

CIRCLE 112 FOR U.S. RESPONSE

CIRCLE 113 FOR RESPONSE OUTSIDE THE U.S.


# QUICKLOOK

EDITED BY SHERRIE VAN TYLE
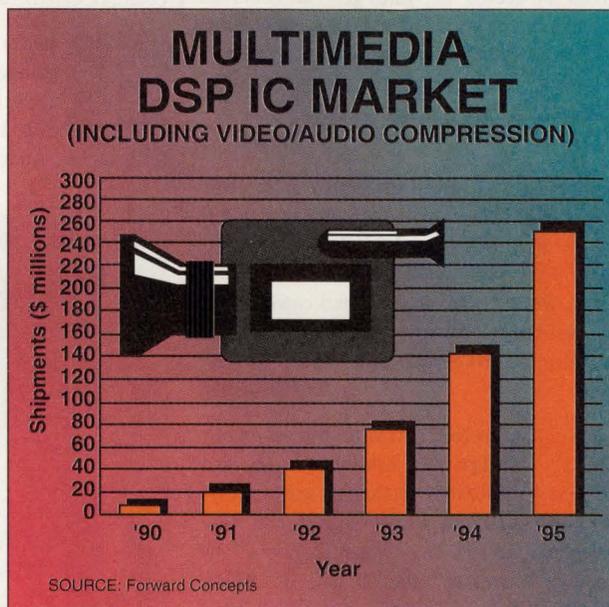
## MARKET FACTS

**M**ultimedia is creating excitement in the IC and systems markets. In its broadest sense, multimedia means imparting data through a combination of display imaging and sound from a single, integrated source. Training, education, teleconferencing, and public information kiosks are but a handful of areas where multimedia is expected to flourish. Besides microprocessors, some multimedia boards/systems contain digital signal processors. By 1995, DSP-based image compression chips will be found in most PCs and workstations, either as part of multimedia circuits or for compact image storage and transmission. Computer systems customized for audio-visual activity will have DSP circuitry for programmed or interactive image and sound manipulation.

The compound annual growth rate for multimedia DSP chips—mostly ASICs—including video/audio compression, will amount to 99% between 1990 and 1995, according to Will Strauss, of Forward Concepts, a Tempe, Ariz., market researcher. That means \$40 million worth of IC shipments this year will skyrocket to nearly \$260 million in 1995. Strauss tempers his prediction by saying that the fast-moving multimedia area outdates projections quickly.



## TALES FROM THE SKUNK WORKS

**W**ithout a leader, there can be no skunkworks. In every case I know of, personal leadership was absolutely critical to success. For instance, the name Kelly Johnson and Lockheed's skunk works are inseparable. The Manhattan project was an extraordinarily effective skunk works. History has judged dozens of scientists on the team as geniuses. At the top, following every detail to a degree his colleagues found mind-boggling, was a leader: Robert Oppenheimer. NASA put a man on the moon in nine years, thanks to a small core team—Wernher von Braun, George Muller, and George Lowe. Yet can you associate any names with NASA's recent debacles? Name for me, if you can, the central individual responsible for the Hubble telescope?

The conventional wisdom is that leaders are much too scarce to "waste" on isolated and risky endeavors such as a skunk works. Yet skunk works and closed loop teams don't consume leaders, they produce them. We have myriads of managers but few leaders. As both Peter Drucker and Warren Bennis say, "Management is doing things right; leadership is doing the right things." Many large companies are hacking through the jungles their founders discovered, measuring progress, and toiling onward. Some foreign leaders moved their companies from tractors to electronics, from ball bearings to semiconductors, and from cigarettes to software. Managing well doesn't help much if you are in the wrong jungle.



Unfortunately, our concept of leadership has become superficial. Stephen R. Covey reports that, until recently, U.S. literature on leadership focused on the "character ethic." A person's character was deemed fundamental to leadership ability. With the proper foundation, things like integrity, humility, fidelity, temperance, courage, justice, industry, perseverance, modesty, and the Golden Rule, one might, after years of work, develop leadership ability.

Today America has embraced the "personality ethic," and our leadership literature reflects this (e.g. Donald Trump's book). The basic thrust now is quick-fix influence techniques, charisma, power strategies, communication skills, and positive attitudes. These methods will not work for a skunk works, and many say that the major problem with our industry and political system is that we can no longer trust our leaders.

Running a skunk works is a *stewardship*, another almost forgotten concept. A stewardship is a job with a trust. The steward becomes his or her own boss, governed by a conscience containing a commitment to agreed-upon desired results. Think how much better our lot might be with seasoned, trustworthy, results-oriented leaders running our industry and our nation.

John D. Trudel: *The Trudel Group*, 52001 Columbia River Hwy., Scappoose, OR 97056; (503) 690-3300, fax (503) 543-6361.

## OFFERS YOU CAN'T REFUSE

**A**n on-line job-listing service covers 39 job categories, including engineering, with most positions in the \$30,000 to \$60,000 salary range. EMPLEX II can be searched on professional category or salary range. Jobs are added weekly, and the database is regularly maintained. Step-by-step instructions are given to access the listings. The service's phone number is (412) 824-4343. Contact United States Information Network Corp., Suite 900, 400 Penn Center Blvd., Pittsburgh PA 15235; (412) 824-2400; fax (412) 824-8112.

CIRCLE 451

**A** free demo of McCAD electronic design tools for the Mac is available from VAMP Inc. The software comes with either stand-alone, work-group, or front-end capabilities. Contact the company at 6753 Selma Ave., Los Angeles, CA 90028; (213) 466-5533; fax 466-8564.

CIRCLE 452

**F**utureNet software for schematic design has continuous zoom and undo/redo commands and supports EDIF. It works in DOS and Sun-based networked environments. For a free demo disk, contact Data I/O, P. O. Box 97046, Redmond, WA 98073-9746.

CIRCLE 453

**S**trawberry Tree's Work Bench data-acquisition and control software needs no programming or user training. Obtain a free demo of the software by contacting Strawberry Tree, 160 South Wolfe Rd., Sunnyvale, CA 94086; (408) 736-1041; fax 736-1041.

CIRCLE 454

**A**ctel Corp. is offering its Action Logic System free in its university program for designing and programming the company's ACT 1 family of devices. Included in the package are ACT 1 macro libraries, place-and-route software, and a timing analyzer. The package is available on a 386 PC with Viewlogic and OrCAD libraries; the Apollo workstation using Mentor Graphics libraries; and Sun workstations with either Valid or Viewlogic libraries. The company is also supplying at no cost ten of its A1010A-PL68C 1200-gate devices with each system shipment. Actel will also supply additional devices to any university using Actel within a VLSI design course. Further information is available by contacting the company at 955 East Arque Ave., Sunnyvale, CA 94086; (408) 739-1010; fax 739-1540.

CIRCLE 455

## QUICK NEWS: EDUCATION

**I**nterest in techniques for digital signal processing is growing as programmable VLSI devices and low-cost array processors have proliferated. A course from Learning Group International instructs designers in applying DSP techniques, using fast Fourier transform (FFT) algorithms, designing filters for real-time applications, and implementing filters in hardware and software. Participants receive Fortran source listings as part of the course material. With these programs, users can specify design parameters and produce complete, computer-designed digital filters. Courses will be held in various U. S. cities from February through July. For pricing and other information, contact Learning Group International, 1805 Library St., Reston, VA 22090-9919; (800) 421-8166, (703) 709-9019, East Coast, fax (703) 709-6405; (310) 417-8888, West Coast, fax (310) 410-1320.

CIRCLE 456

**A** conference and exposition on CASE (computer-aided software engineering) has management/technical seminars on such topics as object-oriented analysis and design and comparison of CASE tools. CASE World will be held in Santa Clara, Calif. Feb. 18-20. Further information is available from Digital Consulting Inc., 204 Andover St., Andover, MA 01810; phone (508) 470-3880; fax 470-0526.

CIRCLE 457

## K M E T S K O R N E R

### ...Perspectives on Time-to-Market



**BY RON KMETOVICZ**

President, Time to Market Associates Inc.  
Cupertino, Calif.; (408) 446-4458; fax (408) 253-6085

**L**et's focus on the interactive properties of measuring TTM and BEAR (break-even after release). Measurement of TTM provides an overall indication of how well an organization can:

- Select product development alternatives from a large supply of potential opportunities.
- Effectively define products so that they can be cross-functionally and concurrently developed with minimal complication and delay.
- Swiftly plan the execution phase of the product-development effort so that full staff can be applied to get the job done in time to meet market requirements.
- Break out of the cerebral definition phase and actually do cross-functional, concurrent product development.
- For all its positive attributes, TTM and its measurement provide little information about how well a product will perform in the marketplace. Because of this limitation, it is necessary to add another dimension—measurement of break-even after release (BEAR).


Measuring BEAR makes visible how well a product development organization can:

- Create a product that is performance and cost competitive.
- Market the product to generate customer demand.
- Manufacture the product to respond to market demand.
- Convince a customer to spend money on the product.
- Distribute the product to satisfy customer expectations.

Should TTM be increased (more development time and money) to trim BEAR (more performance and less cost)? World-class product developers determine the answer in the definition phase as they control remaining TTM and BEAR. Balancing TTM and BEAR within the definition phase means that this issue is confronted and resolved about half way through the TTM interval. This is when to make trade-off decisions between product cost, product performance, development cost, and development time. The goal is not to statically balance TTM and BEAR—it's impossible. The elements need to be properly distributed so that the scale can be kept in balance. Doing the initial effort right makes the execution phase and the revenue phase snap into place.

*Ron Kmetovicz will lead a Time-to-Market seminar entitled "Speeding New Ideas to the Marketplace" at Santa Clara University on March 19. Contact Elmer Luthman, center director, at (408) 554-4521; fax (408) 554-4571.*
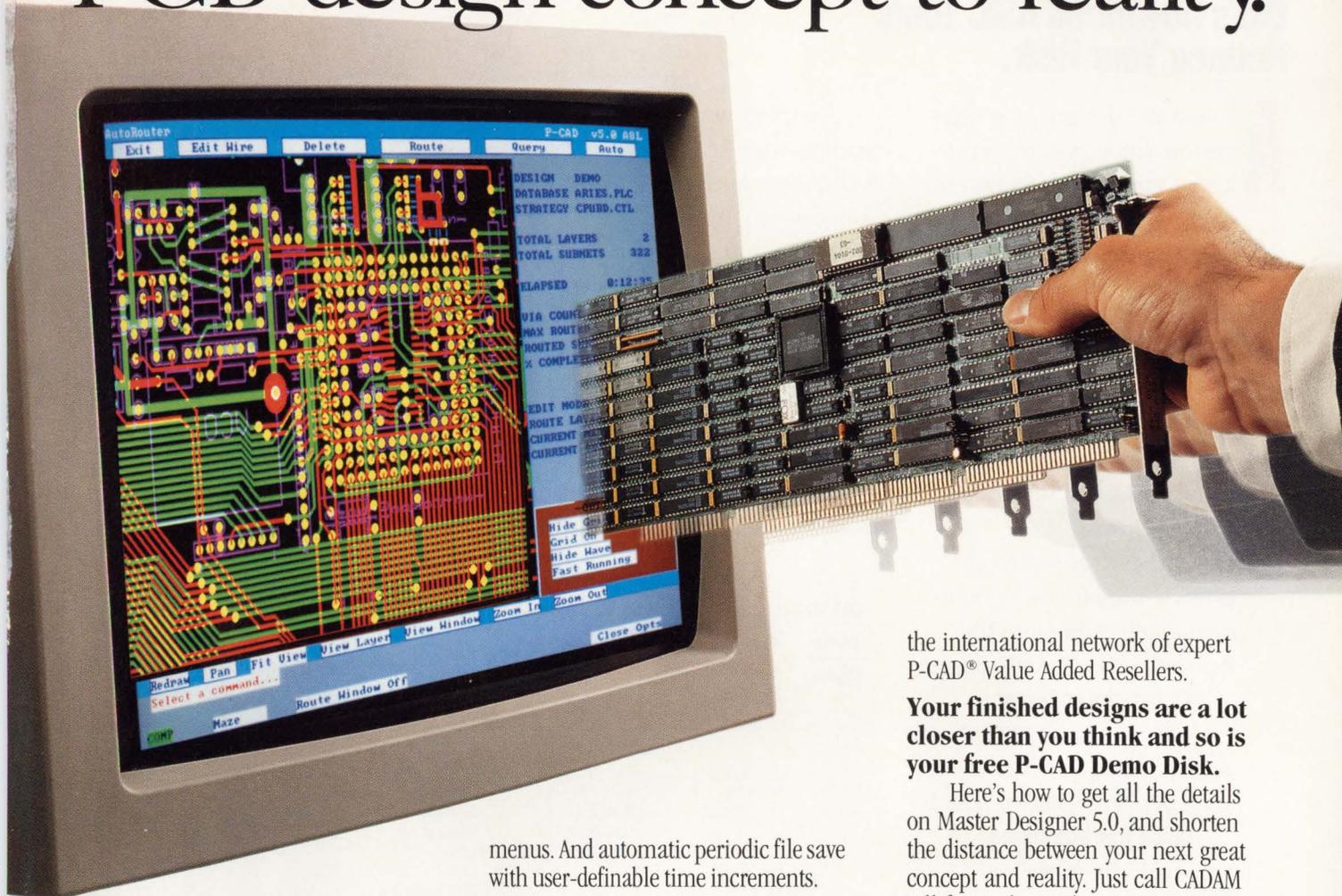
# P-CAD Master Designer, the shortest distance from PCB design concept to reality.



Master Designer™ 5.0 is the shortest distance from PCB design concept to reality. And the fastest, most productive and reliable way to get your designs to market using an IBM® or compatible PC.

And now Master Designer 5.0 has been enhanced with more than 100 new features, requested by PCB master design engineers like you.

### **New features, more productivity.**

Master Designer 5.0 shortens the entire design cycle with new features like extended memory for 4-times larger designs. Automatic real-time on-line design rule checking. User configurable

menus. And automatic periodic file save with user-definable time increments.

### **First with 20,000 PCB designers.**

You can rely on Master Designer 5.0 for the quality and dependability that has made it the choice of more than 20,000 PCB designers worldwide.

Master Designer 5.0 gives you the interactive support of Master Layout™ to handle surface mount, analog, and digital technology. The flexibility of Master Schematic™, fully automated optional Rip-n-Route, and our optional Master Placer™. Not to mention the plus of a consistent menu-driven interface.

With Master Designer 5.0, you're backed by CADAM, the world's leading CAD/CAM/CAE software supplier, and

the international network of expert P-CAD® Value Added Resellers.

**Your finished designs are a lot closer than you think and so is your free P-CAD Demo Disk.**

Here's how to get all the details on Master Designer 5.0, and shorten the distance between your next great concept and reality. Just call CADAM toll-free today and we'll send your free Master Designer 5.0 Demo Disk absolutely free.



**1-800-255-5710**



**CADAM**  
AN IBM COMPANY

*World Class PCB CAD Productivity*

IBM is a registered trademark of International Business Machines Corp. P-CAD is a registered trademark and Master Designer, Master Layout, Master Schematic, and Master Placer are trademarks of CADAM INC. CADAM INC., 1935 N. Buena Vista St., Burbank, CA 91504. ©1992 CADAM INC.

CIRCLE 128 FOR U.S. RESPONSE

CIRCLE 129 FOR RESPONSE OUTSIDE THE U.S.

## Oki's Advanced ASIC Tools Reduce Your Risk.

**A**s an ASIC designer for high-performance systems, you know the sinking feeling of working for weeks on a high-density design—only to have it crash. You know the risks involved in designing with tools that offer no assurances—Will path delays meet spec? Will routed signals violate timing? Will power problems cause unexpected voltage drops?

Oki's advanced tools provide the lift you need to dive comfortably into the highest levels of ASIC design:

### Timing-driven layout -

enables control of critical net and path delays, better ensuring a design-to-silicon match.

### Clock tree structures -

automatically route logic signals where you want them and when you want them, optimizing clock distribution.

**Power calculator -** locates and corrects power distribution and dissipation problems, increasing overall system reliability.

Coupled with our 0.8 $\mu$ m leading-edge sea-of-gate technology and our high-level support—such as Verilog, Synopsys, and IKOS—these Oki software tools not only optimize ASIC performance but also optimize design time.

So go ahead and take the plunge. Call 1-800-OKI-6388, Dept. 050, for Oki's ASIC capabilities brochure. See how risk-free ASIC design can be.

### Oki ASIC Design Tool Support for 0.8 $\mu$ m, 1.0 $\mu$ m, and 1.2 $\mu$ m

Vendor	Platform	Operating System/Rev	Description
Cadence	Sun/SPARC	Sun OS 4.1.1	Simulation
	Solbourne	Verilog 1.5C	Fault grading Design verification
IKOS		4.0 up	Simulation Fault grading
	Mentor Graphics	HP/Apollo DNx Series	DNIX 5.03, Sun OS 4.1.1 Digital application 6.1 Digital application 6.3 Digital application 8.0 (in qualification)
Synopsys	HP9000	Parade	Layout Clock Structures
	Sun/SPARC Solbourne	Sun OS 4.1.1 Interface to Mentor, Valid, Viewlogic	Design synthesis Test synthesis
Valid	Sun/SPARC	Sun OS 4.1.1	Design capture Simulation
	Sun-3	GED, ValidSIM, RapidSIM	Simulation Design check
Viewlogic	DECstation 3100	ULTRIX, ValidSIM, GED	
	IBM RS6000	GED, ValidSIM, RapidSIM	
Viewlogic	Sun/SPARC	Sun OS 4.1.1 Workview 4.0	Design capture Simulation
	PC386	DOS 3.3, Workview 4.0	

TRANSFORMING TECHNOLOGY INTO CUSTOMER SOLUTIONS

WHEN YOU PLUNGE INTO ASIC DESIGN,  
YOU WANT SUPPORT TOOLS THAT WORK.



**OKI**  
Semiconductor

785 North Mary Avenue  
Sunnyvale, CA 94086-2909  
1-800-OKI-6388, Dept. 050



# THE SILICON VALLEY NETWORKING CONFERENCE

**APRIL 27 - 29, 1992**

The Santa Clara Convention Center  
Santa Clara, California

ADD  
THESE TO  
YOUR  
CALENDAR

The  
Silicon  
Valley  
Personal  
Computer

Design Conference focuses on providing solutions to key PC, Workstation, and Peripheral design and integration issues. Unlike

other computer shows that are aimed at distributors and value-added resellers, SVPC is aimed at designers and strategic planners who are evaluating or designing the next-generation desktop and portable computer systems. The conference will provide eight half-day tutorials and over 100 technical paper presentations covering key design and implementation issues for desktop and portable systems. Presentations will cover:

Pen-Based System Design, Portable System Design, Motherboard Design, Memory Card Interfacing and Control, Graphics and Video Subsystem Design, Display Technology, Multimedia Hardware Design, Mass-Storage Subsystem Design, Peripheral Design, Expansion-Bus Interfaces (AT, EISA, MCA, SBus, Turbochannel, others), Memory- and Cache-Subsystem Architectures, Data Communications (fax and modem design, network adapter design, and wireless LAN implementation), Integrating-in Graphical User Interfaces, BIOS and Operating System Implementation. . . . .and many other topics

Keynote Speaker: Eric Benhamou, C.E.O. 3Com Corp.

The Silicon Valley Networking Conference is the only networking conference that focuses on the DESIGN of network related hardware and software. The conference venue consists of six half-day tutorials and more than 70 technical paper presentations. Topics will include:

Distributed Processing, Sonet, HiPPI, FDDI, Internetworking, Wireless LANs, Network Management, Network Diagnostics, Frame Relay, X-Windows, Token Ring, Ethernet, ISDN

**KEYNOTE PRESENTATIONS:**

Dr. Gordon Moore, Chairman of the Board and one of the founders of Intel Corp.  
Roger Ross, President, ROSS Technology, a subsidiary of Cypress Semiconductor Corp.

# SILICON VALLEY PERSONAL COMPUTER DESIGN CONFERENCE

**AUGUST 10 - 12, 1992**

The Santa Clara Convention Center, Santa Clara, California



*These Conferences are a creation of SysTech Research. SVNC is co-sponsored by 3Com Corporation.*

*Electronic Design and Electronics Magazines are co-sponsors of both SVNC and SVPC.*

**ADVANCE REGISTRATION APPLICATION**

(for applications postmarked by 3/6/92 for SVNC, 6/26/92 for SVPC)

	SVNC	SVPC	TOTAL
Tutorials only (one day registration) . . . . .	\$250	\$295	\$ _____
Papers only (two-day registration) . . . . .	\$350	\$395	\$ _____
Full conference (three-day registration) . . . . .	\$450	\$495	\$ _____
Exhibits only pass. . . . .	\$ 25	\$ 25	\$ _____
Extra proceedings (add \$15/domestic mail; \$35/intnl airmail) . . . . .	\$ 85	\$100	\$ _____

Note: Registration fees for either conference include coffee break refreshments, lunch, and one set of tutorial notes and/or conference proceedings

TOTAL ENCLOSED \$ \_\_\_\_\_

Name \_\_\_\_\_ Title \_\_\_\_\_

Company \_\_\_\_\_ Mail Stop \_\_\_\_\_

Address \_\_\_\_\_ City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_


Telephone \_\_\_\_\_ FAX \_\_\_\_\_ Email \_\_\_\_\_

MAIL this completed form with payment (in U.S. Dollars) to: SysTech Research,  
1248 Olive Branch Ln, San Jose, CA 95120; (408) 997-8265 (fax or phone)

CIRCLE 194 FOR U.S. RESPONSE

CIRCLE 195 FOR RESPONSE OUTSIDE THE U.S.
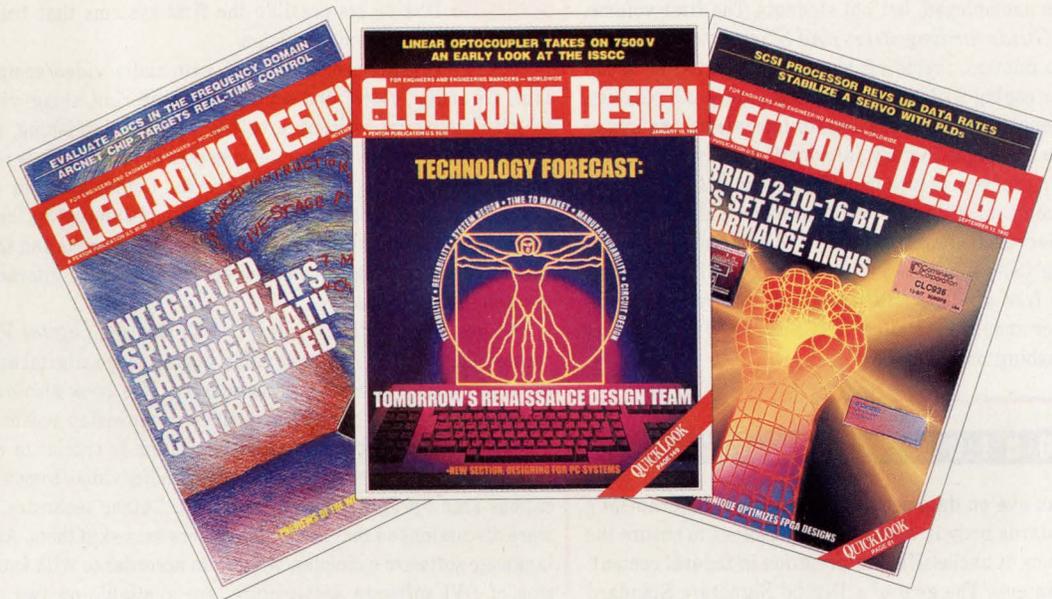
# Get your technology news where the rest of the world does... first!



## Electronic Design: Leader of the pack since 1952

**Electronic Design** is the industry's most-often quoted electronics publication. There's a good reason for this: **Electronic Design** is always the first to report on and describe new technologies as they occur. We're proud of this reputation.

Lots of engineering publications talk about new products, new issues, and new technology. New items are the essence of news reporting.

But when you read about new technology or new implementations of technology in an electronics magazine - any electronics magazine - it's likely that the story was first discussed in **Electronic Design**.

Why do leading manufacturers select **Electronic Design** as the vehicle for their significant product introductions? Because they know that **Electronic Design** is the ideal environment for their important debuts. Each issue contains the latest information on tools and techniques to help shorten the design cycle, helping our readers to incorporate the latest products and technology into their designs.

**Proven leadership in circulation and editorial makes *Electronic Design* the source of critical design**

information for 165,000 global readers. And we're first with the information you need in your job.

After all, why should you wait and read about it somewhere else tomorrow?

**YES!**  
I want my  
technology news as  
it happens.

YES! I want my technology news as it happens.  
Please begin my subscription to *Electronic Design* immediately.

1 year, 24 issues for \$85.00.

Name: \_\_\_\_\_  
Address: \_\_\_\_\_  
City: \_\_\_\_\_ State: \_\_\_\_\_ Zip: \_\_\_\_\_

For subscriptions to Canada, add \$75.00; foreign subscriptions, add \$145.

Send to: Penton Publishing, P.O. Box 95759  
Cleveland, Ohio 44101; attn: Juanita Roman

# ELECTRONIC DESIGN

# QUICKLOOK

## ON THE JOB

**A**s layoffs continue, finding a job is an increasing concern among engineers. The IEEE-USA's third edition of its two-volume employment guide is free to IEEE members who are unemployed, but not students. The first volume, *An Employment Guide for Engineers and Scientists*, is a practical manual for job hunters, including how to get started on a job search, strategies on coping with job loss, writing letters and resumes, establishing a personal network, preparing for interviews, and evaluating compensation packages. Salary information, drawn from the IEEE's annual salary survey, is included. The second volume lists by state hundreds of companies that employ engineers. Guides are sold through the IEEE Service Center at \$14.95 (members) and \$19.95 non-members by calling (800) 678-4333 and requesting IEEE catalog no. UH0186-7. For the free guide, written requests that include IEEE membership number should be mailed to IEEE-USA, 1828 L Street NW, Suite 1202, Washington, DC 20036.

## QUICK NEWS

**W**ith an eye on data security, the federal government's standards body is working on guidelines to ensure the privacy of unclassified information in federal computer systems. The goal of a Digital Signature Standard (DSS) being developed by the National Institute of Standards and Technology (NIST) is to verify data integrity and the sender's identity. NIST is seeking comments from the public and federal, state, and local government users. Written comments, due Feb. 28, 1992, should be sent to the Director, Computer Systems Laboratory, Attn: Proposed FIPS for DS, B154 Technology Bldg., NIST, Gaithersburg, MD 20899. Contact Miles Smid at (301) 975-2938.

## QUICK REVIEWS

**D**igital Video in the PC Environment, second edition, by Arch C. Luther is a guide to implementing digital interactive video on personal computers. As Luther points out, DVI makes possible the first systems that truly merge personal computers and television.


Among the skills needed to work with audio/video/computer systems are audio-, video-, and computer engineering, along with ability in graphics, script writing, creative writing, publishing, programming, and audio/video production and post production. Few readers, of course, have expertise in all these areas. Luther assumes only that readers have an electronics background and interest in the subject. Consequently, Luther gives an overview of these areas and shows how the various technologies come together in creating interactive systems and applications.

Besides covering the i750, Intel's DVI chip set, *Digital Video* discusses fundamentals in analog video, digital video, digital audio, optical storage, and, of course, programming. The book also deals with interfacing the i750 chip set and video compression technology. Although programming a digital-based system is crucial to making a DVI system perform, many developers of audio/video/computer applications aren't programmers. As a result, Luther separates the software discussions so that nonprogrammers may skip them. And new C language software examples, written in accordance with Intel's revision of DVI software architecture, are available on two disks for \$24.95 in 3.5- or 5.25-in. format (Digital Video Software Offer, P.O. Box 6069, Alexandria, VA 33206-6069).

Luther, one of the developers of DVI technology, participated in developing the NTSC color TV standard, broadcast video recorders, and consumer VCRs. He holds 32 U. S. patents. With a list price of \$29.95, the book is published by Intertext Publications, McGraw-Hill Book Co., New York, N. Y., 1991 (ISBN 0-07-039179-3).

## CAD/CAE SURVEY
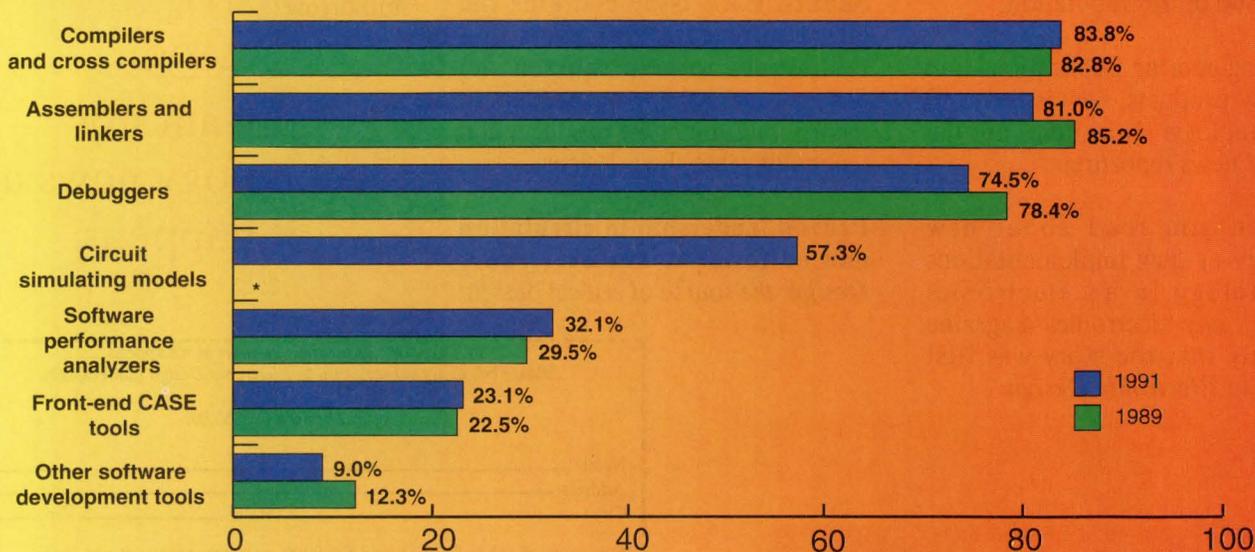
### WHICH SOFTWARE DEVELOPMENT TOOLS DO YOU USE FOR CAD/CAE?



\* Category not measured in 1989 survey

Source: a survey of Electronic Design readers conducted by the Adams Co., Palo Alto, Calif. (415) 325-9822. Readers gave more than one answer to question.

# WHAT'S ALL THIS DEAD CAR STUFF, ANYHOW?

**E**very year, in January, I compile a list of all the Dead Cars I've seen along the highways over the last calendar year. If you want to see a copy, send an SASE and I'll mail it. This year will be the 22nd annual list, going back to when I lived in Massachusetts in 1969. It lists every car according to their manufacturer, and sometimes by type.

For example, I try to keep the GMC cars separate from the Fords or the Chryslers, but I can't possibly segregate the Chevys from the Buicks — for all I know, they have the same engine anyhow.



**BOB PEASE**  
OBTAINED A BSEE FROM MIT IN 1961 AND IS STAFF SCIENTIST AT NATIONAL SEMICONDUCTOR CORP., SANTA CLARA, CALIF.

than one would expect from the number of Saabs on the road. Over the years, I kept on listing all of the cars I saw, dead or abandoned, foreign or domestic.

Now, what's the significance of

these lists? Do they prove that one car is more reliable than another? No, not really, because even though you could tell how many cars are registered in any state, that doesn't tell you the number being *driven*. But I have had a lot of fun keeping notes on the Dead Cars. And my friends find it amusing to look at these lists.

Just the other day, I was writing down the data for one dead Mercedes Benz and one abandoned Ford with a flat tire. My passenger asked, "You mean, every time you see an abandoned car, you write down a note?" I replied, "Sure... doesn't everybody?..."

In the last five years, I began to keep a list of the cars I saw with no brake lights. I carry an envelope that I can hold up to warn a driver, "YOU HAVE NO BRAKE LIGHTS". I really don't like to see cars driving around with no brake lights.

It's all too easy for them to collect an innocent car on their rear when they hit their brakes and the following driver can't make this out all that well. So an accident can happen, and in my neighborhood, insurance rates go up even though many of us have had no accidents at all.

On the other side of the placard it says "YOU HAVE ONLY ONE BRAKE LIGHT". After one brake light burns out, what happens next? The other one burns out, and the car is left with none. So I like to warn these guys to get their brake lights fixed. In 1990, I notified 69 cars that they had no brake lights, and 144 cars that they had only one brake light.

There were about six guys with no brake lights that got away — sometimes they turn off in traffic before I can catch up with them, or sometimes

a light changes against me. I hate to let a car with no brake lights get away. Still, I think I'm doing something useful, even though my wife sometimes gripes that I beep my horn too much just to tell a guy he has only one brake light.

But think about this: A guy has only a right brake light. He starts to signal for a right turn. Then he hits his brakes. In many cars, the brake light and the blinkers are connected to the same bulb, so when he hits the brakes, no change occurs. In some cases, one brake light burned out is as bad as no brake lights at all.

What do I do about brake lights? On each of my four cars, I've rigged extra brake lights up high so that they're really noticeable to the drivers behind me. If 1 or 2 bulbs burn out, I still have a couple left. Best of all, I can look in my mirror and see if the extra bulbs light up when I hit the brakes, so I can tell if the brakes' pressure-switch is working. Now, with a broad pen and a blank envelope, or a piece of paper taped to an envelope, *you, too*, will be able to warn drivers: "YOU HAVE NO BRAKE LIGHTS" and "YOU HAVE ONLY ONE BRAKE LIGHT".


Just what kind of car do *you* drive, Pease, to get good reliability? Ah, yes, I drive a car with exactly the right amount of modern electronic, computerized equipment — a 1968 VW Beetle (my wife drives a newer car, a 1969 Beetle).

Now, as an engineer, I suppose I should say good things about all of the fancy electronic fuel injection and spark computers and diagnostic computers and Lambda sensors. But I get 31 mpg and the car goes just as fast as I want, and that's good enough for me. The bottom line is that I prefer a car that has proven itself by running reliably for 244,000 miles. In fact, until a couple months ago, it was still running on the original engine, and the original crank and pistons and cylinders (though it's true I had replaced the cylinder heads).

Sometimes I do connect a Heathkit electronic ignition system to minimize wear and tear on the breaker points. But right now it's on the blink, so I just
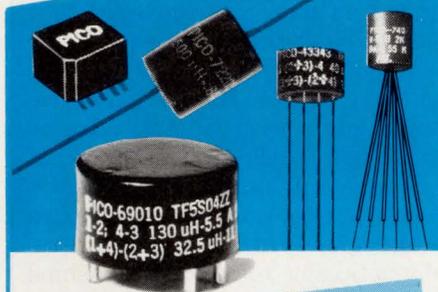
# PICO Transformers & Inductors

**PLUG-IN  
SURFACE MOUNT  
AXIAL INDUCTORS  
TOROIDAL  
INSULATED LEADS**



## TRANSFORMERS

QPL standards available  
MIL-T-27/103-1 thru 16, MIL-T-27/172-1 thru 50,  
MIL-T-27/357-1 thru 114, MIL-T-27/358-1 thru 123,  
MIL-T-27/359-1 thru 147

- Audio Transformers ranging in size from  $\frac{1}{4}'' \times \frac{1}{4}''$  to  $\frac{3}{4}'' \times \frac{1}{4}''$ . 20 Hz to 250 KHz. Up to 3 watts.
- Pulse Transformers .05 $\mu$ SEC to 100 $\mu$ SEC miniaturized construction.
- Ultra-miniature DC-DC Converter Transformers. 40 watts.
- Miniaturized Switchmode Inverter Transformers. 60 watts.
- 400 Hz Power Transformers. Primary voltages of 115V or 26V. Plug-in construction. Ultra-miniature
- Microphone/Transducer Audio Input.
- MIL-STD-1553 Interface Multiplex Data BUS Pulse Transformers.

## POWER INDUCTORS

QPL standards available MIL-T-27/356-1 thru 63

- Inductance values to 20mH with DC currents to 23 amps

## COMMON MODE INDUCTORS

## HIGH "Q" INDUCTORS

See EEM  
or send direct for  
FREE PICO Catalog

# PICO Electronics, Inc.

453 N. MacQuesten Pkwy. Mt. Vernon, N.Y. 10552

Call Toll Free **800-431-1064**  
IN NEW YORK CALL **914-699-5514**  
FAX **914-699-5565**

CIRCLE 130 FOR U.S. RESPONSE  
CIRCLE 131 FOR RESPONSE OUTSIDE THE U.S.

## PEASE PORRIDGE

went back to the old conventional (Kettering) ignition system, points and coil and distributor and "condenser". I set my own timing and I adjust my own valves. That's one good thing about old, simple cars — if something does go wrong (which is rarely) you can fix it yourself.

Do you ever count your own car, Pease, when it's dead? Yes, but that's not very often. One time my coil burned out. One time my distributor got loose and lifted out of its spigot, and it took me a full hour to figure out that when the engine turned, there had to be a reason why the distributor and its rotor did not. Another time a fuel hose fell off, but I fixed that and got going quickly, so I only counted it as 1/2.

There are several cases where I count a car as 1/2. For example, if a guy with a Volvo is talking to a guy with a Datsun, and they both have their hoods up, I may count 1/2 Datsun, 1/2 Volvo, 1 Helper. I count people who are obviously helping out as a Helper, not as a Dead Car. If I'm not sure it's a Rabbit on the other side of the road on a rainy night, I may count 1/2 Rabbit and 1/2 Modern Boxy Car (1/2 Modbox). If I can't even tell if it was probably foreign or U.S.-made, it gets scored as "1 car".

Do I think that electronic systems are going to improve the reliability of vehicles? Well, maybe. I recall the story of one of the first trucks that had an anti-lock brake system. They were driving innocently down the road when a nearby driver keyed the transmitter on his CB radio and the truck immediately locked up all its brakes. It turned out somebody had decided it would *hurt* the reliability to add bypass capacitors across all of the sensors and the inputs of the sensor amplifiers.

That's what you learn from MIL-HDBK-217...remember? So when the transmitter went on, all of the amplifiers went berserk. Oh, the *amplifiers* were perfectly "reliable," but the system had not been engineered properly. It was a miracle that nobody was behind the truck when it locked up all its brakes.

Are the new electronic systems better for the environment? Maybe so.

Maybe a new sedan can travel down the road emitting even less smog and emissions than my VW, so long as its computer is working right. But in 10 years, what happens when you can't get parts for the computerized systems? My car will still be running just fine. I think I'll stand pat.

After all, I have all of the tools and techniques I need to keep old VWs running forever. Forever? Well, there are old VWs around here that are over 35 years old, and if I can keep my good new beetles running 35 more years, they may outlive me. You would not want to bet that I can't keep them running. Meanwhile, if I see another VW broken down along the road, I stop and see if I can help.


Sometimes I have a tool or a gallon of gas, or the spare part they're in need of — a fan belt, or some points, or a clamp for a fuel hose. So I try to help solve their problem. If we can't figure out what's wrong, I leave them a SASE so they can write to me and explain what was the problem once they find out.

For example, one guy sent me a letter stating that the 1969 bus he had just bought was merely out of gas. The gas gauge was broken, but the previous owner, of course, had not warned him about that.

So, when I see a dead, abandoned, or broken-down car along the freeway, I score it. I categorize and count it. Now, if a guy is just changing a tire, or pouring in a spare gallon of gas, I list that problem, but I don't count the car as dead or abandoned. In 1990, I saw 24 people that ran out of gas, 139 with a flat tire, 211 pulled over by a cop, and 16 with a broken drive shaft (remember, none of my cars has a drive shaft). I counted 293.5 GMC cars, 146 VWs, and one Citroen. What are the corresponding totals for 1991? I'll let you know as soon as I have them all added up.

All for now. / Comments invited!  
RAP / Robert A. Pease / Engineer

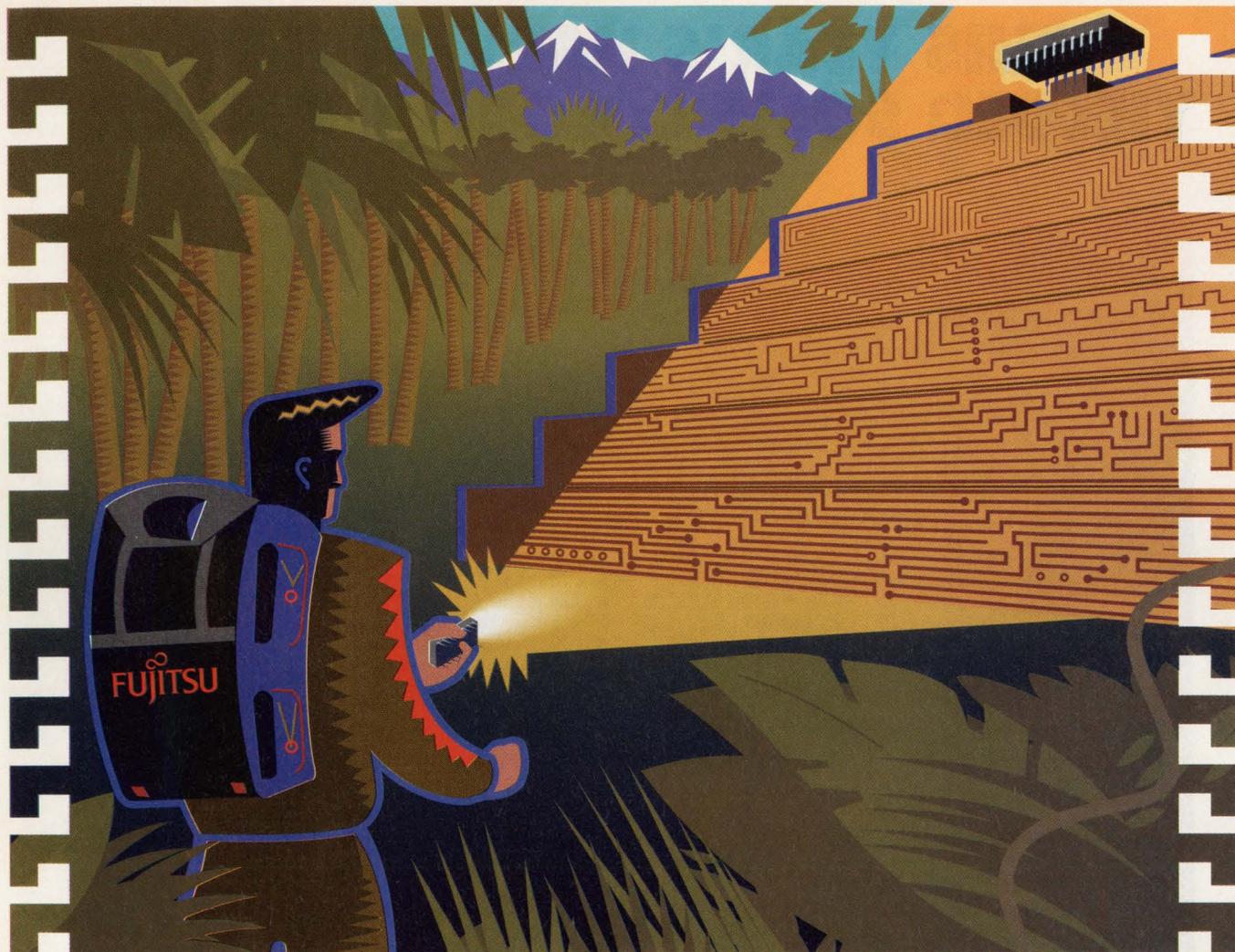Address:  
Mail Stop C2500A  
National Semiconductor  
P.O. Box 58090  
Santa Clara, CA 95052-8090



## Searching for embedded solutions? Let us shed a little SPARC<sup>®</sup>lite.

VISIT  
BOOTH #940  
AT SUNWORLD  
EXPO

We're blazing a trail for designers of embedded control systems. And now the unparalleled performance, innovation, simplicity and cost efficiency of RISC technology are finally in sight.

Introducing SPARC<sup>®</sup>lite™. A complete family of RISC processors from the Advanced Products Division of Fujitsu Microelectronics. Designed from the ground up for high-performance embedded applications.

Our first SPARC<sup>®</sup>lite family member, the MB86930 processor, provides a new generation of solutions that can easily be designed into your embedded applications — for much greater performance at very competitive prices. Operating at clock speeds up to 40 MHz — and providing



# FUJITSU

*Delivering the Creative Advantage.*

40 MIPs peak and 37 MIPs sustained performance.

Software compatible with the industry-standard SPARC<sup>®</sup> architecture, our MB86930 provides the on-chip cache memory needed to meet the demands of performance-critical real-time routines. As well as a unique cache-locking mechanism and many other on-chip peripheral functions.

What's more, Fujitsu's SPARC<sup>®</sup>lite program is complemented by a full range of multi-platform support tools from the leading names in development systems. To help you get to market more quickly than ever before.

So why keep searching in the dark? Call us at 1-800-523-0034. And turn on SPARC<sup>®</sup>lite for the best in embedded solutions.

FUJITSU MICROELECTRONICS, INC., Advanced Products Division, 77 Rio Robles, San Jose, CA 95134-1807. Ph: 408-456-1161 Fax: 408-943-9293.

FUJITSU MICROELECTRONICS ASIA PTE LTD. (Head Office, Singapore): Ph: 65-336-1600 Fax: 65-336-1609. HONG KONG SALES OFC: Ph: 852-723-0393 Fax: 852-721-6555.  
TAIPEI SALES OFC: Ph: 886-2-757-6548 Fax: 886-2-757-6571. JAPAN SALES OFC: Ph: 81-3-3216-3211 Fax: 81-3-3216-9771. KML CORP. (Rep., Korea): Ph: 82-2-588-2011 Fax: 82-2-588-2017.  
PACIFIC MICROELECTRONICS, PTY. LTD., (Rep., Australia): Ph: 61-2-481-0065 Fax: 61-2-484-4460.


FUJITSU MIKROELEKTRONIK GmbH (Dreieich-Buchschlag, Germany): Ph: 06103-6900 Fax: 06103-690122.

SPARC<sup>®</sup>lite is a trademark of SPARC International, exclusively licensed to Fujitsu Microelectronics, Inc. SPARC is a registered trademark of SPARC International, Inc.

CIRCLE 102 FOR U.S. RESPONSE

CIRCLE 103 FOR RESPONSE OUTSIDE THE U.S.
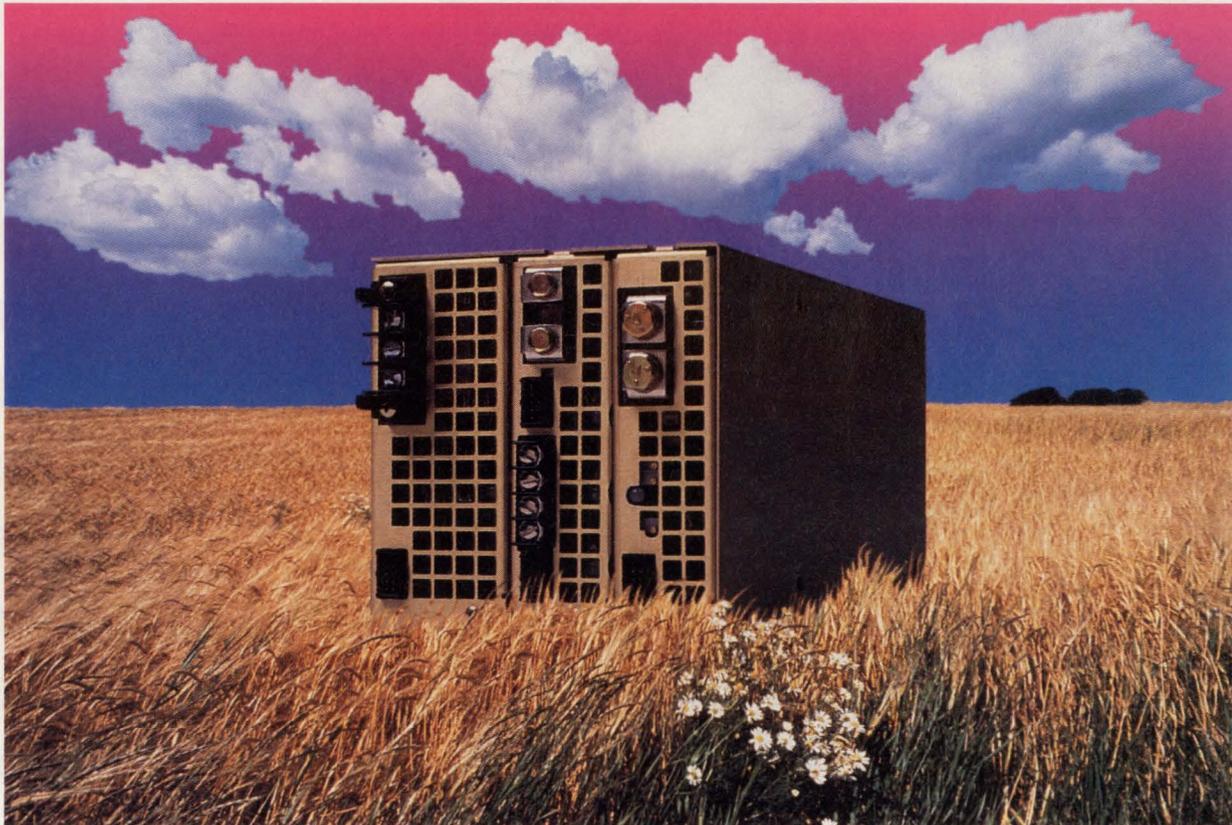
# THIS YEAR'S HARVEST HAS YIELDED SOME COLORFUL RESULTS



## LIKE THE NEW SPECTRUM SERIES, THE MODULAR DESIGN THAT OFFERS AN ARRAY OF STANDARD FEATURES INCLUDING PFC.

Astec introduces a new high power product of unmatched versatility and value. Its compact footprint and standard PFC front-end make the Spectrum Series compliant with IEC 555-2 while bringing significant space savings to countless designs. With up to 12 outputs plus a full range of output currents and voltages, Spectrum will accommodate any configuration of power between 500 and 2000 watts.

Many features, considered options in the industry, are standard in the Spectrum Series, including current share, remote sense, voltage adjustment, margining, power fail and level A EMI filtering - all at no additional cost.

Standard modules are stocked for fast delivery. To reap the many benefits from Astec's new Spectrum Series, call the toll free number below.



ASTEC STANDARD POWER  
Division of Astec America, Inc.  
401 Jones Rd.  
Oceanside, CA 92054-1216  
Telephone: 619-757-1880  
Facsimile: 619-439-4243

**1-800-233-9973**

For Literature or Information

CIRCLE 88 FOR U.S. RESPONSE

CIRCLE 89 FOR RESPONSE OUTSIDE THE U.S.

A SEXTET OF ELECTROMAGNETIC-INTERFERENCE TESTERS SPORTS A PRICE/PERFORMANCE RATIO AND MODULARITY TO SUIT ANY BUDGET.

# SOPHISTICATED INSTRUMENTS TAKE ON EMI TESTING


JOHN GOSCH

**W**hen the 12 countries of the European Community become a single market in 1993, West Europe will be a region where people, goods, and capital can move freely across national borders. It will also be a region with common, mutually recognized standards in all EC countries. One standard will apply to electromagnetic compatibility (EMC)—the ability of equipment or a device to function satisfactorily in its electromagnetic environment without introducing intolerable interference to anything in that environment. Consequently, if companies want to continue doing business in Europe's upcoming barriers-free market—with 345 million consumers, it will be the world's biggest—designers must make certain their equipment meets the new EMC standards, which will be effective sometime in the mid-1990s.

In light of this, Germany's Rohde & Schwarz has a new family of EMC testing instruments that sport what the company claims are "performance firsts." The ESHS/ESVS family combines dedicated commercial EMI testing capability with an exceptional price/performance ratio, setting new standards for EMI test receivers.

Until now, test engineers often used simple spectrum analyzers or manually tuned test receivers to determine the EMI profile of the equipment under test, and to ascertain that the interference did not exceed prescribed limits. But these types of instruments have their technical shortcomings, such as intermodulation problems at the receiver front end, which may lead to unpleasant surprises during final testing of the finished product.

This is where the new tester family comes in: Performing EMI measurements up to 1 GHz, the ESHS/ESVS testers deliver precise results in a matter of seconds and put out legally binding test protocols (see "The importance of EMI testing," p. 96). Thanks to built-in microprocessors and sophisticated firmware, they sport automatic measuring capabilities, besides being manually operable. The testers handle measurements according to

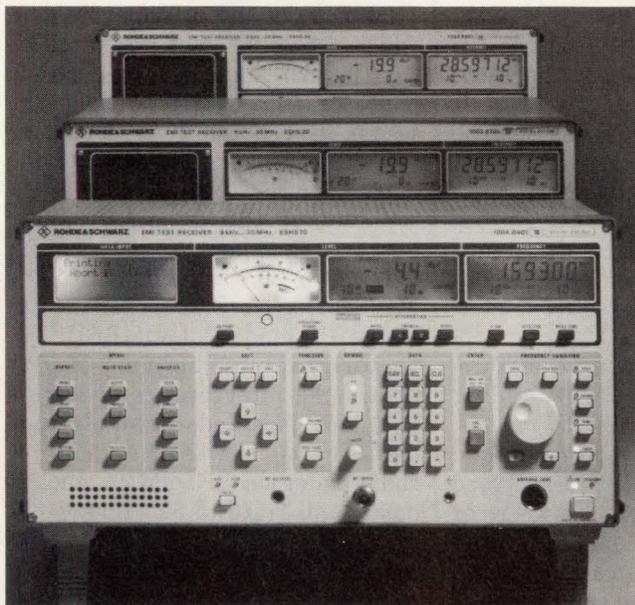

**DEDICATED TO EMI TESTING**, this trio of instruments from Rohde & Schwarz with analog readouts covers the frequency range of 9 kHz to 30 MHz. The series ESHS includes the ESHS10 (front), ESHS20 (center), and ESHS30 (rear). The -10 unit employs a 4-line LCD, whereas the -20 and -30 use CRT displays. The -20 and -30 units also include a 3.5-in. floppy-disk drive, while the -30 unit also has a tracking generator for 2-port measurements, as well as an IF analyzer for assessing interference visually. Another series with three models, the ESVS, covers the frequency range of 20 MHz to 1 GHz.

# SOPHISTICATED EMI TESTERS

## THE IMPORTANCE OF EMI TESTING

**H**istorically, EMC testing was considered a luxury because it required specialized equipment with high price tags. Though some might question the need for rigid EMC testing, there's a growing awareness of its importance. Immunity to electromagnetic interference is now considered a key characteristic of product quality. A number of sensational mishaps, such as airplane crashes, uncontrolled robot movements, and snags on automated production lines, were attributed to electro-

magnetic emissions from nearby equipment. Such events have highlighted the need for EMC testing.

Given the increasing sensitivity of the ever shrinking and faster ICs used today, even the slightest influence from electromagnetic waves must be ruled out. This is best accomplished by planning and designing EMC into the equipment at an early phase of its development. Measures to solve compatibility problems after the equipment is built are compromises, at best, and costly, as well.

such standards as the U.S.'s ANSI C63.2, Germany's DIN/VDE 0876, and Japan's VCC.

The new EMI tester family is available in two different series, each with three models. The ESHS10, 20, and 30 series cover the frequency range of 9 kHz to 30 MHz (see the figure). The ESVS10, 20, and 30 series cover 20 MHz to 1 GHz. The two series differ mainly in configuration, operating features, and price.

Such modularity should especially suit the small budget-conscious company, as it allows for equipment expansion at a later date by adding models in the upper- or lower-frequency ranges, says Wolf E. Schreyer, Rohde & Schwarz's product marketing manager for EMI testers. Modularity also offers the advantage of using different models for different tasks at different locations. For example, while one tester measures interference voltage in a shielded room, the other checks field strength on the outside.

Even the least-expensive models, the ESHS10 and ESVS10, are tough to beat by competitive test set-ups, Schreyer asserts. Used with a coupling network and a plotter, they automatically put out detailed test reports showing whether the EMI limits that the different standards prescribe for the equipment under test are exceeded or not.

The two -10 models are the basis for the new tester family. Operated manually or automatically (with or without an IEC/IEEE-bus controller), they're used for routine EMI measurements, such as interference voltage, current and power checks, as well as field-strength determinations. In addition to external batteries, they can be powered from internal batteries, suiting them for mobile applications or for measurements under difficult grounding conditions. The -20 and -30 models, which boast enhanced operating and measuring capabilities, can be used for measurements on all kinds of equipment, from small electric tools to big computing systems.

Common for all models are controls, LCDs, and an analog pointer-type indicator familiar to any instrument operator. Frequencies are

set in coarse, medium, and fine steps with a rotary control, or entered into the instrument via a keyboard. A 4-line LCD on the -10 models is for the man/machine dialogue, and two other LCDs for showing the selected settings and test results. The displays are easy to read both in bright light and (thanks to backlighting) shielded rooms.

While the controls and the indicator are used in manual operation, input keys call up the menus for automatic operation. The keys enter the start and stop frequencies, step sizes in the frequency scans, limit lines, transducer factors, printer and plotter configuration, and complex test routines.

The results are shown either by the analog indicator, or digitally on the appropriate LCD with 0.1-dB resolution and in the correct units—for example, in dB $\mu$ V, dB $\mu$ V/m, dB $\mu$ A, or dBm. A built-in loudspeaker allows audible evaluation of interference, and a special mode helps to detect weak continuous-wave signals.

Of note is the analog indicator, which not only shows measured results in dB, but also serves as a trend indicator. Only with an analog indication is it possible to determine whether a measurement is being made near the noise floor or at the top end of the dynamic range, Schreyer explains.

The two -20 models (ESHS20 and ESVS20) have a CRT screen instead of the -10 models' 4-line LCD. The vector-graphics screen display shows the interference spectrum and limit lines and, on an alphanumeric basis, serves the man/machine dialogue. In addition, the -20 models integrate a 3.5-in. floppy-disk drive that records the measured results. It also stores the measuring routines or loads them into the tester. The two -30 models (ESHS30 and ESVS30) are similar to the -20 models except that they have a tracking generator for 2-port measurements, and an IF analyzer for assessing the interference visually (see the table).

Europe's upcoming EMC standards reflect a radical change in how interference is assessed. The existing national norms, such as Germa-

## ROHDE & SCHWARZ'S SERIES ESHS/ESVS EMI TESTERS

Feature	Model 10	Model 20	Model 30
RF analysis		X	X
3.5-in. floppy disk		X	X
CRT display		X	X
Tracking generator		X	X
IF analysis			X
Battery installable	X		
Battery operation	X	X	X
Analog readout	X	X	X
Digital display	X	X	X
Calibration generator	X	X	X

## SOPHISTICATED EMI TESTERS

ny's VDE standards, define two classes of interference, narrowband, and broadband, and have different limits for each. But as electronics equipment proliferates, the equipment itself is growing as the main source of interference, and it becomes more difficult to distinguish between narrowband and broadband interference generated by an outside source, or by the equipment itself. So the present distinction (narrowband and broadband interference) will be abandoned when the new EMC standards are in force.

New standards will specify only average values and quasi-peak limits for interference. This means that both pulse and sinewave interference must be averaged or weighted. For this, the ESHS and ESVS testers use group-delay IF filters.

The new testers feature a number of innovations that clearly set them apart from competitive test set-ups. Among them are the parallel use of several measuring detectors, built-in intelligence in the form of firmware, the use of flash EPROMs for storing the firmware, fast frequency synthesis, and the output of a detailed test report.

In the patented parallel measuring scheme, the detectors for the peak, average, and quasi-peak display operate simultaneously. The weighted results are present after the first frequency scan and can then be further processed by the built-in intelligence or an external controller. Parallel use of detectors considerably cuts the measuring time and thus overall testing costs.

Rohde & Schwarz's engineers put much effort into developing the firmware, the built-in intelligence which specifies the tester's basic performance data. Even without controller support and with no extra software, the firmware allows fast measurements to be made with the average- and peak-value detectors. Using the limit lines, it also fixes the critical frequencies and, in the case of interference-voltage tests, permits repeat measurements at these frequencies to be performed with average- and/or quasi-peak detectors.

The firmware is stored in flash

EPROMs and, with the aid of a PC, can be loaded from a floppy disk via the serial interface in 5 minutes. Therefore, the firmware can be modified easily, without opening the tester and replacing the EPROMs. This makes it much easier and faster to upgrade programs—even via international data transmission lines—or to correct and update them in case of errors.

For fast results, the testers use frequency synthesis with short settling times. At a frequency resolution of 10 Hz and 100 Hz for the ESHS and ESVS series, respectively, the synthesizers allow frequency jumps of any step length within 10 or 30 ms. At a 1-ms measuring time, it takes only 20 seconds to completely scan the 9-kHz-to-30-MHz frequency range and obtain results with the ESHS testers.

Given the importance of EMI measurements these days, the test report, or measuring protocol, should constitute a legally binding document. Consequently, in addition to the measured values, the protocol contains such information as designation and operating mode of the equipment under test, the specifications used, the tester settings, the test date, and the name of the test engineer. Test date and settings are recorded automatically; other pertinent test information is entered manually.

### PRICE AND AVAILABILITY

Prices for testers marketed in the U.S. range from \$20,830 for the ESHS10 (the simplest model) to \$41,000 for the ESVS30 (the most sophisticated model). Accessories (prices are not included in the figures above) encompass coupling networks, such as artificial mains, current clamps, and power clamps, and measuring antennas for the higher frequencies.

In the U.S., Rohde & Schwarz, 4425 Nicole Dr., Lanham, MD 20706. Contact: Scott Elkins, (301) 459-0800. Rest of world: Rohde & Schwarz GmbH, Dept. 1EV, P.O. Box 80 14 69, D-8000 Munich 80, Germany. Phone: (0049)-89-41290 (ask for 1EV department).

CIRCLE 513

HOW VALUABLE?	CIRCLE
HIGHLY	541
MODERATELY	542
SLIGHTLY	543

## ATTENTION MARKETERS!

### REACH DESIGN AND DEVELOPMENT ENGINEERS



### ELECTRONIC DESIGN


subscribers are highly educated engineers and managers in the electronics original equipment market.

Select by:  
Job Function, Type of Industry, Project Responsibility, Purchasing Influence, Employment Size and Geography

Guaranteed 99% deliverable  
100% BPA audited

Call the List Department at 216(696)7000 for your FREE catalog

# Penton Lists

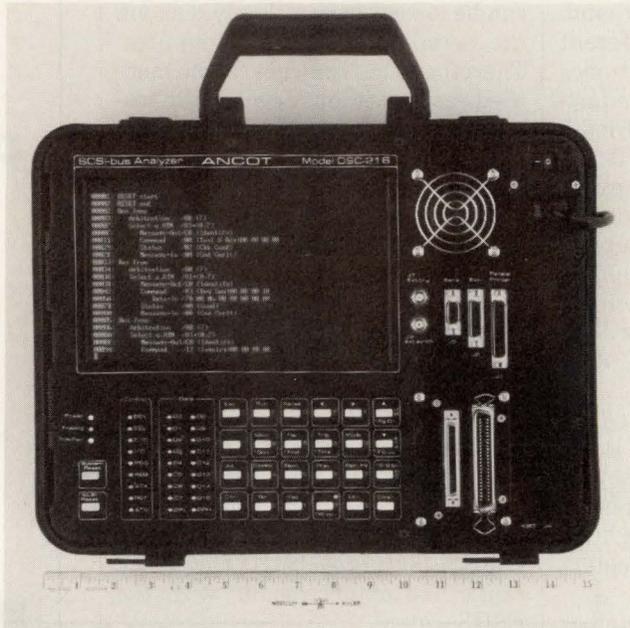

**1. THE DSC-216 SCSI BUS ANALYZER** fits into a compact attache-style case. The display is an 80-character-by-24-line electroluminescent panel.

# PORTABLE ANALYZER AUTOMATES SCSI TESTING

WITH 16-BIT-WIDE CAPABILITY AND 20-NS TIME STAMPING, THIS ANALYZER HANDLES THE FASTEST AND WIDEST SCSI BUSES.

**JOHN NOVELLINO**


**A**utomated measurements are becoming the norm rather than the exception these days. High-level automation has arrived for designers and integrators of SCSI bus peripherals in the form a SCSI bus analyzer that makes more measurements at faster speeds than previously available instruments.

The DSC-216 SCSI bus analyzer performs command profiling, histogram analysis, and

data-transfer rate calculations. The instrument features time stamping with 20-ns resolution so it can capture all phase, handshake, and timing information for transactions at the full 10-MHz rate specified by SCSI-2 Fast. The DSC-216 also handles 16-bit wide transactions, making it possible to track data at the 20-Mbyte/s asynchronous or synchronous rate of SCSI-2 Fast and Wide specifications. An LED display covers the eight control lines as well as the 16 data lines, allowing users to monitor real-time activity at a glance. A SCSI reset key simplifies resetting of the bus.

All this capability fits into a highly portable 15-by-11-by-6-in. attache-case style package

# AUTOMATED SCSI ANALYZER

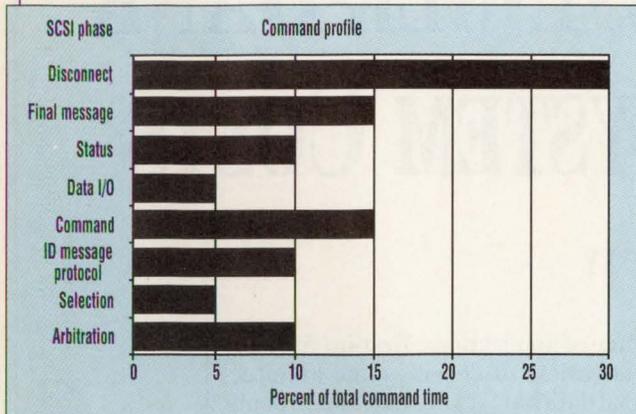

**2. THE ANALYZER'S COMMAND** profiling capability helps users identify SCSI command overhead during bus utilization. The report shows the time spent on each phase of a SCSI command.

(Fig. 1). The unit's display is an 80-character-by-24-line electroluminescent panel. With the panel-mounted keyboard, users can select most functions with one keystroke. Another unique feature of the DSC-216 is the ability to trigger in or out to external instruments—such as oscilloscopes or logic analyzers—via two front-panel BNC connectors. An RS-232 port, an expansion port, and a printer port are included.

Users can connect virtually any SCSI system to the DSC-216. The front panel has connectors for Centronics-type 50-pin SCSI cables and 68-pin high-density SCSI cables. An optional interconnect adapter offers seven other types of high- and low-density connectors, including the DB-25 Apple device. All are interconnected, so designers or integrators can use them simultaneously.

Among the new reports supplied by the analyzer is the command profile. This function is particularly useful in comparing SCSI devices and the efficiency of SCSI chips. The report indicates the time spent on each phase of a SCSI command, with the results displayed numerically or in graphical form (Fig. 2). This report quickly tells users which peripherals are taking the longest time to respond and eliminates the need to sift through the trace data and calculate the time spent on each phase.

Three types of data-transfer rates are calculated by the DSC-216. The

*maximum burst rate* is calculated over a limited number of bytes within a block. This figure does not include overhead and is the maximum rate the device can support under ideal conditions. The analyzer also measures the *sustained rate*, which is the average speed per byte over multiple consecutive blocks—for example, 100 blocks of 512 bytes each. This is the

maximum rate at which the device pair can communicate indefinitely. Finally, the *average throughput* is the transfer rate over a large number of small random transfers, which includes overhead. This figure is a realistic estimate of hardware's speed in an application program.

A powerful triggering system also eases the bus-analysis task. Users can select from 14 trigger conditions, including SCSI reset, select/reselect, select/reselect time out, status, command and status, parity error, and message. The conditions can also be used in combination. Besides starting a trace, the trigger can also stop a trace.


The DSC-216 has a deep trace memory—32k events in a circular buffer. A 128k-event memory is also available. Because the trace is event-driven, the analyzer captures 10-MHz data transfers and multisecond disconnects equally well. □

## PRICE AND AVAILABILITY

The Model DSC-216 portable SCSI bus analyzer costs \$8550 with the 32k-event memory and \$9950 with the 128k-event memory. The optional interconnect board is \$360. Delivery is 30 days after receipt of an order.

Ancot Corp., 115 Constitution Dr., Menlo Park, CA 94025; (415) 322-5322. CIRCLE 514

HOW VALUABLE?	CIRCLE
HIGHLY	544
MODERATELY	545
SLIGHTLY	546

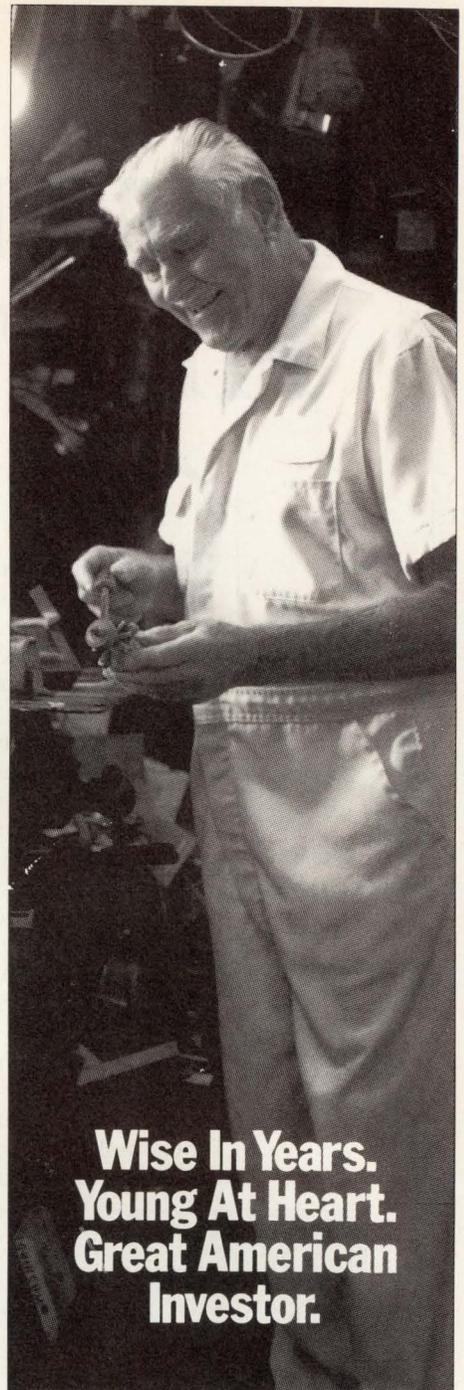

**Wise In Years.  
Young At Heart.  
Great American  
Investor.**

If you stop for gas at Wally Bonfield's service station, be prepared to fill up on a few good stories. One of his favorites is how he built his retirement nestegg—with U.S. Savings Bonds, the Great American Investment. "Bonds have always been there for me," he says proudly. Become the next Great American Investor. Call us to find out more.

**U.S. SAVINGS BONDS**



THE GREAT AMERICAN INVESTMENT

**1-800-US-BONDS**

A public service of this publication.

# BIDIRECTIONAL SINGLE-BANK FIFOS TRIM SYSTEM COSTS

DAVE BURSKY


**S**erving as data buffers in a wide range of applications, first-in/first-out memories have appeared in a wide variety of densities and architectures to suit many uses. Bidirectional data buffers are extremely popular for storage and data-communication systems applications. However, to make a bidirectional FIFO buffer, a system designer must either connect two unidirectional FIFO chips in back-to-back fashion, or the FIFO chip designer must integrate two banks of storage on the substrate, almost doubling the chip area. Either approach increases system cost and might reduce the economic viability of the approach.

To keep the chip more cost effective, designers at Integrated Device Technology came up with an asynchronous sharing scheme that allows a single internal memory bank to serve both directions. That keeps the chip size to within a reasonable percentage of a unidirectional FIFO memory, and also keeps down cost. The company's new family of three devices differ only in storage density. The IDT7271, 7272, and 7273, are organized as 512-, 1024-, or 2048, 9-bit words, respectively.

The FIFO buffers can be accessed in just 25 ns. Although they are bidirectional, the control scheme allows data to flow in only one direction at a time. This limitation will probably not impact over 90% of the system designs, according to Mike Shamshirian, IDT's FIFO product manager. Most applications, he says, only require that data transfers be done in one direction at a time—disk-drive data buffers for example either accept data from the host system or hold data being read from the disk. Only in the highest-performance applications will simultaneous data

transfers be required, and for those needs dual-bank FIFOs can meet the transfer requirements.

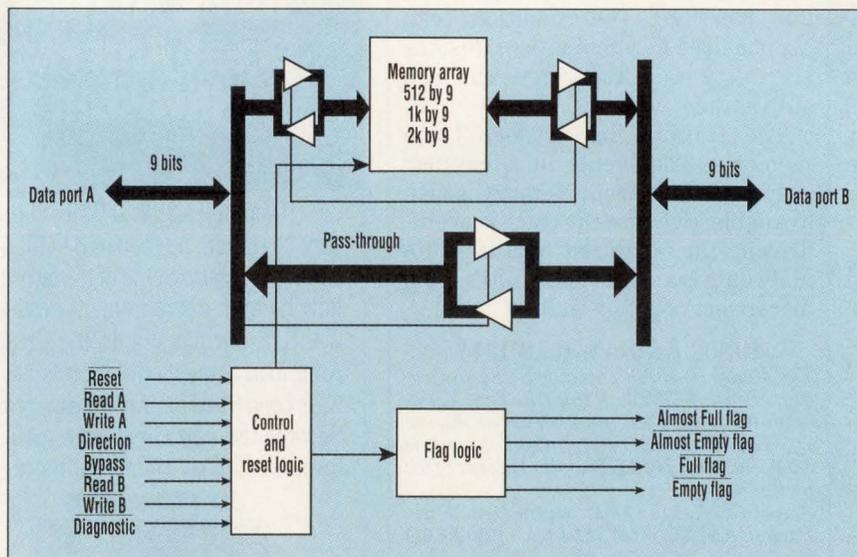Controlling data-flow direction is a direction pin, which sets the flow from Port A to Port B or vice versa. When that pin switches states, it changes the direction of the I/O buffers, re-sets the Read



**REQUIRING A SINGLE** bank of memory, Integrated Device Technology's bidirectional FIFO chip uses a Direction pin to control the direction of data flow between Ports A and B. A memory bypass feature lets critical data skirt the memory array and the delay it imposes, thereby allowing time-critical data to immediately reach the opposite port.

## SINGLE-BANK FIFO MEMORY

and Write pointers, sets flags to their proper states, and disables the opposite direction's control signals. Port A, however, is predefined as the priority default port and can be used to control all accesses. Because data flows in one direction at a time, the port pins can be shared, thus keeping the package pin count to just 32 pins for either the DIP, plastic leaded chip carrier, or small-outline J-leaded cases.

As noted, the chip area of the single-bank bidirectional FIFO is almost 50% smaller than the dual-bank bidirectional FIFO. The smaller chip area lets the single-bank memory fit into smaller packages, such as the SOJ, which could not handle a larger-size chip. The smaller packages, in turn, lets the memory occupy less pc-board area so designers can reduce system size.

A bypass capability is built into the FIFO array. This feature allows critical data to bypass the delay imposed by going through the on-chip memory array, and flow directly from one port to the other (see the figure). The memory also includes several flags, similar to flags on other FIFOs: There are fixed Full and Empty, as well as fixed Almost Full and Almost Empty. The almost flags have fixed offsets of eight bytes, which gives the system time to respond as system conditions change.

A Chip Reset signal allows the system to reset the contents of all pointers and flags, but leaves the contents of the memory unchanged. Consequently, certain operations can be set up as repeat loops, especially if the loop length doesn't extend to the full depth of the register. The memories also include a dedicated diagnostic pin that invokes a test mode that allows data written into one port to be read back by the same port. That permits the system to test the memory cells, and to ensure that data written into the chip is unchanged when read out. If a change occurs, memory cells may be defective and a diagnostic routine can notify the host system of a service need. □

### PRICE AND AVAILABILITY

Samples of the single-bank bidirectional FIFOs will be available later this month

for DIP and PLCC form, and next month for SOJ packages. In lots of 1000, the largest member of the family, the 2k-by-9 IDT7273L25, sells for \$39.90 apiece (plastic DIP version). Prices for the smaller 1k-by-9 and 512-by-9 devices are \$30.70 and \$25.60 each, respectively, also in lots of 1000 and plastic DIPs.

Integrated Device Technology Inc., 3236 Scott Blvd., P.O. Box 58015, Santa Clara,

CA 95052-8015; Mike Shamshirian, (408) 944-2082. CIRCLE 512

How VALUABLE?	CIRCLE
HIGHLY	547
MODERATELY	548
SLIGHTLY	549

# Put Our List On Your List

Our list can help you do the other things you have on your list. Such as buy a car... estimate social security... start the diet... check out investments...



Our list is the *Consumer Information Catalog*. It's free and lists more than 200 free and low-cost government booklets on employment, health, safety, nutrition, housing, Federal benefits, and lots of ways you can save money.


So to shorten your list, send for the free *Consumer Information Catalog*. It's the thing to do. Just send us your name and address. Write:

**Consumer Information Center  
Department LL  
Pueblo, Colorado 81009**

A public service of this publication and the Consumer Information Center of the U.S. General Services Administration



ANNOUNCING THE FIRST ANNUAL

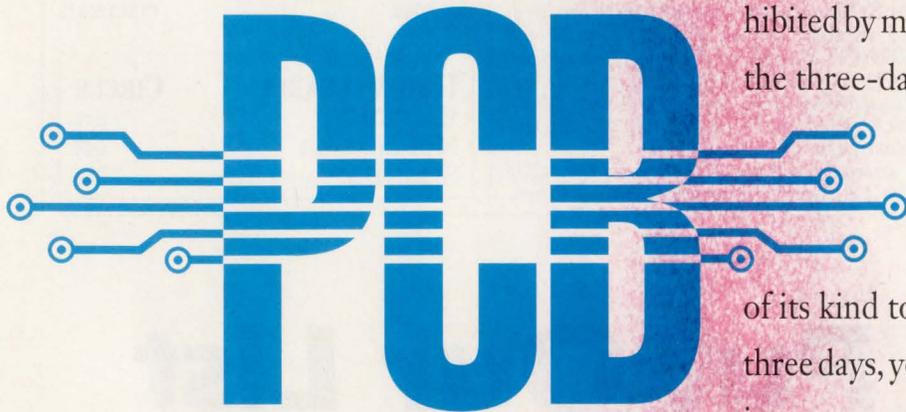

# DESIGN CONFERENCE

WHERE TODAY'S CHALLENGES MEET TOMORROW'S SOLUTIONS

see the latest EDA tools and technologies, exhibited by major CAE/CAD vendors throughout the three-day conference.

Sponsored by Printed Circuit Design magazine, the PCB Design Conference is the only forum of its kind to focus 100% on your needs. In just three days, you'll improve your PCB design skills, increase your productivity, and get practical solutions to specific design and layout problems that you face every day.



Sponsored by:

Printed Circuit Design Magazine

Produced by:

Miller Freeman Inc.

P.O. Box 7843

San Francisco, CA 94120-7843

Phone (415) 905-2354

FAX (415) 905-2220

March 30-April 1, 1992

Fairmont Hotel

San Jose, California

**B**ring your PCB design and layout problems to the only conference and exhibition dedicated solely to the design of printed circuit boards.

Increasing density, higher circuit speeds, smaller packages, finer lines and spaces, and new technologies are just a few of the problems slated for solutions at the PCB Design Conference, March 30-April 1, 1991 at the Fairmont Hotel in San Jose.

More than 50 workshops, lectures and tutorials will provide practical solutions and innovative techniques, presented by leading board design practitioners and authorities. And you'll



### MY SIGHTS ARE SET ON SOLUTIONS.

Please send me free details on the first annual PCB Design Conference, March 30-April 1, 1992, at the Fairmont Hotel in San Jose, California.

I am interested in:  Attending  Exhibiting

Name \_\_\_\_\_

Title \_\_\_\_\_

Company \_\_\_\_\_

Address \_\_\_\_\_

City/State/Zip \_\_\_\_\_

Phone \_\_\_\_\_ FAX \_\_\_\_\_

MAIL OR FAX TO: PCB DESIGN CONFERENCE, Miller Freeman Inc., P.O. Box 7843, San Francisco, Ca 94120-7843; FAX (415) 905-2220 or call Susie Chapman at (415) 905-2354.

PCBED

# VGA CHIP UPS COLORS, SPEEDS GRAPHICS WITH LOCAL BUS INTERFACE


DAVE BURSKY

The OTI-087 graphics controller outperforms other VGA chips. It addresses up to 2 Mbytes of memory and implements a direct processor interface that bypasses the traditional AT-bus interface for VGA controllers. The Oak Technology circuit can provide 24-bit color (16.8 million colors) with a resolution of 640 by 480 pixels or deliver high-resolution 1024-by-768 non-interlaced, or 1280-by-1024 interlaced images, both with 256 colors.

An on-chip write-cache supports high-speed transfers over the local processor bus at maximum bus speed while a read-cache provides zero-wait-state bit-block-transfer operations for fast image movement on the screen. The local-bus interface also implements XT or AT bus control signals if the designer opts not to use the local-bus interface. However, by tying directly into the processor's system bus, the OTI-087 Ultra-Color control chip can transfer image data at CPU bus speeds of 33 MHz (80386 or 486 CPUs). That moves data into the video memory at speeds three to four times faster than by using the XT or AT expansion buses, which are usually limited to below 10 MHz.

The chip's video memory interface allows 8, 16, or 32-bit wide data paths to the display memory as well as the use of the fast page mode in standard DRAMs. Video clock rates of up to 80 MHz can be driven by the controller, and that allows CRT refresh rates of over 70 Hz (meet or exceed the Video Equipment Standards Association refresh standard) are supported by the controller.

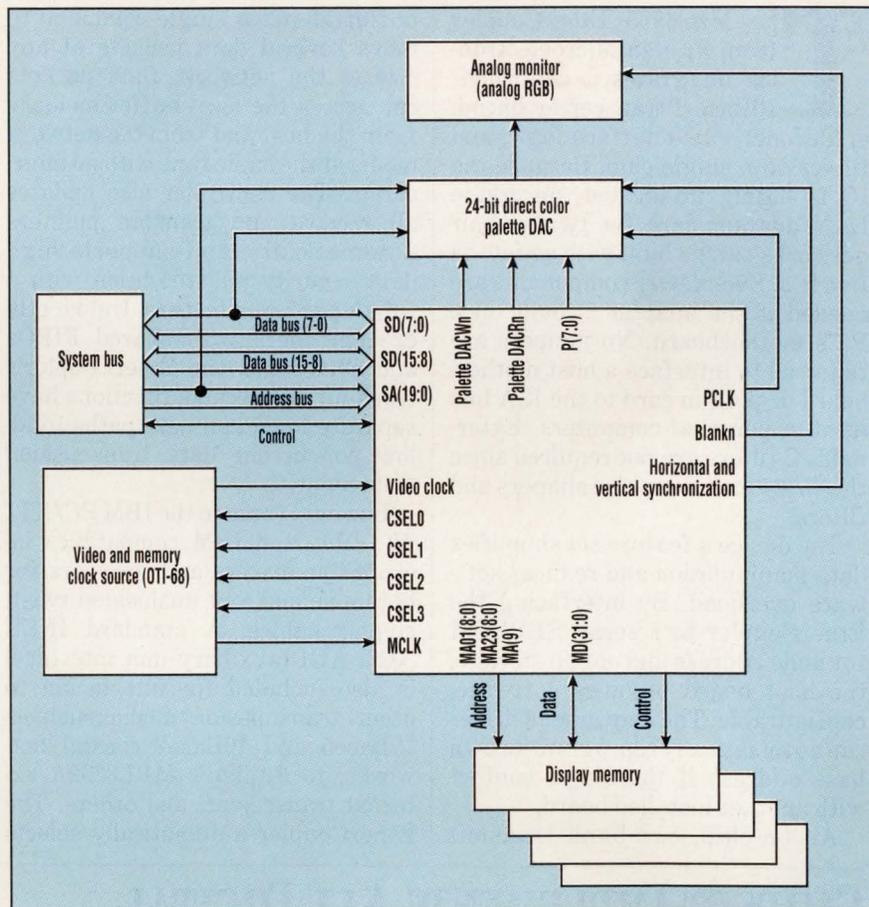On-chip foreground/background color expansion registers also help improve the speed of text output, especially when the chip employs the packed-pixel operating mode. The registers allow eight consecutive bytes to be expanded from one byte that contains the foreground and background bits. Hardware cursor



support in the form of a 64-by-64 by 2-bits/pixel writable memory allows the user to download a custom cursor image and change it depending on the application or system user's mood. A 16-bit graphics latch permits true 16-bit operations in the planar modes and special 256-color pattern and fill modes improve the drawing speed of complex images.

In most VGA systems some configuration data must be provided to the video BIOS firmware. The OTI-087 can tie into a small serial, electrically erasable memory that provides non-volatile storage of software-alterable configuration settings.

Since the local bus interface is not a universal standard, Oak has worked with a number of chip-set suppliers to ensure that several PC motherboard chip sets would be fully

functional with the VGA chip while minimizing the amount of glue logic needed to tie in the 087 controller. Some of the motherboard chip-set suppliers include OPTi Inc., Santa Clara, Calif., Elite Microelectronics Inc., San Jose, Calif., and VLSI Technology Inc., Tempe, Ariz. Oak has also developed true-color driver software as well as high-resolution drivers and a video BIOS. Software drivers are available for many popular application packages. An evaluation board is scheduled to be available this month. Housed in a 160-lead plastic quad-sided flat package, the controller will sell for \$31 apiece in thousands. Samples are available now.

Oak Technology Inc., 139 Kifer Court, Sunnyvale, CA 94086; Brian Davis, (408) 737-0888. CIRCLE 458

## 10BASE-T ETHERNET LAN CHIP INTEGRATES KEY CONTROL FEATURES

MILT LEONARD

The MB86965 EtherCoupler from Fujitsu Microelectronics integrates a controller, 10Base-T transceiver, encoder/decoder, bus-interface logic, and filters on a single chip. Because the IC is highly integrated, an add-in LAN adapter card for twisted-pair networks can be built with as few as five ICs. Even fewer components are needed if the adapter is built on a PC's motherboard. No jumpers are required to interface a host motherboard or plug-in card to the ISA bus used in personal computers. External L-C filters are not required since the 86965 includes pulse shapers and filters.

The device's feature set simplifies data manipulation and reduces software overhead. By interfacing the EtherCoupler to a serial EEPROM for node address and option storage, the host board becomes software-configurable. The chip and its driver can automatically reprogram its own base address if there is a conflict with another installed board.

An on-chip, two-bank transmit

buffer allows a single command to move several data packets of any size to the network. Data packets can access the local buffer memory from the host and from the network media at the same time with no interaction. The controller also updates all receive and transmit pointers automatically, and supports high data security and retention with a full-duplex architecture. Unlike other controllers with shared FIFOs and CRC logic, the EtherCoupler's transmit and receive functions have separate logic and data paths to allow concurrent data transmission and reception.

Bus interfaces to the IBM PC/XT/AT, ISA, and IBM compatibles include line drivers and receivers for both shielded and unshielded twisted-pair cables. A standard IEEE 802.3 AUI (auxiliary unit interface) is also included for interfacing to other transmission media such as 10Base5 and 10Base2 coaxial networks, to Fujitsu's MBL8392A external transceiver, and others. The EtherCoupler automatically selects

the active media.

The chip is also software-compatible with Fujitsu's NICE MB86960 Ethernet LAN device and is supported on all popular PC network operating systems with the use of the company's node drivers. The driver set includes support for Novell's NetWare 286 IPX and 386 ODI, 3Com's 3+ Open, Microsoft's LAN Manager, Banyan's VINES, TCP/IP on DOS, Windows, OS/2 and UNIX, Netbios, and Network File System.

Packaged in a 160-pin plastic quad flat package, the controller is made with mixed-mode CMOS technology and operates from 5 V. Samples of the EtherCoupler are available now, along with evaluation boards and sample hardware designs. Production quantities will be available in the second quarter of this year. Prices begin at \$30.60 and \$24.45 each in quantities of 1000 and 10,000, respectively.

*Fujitsu Microelectronics Inc., 77 Rio Robles Ave., San Jose, CA 95134-1807; Betsy Taub, (408) 456-1160.*

**CIRCLE 481**

## CHIPSET IMPLEMENTS ALL-DIGITAL PHONE AND ANSWERING MACHINE

Intended to displace mechanical tape drives in telephone-answering machines, a chip set for integrated all-digital phones and answering machines from DSP Group stores both outgoing and incoming messages in dynamic RAM. The D6055A chipset is based on the company's proprietary Digital SpeakerPhone speech-processing algorithms running on the TMS320 digital-signal processor (DSP) from Texas Instruments Inc.

Besides the TMS320 DSP chip (64-pin PQFP), the chipset consists of an ASIC (80-pin PQFP), an analog I/O interface (16-pin DIP), and from 1 to 16 Mbits of audio RAM (ARAM). The combined chips and speech-processing algorithms eliminate the problems that are associated with common speakerphone operation—in particular, one-

way communication, blocking, and word cut-off, to afford comfortable communications that can simulate regular two-way conversation.

Under control of a host microcontroller, the DSP provides voice-activated switching (VOX) functions, receive and transmit dual-tone, multiple-frequency signaling, line monitoring, speech compression, error coding, echo cancellation, and command decoding. The ASIC controls and refreshes the ARAM, and provides interfaces to the host processor, the analog I/O interface chip, and to external static RAM which stores calculation coefficients and phone numbers. The analog I/O interface performs A-D and D-A conversion, converts 14-bit linear code to 8-bit  $\mu$ -Law PCM code, and interfaces to the analog front-end of the speakerphone. Computer-controlled digital storage al-

lows for advanced features such as multiple mailboxes and message forwarding, enabling a speakerphone to perform as a personal voice-mail system.

The D6055A provides all the level detectors, attenuators, and switching control that are necessary for proper speakerphone operation. Detection sensitivity, path attenuation, and switching speed can be controlled by the host. Gain distribution between the transmit and receive paths is optimized to the inputs from the VOX level detectors.

These circuits control the transmit and receive paths to provide the half-duplex operation required in a speakerphone. Total loop-gain attenuation is programmable in 4-dB increments from 12 to 40 dB. Pricing for the D6055A chipset ranges from \$18 to \$25 each in high volume.

*DSP Group Inc., 4050 Moorpark Ave., San Jose, CA 95117; (408) 985-0722*

**CIRCLE 482**

■ MILT LEONARD

## NEW PRODUCTS

PACKAGING

### IEEE-488



Control any IEEE-488 (HP-IB, GP-IB) device with our cards, cables, and software for the PC/AT/386, EISA, MicroChannel, and NuBus.

### PC ENCLOSURE STANDS UP TO HARSH ENVIRONMENTS

The A-bus is a toughened enclosure that offers a rugged and safe housing for industrial PCs. High-integrity shielding techniques, such as seam-welded construction, help deliver a system housing that can meet the most stringent electromagnetic compatibility standards. The enclosure is a 4U-high, 19-in. rack that comes ready to use with an integral backplane, power supply, and cooling fans. Different configurations are available, including six or twelve slots. The enclosure can be fitted with full RFI gasketing and high-attenuation cutoff air filters to supply immunity from noise and unwanted emissions. Some accessories are available, including a front-panel with a two-digit diagnostic display that links directly to the CPU card. This simplifies fault finding and maintenance.

*Arcom Control Systems Ltd., Units 8-10 Clifton Rd., Cambridge, England CB1 4WH; (0223) 411 200. CIRCLE 460*

### COLD-FORMED PGA SOCKET SAVES COST

A line of precision cold-formed PGA sockets offer consistent performance and a cost-saving potential of up to 30% compared with screw-machined sockets. The Series MD sockets can be used interchangeably with screw-machined sockets and incorporate the company's Omni-Tact seamless beryllium copper, low-insertion-force, four-tine contacts to get a high-reliability contact system. Five of the most popular grid sizes from 11 by 11 to 11 by 17 are available, as well as eight of the higher volume footprints, with pin counts covering 68 to 168 positions. Electrical characteristics include a 10-mΩ bulk contact resistance, 3-A contact rating, and 2-pF contact-to-contact capacitance. Prices


range from \$0.010 to \$0.018 per line in large lots. Delivery is from two to four weeks.

*Mark Eyelet Inc., 63 Wakelee Rd., Wolcott, CT 06716; (203) 756-8847.*

**CIRCLE 461**
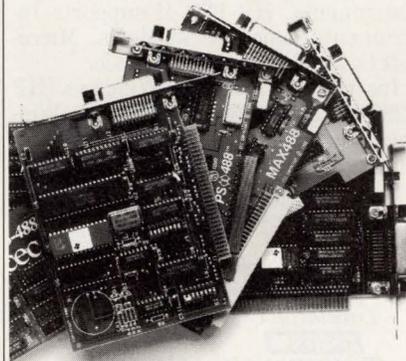
### SURFACE-MOUNT MCM IS TWO-FACED

Higher levels of functionality in one package are now possible with a standard surface-mountable multichip-module (MCM) package. The package



You get fast hardware and software support for all the popular languages. A software library and time saving utilities are included that make instrument control easier than ever before. Ask about our no risk guarantee.

features dual-sided mounting capability for semiconductor die. The MCM features high-density, thick-film wiring technology that permits up to three conductor layers on each side of the ceramic substrate. Almost any type of IC may be mounted in the package. Housed in a 168-pin plastic quad flat pack, the MCM offers a lead pitch of 0.8 mm and measures 1.5 by 1.5 in. Power dissipation is up to 3 W with still air at 70°C. Samples are available in eight weeks with volume quantities in 12 to 16 weeks. NRE charges typically range from \$5000 to \$15,000.

*Fujitsu Microelectronics Inc., IC Division, 3545 N. First St., San Jose, CA 95134-1804; (800) 642-7616. CIRCLE 462*

### USE THERMAL-TRANSFER PRINTER IN-HOUSE

A thermal-transfer printing system and a full line of label materials is avail-

able for OEMs requiring in-house, on-demand label printing. The system's Bradyprinter THT model 203 thermal-transfer printer produces clear identification for boards, wires, flat-ribbon cables, rating plates, and other general-use applications. The company's Thermatab labels accept high-density printing of bar codes, graphics, and text, and withstand chemicals, solvents, extreme temperatures, and repeated handling. Call for pricing and delivery information.

*W. H. Brady Co., Industrial Products Div., P. O. Box 2131, Milwaukee, WI 53201; (800) 537-8791. CIRCLE 463*

### FINE-PITCH SOLDERING COMES TO ITS SENSES

A soldering system designed for fine-pitch surface-mounted work is available with a 0.010-in. stainless-steel soldering tip that heats up in less than 1 second. The MicroSol 9001 system's tool has a thermocouple at the tip that senses the temperature and controls the applied heat. The tip temperature, digitally displayed, is continuously adjustable from 400 to 800°F. A panel switch selects among touch-control, continuous, or idle operating modes. Pricing for the main unit starts at \$625, and individual tips start at \$24.50. Call for delivery information.

*Analytic Technology, 15233 N. E. 90th St., Redmond, WA 98052; (800) 428-2808. CIRCLE 464*



Free: Informative catalog 800-234-4232 Applications help (617) 273-1818

**cec**

Capital Equipment Corp.  
Burlington, MA. 01803


CIRCLE 94 FOR U.S. RESPONSE  
CIRCLE 95 FOR RESPONSE OUTSIDE THE U.S.

## WINDOWS TOOLS SIMPLIFY TEST DEVELOPMENT

With its many I/O commands, HP Instrument Basic for Windows is the only Windows-based language designed specifically for measurement applications. The language combines an extensive command set with built-in tools for engineering graphics and user interfaces. The language can control both HP-IB (IEEE-488) and RS-232C instruments.

A companion product, HP-IB for Windows and DOS, supplies software utilities and interface hardware for instrument-control applications. The utilities complement many Windows and DOS programming languages, giving the user flexibility in test development.

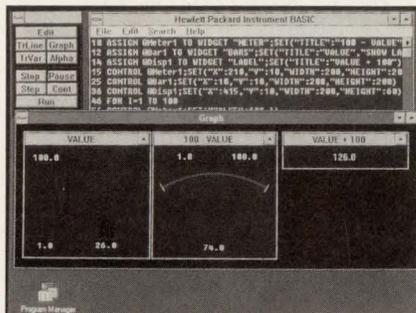A third product, HP ITG (Interactive Test Generator) II, provides an interactive graphical environment that speeds development of programs to control instruments, make measurements, and analyze and display data. The package includes a library of instrument drivers for 220 HP instruments. It also offers a menu-based driver-writing tool so users can quickly write drivers for other



instruments. HP ITG II supports Instrument Basic for Windows, Microsoft C, QuickC, and QuickBasic.


Instrument Basic for Windows (HP E2200A) costs \$395. HP-IB for Windows and DOS (HP 82335B), which includes software utilities, documentation, and an HP-IB interface card, costs \$525. HP ITG II (HP E2020B) goes for \$1495.

*Hewlett-Packard Co. Measurement Systems Operation, P. O. Box 301, Loveland, CO; (800) 452-4844.*

**CIRCLE 465**

■ JOHN NOVELLINO
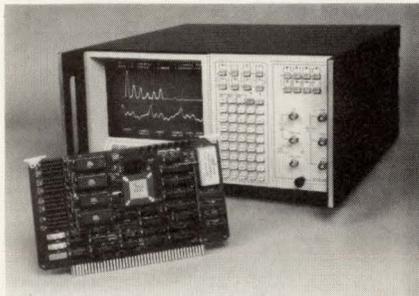
## DSP OPTION BOOSTS WAVE ANALYZER PERFORMANCE



A high-speed digital signal processor (DSP) option for the Model 6100 waveform analyzer increases the instrument's performance by a factor of more than 300. The Model 683 is a user-installable board that employs a 25-MFLOP, 32-bit floating-point DSP that is slaved directly to the Model 6100. Data is exchanged by fast direct memory access and simultaneous register transfers. The board can process time- or frequency-domain records as large as 32-kpoints in real time. The Model 683 works with any of the analyzer's more than 50 mathematical operations. It computes and displays an 8-kpoint FFT in milliseconds, and a computa-

tion-intensive 16K-by-16K cross-correlation analysis within 1 sec. The Model 683 costs \$2995 and is available from stock.

*Analogic Corp., 8 Centennial Dr., Peabody, MA 01961; (508) 977-3000.*

**CIRCLE 466**

## CARD SIMULTANEOUSLY SAMPLES 4 CHANNELS

The PC-414A analog input board is suited for applications that need multiple analog channels sampled simultaneously. The board has four simultaneous sample-and-hold amplifiers multiplexed into a 1.5-MHz, 12-bit analog-to-digital converter. The unit runs in IBM PC/AT, PS-30, EISA, and compatible computers. In 4-channel mode each channel can be sampled at 250 kHz. Single-channel sampling can extend to 1.5 MHz. Total harmonic distortion is -72 dB. Optional software includes a windowed setup-and-go program and a source code library. PC-414A prices start at \$1850 for single-unit quantities. OEM discounts are available. Delivery is from stock to 4 weeks.

*Datel Inc., 11 Cabot Blvd., Mansfield, MA 02048; (508) 339-3000.* **CIRCLE 467**

## LOGIC ANALYZER GETS FAST CAPTURE SYSTEM

A new capture system, called Paladin, adds 200-MHz synchronous data capture and capability for 1-GHz synchronous timing analysis to the ML4400 logic analyzer. The system can be added to an existing ML4400 without degrading any other features.

Paladin's three operating modes offer the user flexibility. The basic mode provides 100 channels at 100 MHz or 50



channels at 200 MHz, both synchronously and asynchronously. This mode includes eight clock inputs with full Boolean, master-slave, or double-edge clocking. In the split mode Paladin offers 80 channels of 100-MHz synchronous data collection along with 20 asynchronous channels. In the high-speed mode the system supplies 10 asynchronous channels at 1 GHz and 20 asynchronous channels at 500 MHz. Multiple modules can be connected together.

Users can connect high-speed, coaxial, tip-compensated probes to the target system in several ways. Special probe connectors, which include the compensation elements, support hook connection, as well as one- or two-wire and socket connection. Channel-to-channel skew is less than 1 ns at 1 GHz. Each module comes with five active-element logic pods, each accommodating 20 data probes and two clocks. An available adapter allows the use of all microprocessor support packages for the ML4400 line. Paladin includes both classical and transitional clocks as well as a 24-bit time stamp.

Paladin, including 100 probes, costs \$13,950. Base price for a complete analyzer system starts at \$17,945.

*American Arium 14281 Chambers Rd., Tustin, CA 92680; (714) 731-2138.* **CIRCLE 468**

■ JOHN NOVELLINO


## SURFACE-MOUNTED CRYSTALS AND OSCILLATORS REACH 300 MHz

A family of four surface-mounted crystals and oscillators have output frequencies from 625 kHz to 300 MHz. The devices have applications in telephone and radio communication products and in high-speed ECL and GaAs logic circuits.

Three of the family are fundamental quartz resonators, two of which, the HC-49 and TT-SMD lines, are produced from ultra-small AT-strip crystals. These devices are available from 3 to 50 MHz. The HC-49 comes in a metal SMD can and the TT-SMD comes in a plastic SMD package. The third quartz resonator, the HC-45, is made using the larger-but-higher-performance AT-cut crystal. Frequencies range from 3.579545 MHz (for TV color burst) to 300 MHz (for high-speed logic).

The HC-45 resonator is made by taking the AT-cut crystal form, extracting its ninth harmonic, and packaging it in what would typically be a through-hole metal can. The leads are cut and formed for surface mounting, and a clip is applied that permits mounting the device and soldering it flat on a pc board.

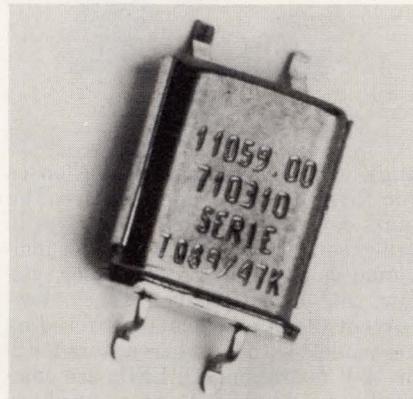The fourth part, model CO-99100, is a complete, integrated SMD clock-oscil-




lator circuit with an internal AT-cut crystal. The unit operates from 625 kHz to 24 MHz and is mounted in a 28-pin PLCC. It delivers a square-wave output with TTL fanout of 10, or 50 pF of high-speed CMOS loading.

Pricing in lots of 1000 is \$0.70 for the HC-49, \$0.90 for the TT-SMD, \$0.75 to \$0.95 for the HC-45, and \$2.50 for the CO-99100. All are available from stock to 12 weeks.

**Raltron Electronics Corp.**, 2315 N.W. 107th Ave., Miami, FL 33182; (305) 593-6033. **CIRCLE 469**

■ DAVID MALINIAK

## LED LIGHT BARS OFFER HIGH BRIGHTNESS

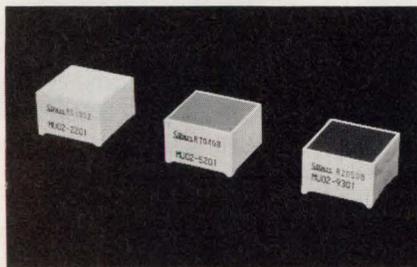


Super brightness, long life, and low power consumption are featured in a line of LED light-bar modules. Various combinations of shape, size, and color are available to suit many display applications. Brightness levels up to 42 mcd/unit are attainable. Package styles include square, rectangular, round, SIPs, and DIPs. Colors include red, orange, yellow, green, and pure green. Call for pricing and delivery.

**Il Stanley Co. Inc.**, 2661 Gates Ave., Irvine, CA 92714; (800) 533-5231.

**CIRCLE 470**
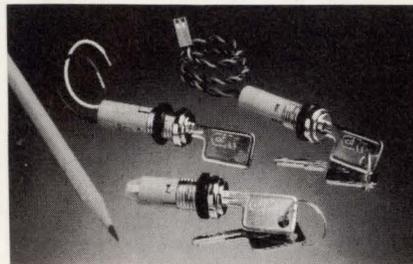
## MINI POWER SWITCHLOCKS FIT 12-MM PANEL HOLES

A space-saving miniature power switchlock that fits 12-mm-diameter panel holes addresses the need for a small, good-looking key-operated



switch. The YM Series switchlock offers 0.110-in. quick-connect terminals or wire-lead terminations. Switch function is single-pole, single-throw on-off. Silver-plated contacts are rated for 4 A at 125 V ac or 28 V dc. Prices start at \$5.71 in lots of 1000. Delivery is in six weeks.

**C&K Components Inc.**, 15 Riverdale Ave., Newton, MA 02158-1082; (617) 964-6400. **CIRCLE 471**

## SMD RESISTORS HAVE HIGH STABILITY

Available in values as low as 1  $\Omega$ , precision thick-film resistors in the new RC12 range from Philips Components feature excellent high-frequency performance, high stability and small case size. Their 1% tolerance, low temperature coefficient and availability in values of up to 1 M $\Omega$  suit them for use in a wide range of analog circuit applications where precision and surface-mount miniaturization need to be combined—for example, in hand-portable communication equipment and high-frequency test and measuring instruments.

RC12 resistors are housed in an industry-standard 0805 package measuring 2.0 by 1.25 by 0.6 mm, and are available with temperature coefficients of 50 parts per million/ $^{\circ}$ C or 100 ppm/ $^{\circ}$ C for values above 10  $\Omega$ . Their low temperature coefficient, combined with good temperature tracking, allow them to maintain their precision in equipment that is subject to wide temperature variations. The RC12H type of resistors cover the resistance range from 1  $\Omega$  to 1 M $\Omega$ , while the RC12G types range in value from 100  $\Omega$  to 1 M $\Omega$ .

The RC12 resistors sell for around \$1.10 per 100 devices in high-volume quantities. Delivery time is about six weeks after receipt of order.

**Philips Components, Discrete Products Div.**, 2001 West Blue Heron Blvd., Riviera Beach, FL 33404-5099; (407) 881-3257 (Miriam Coleman).

**CIRCLE 472**

## PALMTOP LCD DISPLAY IS CGA-COMPATIBLE

A 640-by-200-dot, CGA-compatible LCD module is available for the fast-growing palmtop-computer market. The TCM-A9108 display features a metal bezel for ruggedness, measures just 215.0 mm wide by 99.0 mm tall by 6.3 mm deep, and weighs only 190 g. Dot pitch is 0.27 mm by 0.36 mm, which lends the display to alphanumeric characters as well as special characters, graphs, patterns, and charts. The display incorporates formulated-twisted-nematic, liquid-crystal technology and a 1/200 duty ratio for high contrast and fast response time. Average power consumption is 130 mW. Samples, available now, cost \$240. Call for delivery and OEM pricing.

**Epson America Inc., OEM Div.**, 20770 Madrona Ave., Torrance, CA 90503; (310) 787-6300. **CIRCLE 473**

## NEW PRODUCTS

COMPONENTS


### QUIET CERAMIC CAPS HAVE BEST ESR IN CLASS

A line of chip capacitors has the industry's best equivalent series resistance (ESR) in its price class, its manufacturer says. The MCH Series capacitors' NPO/C0G "A" dielectrics are fabricated with pure palladium electrodes and fired at higher temperatures than those of competing ceramic chips. Also, the chips are made in Class 10 clean-room conditions with highly accurate electrode alignment. The chips come in 0805 and 1206 sizes with a capacitance range of 0.5 to 2700 pF for NPO dielectrics, and 680 pF to 0.22  $\mu$ F for X7R dielectrics. Prices range from \$15.80 to \$45.10 in lots of 1000. Delivery is from stock to 10 weeks.

**Rohm Corp., 3034 Owen Dr., Antioch, TN 37013; (615) 641-2020. CIRCLE 474**
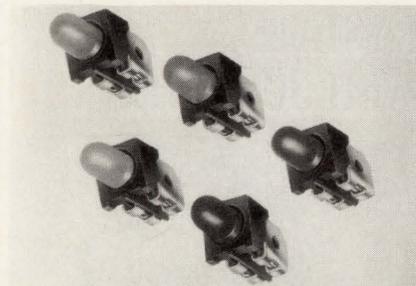
### SURFACE-MOUNT LEDs HAVE HIGH BRIGHTNESS

A line of right-angle, surface-mounted LEDs features high brightness, wide-




angle visibility, and high-profile lenses for through-panel applications. The units come in T-1 and T-1-3/4 sizes in red-green bicolor style and in five individual colors (red, green, amber, yellow, and blue). High-efficiency, low-current (2-mA) models are offered as are models with built-in resistors for 5- or 12-V operation. All LEDs are compatible with infrared and vapor-phase soldering, and have standoffs for easy cleaning. Pricing starts at \$0.78 in lots of 1000. Small quantities are delivered from stock.

**Industrial Devices Inc., 260 Railroad Ave., Hackensack, NJ 07601; (201) 489-8989. CIRCLE 475**
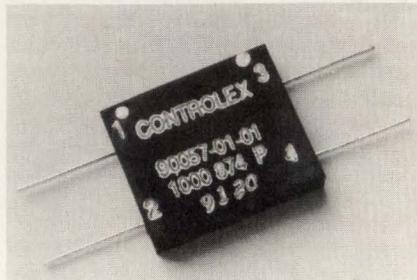
### SMD PULSE TRANSFORMER HANDLES 2500 V/ $\mu$ S


A family of low-profile pulse transformers occupies just 0.65 by 0.85 in., stands only 0.2 in. tall, and is suitable for either surface- or through-hole mounting. Thanks to a proprietary



winding geometry and a high flux-density core, the transformers support 2500 V/ $\mu$ s voltage changes while delivering rise times of under 100 ns. Applications are in dc-ac inverters, ac-power controllers, pulse-width modulators, and high-frequency power transformation. Typical pricing is in the \$25 range for OEM lots. Delivery is from stock to 60 days.

**Controlex Corp., 16005 Sherman Way, Van Nuys, CA 91406; (818) 780-8877. CIRCLE 476**
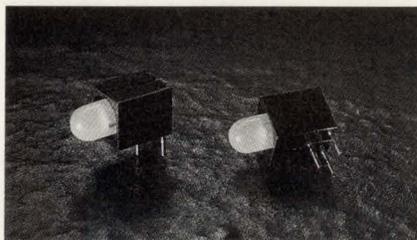
### BICOLOR INDICATOR SHUNS RED FOR YELLOW






Not everyone needs a bicolor indicator in red and green—some applications call for "waiting" and "active" indication rather than go/no go. That's the need addressed by the Series 550-3605 three-leaded yellow-green indicator. The single right-angle, 5-mm package eliminates multiple lamp requirements and simplifies drive circuitry. One possible application might be a LAN-controller card that uses the indicator to signal that a channel is either available or in use. The LEDs are packaged in a black housing for optimal contrast ratio and increased visibility. Pricing is \$0.97 in lots of 1000. Delivery is from stock to eight weeks.

**Dialight Corp., Dept. C550-36, 1913 Atlantic Ave., Manasquan, NJ 08736; (908) 223-9400. CIRCLE 477**
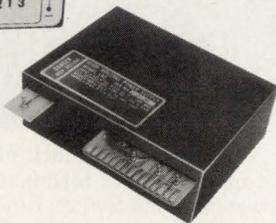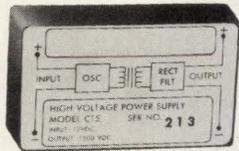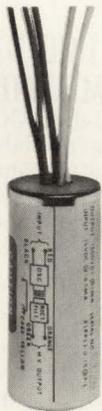
### MINIATURE PHOTODETECTOR POWER SUPPLIES

For  
Photomultiplier Tubes & Photodiodes

Short Circuit & Reverse Polarity Protected  
Mounts On Printed Circuit Boards  
Input & Output Floating  
Small & Lightweight  
Excellent Stability  
Low Ripple



#### Ferranti Venus

399 SMITH STREET, FARMINGDALE, N.Y. 11735  
(516) 293-4100 • TWX: 510-224-6492 • FAX: 516-752-7976

CIRCLE 100 FOR U.S. RESPONSE  
CIRCLE 101 FOR RESPONSE OUTSIDE THE U.S.


## NEW PRODUCTS

COMPUTER BOARDS
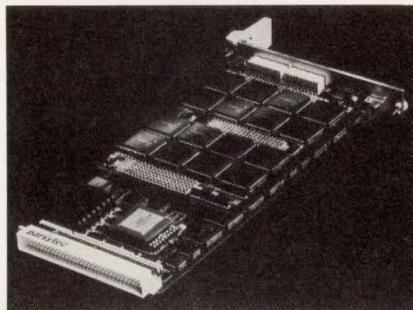
### TRANSPUTER-BASED SYSTEMS GET EXPANDED I/O FUNCTIONS

**W**ith the introduction of the Transputer Imaging Processing (TIP) I/O architecture, users can combine unlimited scalability of a Transputer-based system with 100-Mbyte/s data distribution over each TIP broadcast bus. Multiple independent broadcast subsystems can be integrated into one system to increase the total I/O bandwidth required for any application. While the name denotes image processing, the TIP I/O architecture is suitable for any application requiring the increased bandwidth.

The TIP bus transmits data simultaneously, in parallel, to multiple Transputer nodes using the broadcast function. It can also function in a gathering mode for applications where distributed data must be accessed in total for display or subsequent processing. Using 48 T805 nodes and a TIP interface, 100-MFLOPS, 750-MIPS performance can be achieved. The balance between I/O and processing capabilities enables TIP-based systems to perform real-time processing and fast Fourier trans-




forms over data channels.

The TIP-based series of boards now includes the TIP-VPU/T8 T805 processor board, the TIP-MFG monochrome frame grabber, and the TIP-CGD color graphics display board. The TIP-VPU/T8 (1 Mbyte DRAM) sells for \$4600, the TIP-MFG costs \$5200, and the TIP-CGD is priced at \$5800. Systems designed with the TIP technology start at \$6950.

*Parsytec Inc., Bldg. 9, Unit 60/61,  
245 W. Roosevelt Rd., West Chicago,  
IL 60185. **CIRCLE 478***  
■ RICHARD NASS
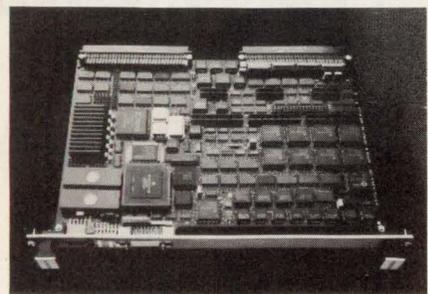
### 68030-BASED VMEBUS I/O BOARD HAS 18 RS-232 PORTS

**D**esigned around a 68EC030 microprocessor, the HK68/VSIO VME serial interface board from Heurikon furnishes users with 18 RS-232 I/O ports. They are all based on



Zilog's Z85C30 serial I/O controller. Featuring a software controllable bit-rate generator, the Z85C30 supports asynchronous transfer rates up to 56 kbits/s and synchronous transfer rates up to 1 Mbit/s.

Sixteen of the I/O ports are accessed through the board's VMEbus P2 connector. They support sixteen asynchro-

nous ports with four lines each or ten synchronous ports, each with six lines. The remaining two ports are accessed through the front panel and can be operated in either an asynchronous or synchronous mode.

The HK68/VSIO can hold up to 4 Mbytes of DRAM and up to 2 Mbytes of EPROM. It can operate either as a slave or a master on the VMEbus. It supplies a full VMEbus interface, including 32-bit addresses and data, seven bus interrupts, and system-level control functions. Plug-over module connectors are supplied to support custom serial I/O interfaces such as RS-422, RS-485, or V.35, or front-panel I/O. The board also features a user-programmable seven-segment display that can indicate the status of the system, board or CPU. With 1 Mbyte of RAM, the HK68/VSIO sells for \$2195 and is available now.

*Heurikon Corp., 8000 Excelsior Dr.,  
Madison, WI 53717; (608) 831-  
0900. **CIRCLE 479***  
■ RICHARD NASS

## CLASSIFIEDS

### EMPLOYMENT OPPORTUNITIES

#### SENIOR ELECTRONIC DESIGN ENGINEER

Design, develop, and modify electronic instruments using analog transducers and microprocessor controls to measure gas airflow, temperature, humidity, and pressure using principles of fluid mechanics. Will design and develop low power circuits to be embedded into such instrumentation by using precision operational amplifiers, switching power supplies, and embedded microprocessors. Will develop digital signal processing schemes for spectrum analysis. Will develop procedures leading to radio and electromagnetic frequency compliance. Will write assembly, calibration and inspection procedures. Requires Master of Science degree in Electrical Engineering. Also requires two years experience in the job to be performed or two years experience as a Research Assistant. If experience is in related field, entire experience must include design, development, and modification of complex electronic circuits using microprocessors to develop electronic instrumentation used to measure air flow and air temperature. Hours: 8:15am-4:45pm. 40 hours per week at \$17.89 per hour salary. Must have proof of legal authority to work permanently in the U.S. Please send resume to: Illinois Department of Employment Security, 401 S. State St.--3 South, Chicago, IL 60605, ATTN: Bessie M. King, Ref. #V-IL 4126-H, No Calls, 2 copies of your resume required, An Employer Paid Ad.

### BUSINESS SERVICES

#### HARDWARE AND SOFTWARE DEVELOPMENT SERVICES

- We specialize in developing microprocessor/FPGA based products/systems and embedded software development.
- Custom Windows V3.0 and networking software development.
- Can help with part of or handle the entire project.
- Full Microprocessor Development Systems, <sup>2</sup>ICE, CAD/CAM, and PCB layout system.
- Development for LAN, Multibus, VME, PC, MCA, and STD.

**ACT** Applied Computer Techniques, Inc.  
Tel. (407) 851-2525  
Incorporated 1978

#### TECHNICAL WITTS, INC.

Switchmode Power Supply Design  
Software Engineering - Windows, C, C++  
6319 W. Villa Theresa Drive  
Glendale, AZ 85308  
Voice: (602) 439-1833  
FAX: (602) 547-1123

#### FAX YOUR ORDER!

To Advertise in  
Penton Classifieds,

**FAX: (216) 696-1267**

# IEEE 488.2



Hardware for IBM PC/AT, Micro Channel, Sun, Macintosh, DEC, and NeXT.

Software for DOS, UNIX, VMS, menu-driven and icon-driven environments.

IEEE 488 extenders, analyzers, converters, analog I/O, and digital I/O.

Call for your free IEEE catalog



IOtech, Inc. • 25971 Cannon Road  
Cleveland, Ohio 44146 • (216) 439-4091

IO TECH

CIRCLE 417



## Industrial PC Solutions

20-page, solution oriented reference guide detailing a complete line of PC-based industrial automation and control products: industrial PCs, 486/386/286 CPU Cards, RAM/ROM disks, rack mount keyboards and monitor enclosures. All of the latest technology at budget-conscious prices. Call for FREE reference guide (408) 293-6786.


**American Advantech**

ADVANTECH

CIRCLE 404

## Analog Circuit Simulation

SPICE FOR THE PC

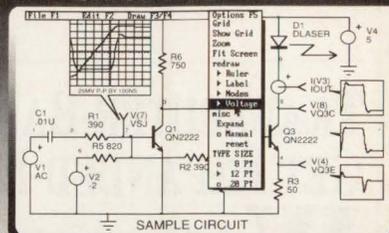

- Schematic Entry • SPICE Simulation
  - Model Libraries • Waveform Graphics
- Intusoft has it all at an Affordable Price!**

INTEGRATED, EASY TO USE SIMULATION ENVIRONMENT, FEATURING:  
A powerful SPICE (IsSPICE) simulator performing AC, DC, Transient, Noise, Fourier, Distortion, Sensitivity, Monte Carlo, and Temperature analyses. Extensive model libraries, Schematic entry, and Waveform processing. Starting at \$95 for IsSPICE, complete systems are available for \$815.

Call Or Write For Your Free Demo and Information Kit!  
**intusoft** P.O. Box 710 San Pedro, CA 90733-0710  
Tel. 213-833-0710 Fax 213-833-9658

INTUSOFT

CIRCLE 414

## MIXED-MODE CIRCUIT SIMULATION

ENTER THE FUTURE OF ANALOG DESIGN!

Upgrade to the power and speed of topSPICEplus

True Analog/Digital/Behavioral Mixed-Mode Circuit Simulator for PC

Introductory Offer \$259

- Complete SPICE analog simulator with extended syntax.
- Fully integrated event-driven logic simulator.
- Analog Behavioral modeling using arbitrary equations, Laplace transforms and look-up tables. • Analog and digital model libraries. • Graphics post-processor.
- Compatible with most SPICE CAE products.



Call or write for FREE DEMO disk  
800-272-0674  
Fax (818) 340-6316


P.O. Box 10358  
Canoga Park, CA 91309, (818) 594-0363

PENZAR DEVELOPMENT

CIRCLE 408

## 68HC11

PC-based emulator for 68HC11

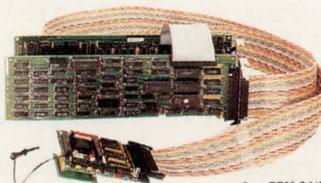

See EEM 91/92  
Pages D 1300-1303

- PC plug-in or RS-232 box.
- Pull-down menus with full window support, combined with command-driven User Interface.
- Up to 16 MHz real time emulation.
- No intrusions to the 68HC11's resources.
- 64 bit wide 16K deep trace. All functions usable without disturbing emulation. Time stamping. Two level trigger.
- Symbolic and C Source Level Debugging, including in-line assembler and disassembler.
- Supports A, D, E, F, G, J, K and L parts

CALL OR WRITE FOR FREE DEMO DISK!  
Ask about our demo video




51 E. Campbell Avenue  
Campbell, CA 95008  
FAX (408) 378-7869

Call 408-378-2912  
Nohau's 24-hour information center to receive info via your FAX

NOHAU CORP.

CIRCLE 407

New!

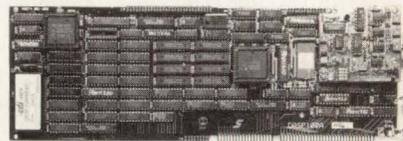

## DASP100A

DATA ACQUISITION & SIGNAL PROCESSING

- ★ 100 MILLION SAMPLES PER SECOND
- ★ 256K SIGNAL MEMORY (EXPAND TO 8 MB)
- ★ 10 MIPS DSP (320C25)
- ★ EXTENSIVE HARDWARE & SOFTWARE SUPPORT
- ★ 3 DATA ACQUISITION MODES
- ★ EXTERNAL CLOCK & TRIGGER

ALSO ASK ABOUT OUR DASP25!



357 N. Sheridan St. #119  
CORONA, CA 91720  
(714) 734-3001  
FAX: (714) 734-4356

SIGNATEC

CIRCLE 405

## DREAM METER



FRONT

BACK

**80% SMALLER MOVEMENT,  
66% FEWER PARTS.**

Core magnet design • Dramatically reduced total volume • Taut band suspension

- Accuracy to ± 1.5% of full scale
- Four sizes • AC and DC versions
- Standards conformance
- Custom Marking Services

**selco PRODUCTS CO.**


7580 Stage Road, Buena Park, CA 90621  
(213) 921-0681 • (800) 229-2332  
FAX (714) 739-1507

SELCO PRODUCTS

CIRCLE 400

## Instant Microcontroller

+  
Instant C  
=  
Instant New Product

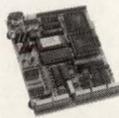

Use our Little Giant™ and Tiny Giant™ miniature microprocessor-based computers to instantly computerize your product. Our miniature controllers feature built-in power supplies, digital I/O, serial I/O (RS232 / RS485), A/D converters (to 20 bits), solenoid drivers, time of day clock, battery backed memory, watchdog, field wiring connectors, and more! Designed to be easily integrated with your hardware and software. Priced from \$159. Core modules as low as \$59. Low cost, interactive Dynamic C™ makes serious software development easy.


**Z-World Engineering**

1724 Picasso Ave., Davis, CA 95616 USA  
Tel: (916) 757-3737 Fax: (916) 753-5141  
Automatic Fax: (916) 753-0618  
(Call from your fax, request catalog #18)

Z-WORLD ENGINEERING

CIRCLE 406

## GraphiC 6.0

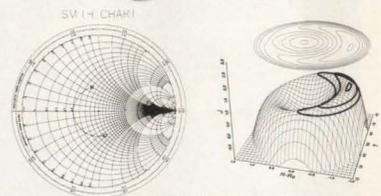

"All of the C language routines you need to write an impressive scientific graphing program of your own. Highly Recommended."

—PC Magazine

- Linear, log, polar plots
- 3-D curves & surfaces
- Shaded contour plots
- Smith and 3-D bar Charts
- '286-extender version
- Output Tek 4105, HPGL/2, color PostScript, PIC, GEM
- TIGA, DGIS, 8514, VGA
- Source code for full control
- Licensed for personal use

**Scientific Endeavors**

508 North Kentucky St., Kingston, TN 37763  
(615) 376-4146 FAX: (615) 376-1571

SCIENTIFIC ENDEAVORS

CIRCLE 410

## Tap a reliable source of DSP-based imaging solutions with the DSP32C Imaging Board

- 25 Mflop AT&T DSP32C.
- PC/AT plug-in board.
- On-board frame grabber (Brooktree).
- 256K Bytes VRAM and up to 640K x 32 SRAM.
- Library of imaging routines.



Putting DSP to work

Spectrum Signal Processing, Inc. 1-800-663-8986 (Western US)  
1-800-323-1842 (Eastern US) or 604-438-7266 (Canada).

SPECTRUM SIGNAL PROCESSING CIRCLE 402



**FREE!**  
**120**  
**Page**  
**Catalog**  
-----  
**"Optics**  
**for**  
**Industry"**

ROLYN OPTICS supplies all types of "Off-the-Shelf" optical components. Lenses, prisms, mirrors, irises, microscope objectives & eyepieces plus hundreds of others. All from stock. Roly also supplies custom products & coatings in prototype or production quantities. Write or call for our free 120 page catalog describing products & listing off-the-shelf prices. **ROLYN OPTICS CO.**, 706 Arrowgrand Circle, Covina, CA 91722, (818) 915-5707 & (818) 915-5717. TELEX: 67-0380. FAX: (818) 915-1379.

ROLYN OPTICS CIRCLE 401



### RS232 EE/EPROM, MICRO & MEMORY CARD PROGRAMMER \$345/495

- Programs EE/Proms, Flash Eproms, ZPRams, Intel Micros, Memory Cards.
- Stand-Alone Mode for EE/Proms and Memory Card Duplication / Verify.
- All 24/28/32 pin EE/Proms to 8 MBits (upgradable to 32 Megabits).
- Micros: 8741A, 2/A, 4, 8, 9, 51, C51, C51A/B, 52, 53, 55, C521, C541, 9761.
- Accepts dedicated modules: Memory Card Programming Module (Seiko/Epson) - \$145, Eraser/Timer Module - \$50, Gang Module (4 sockets) - \$145. Simultaneously duplicates up to 5 devices in stand-alone mode (with Gang).
- Can be operated with any computer containing an RS-232 serial port.
- User friendly Menu-Driven Interface Program for IBM-PC or compatible.
- Full 1 year warranty. Customer support via voice line, fax or dedicated BBS.

### INTELLIGENT ROM EMULATOR \$445

- Emulates 2716 through 27512 EProms with a single unit. Access time 120ns.
- Connects to the standard parallel printer port via a standard printer cable.
- User friendly software. Command set includes: Load(data), Write(data), Display(memory), Type(of EProm), Edit(memory), Calculator, Reset(target system), Activate(debugging feature), Monitor(selected feature).
- Address Compare with Halt output, Address Snapshot, Trigger input.
- Fast data loading via parallel printer port (64k bytes in less than 10 sec).
- Caseloadable up to 8 units. Includes target cable with Trigger/Reset/Halt clips.
- CMOS RAM chips with rechargeable NiCad battery backup.

MC / VISA / AMEX All prices are U.S. list only.



B&C MICROSYSTEMS CIRCLE 413

## Tango®

The Complete Electronic Design Solution.

For FREE evaluation software and product specs, call 800 488-0680



Tango, the leader in PC-based tools for:



- Schematic entry
- PCB layout and autorouting




- PLD design
- Simulation, timing verification and thermal reliability



ACCEL Technologies, Inc.  
6825 Flanders Drive  
San Diego, CA 92121-2986  
Service 619 554-1000  
Fax 619 554-1019

ACCEL TECHNOLOGY CIRCLE 412

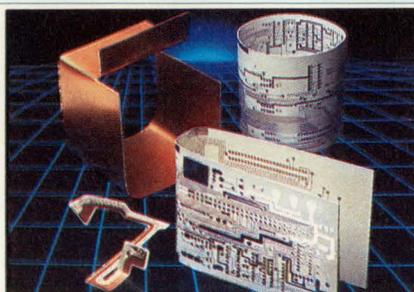

### WE'RE BENDING THE RULES FOR CIRCUIT DESIGNERS

BEND/FLEX™, the bendable circuit board material that's flexible enough to bend into any multi-plane shape. Eliminates stiffener boards, flexible hardboard connectors, and may reduce the cost of two - and three - plane interconnection systems by as much as 30%!

ROGERS CORP.  
COMPOSITE MATERIALS DIVISION  
One Technology Drive, Rogers, CT 06263

ROGERS CORP. CIRCLE 409

## PRECISION JACK SCREWS



Globe's precision jack screws are available from stock in either American or Metric standards.

Finishes include color chromate (Type 2).

Globe will also fabricate a jack screw to your specifications.

Call, write or fax to receive Globe's NEW, FREE comprehensive 240-page catalog on jack screws and our complete line of electronic hardware.



GLOBE ELECTRONIC HARDWARE  
34-24 56TH STREET • WOODSIDE, NY 11377  
(800) 221-1505 • NEW YORK: (718) 457-0303  
FAX: (718) 457-7493

GLOBE ELECTRONIC CIRCLE 403

## RELIABILITY PREDICTION SOFTWARE


### ARE YOUR PRODUCTS RELIABLE?

The RelCalc 2 Software Package predicts the reliability of your system using the part stress procedure of MIL-HDBK-217E, and runs on the IBM PC and full compatibles. Say goodbye to tedious, time consuming, and error prone manual methods! RelCalc 2 is very easy to use, and features menu windows, library functions, global editing for what-if? trials, and clear report formats. Try our Demo Package for \$25.

T-CUBED SYSTEMS, 31220 La Baya Drive # 110, Westlake Village, CA 91362. (818) 991-0057 • FAX: (818) 991-1281

T-CUBED SYSTEMS CIRCLE 415

## Interactive/Real-Time

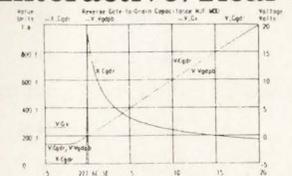

**ECA-2**  
Engineering a Better Way

### Analog Circuit Simulation


- AC, DC, Transient, Fourier, Temperature, MonteCarlo and/or Worst-Case Analysis • Interactive or batch modes
- Full nonlinear simulation • On-line real time graphics
- Multiple plots • 2 to 50 times faster than SPICE
- Component optimization sweeping • New 424 pg. manual

All the Features, Twice the Speed at Half the Cost

Call for FREE DEMO!



TATUM LABS, INC. CIRCLE 411

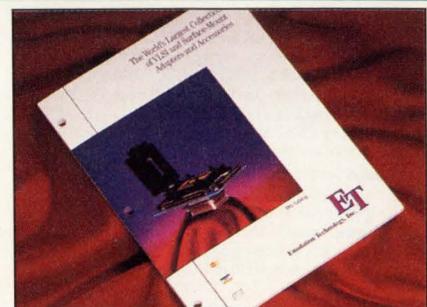

## Free Catalog

The World's Largest Collection of Adapters & Accessories for VLSI/Surface Mount Devices

- Emulator Pods & Adapters
- Debugging Accessories
- Debug Tools
- Prototyping Adapters
- Programming Adapters
- Custom Engineering
- Socket Converters

Emulation Technology, Inc.  
2344 Walsh Ave. Santa Clara, CA 95051  
Phone: 408-982-0660 FAX: 408-982-0664



EMULATION TECHNOLOGY CIRCLE 416

# ELECTRONIC DESIGN

**Chairman and CEO:** Sal F. Marino  
**President and COO:** Daniel J. Ramella  
**President, Electronics Group:** James D. Atherton

**Advertising Sales Staff**

**Publisher:** Paul C. Mazzacano  
 Hasbrouck Heights, NJ; (201) 393-6060  
 San Jose, CA; (408) 441-0550

**National Sales Manager:** Andrew M. Dellins  
 San Jose, CA; (408) 441-0550

**General Manager, European Operations:** John Allen  
 Four Seasons House  
 102B Woodstock Rd., Witney, Oxford OX8 6DY England  
 Phone: 0993-778-077 FAX: 44-993-778-246

**Hasbrouck Heights:** Judith L. Miller, Robert Zaremba  
**Sales Support Supervisor:** Betsy Tapp  
 611 Route # 46 West, Hasbrouck Heights, NJ 07604;  
 Phone: (201) 393-6060 TWX: 710-990-5071

**Boston:** Ric Wasley  
 400 Fifth Ave., Waltham, MA 02154;  
 Phone: (617) 890-0891 FAX: (617) 890-6131

**Colorado:** Lou Demeter (408) 441-0550

**Chicago/Midwest:** Russell Gerches  
**Sales Assistant:** Susan Johnson  
 2 Illinois Center Bldg., Suite 1300  
 Chicago, IL 60601; (312) 861-0880  
 FAX: (312) 861-0874

**Arizona:** James Theriault (408) 441-0550

**Los Angeles/Orange County/San Diego:** Ian Hill  
**Sales Coordinator:** Debi Neal  
 16255 Ventura Blvd., Suite 300  
 Encino, CA 91436; (818) 990-9000  
 FAX: (818) 905-1206

**Pacific Northwest:** Bill Giller (408) 441-0550

**San Jose:**

Lou Demeter (408) 441-0550  
 Bill Giller (408) 441-0550  
 James Theriault (408) 441-0550  
**Sales Administrator:** Amber Hancock  
 2025 Gateway Pl., Suite 354  
 San Jose, CA 95110; (408) 441-0550  
 FAX: (408) 441-6052 or (408) 441-7336

**Texas/Southeast:** Bill Yarborough  
 12201 Merritt Dr., Suite 220, Dallas, TX 75251;  
 (214) 661-5576 FAX: (214) 661-5573

**Direct Connection Ad & DAC Sales Representative:**  
 Jeanie Griffin (201) 393-6080

**Canada:** Tony Chisholm  
 Action Communications  
 135 Spy Court, Markham, Ontario L3R 5H6  
 Phone: 416-477-3222 FAX: 416-477-4320

**Netherlands:** W.J.M. Sanders, S.I.P.A.S.  
 Oosterpark 6-P.O. Box 25  
 1483 DeRyp, Holland Phone: 02997-1303  
 Telefax: 13039 SIPAS NL Telefax: (02997)-1500

**France, Belgium, Spain:** Claude Brill  
 IMS Paris, c/o IDG Communications France  
 Cedex 65, 92051 Paris la Defense—France  
 Phone: 33 149 047 900 FAX: 33 149 047 878

**Germany, Austria, Switzerland:** Friedrich Anacker  
 InterMedia Partners GmbH  
 Katernberger Strasse 247, 5600 Wuppertal 1  
 West Germany Phone: 02-02-711-091/92

**Hong Kong:** Tom Gorman, China Consultant Intl.  
 Guardian Hse, Ste 905  
 32 Oi Kwan Road, Happy Valley, Hong Kong  
 Phone: 852 833 2181 FAX: 852 834 5620

**Israel:** Igal Elan, Elan Marketing Group  
 22 Daphna St., Tel Aviv, Israel  
 Phone: 972-3-6952967 FAX: 972-3-268020  
 Toll Free in Israel only: 177-022-1331

**Italy:** Cesare Casiraghi, Casiraghi Cesare, S.A.S.  
 Via Cardano 81 1, 22100 Como, Italy  
 Phone: 39 31 536 003 FAX: 39 31 536 007

**Japan:** Hirokazu Morita, Japan Advertising Communications  
 New Gunza Buiding 3-13  
 Gunza 7-chome, Chuo-Ku, Tokyo 104 Japan  
 Phone: 011-81-3-3571-8748 FAX: 011-81-3-511-8710

**Korea:** Young Sang Jo, Business Communications Inc.  
 K.P.O. Box 1916, Midopa Building 146,  
 Dangu-Dong, Chonggo-Ku, Seoul, Korea  
 Phone: 011-82-2-739-7840 FAX: 011-82-2-732-3662

**Singapore, Australia, New Zealand:** Omer Soker  
 Media Development Ltd., 17B Washington Plaza  
 230 Wanchai Road, Hong Kong  
 Phone: 834-5978 FAX: 893-9411

**Taiwan:** Tomung Lai, United Pacific International  
 No. 311 Nanking E. Rd., Sec. 3  
 Taipei, Taiwan R.O.C. Phone: 011-886-27-150-751  
 FAX: 011-886-27-169-493

**United Kingdom:** John Maycock  
 Huttons Buildings, 146 West St.  
 Sheffield, England S1 4ES Phone: 742-759186

## INDEX OF ADVERTISERS

ADVERTISER	READER SERVICE	PAGE NUMBER	ADVERTISER	READER SERVICE	PAGE NUMBER
	U.S. / OUTSIDE U.S.			U.S. / OUTSIDE U.S.	
ACCEL Technologies	411	111	Motorola		
Advanced Micro Device	80, 81	2-3	Semiconductor	◊	6-7*
Advantech	404	110		161, 162	49
Altera	147, 148	31	National Instruments	122, 123	19
AMP	144, 145	61	NEC	124, 125	45
	82, 83	63	Nohau	407	110
Analog Devices	84, 85	51*, 85**	Oki Semiconductor	◊	88D-88E
Apex Microtechnology	86, 87	25	P-Cad	128, 129	88C
Astec America	88, 89	94	Penzar Development	408	110
AT&T	90, 91	32-33*	Peritek	163, 164	37
	151, 152	76-77*	Philips Test		
B&C Microsystems	413	111	& Measurement	◊	51**
Bud Industries	92, 93	85*	Pico Electronics	130, 131	78, 92
Burr-Brown	153, 154	79	Power Convertibles	165, 166	8
Capital Equipment	94, 95	105	Radstone	167, 168	34
Comdisco	182, 183	Cover II	Rogers	173-179	75
Cybernetic Micro				409	111
Systems	155, 156	14	Rolyn Optics	401	111
Cypress Semiconductor	◊	Cover IV	Scientific Endeavours	410	110
Dale Electronics	96, 97	83	Selco Products	400	110
Data Translation	98, 99	66	Siemens AG	132, 133	52
Emulation Technology	416	111	Signatec	405	110
Ferranti Venus	100, 101	108	Spectrum Signal		
Fortron/Source	157, 158	18	Processing	169, 170	40-41
Fujitsu APD	102, 103	93		402	111
Globe Electronic			Stanford Research	184, 185	28
Hardware	403	111	Systech Research	194, 195	88F
Harris Scientific	180, 181	46	Tatum Labs	411	111
Hewlett-Packard Co.	146	1	T-Cubed Systems	415	111
	104, 105	9	Tektronix	136, 137	55
Intel	1	12-13	Teradyne	196, 197	70-71
International			Texas Instruments	◊	16-17
Rectifier	149, 150	22	TriQuint		
I-Tech	159, 160	62	Semiconductor	134, 135	43
Intusoft	414	110	Vicor	138, 139	69
Lambda Electronics	110, 111	72A-72D*	Victory Engineering	171, 172	8
Micrel	186, 187	64-65	Viewlogic Systems	?140, 141	10-11
MicroSim	112, 113	86	Yokogawa	142, 143	33**
Mini-Circuits Laboratory,			Z-World Engineering	406	110
a Div. of Scientific					
Components Corp.	118, 119	15			
	114, 115	20-21			
	116, 117	26-27			
	188, 189	80			
	120, 121	Cover III			
Miller-Freeman	192, 193	102			


\* Domestic Advertiser Only

\*\* International Advertiser Only

The advertisers index is prepared as an extra service.

Electronic Design does not assume any liability for omissions or errors.

# incredible!

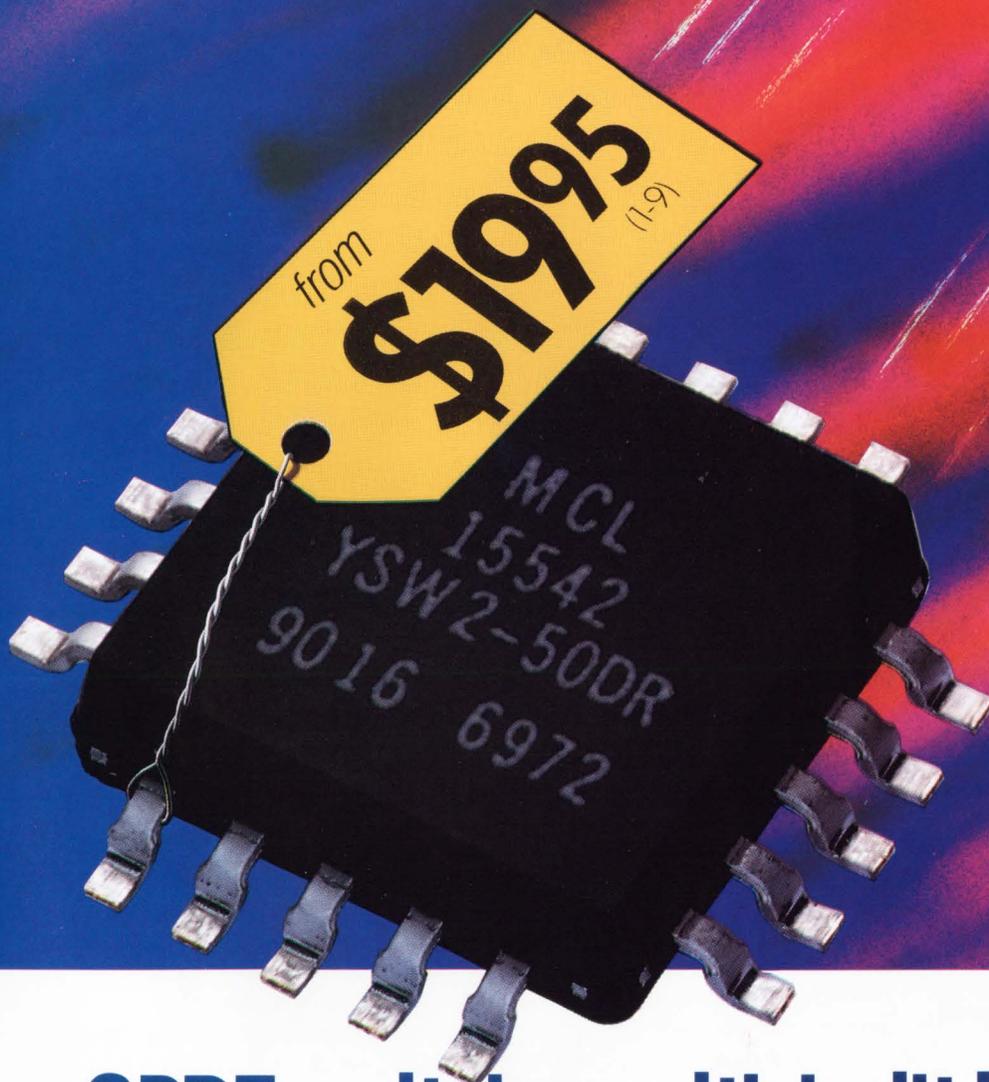

## SPDT switches with built-in driver

**ABSORPTIVE or REFLECTIVE dc to 5GHz**

Truly incredible...superfast 3nsec GaAs SPDT reflective or absorptive switches with built-in driver, available in pc plug-in or SMA connector models, from only \$19.95. So why bother designing and building a driver interface to further complicate your subsystem and take added space when you can specify Mini-Circuits' latest innovative integrated components?

Check the outstanding performance of these units...high isolation, excellent return loss (even in the "off" state for absorptive models) and 3-sigma guaranteed unit-to-unit repeatability for insertion loss. These rugged devices operate over a -55° to +100°C span. Plug-in models are housed in a tiny plastic case and are available in tape-and-reel format (1500 units max, 24mm). All models are available for immediate delivery with a one-year guarantee.

### SPECIFICATIONS (typ)

	Absorptive SPDT YSWA-2-50DR ZYSWA-2-50DR			Reflective SPDT YSW-2-50DR ZYSW-2-50DR		
	dc- 500	500- 2000	2000- 5000	dc- 500	500- 2000	2000- 5000
Frequency (MHz)						
Ins. Loss (dB)	1.1	1.4	1.9	0.9	1.3	1.4
Isolation (dB)	42	31	20	50	40	28
1dB Comp. (dBm)	18	20	22.5	20	20	24
RF Input (max dBm)	20			22	22	26
VSWR "on"	1.25	1.35	1.5	1.4	1.4	1.4
Video Bkthru (mV,p/p)	30	30	30	30	30	30
Sw. Spd. (nsec)	3	3	3	3	3	3
Price, \$	YSWA-2-50DR (pin) 23.95			YSW-2-50DR (pin) 19.95		
(1-9 qty)	ZYSWA-2-50DR (SMA) 69.95			ZYSW-2-50DR (SMA) 59.95		



finding new ways ...  
setting higher standards

## Mini-Circuits

P.O. Box 350166, Brooklyn, New York 11235-0003 (718) 934-4500 Fax (718) 332-4661 Telexes: 6852844 or 620156

CIRCLE 120 FOR U.S. RESPONSE

CIRCLE 121 FOR RESPONSE OUTSIDE THE U.S.

F141 REV. C

# A REVOLUTIONARY ADVANCE IN SPARC MULTIPROCESSING.

## **The industry's first integrated SPARC® multiprocessing solution — the CY7C605 Multiprocessing Cache Controller/MMU.**

High-performance systems designers have migrated to RISC in a race for performance. Just as rapidly, there is a movement to multiprocessing, which represents the most cost-effective way to load more power into a single system.

Multiprocessing RISC design is not simple. There are substantial technological challenges, particularly in the area of multi-level memory systems.

Now we offer a breakthrough to help you implement multiprocessing systems rapidly.


## **Cache coherency without stealing processor cycles — a leap in performance.**

Maintaining cache coherency is one of the biggest problems to solve in shared memory multiprocessing systems.

This approach solves it.



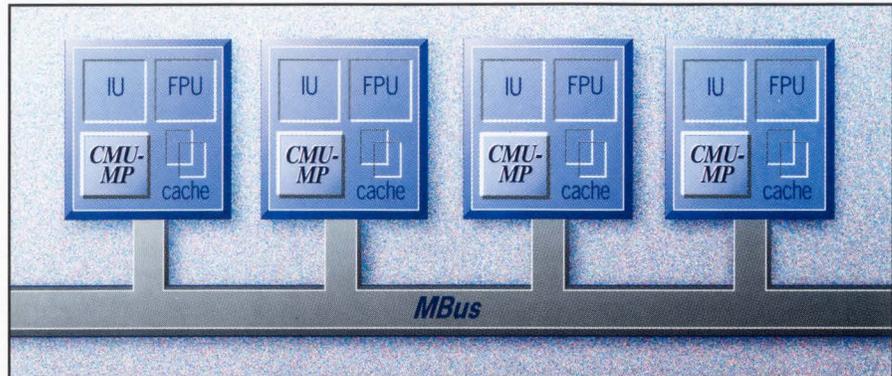*Pin compatible with our CY7C604 Uniprocessing Cache Controller/MMU, this new device lets you cascade to build cache size to 256K.*



*SPARC multiprocessing is now enabled. Now you can design-in multiple high-performance SPARC chipsets. Our revolutionary Multiprocessing Cache Controller and Memory Management Unit (CMU-MP/CY7C605) provides memory management facilities and a unique cache architecture for higher performance. Our complete SPARC chipset solution shortens your time to market.*

It is the only VLSI solution that performs concurrent bus snooping and processor execution.

Our unique dual cache tag directories provide for simultaneous bus snooping and processor access to cache. No other cache management unit provides dual tags on-chip.

As a result, your system maintains cache coherency without stealing execution cycles from the microprocessor.

You get multiprocessing with the most efficient cache coherency protocol available, allowing data to pass from CPU to CPU in a single clock cycle. That translates directly to higher performance systems.

### **MBus compliant.**

MBus compliance means you have a SPARC-standard, plug-and-play route to even more powerful, higher performing systems.


## **An integrated part of the industry's highest performance SPARC chipset.**

Our chipset approach simplifies the complexities of multiple CPUs working together in a shared memory system.

This VLSI solution means you don't have to design and pay for boards full of logic to accomplish fast multiprocessing.

It is all available now.

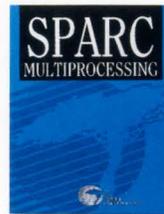For more information on the industry's most complete multiprocessing solution, please call for our literature package today.



**Multiprocessing  
Information  
Hotline:  
1-800-952-6300.\*  
Ask for Dept. C3V.**

